

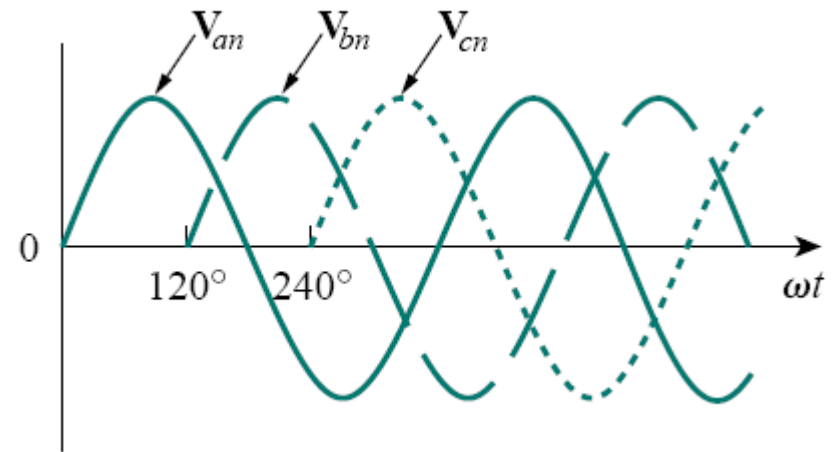


3 phase circuits

# Three-phase four-wire system.

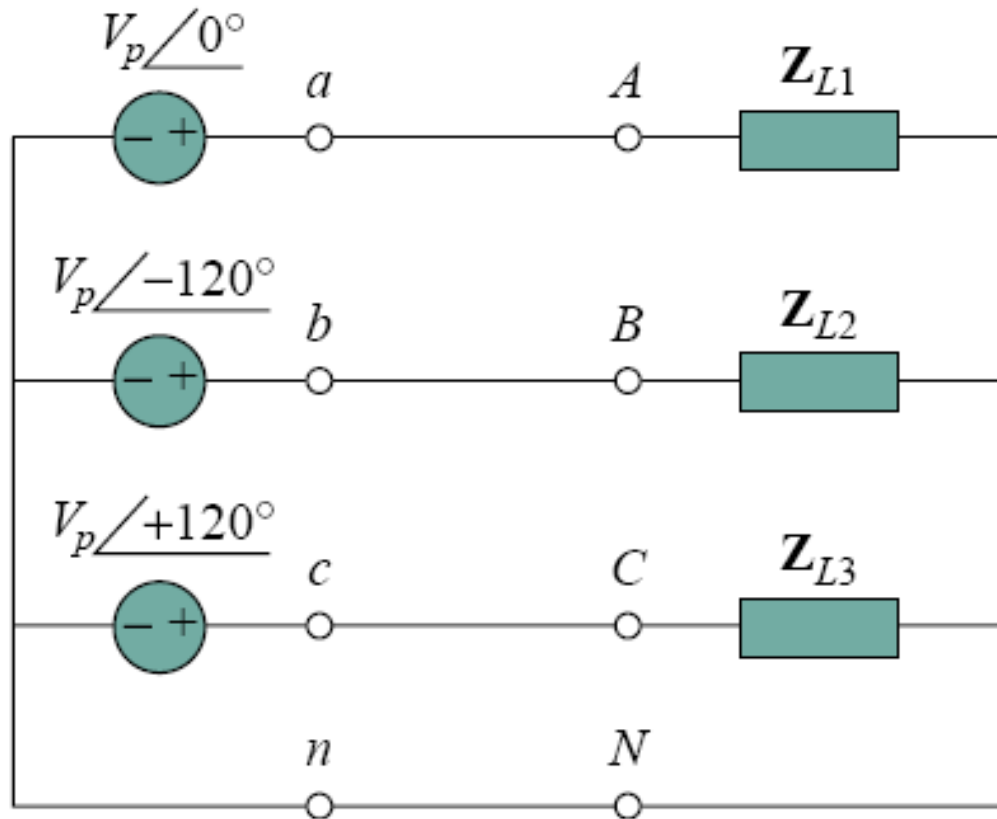


# A three-phase generator.

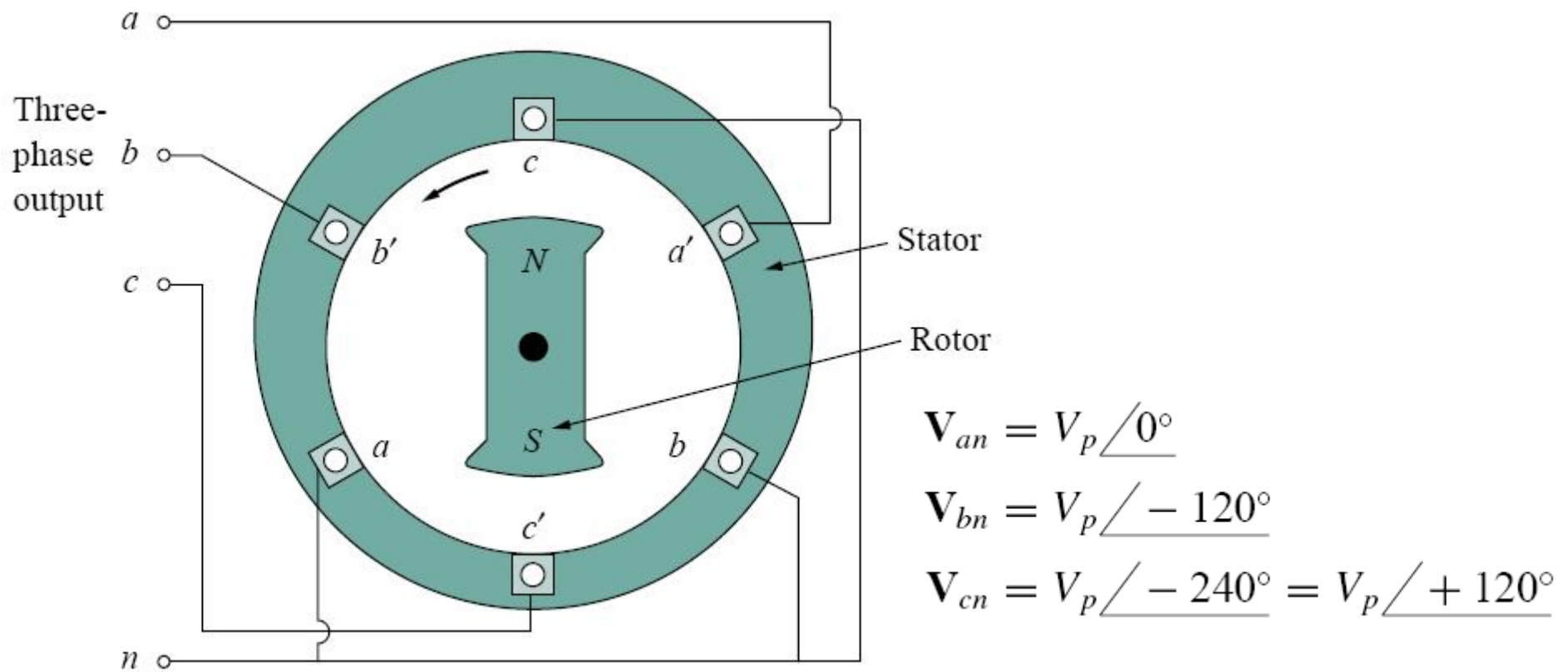


$$\mathbf{V}_{an} + \mathbf{V}_{bn} + \mathbf{V}_{cn} = 0$$

$$|\mathbf{V}_{an}| = |\mathbf{V}_{bn}| = |\mathbf{V}_{cn}|$$

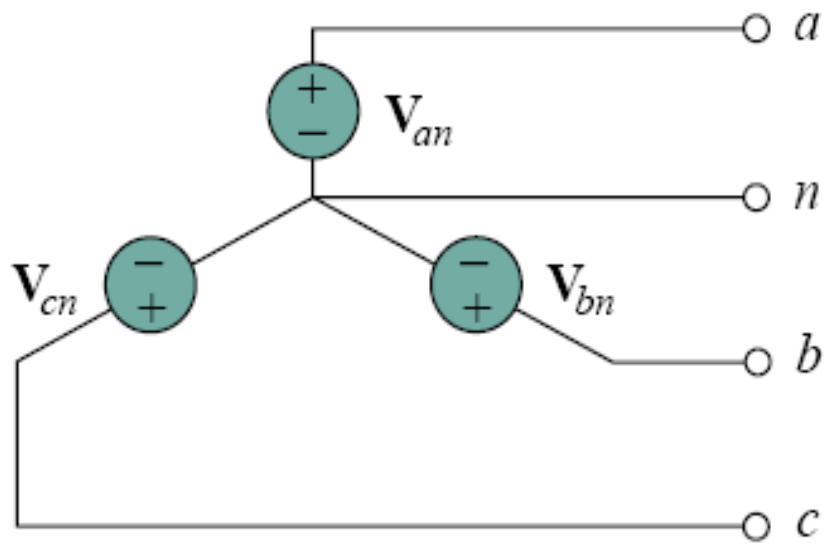Balanced phase voltages are equal in magnitude and are out of phase with each other by  $120^\circ$ .




(a)

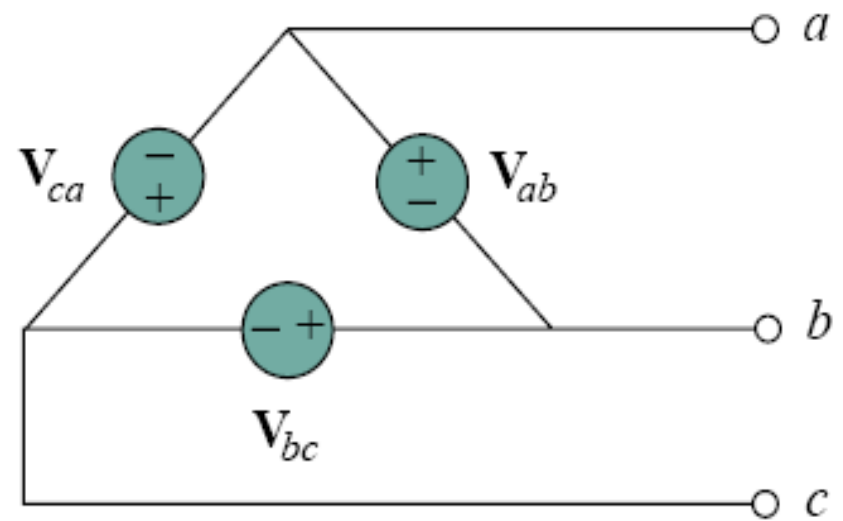


(b)

Three-phase voltage sources: (a) Y-connected source, (b)  $\Delta$ -connected source.

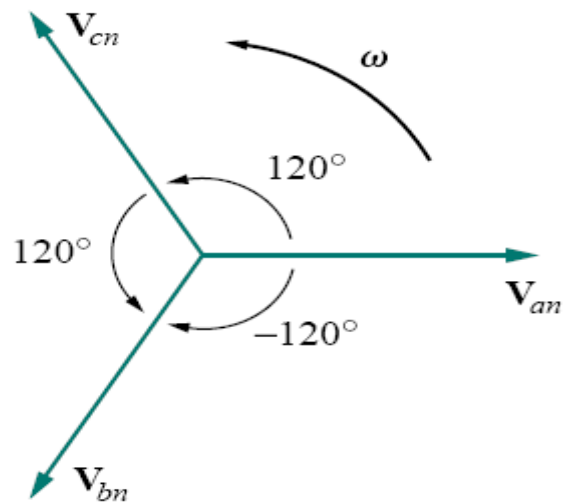Phase sequences: (a) *abc* or *positive sequence*, (b) *acb* or *negative sequence*.




(a)

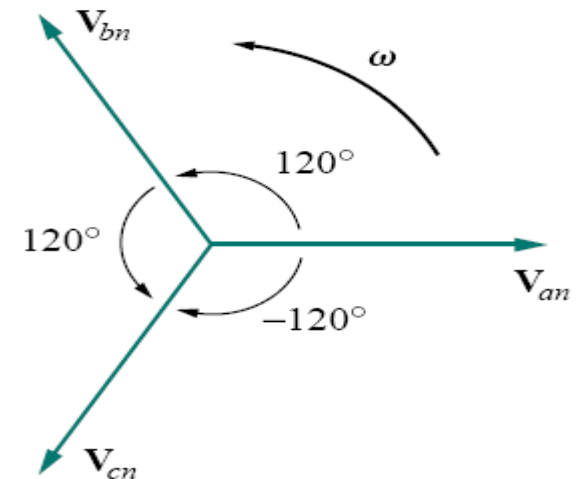


(b)

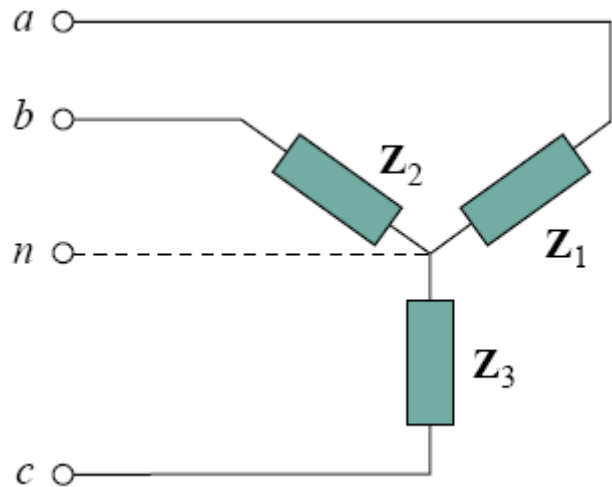A **balanced load** is one in which the phase impedances are equal in magnitude and in phase.



$$Z_1 = Z_2 = Z_3 = Z_Y$$

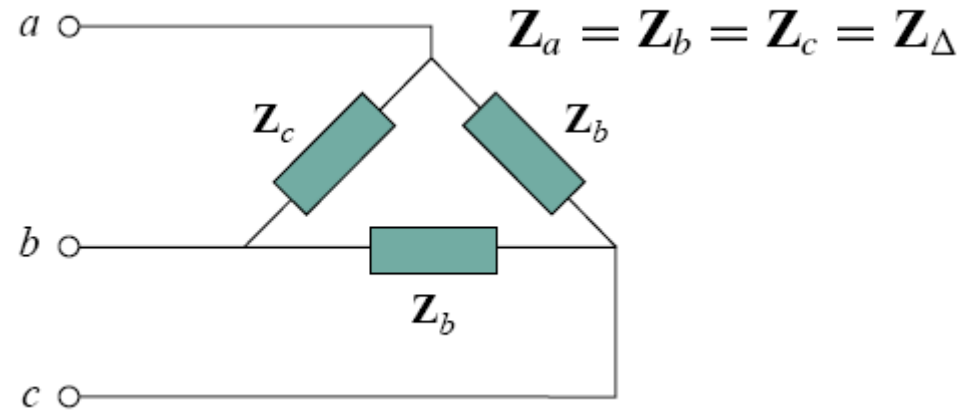


$$Z_{\Delta} = 3Z_Y \quad \text{or} \quad Z_Y = \frac{1}{3}Z_{\Delta}$$


Since both the three-phase source and the three-phase load can be either wye- or delta-connected, we have four possible connections:


- Y-Y connection (i.e., Y-connected source with a Y-connected load).
- Y- $\Delta$  connection.
- $\Delta$ - $\Delta$  connection.
- $\Delta$ -Y connection.

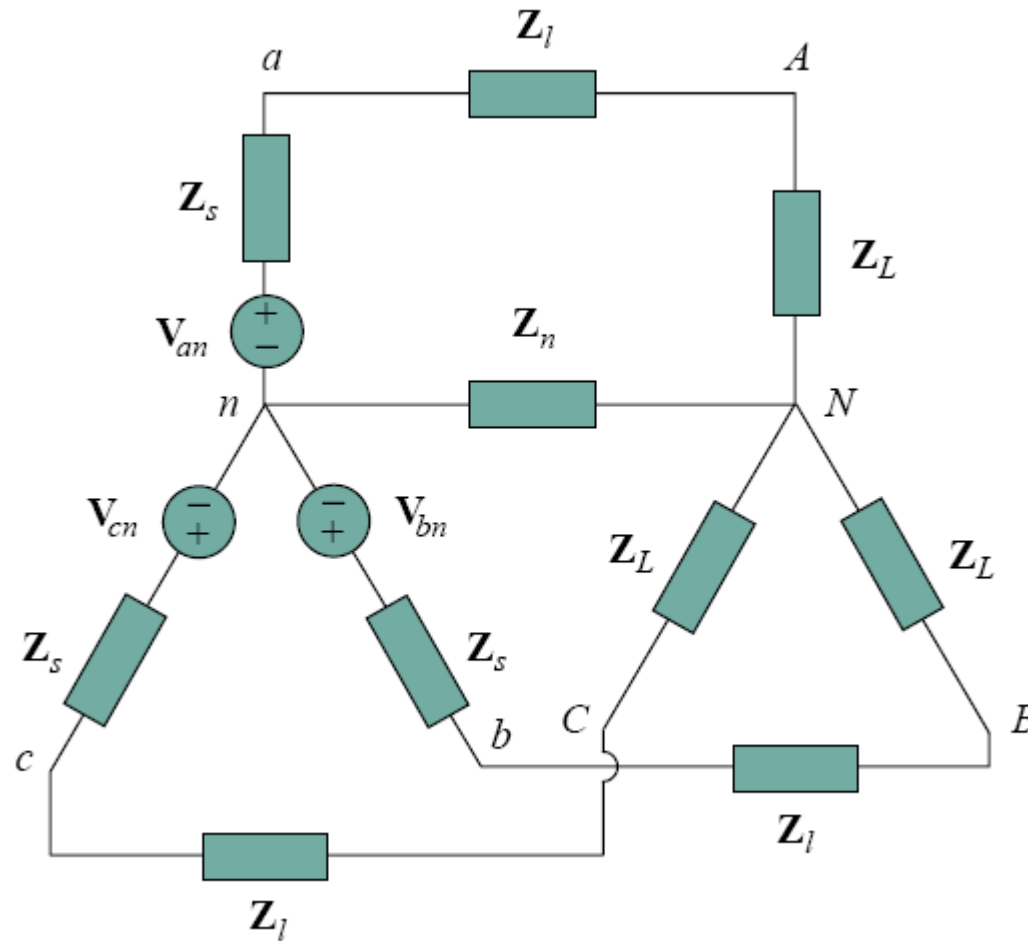A balanced Y-Y system, showing the source, line, and load impedances.



# Balanced Y-Y connection.

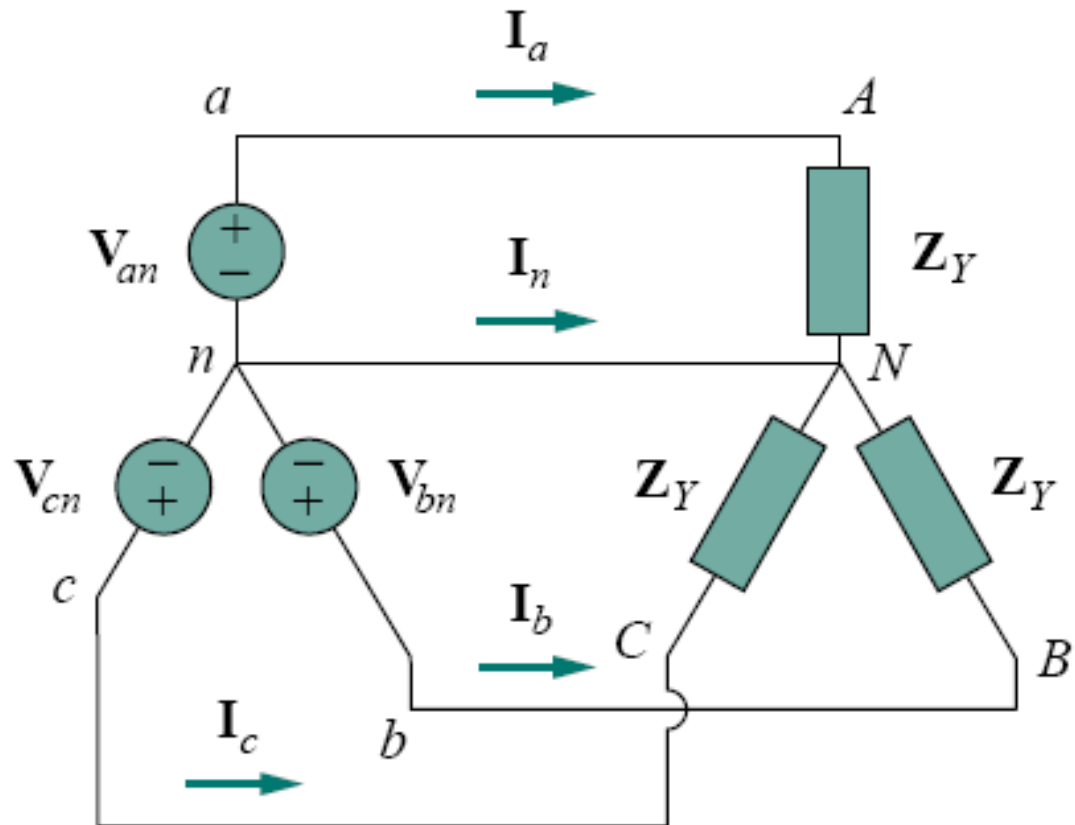

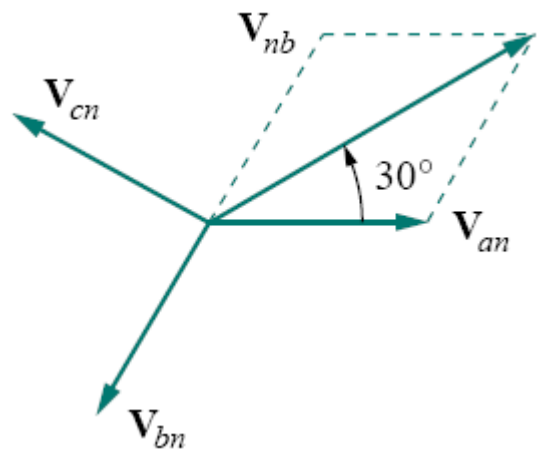


$$V_{ab} = V_{an} + V_{nb} = V_{an} - V_{bn} = V_p \angle 0^\circ - V_p \angle -120^\circ$$

$$= V_p \left( 1 + \frac{1}{2} + j \frac{\sqrt{3}}{2} \right) = \sqrt{3} V_p \angle 30^\circ$$

$$V_{bc} = V_{bn} - V_{cn} = \sqrt{3} V_p \angle -90^\circ$$
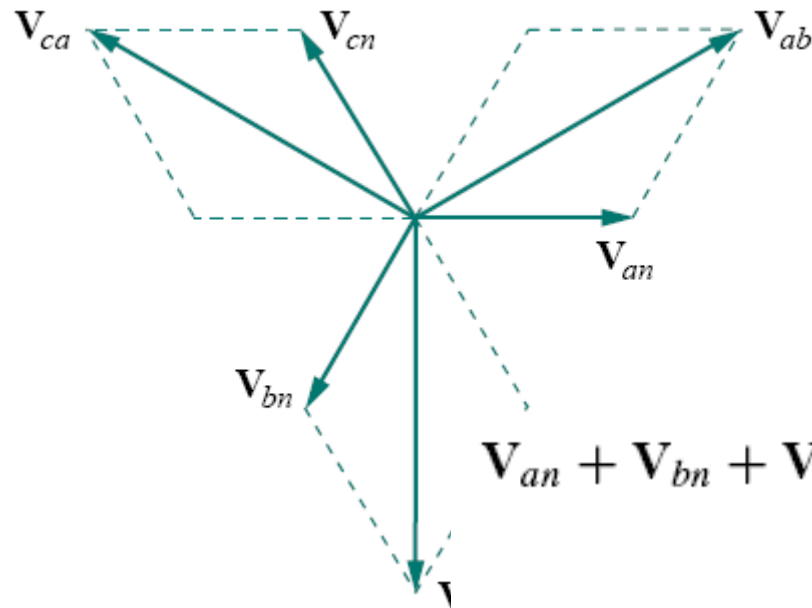
$$V_{ca} = V_{cn} - V_{an} = \sqrt{3} V_p \angle -210^\circ$$



$$\begin{aligned} V_{an} + V_{bn} + V_{cn} &= V_p \angle 0^\circ + V_p \angle -120^\circ + V_p \angle +120^\circ \\ &= V_p (1.0 - 0.5 - j0.866 - 0.5 + j0.866) \\ &= 0 \end{aligned}$$

Power in a balanced three-phase system

For a Y-connected load, the phase voltages are

$$v_{AN} = \sqrt{2}V_p \cos \omega t, \quad v_{BN} = \sqrt{2}V_p \cos(\omega t - 120^\circ)$$

$$v_{CN} = \sqrt{2}V_p \cos(\omega t + 120^\circ)$$

$$i_a = \sqrt{2}I_p \cos(\omega t - \theta), \quad i_b = \sqrt{2}I_p \cos(\omega t - \theta - 120^\circ)$$

$$i_c = \sqrt{2}I_p \cos(\omega t - \theta + 120^\circ)$$

$$p = p_a + p_b + p_c = v_{AN}i_a + v_{BN}i_b + v_{CN}i_c$$

$$= 2V_p I_p [\cos \omega t \cos(\omega t - \theta)$$

$$+ \cos(\omega t - 120^\circ) \cos(\omega t - \theta - 120^\circ)$$

$$+ \cos(\omega t + 120^\circ) \cos(\omega t - \theta + 120^\circ)]$$

Applying the trigonometric identity

$$\cos A \cos B = \frac{1}{2} [\cos(A + B) + \cos(A - B)]$$

gives

$$p = V_p I_p [3 \cos \theta + \cos(2\omega t - \theta) + \cos(2\omega t - \theta - 240^\circ) + \cos(2\omega t - \theta + 240^\circ)]$$

$$= V_p I_p [3 \cos \theta + \cos \alpha + \cos \alpha \cos 240^\circ + \sin \alpha \sin 240^\circ + \cos \alpha \cos 240^\circ - \sin \alpha \sin 240^\circ]$$

$$\text{where } \alpha = 2\omega t - \theta$$



$$= V_p I_p \left[ 3 \cos \theta + \cos \alpha + 2 \left( -\frac{1}{2} \right) \cos \alpha \right] = 3 V_p I_p \cos \theta$$

$$P = P_a + P_b + P_c = 3 P_p = 3 V_p I_p \cos \theta = \sqrt{3} V_L I_L \cos \theta$$

$$Q = 3V_p I_p \sin \theta = 3Q_p = \sqrt{3}V_L I_L \sin \theta$$

and the total complex power is
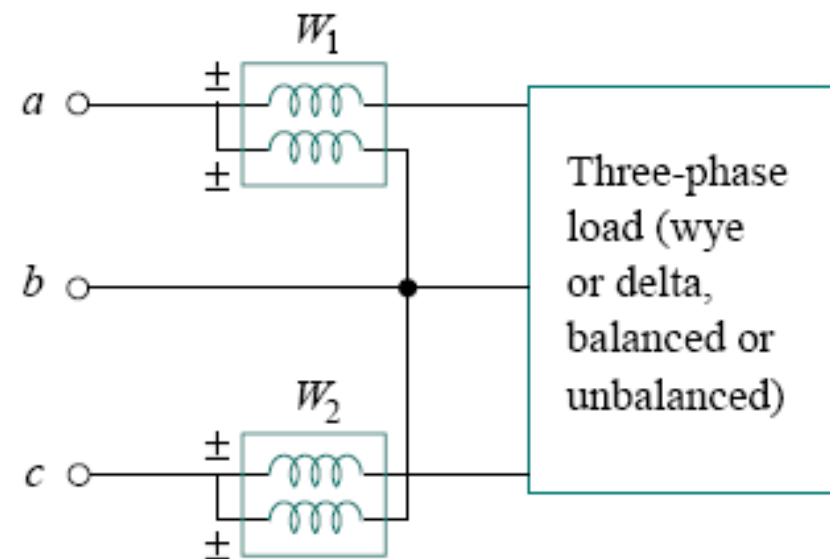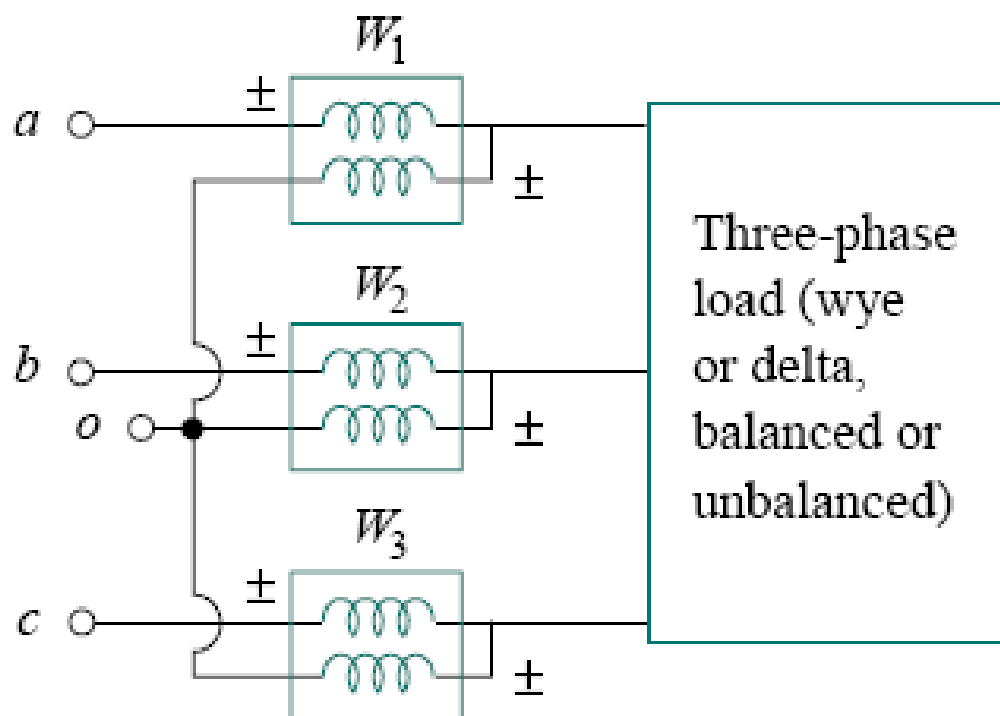
$$\mathbf{S} = 3\mathbf{S}_p = 3\mathbf{V}_p \mathbf{I}_p^* = 3I_p^2 \mathbf{Z}_p = \frac{3V_p^2}{\mathbf{Z}_p^*}$$



$$P_1 = \operatorname{Re}[\mathbf{V}_{ab}\mathbf{I}_a^*] = V_{ab}I_a \cos(\theta + 30^\circ) = V_L I_L \cos(\theta + 30^\circ)$$

$$P_2 = \operatorname{Re}[\mathbf{V}_{cb}\mathbf{I}_c^*] = V_{cb}I_c \cos(\theta - 30^\circ) = V_L I_L \cos(\theta - 30^\circ)$$

$$P_1 + P_2 = V_L I_L [\cos(\theta + 30^\circ) + \cos(\theta - 30^\circ)]$$

$$= V_L I_L (\cos \theta \cos 30^\circ - \sin \theta \sin 30^\circ$$

$$+ \cos \theta \cos 30^\circ + \sin \theta \sin 30^\circ)$$

$$= V_L I_L 2 \cos 30^\circ \cos \theta = \sqrt{3} V_L I_L \cos \theta$$

$$P_1 - P_2 = V_L I_L [\cos(\theta + 30^\circ) - \cos(\theta - 30^\circ)]$$

$$= V_L I_L (\cos \theta \cos 30^\circ - \sin \theta \sin 30^\circ$$

$$- \cos \theta \cos 30^\circ - \sin \theta \sin 30^\circ)$$

$$= -V_L I_L 2 \sin 30^\circ \sin \theta$$

$$P_2 - P_1 = V_L I_L \sin \theta$$

$$Q_T = \sqrt{3}(P_2 - P_1)$$

$$\tan \theta = \frac{Q_T}{P_T} = \sqrt{3} \frac{P_2 - P_1}{P_2 + P_1}$$

1. If  $P_2 = P_1$ , the load is resistive.
2. If  $P_2 > P_1$ , the load is inductive.
3. If  $P_2 < P_1$ , the load is capacitive.

The two-wattmeter method produces wattmeter readings  $P_1 = 1560$  W and  $P_2 = 2100$  W when connected to a delta-connected load. If the line voltage is 220 V, calculate: (a) the per-phase average power, (b) the per-phase reactive power, (c) the power factor, and (d) the phase impedance.

**Solution:**

We can apply the given results to the delta-connected load.

(a) The total real or average power is

$$P_T = P_1 + P_2 = 1560 + 2100 = 3660 \text{ W}$$

The per-phase average power is then

$$P_p = \frac{1}{3} P_T = 1220 \text{ W}$$

(b) The total reactive power is

$$Q_T = \sqrt{3}(P_2 - P_1) = \sqrt{3}(2100 - 1560) = 935.3 \text{ VAR}$$

so that the per-phase reactive power is

$$Q_p = \frac{1}{3} Q_T = 311.77 \text{ VAR}$$

(c) The power angle is

$$\theta = \tan^{-1} \frac{Q_T}{P_T} = \tan^{-1} \frac{935.3}{3660} = 14.33^\circ$$

Hence, the power factor is

$$\cos \theta = 0.9689 \text{ (leading)}$$

It is a leading pf because  $Q_T$  is positive or  $P_2 > P_1$ .

(c) The phase impedance is  $\mathbf{Z}_p = Z_p \angle \theta$ . We know that  $\theta$  is the same as the pf angle; that is,  $\theta = 14.57^\circ$ .

$$Z_p = \frac{V_p}{I_p}$$

We recall that for a delta-connected load,  $V_p = V_L = 220$  V. From Eq. (12.46),

$$P_p = V_p I_p \cos \theta \quad \Longrightarrow \quad I_p = \frac{1220}{220 \times 0.9689} = 5.723 \text{ A}$$


Hence,

$$Z_p = \frac{V_p}{I_p} = \frac{220}{5.723} = 38.44 \Omega$$

and

$$\mathbf{Z}_p = 38.44 \angle 14.33^\circ \Omega$$

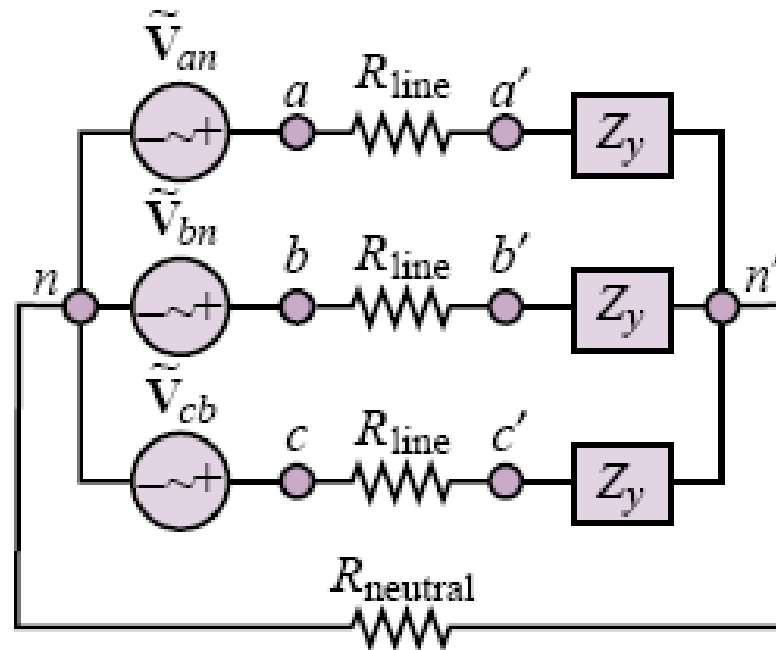Compute the power delivered to the load by the three-phase generator in the circuit shown in Figure



**Schematics, Diagrams, Circuits, and Given Data:**  $\tilde{V}_{an} = 480 \angle (0) \text{ V}$ ;  
 $\tilde{V}_{bn} = 480 \angle (-2\pi/3) \text{ V}$ ;  $\tilde{V}_{cn} = 480 \angle (2\pi/3) \text{ V}$ ;  $Z_y = 2 + j4 = 4.47 \angle (1.107) \Omega$ ;  
 $R_{line} = 2 \Omega$ ;  $R_{neutral} = 10 \Omega$ .


$$P_a = |\tilde{\mathbf{I}}|^2 R_L$$

where


$$|\tilde{\mathbf{I}}| = \left| \frac{\tilde{\mathbf{V}}_a}{Z_y + R_{\text{line}}} \right| = \left| \frac{480 \angle 0}{2 + j4 + 2} \right| = \left| \frac{480 \angle 0}{5.66 \angle \left(\frac{\pi}{4}\right)} \right| = 84.85 \text{ A}$$

and  $P_a = (84.85)^2 \times 2 = 14.4 \text{ kW}$ . Since the circuit is balanced, the results for phases  $b$  and  $c$  are identical, and we have:

$$P_L = 3P_a = 43.2 \text{ kW}$$

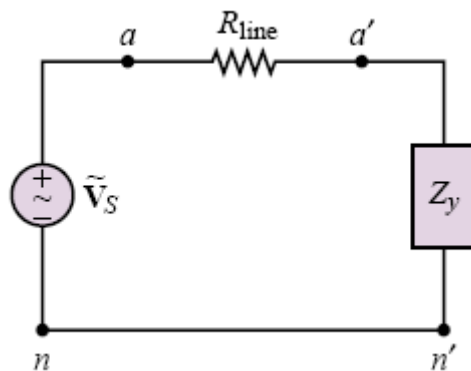

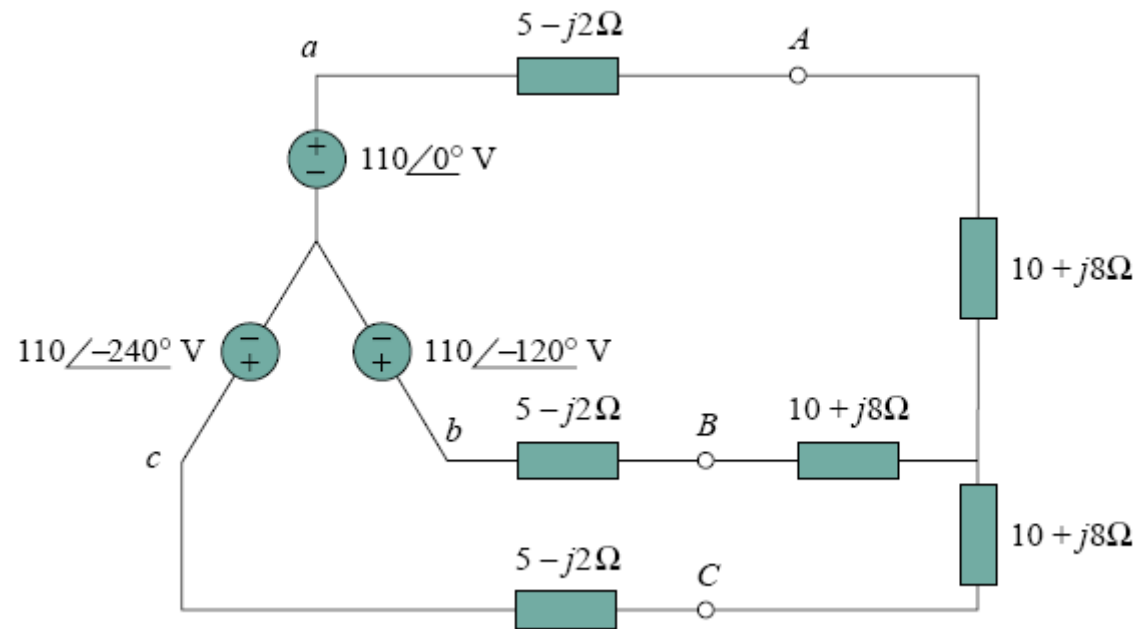Determine the total average power, reactive power, and complex power at the source and at the load.



**Solution:**

It is sufficient to consider one phase, as the system is balanced. For phase  $a$ ,

$$\mathbf{V}_p = 110 \angle 0^\circ \text{ V} \quad \text{and} \quad \mathbf{I}_p = 6.81 \angle -21.8^\circ \text{ A}$$

Thus, at the source, the complex power supplied is

$$\begin{aligned} \mathbf{S}_s &= -3\mathbf{V}_p\mathbf{I}_p^* = 3(110 \angle 0^\circ)(6.81 \angle 21.8^\circ) \\ &= -2247 \angle 21.8^\circ = -(2087 + j834.6) \text{ VA} \end{aligned}$$

The real or average power supplied is  $-2087$  W and the reactive power is  $-834.6$  VAR.

At the load, the complex power absorbed is

$$\mathbf{S}_L = 3|\mathbf{I}_p|^2\mathbf{Z}_p$$


where  $\mathbf{Z}_p = 10 + j8 = 12.81 \angle 38.66^\circ$  and  $\mathbf{I}_p = \mathbf{I}_a = 6.81 \angle -21.8^\circ$ .  
Hence

$$\begin{aligned} \mathbf{S}_L &= 3(6.81)^2 12.81 \angle 38.66^\circ = 1782 \angle 38.66^\circ \\ &= (1392 + j1113) \text{ VA} \end{aligned}$$

The real power absorbed is  $1391.7$  W and the reactive power absorbed is  $1113.3$  VAR. The difference between the two complex powers is absorbed by the line impedance  $(5 - j2) \Omega$ . To show that this is the case, we find the complex power absorbed by the line as

$$\mathbf{S}_\ell = 3|\mathbf{I}_p|^2\mathbf{Z}_\ell = 3(6.81)^2(5 - j2) = 695.6 - j278.3 \text{ VA}$$

A balanced positive-sequence wye-connected 60-Hz three-phase source has line-to-neutral voltages of  $V_Y = 1000$  V. This source is connected to a balanced wye-connected load. Each phase of the load consists of a 0.1-H inductance in series with a  $50\text{-}\Omega$  resistance. Find the line currents, the line-to-line voltages, the power, and the reactive power delivered to the load. Draw a phasor diagram showing the line-to-neutral voltages, the line-to-line voltages, and the line currents. Assume that the phase angle of  $\mathbf{V}_{an}$  is zero.

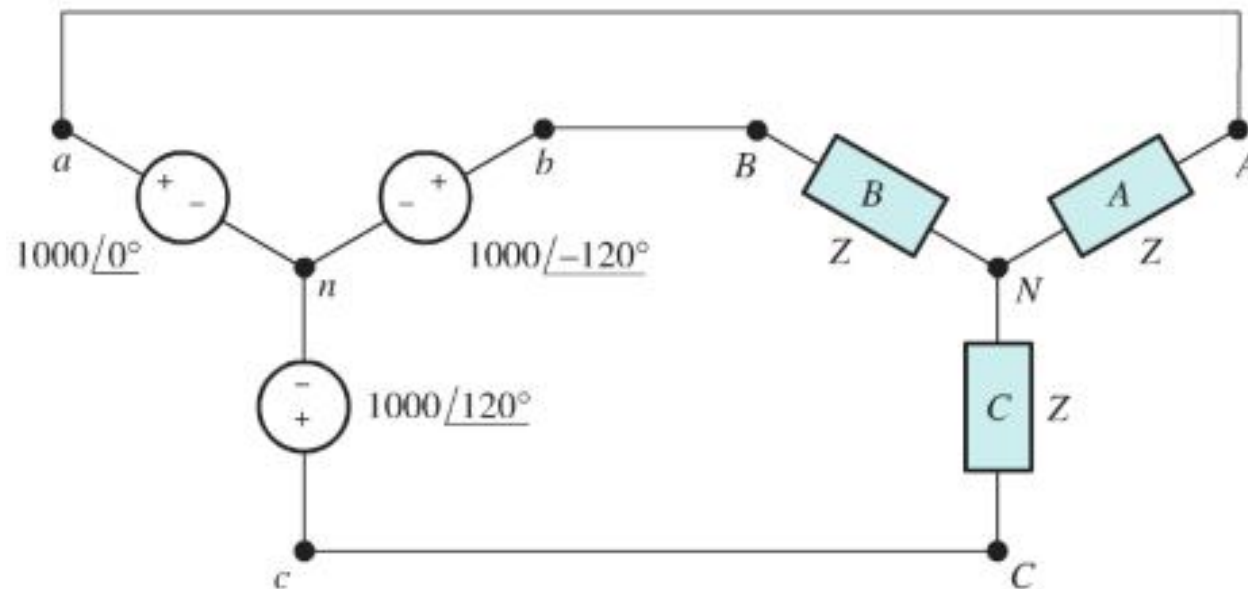

**Solution** First, by computing the complex impedance of each phase of the load, we find that

$$\begin{aligned} Z &= R + j\omega L = 50 + j2\pi(60)(0.1) = 50 + j37.70 \\ &= 62.62 \angle 37.02^\circ \end{aligned}$$

$$\mathbf{I}_{aA} = \frac{\mathbf{V}_{an}}{Z} = \frac{1000 \angle 0^\circ}{62.62 \angle 37.02^\circ} = 15.97 \angle -37.02^\circ$$

$$\mathbf{V}_{ab} = \mathbf{V}_{an} \times \sqrt{3} \angle 30^\circ = 1732 \angle 30^\circ$$

$$\mathbf{I}_{bB} = \frac{\mathbf{V}_{bn}}{Z} = \frac{1000 \angle -120^\circ}{62.62 \angle 37.02^\circ} = 15.97 \angle -157.02^\circ$$


$$\mathbf{V}_{bc} = \mathbf{V}_{bn} \times \sqrt{3} \angle 30^\circ = 1732 \angle -90^\circ$$

$$\mathbf{I}_{cC} = \frac{\mathbf{V}_{cn}}{Z} = \frac{1000 \angle 120^\circ}{62.62 \angle 37.02^\circ} = 15.97 \angle 82.98^\circ$$

$$\mathbf{V}_{ca} = \mathbf{V}_{cn} \times \sqrt{3} \angle 30^\circ = 1732 \angle 150^\circ$$

$$P = 3 \frac{V_Y I_L}{2} \cos(\theta) = 3 \left( \frac{1000 \times 15.97}{2} \right) \cos(37.02^\circ) = 19.13 \text{ kW}$$
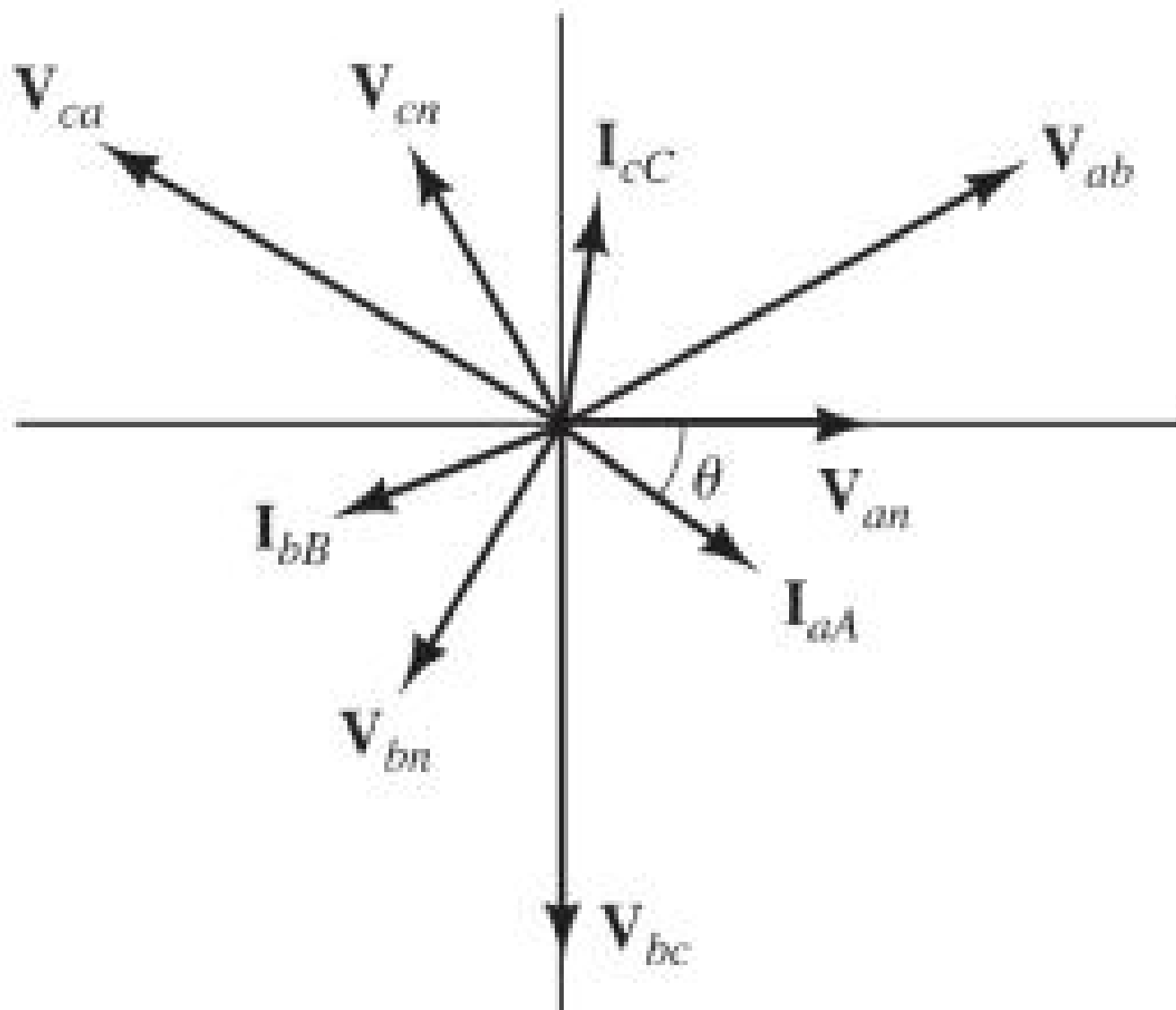
$$Q = 3 \frac{V_Y I_L}{2} \sin(\theta) = 3 \left( \frac{1000 \times 15.97}{2} \right) \sin(37.02^\circ) = 14.42 \text{ kVAR}$$



Three identical coils, each of resistance 10  $\Omega$  and inductance 42 mH are connected (a) in star and (b) in delta to a 415 V, 50 Hz, 3-phase supply. Determine the total power dissipated in each case.

(a) **Star connection**

$$\begin{aligned}\text{Inductive reactance } X_L &= 2\pi fL = 2\pi(50)(42 \times 10^{-3}) \\ &= 13.19 \Omega\end{aligned}$$

$$\begin{aligned}\text{Phase impedance } Z_p &= \sqrt{(R^2 + X_L^2)} = \sqrt{(10^2 + 13.19^2)} \\ &= 16.55 \Omega\end{aligned}$$

Line voltage  $V_L = 415$  V and

$$\text{phase voltage, } V_p = \frac{V_L}{\sqrt{3}} = \frac{415}{\sqrt{3}} = 240 \text{ V}$$

$$\text{Phase current, } I_p = \frac{V_p}{Z_p} = \frac{240}{16.55} = 14.50 \text{ A}$$

Line current,  $I_L = I_p = 14.50$  A

$$\text{Power factor} = \cos \phi = \frac{R_p}{Z_p} = \frac{10}{16.55} = 0.6042 \text{ lagging}$$

$$\begin{aligned}\text{Power dissipated, } P &= \sqrt{3}V_L I_L \cos \phi = \sqrt{3}(415)(14.50)(0.6042) \\ &= \mathbf{6.3 \text{ kW}}\end{aligned}$$

$$\text{(Alternatively, } P = 3I_p^2 R_p = 3(14.50)^2(10) = \mathbf{6.3 \text{ kW}})$$

(b) **Delta connection**

$$V_L = V_p = 415 \text{ V}, Z_p = 16.55 \Omega,$$

$\cos \phi = 0.6042$  lagging (from above).

$$\text{Phase current, } I_p = \frac{V_p}{Z_p} = \frac{415}{16.55} = 25.08 \text{ A}$$

$$\text{Line current, } I_L = \sqrt{3}I_p = \sqrt{3}(25.08) = 43.44 \text{ A}$$

$$\begin{aligned} \text{Power dissipated, } P &= \sqrt{3}V_L I_L \cos \phi = \sqrt{3}(415)(43.44)(0.6042) \\ &= \mathbf{18.87 \text{ kW}} \end{aligned}$$

$$\text{(Alternatively, } P = 3I_p^2 R_p = 3(25.08)^2(10) = \mathbf{18.87 \text{ kW}})$$

*Hence loads connected in delta dissipate three times the power than when connected in star, and also take a line current three times greater.*