

## BEEE203L Circuit Theory

### Digital Assignment I

1. The switch in fig. 1 has been in position a for a long time, until  $t=4$  s when it is moved to position b and left there. Determine  $v(t)$  at  $t=10$  s.

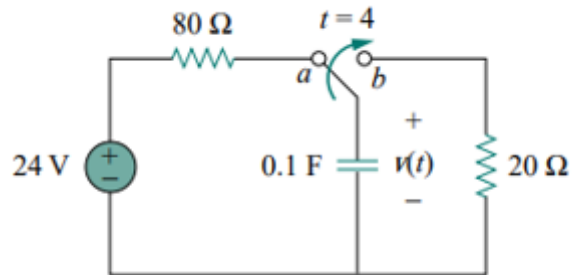


Fig. 1

2. If  $v(0) = 20$  V in the circuit in Fig. 2, obtain  $v(t)$  for  $t > 0$ .

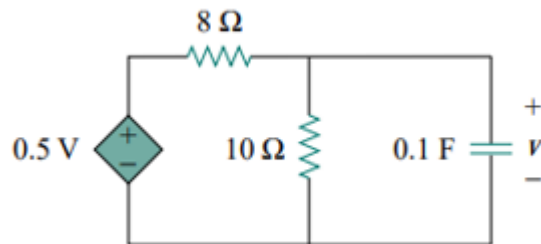


Fig. 2

3. The switch in Fig. 3 has been in position a for a long time. At  $t = 0$ , it moves to position b. Calculate  $i(t)$  for all  $t > 0$ .



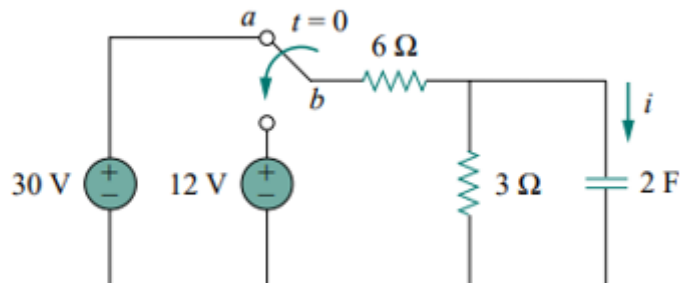


Fig. 3

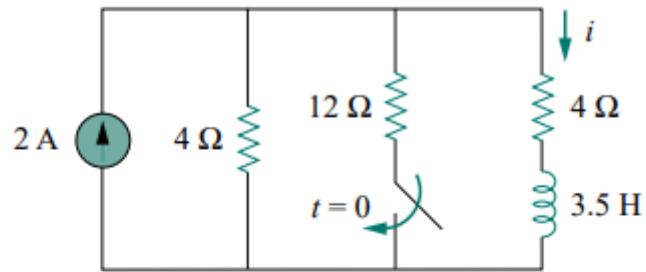4. Obtain the inductor current for both  $t < 0$  and  $t > 0$  in each of the circuits in fig. 4 a and b.



(a)

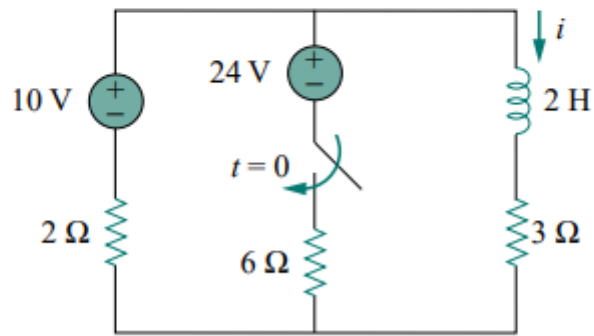

(b)

Fig. 4

5. Find  $v(t)$  for  $t > 0$  in the RLC circuit of fig. 5.

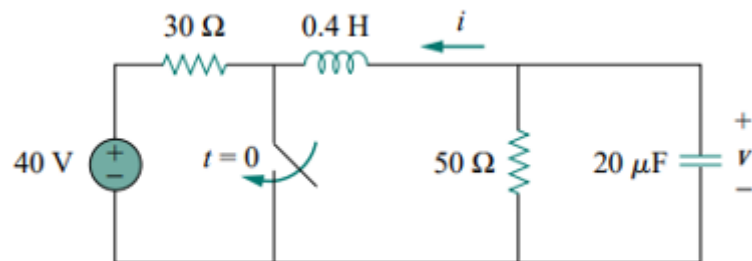


Fig. 5

6. Obtain the admittance parameter equivalent circuit of the two port in Fig. 6.

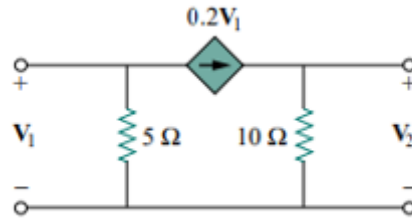


Fig. 6

7. Find the transmission parameters for the circuit in Fig. 7.

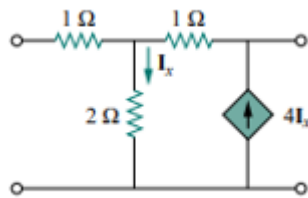


Fig. 7

8. What is the Y parameter presentation of the circuit in Fig.8.

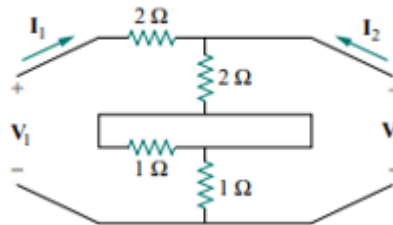


Fig. 8

9. Find  $V_2/V_s$  in the circuit in Fig. 9.

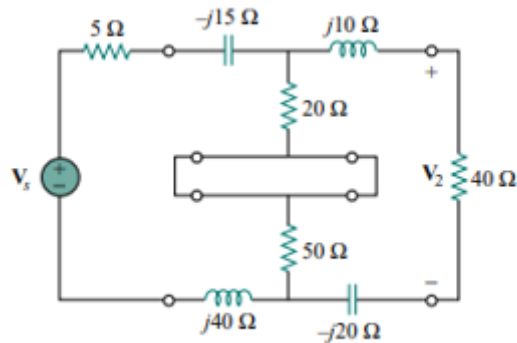


Fig. 9

10.