



# **BEEE203L**

# **CIRCUIT THEORY**

**DR. P. VIJAYAPRIYA**  
**PROFESSOR/ SELECT**

# **MODULE – VII**

## **TWO PORT NETWORKS**

# Contents

- ▶ Open circuit impedance parameters
- ▶ Short circuit admittance parameters
- ▶ Transmission parameters
- ▶ Hybrid parameters
- ▶ Relationship between parameter sets
- ▶ Interconnection of two port networks

# Hybrid parameters

## 4

- The hybrid parameters of a two-port network may be defined by expressing the voltage of input port  $V_1$  and current of output port  $I_2$  in terms of current of input port  $I_1$  and voltage of output port  $V_2$ .

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$


- They are very useful for describing electronic devices such as transistors ; it is much easier to measure experimentally the  $h$  parameters of such devices than to measure their  $z$  or  $y$  parameters
- The individual  $h$  parameters can be defined by setting  $I_1 = 0$  and  $V_2 = 0$ .

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \quad h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$
$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} \quad h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

Since  $h$  parameters represent dimensionally an impedance, an admittance, a voltage gain and a current gain, these are called hybrid parameters.

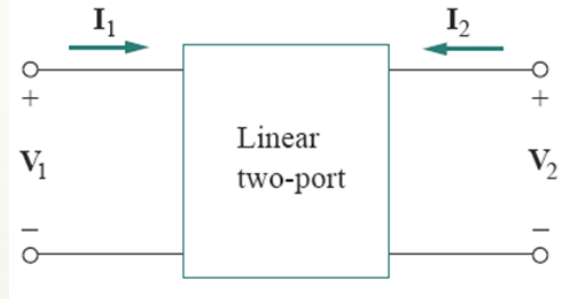- ▶  $h_{11}$  is the short-circuit input impedance.
- ▶  $h_{21}$  is the short-circuit forward current gain.
- ▶  $h_{12}$  is the open-circuit reverse voltage gain.
- ▶  $h_{22}$  is the open-circuit output admittance.





**When  $h_{11} h_{22} - h_{12} h_{21} = 1$ , the two-port network is said to be *symmetrical*. For reciprocal networks,  $h_{12} = -h_{21}$**
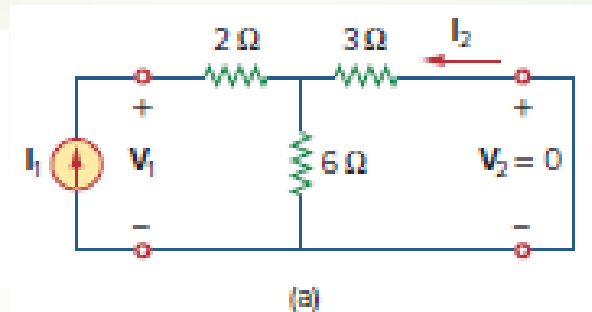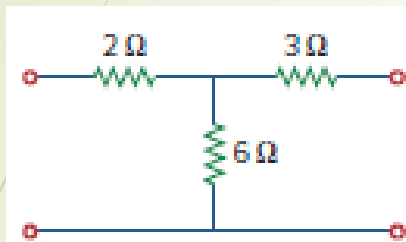
# Problems

6

**P.7.15** Find the hybrid parameters for the two-port network of Fig



$$V_1 = I_1(2 + 3 \parallel 6) = 4I_1 \quad \mathbf{h_{11} = \frac{V_1}{I_1} = 4 \Omega}$$

Also, from Fig. (a) we obtain, by current division,

$$\mathbf{-I_2 = \frac{6}{6 + 3} I_1 = \frac{2}{3} I_1}$$

Hence,

$$\mathbf{h_{21} = \frac{I_2}{I_1} = -\frac{2}{3}}$$

7

To obtain  $\mathbf{h}_{12}$  and  $\mathbf{h}_{22}$ , we open-circuit the input port and connect a voltage source  $V_2$  to the output port as in Fig. (b).

By voltage division,

$$\mathbf{V}_1 = \frac{6}{6+3} \mathbf{V}_2 = \frac{2}{3} \mathbf{V}_2$$

Hence,


$$\mathbf{h}_{12} = \frac{\mathbf{V}_1}{\mathbf{V}_2} = \frac{2}{3}$$

Also,


$$\mathbf{V}_2 = (3 + 6)\mathbf{I}_2 = 9\mathbf{I}_2$$

Thus,
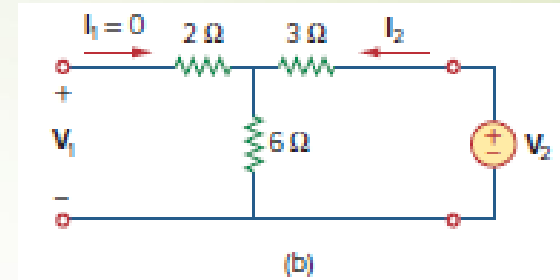
$$\mathbf{h}_{22} = \frac{\mathbf{I}_2}{\mathbf{V}_2} = \frac{1}{9} \text{ S}$$



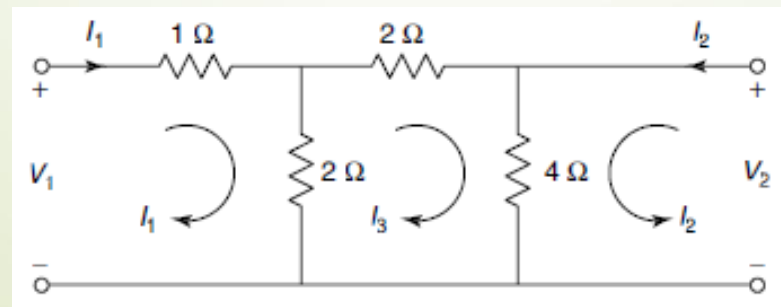**P.7.16** Determine hybrid parameters for the network of Fig. Also Determine whether the network is reciprocal.



**8**

Applying KVL to Mesh 1,

$$V_1 = 3I_1 - 2I_3 \quad \dots(i)$$

Applying KVL to Mesh 2,

$$V_2 = 4I_2 + 4I_3 \quad \dots(ii)$$

Applying KVL to Mesh 3,

$$\begin{aligned} -2(I_3 - I_1) - 2I_3 - 4(I_3 + I_2) &= 0 \\ 8I_3 &= 2I_1 - 4I_2 \end{aligned}$$

or

$$I_3 = \frac{I_1}{4} - \frac{I_2}{2} \quad \dots(iii)$$

Substituting Eq. (iii) in Eq. (i),

$$V_1 = 3I_1 - 2\left(\frac{I_1}{4} - \frac{I_2}{2}\right) = \frac{5}{2}I_1 + I_2 \quad \dots(iv)$$

Substituting Eq. (iii) in Eq. (ii),

$$V_2 = 4I_2 + 4\left(\frac{I_1}{4} - \frac{I_2}{2}\right) \quad \text{or} \quad I_2 = -\frac{1}{2}I_1 + \frac{1}{2}V_2 \quad \dots(v)$$

Substituting Eq. (v) in Eq. (iv),


$$V_1 = \frac{5}{2}I_1 - \frac{1}{2}I_1 + \frac{1}{2}V_2 = 2I_1 + \frac{1}{2}V_2 \quad \dots(\text{vi})$$

Comparing Eqs (v) and (vi) with h-parameter equations,

$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} 2 & \frac{1}{2} \\ -\frac{1}{2} & \frac{1}{2} \end{bmatrix}$$

Since  $h_{12} = -h_{21}$ , the network is reciprocal

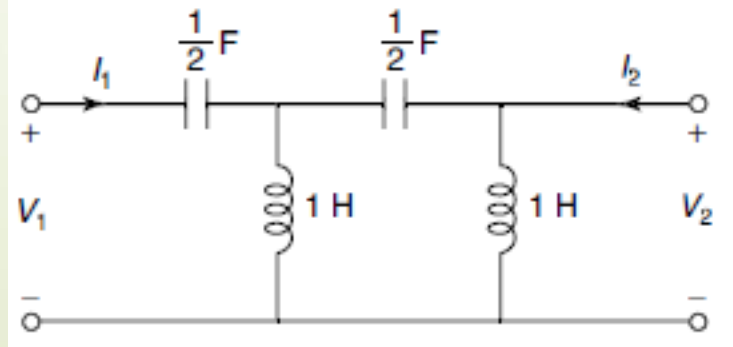**P.7.17** Find h-parameters for the network shown in Fig.



From Y parameter problem, we have

10

$$I_1 := \frac{s^3 + 2s}{4(s^2 + 1)} V_1 - \frac{s^3}{4(s^2 + 1)} V_2$$

Or

$$V_1 = \frac{4(s^2 + 1)}{s(s^2 + 2)} I_1 + \frac{s^2}{s^2 + 2} V_2$$

And

$$I_2 = -\frac{s^3}{4(s^2 + 1)} V_1 + \frac{s^4 + 6s^2 + 4}{4s(s^2 + 1)} V_2$$


Or

$$\begin{aligned} I_2 &= -\frac{s^3}{4(s^2 + 1)} \left[ \frac{4(s^2 + 1)}{s(s^2 + 2)} I_1 + \frac{s^2}{s^2 + 2} V_2 \right] + \frac{s^4 + 6s^2 + 4}{4s(s^2 + 1)} V_2 \\ &= -\frac{s^2}{s^2 + 2} I_1 + \frac{2(s^2 + 1)}{s(s^2 + 2)} V_2 \end{aligned}$$

Hence

$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} \frac{4(s^2 + 1)}{s(s^2 + 2)} & \frac{s^2}{s^2 + 2} \\ -\frac{s^2}{s^2 + 2} & \frac{2(s^2 + 1)}{s(s^2 + 2)} \end{bmatrix}$$

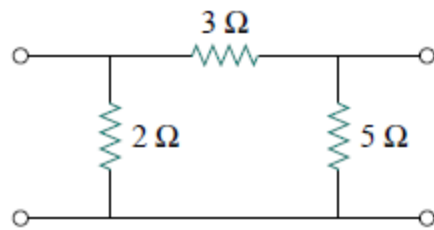**P.7.18** Determine the h parameters for the circuit shown in figure below



**Answer:**  $h_{11} = 1.2\ \Omega$ ,  $h_{12} = 0.4$ ,  $h_{21} = -0.4$ ,  $h_{22} = 0.4\ \text{S}$ .