



VIT[®]

Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)

REG.NO.:




SCHOOL OF ELECTRICAL ENGINEERING
CONTINUOUS ASSESSMENT TEST - I
WINTER SEMESTER 2024-2025

SLOT: C2

Programme Name & Branch : B.Tech. EEE & EIE
Course Code and Course Name : BEEE205L - Electronic Devices and Circuits
Faculty Name(s) : Dr. N. Sudhakar & Dr. G. Arunkumar
Class Number(s) : VL2025260101212 & VL2025260101213
Date of Examination : 19-08-2025, Tuesday, 2.00 PM to 3.30 PM
Exam Duration : 90 minutes Maximum Marks: 50

General instruction(s):

- Answer All Questions
- M - Max mark; CO - Course Outcome; BL - Blooms Taxonomy Level (1 - Remember, 2 - Understand, 3 - Apply, 4 - Analyse, 5 - Evaluate, 6 - Create)
- Course Outcomes (Type the CO statements covered in this question paper. Use the CO number as per the syllabus copy)
CO1 - Solve diode circuits for various applications.
CO2 - Analyze and design BJT and MOSFET DC circuits and their amplifier configurations

  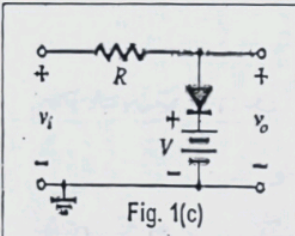Q. No	Question	M	CO	BL
1.	(a) Find the V_o for the multi-diode circuit of Fig. 1(a) (b) Sketch the input and output waveforms for the following clamper circuit with a sine wave input of $12\text{ V}_{(p-p)}$, 50 Hz, and a DC battery value of 4 V in Fig. 1(b) (c) Sketch the input and output waveforms for the following clipper circuit with a sine wave input of $12\text{ V}_{(p-p)}$, 50 Hz, and a DC battery value of 4 V in Fig. 1(c)    $V_o = 11.66\text{ V}$ Fig. 1	2	1	3
2.	(a) Sketch neatly the PN junction diode forward bias circuit, reverse bias circuit, and plot its Volt-Ampere characteristics curve (b) Sketch neatly the half-wave rectifier circuit, and plot its input and output waveforms with input voltage $8\text{ V}_{(p-p)}$. Also, provide the PIV in the diode	5	1	2
3.	(a) What is a transistor? List its types. Also, write a note on the principle operation of a transistor with a neat sketch (b) Sketch neatly the BJT common emitter input and output characteristics curve. Also, write its h-parameter	5	2	2



VIT

Vellore Institute of Technology
(Deemed to be University under section 3 of UDO Act, 1956)

REG.NO.:

SCHOOL OF ELECTRICAL ENGINEERING
CONTINUOUS ASSESSMENT TEST - I
WINTER SEMESTER 2024-2025

SLOT: C2

4.	Determine the following parameters for the given fixed-bias configuration shown in Fig. 2 a) Collector current (I_C) b) Collector bias voltage (V_{CC}) c) Current gain (β) d) Base resistor (R_B) e) Sketch the DC load-line curve Assume: $R_C = 2.2 \text{ k}\Omega$, $V_{CC} = 7.2 \text{ V}$, $I_E = 4 \text{ mA}$ and $I_B = 40 \mu\text{A}$ Fig. 2	10	2	3
5.	Determine the following parameters for the self-bias configuration: a) Base current and collector current b) Collector-emitter voltage c) Base voltage and Collector voltage, d) Collector saturation current and Cut-off voltage. e) Sketch the DC load-line curve Assume: $V_{CC} = 20 \text{ V}$, $V_{BE} = 0.7 \text{ V}$, $R_B = 470 \text{ k}\Omega$, $R_C = 2 \text{ k}\Omega$, $R_E = 900 \Omega$ and the current gain $\beta = 110$	10	2	3

4. Fixed Bias configuration:

$$I_E = I_B + I_C$$

$$\therefore I_C = I_E - I_B = 3.98 \text{ mA}$$

$$V_{CC} = (2.2 \times 10^3)(3.98 \times 10^{-3}) + 7.2$$

$$V_{CC} = 15.956 \text{ V}$$

$$\beta = I_C / I_B = 199$$

$$R_B = \frac{V_{CC} - V_{BE}}{I_B} = 762.8 \text{ k}\Omega$$

$$I_{C_{sat}} = \frac{V_{CC}}{R_C} = 7.252 \text{ mA}$$

$$V_{CE_{sat}} = V_{CC} = 15.956 \text{ V}$$

$$Q = (7.2 \text{ V}, 3.98 \text{ mA})$$

$$5. I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta) R_E} = 33.919 \mu\text{A}$$

$$I_C = 3.731 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C(R_C + R_E) = 9.18 \text{ V}$$

$$V_B = V_{BE} + V_E = 4.057 \text{ V}$$

$$V_C = V_{CE} + V_E = 12.537 \text{ V}$$

$$I_{C_{sat}} = \frac{V_{CC}}{R_C + R_E} = 6.896 \text{ mA}$$

$$V_{CE_{sat}} = V_{CC} = 20 \text{ V}$$

$$Q = (9.18 \text{ V}, 3.731 \text{ mA})$$