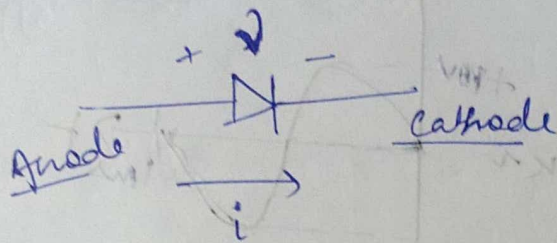



-: Diode circuit :-




Forward Bias (or) ∞

The concept of Ideal diode





Reverse Bias (or) OFF

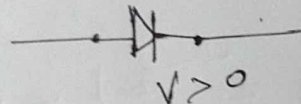


$V < 0$

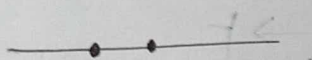



$I = I_s \approx 10 \mu A$

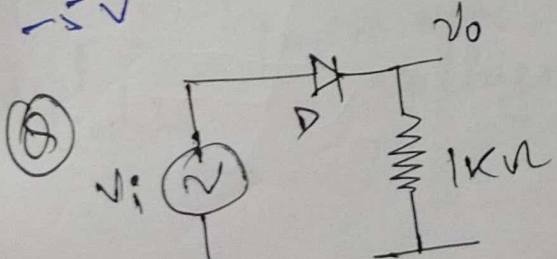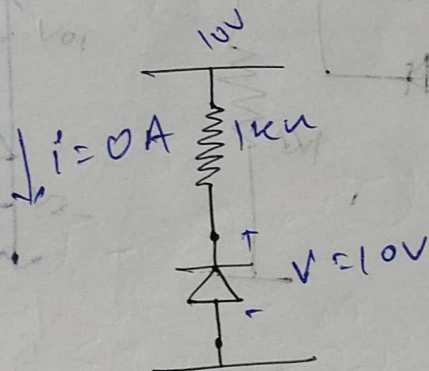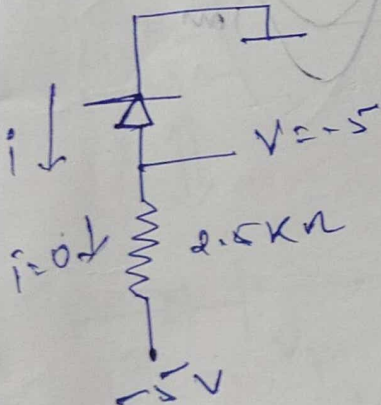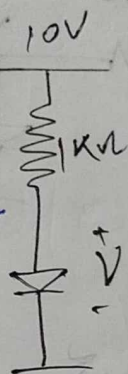


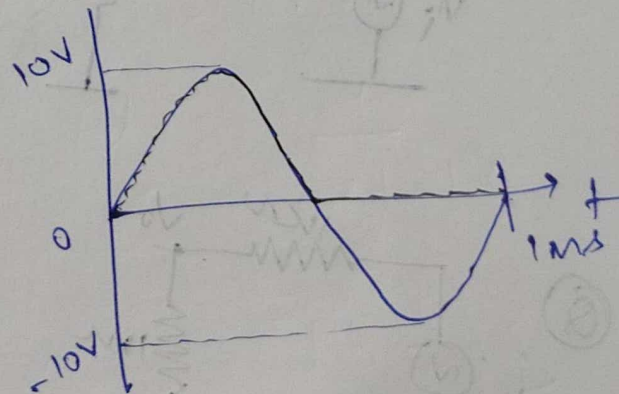
$V_i = 10 \sin(1000t) V$
 $f = 1 kHz$
 $f = 2\pi \omega$






③

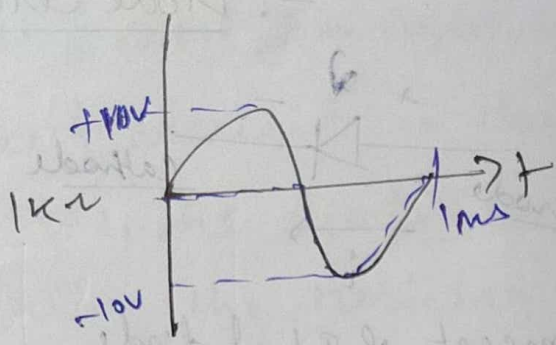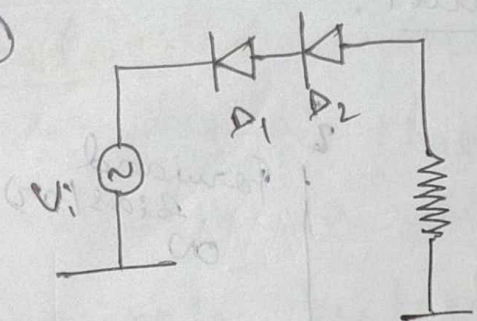


④

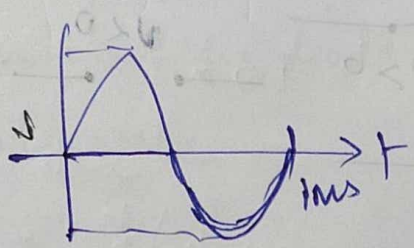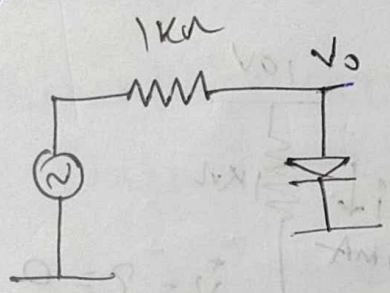

⑤

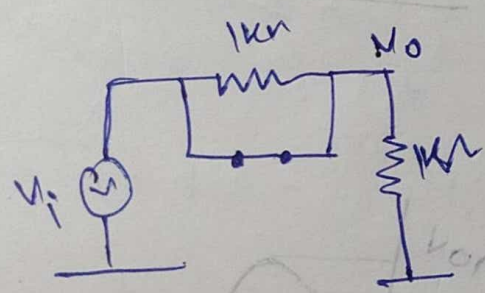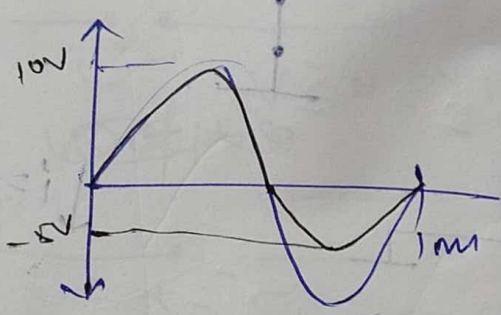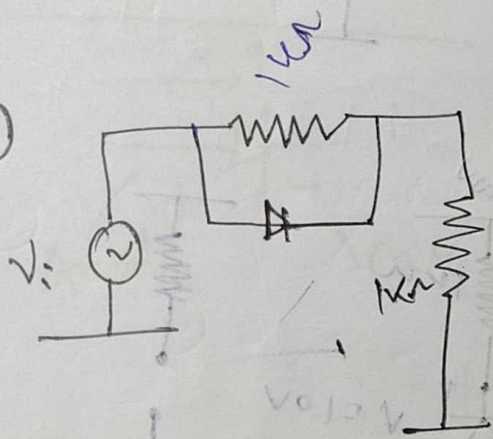

⑦

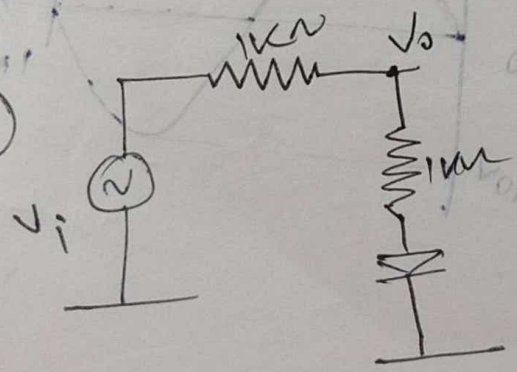

Real diode is Extension of Ideal diode -

$$= I_s \left[e^{\frac{qV}{kT}} - 1 \right]$$


$$i = I_s \left[\exp\left(\frac{qV}{kT}\right) - 1 \right]$$

Si - Silicon Diode

$I_s \rightarrow$ Reverse saturation current $0.1 \text{ nA} \sim \text{pA}$



$$\frac{kT}{q} = V_T = 26 \text{ mV} @ 300^\circ \text{K}$$

↑
thermal voltage

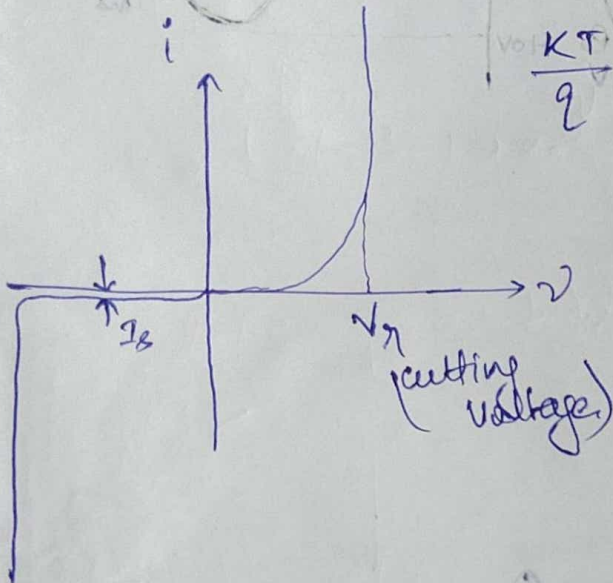

$$i = I_s e^{V/V_T} \quad V \geq V_T$$

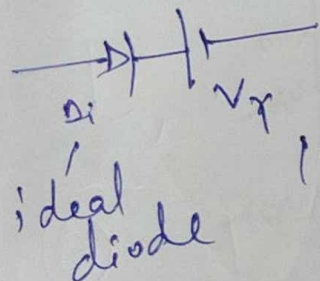
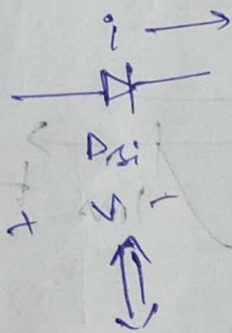
$$i = I_s \left[e^{V/V_T} - 1 \right] \quad V < 0$$



(with opposing voltage)

Clippers

⑧

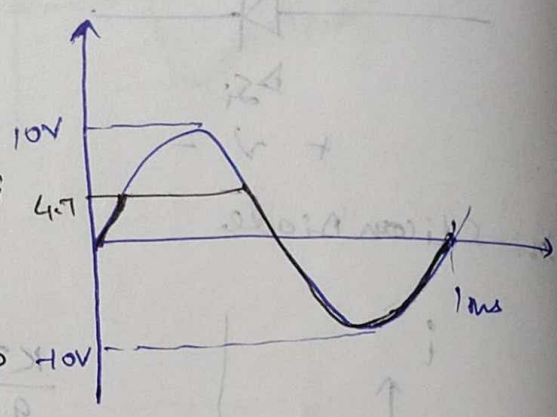
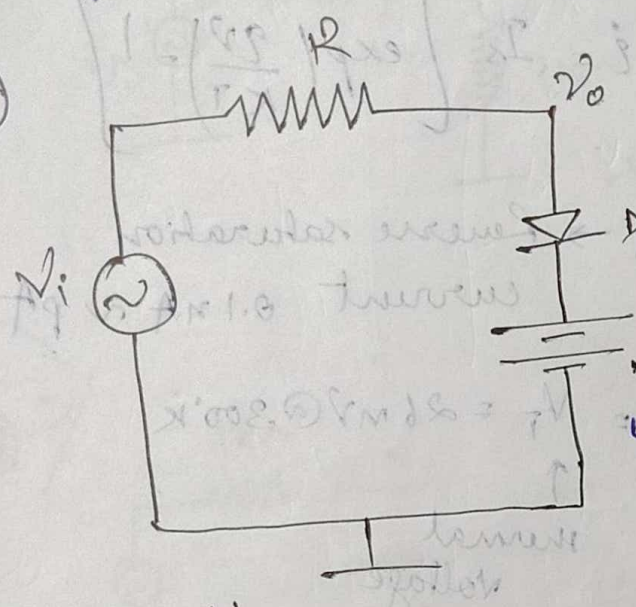








$V_A \sin(\omega t)$

$$V_A > V_B$$


$$10 > 4$$

⑨

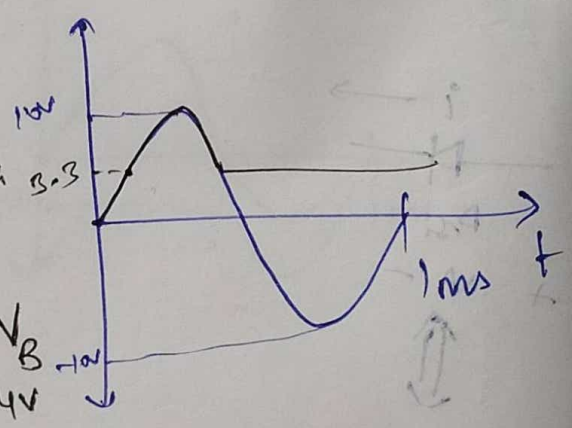
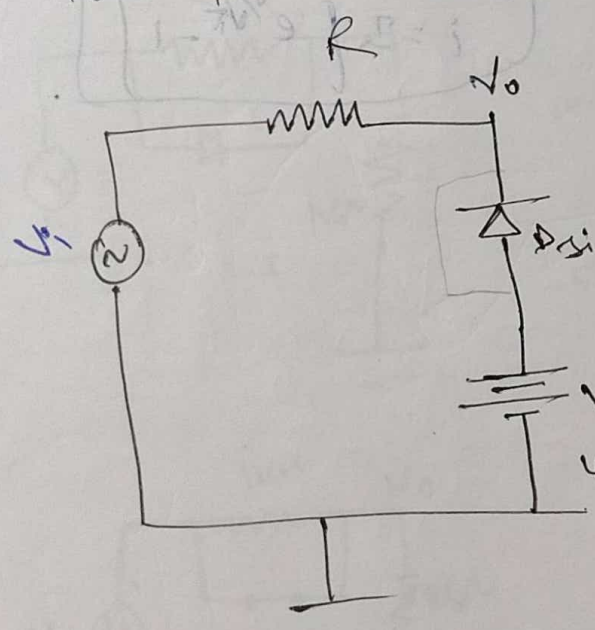


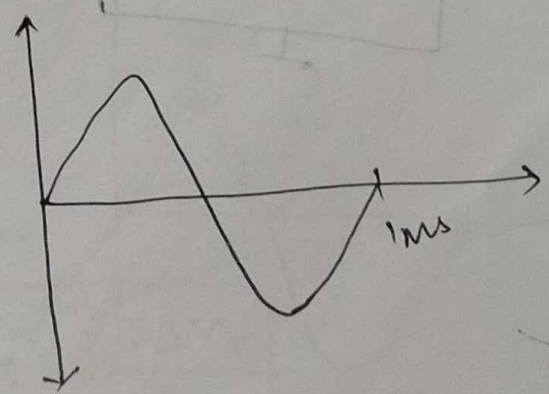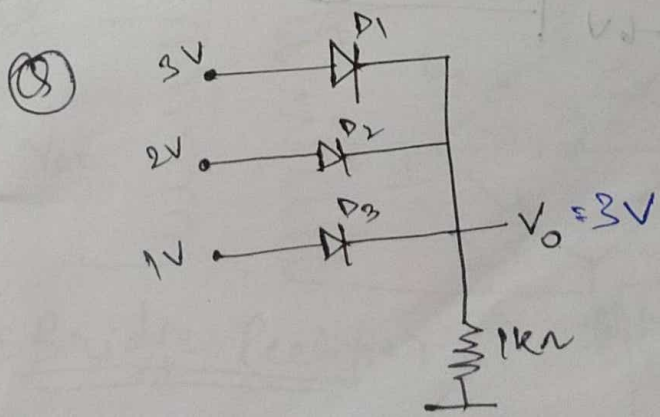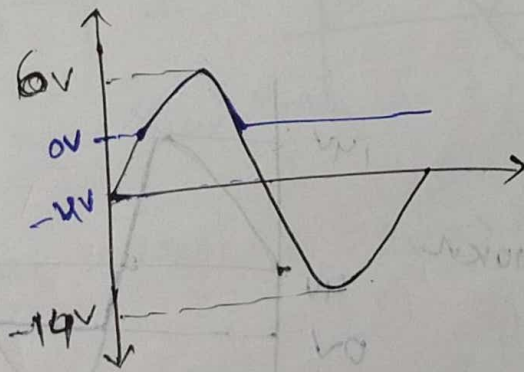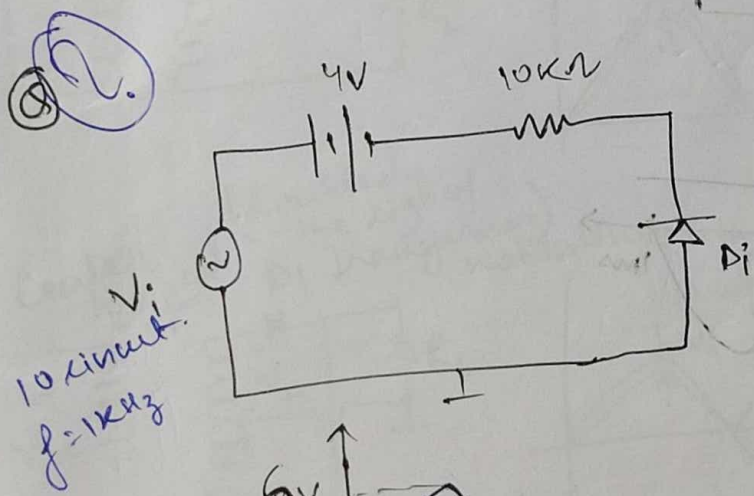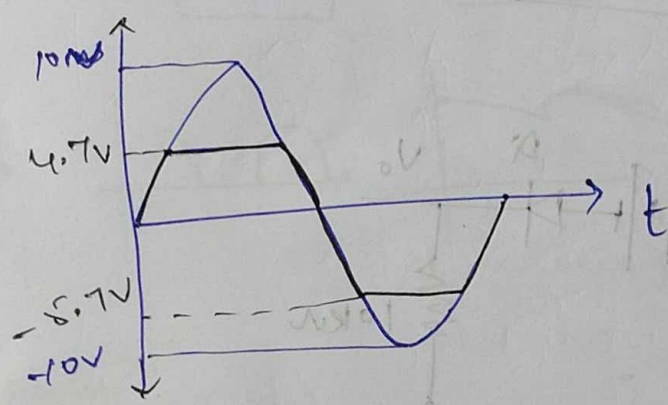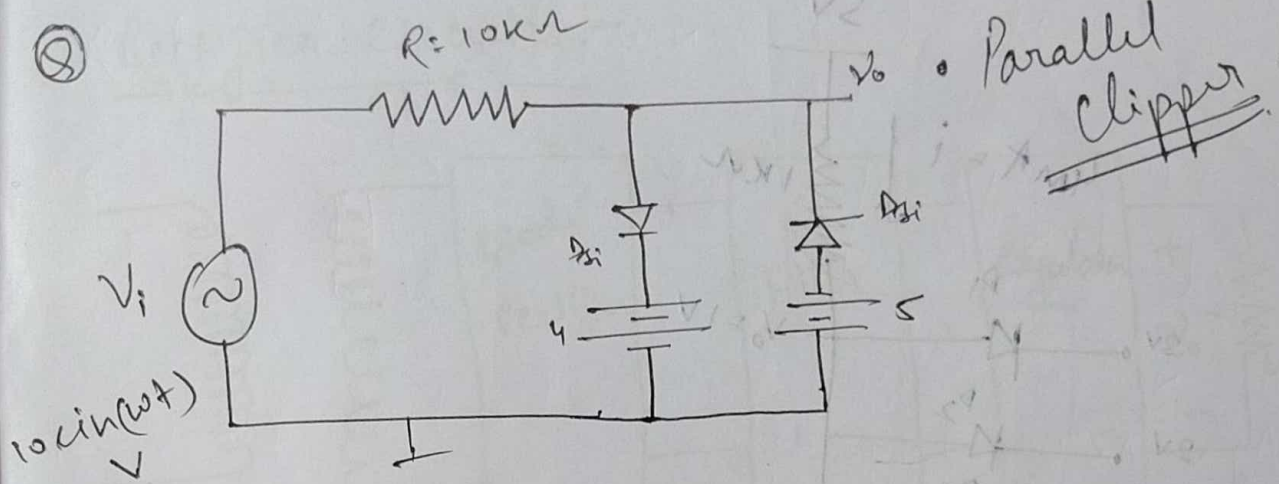



Q

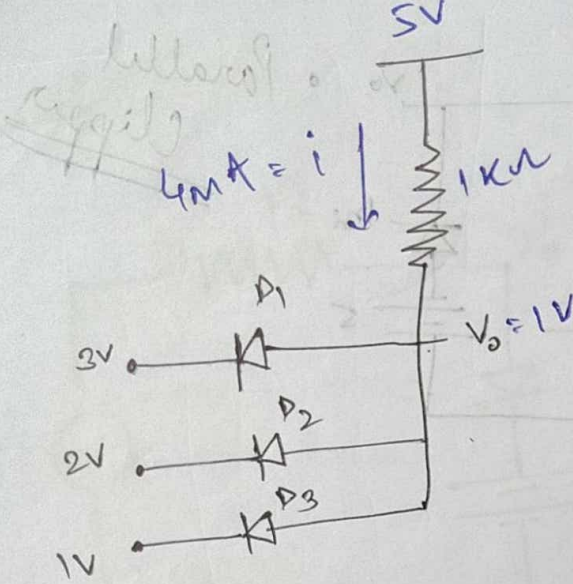







Q

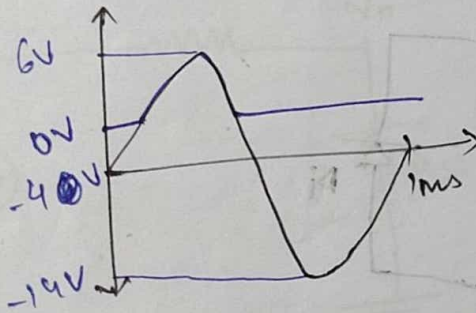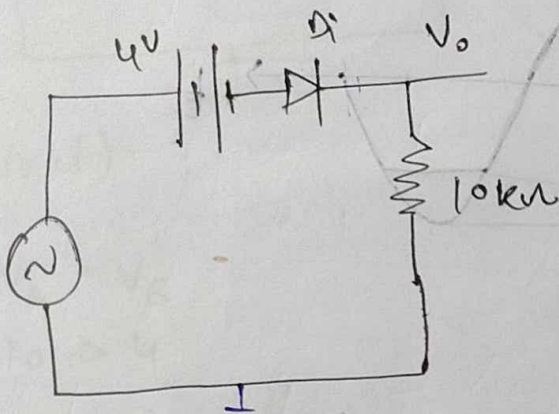

Q

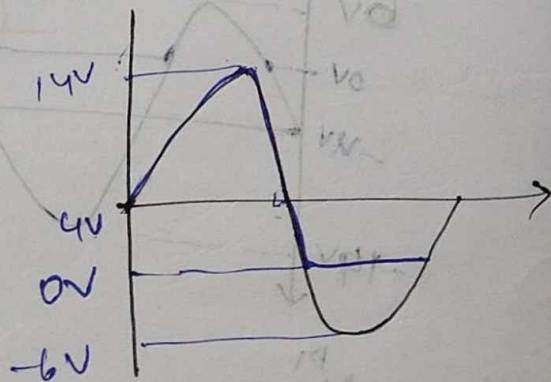
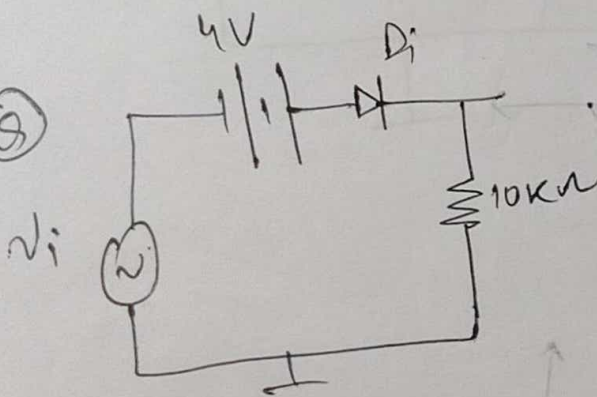


Rectifier Circuits:-

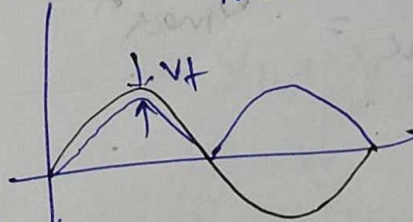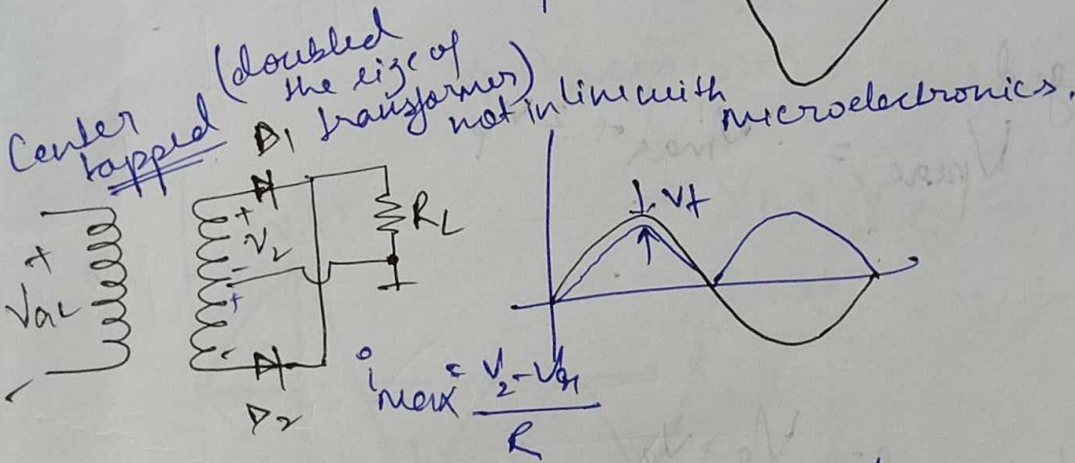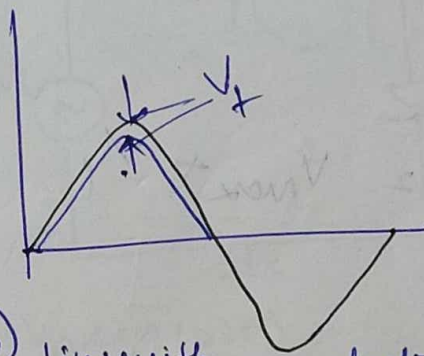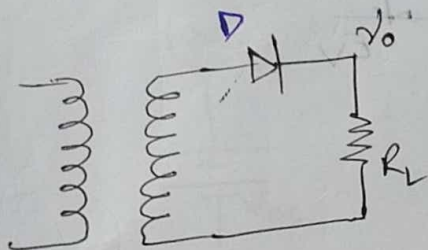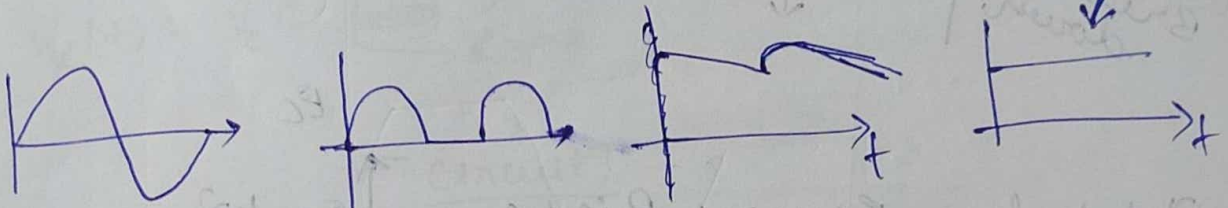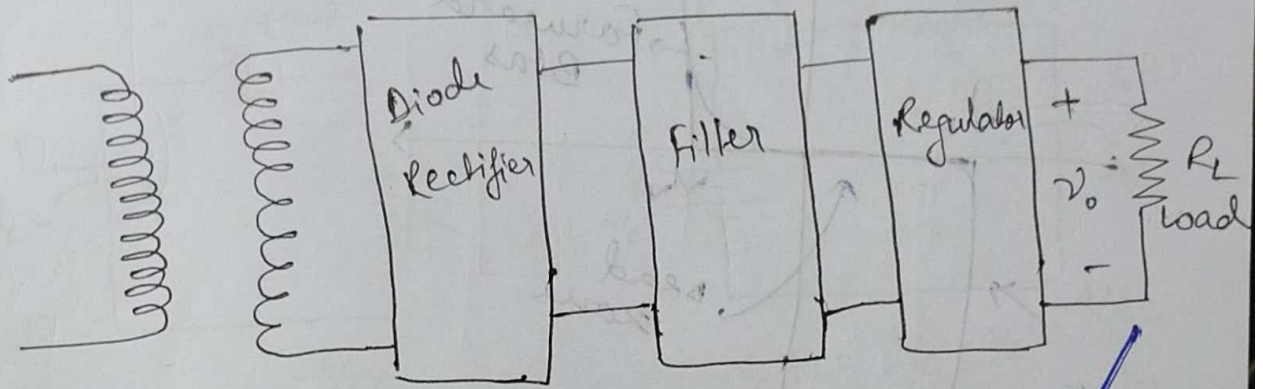


* Peak inverse voltage - $P.I.V \Rightarrow 2V_2 - V_T$

$P.I.V = V_{peak} - V_T$

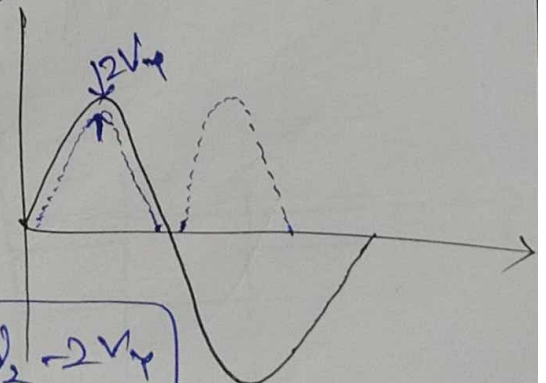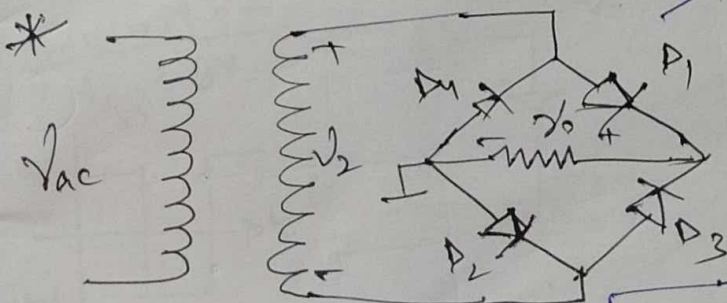


* Bridge Rectifier
$$i_{max} = \frac{V_2 - 2V_T}{R_L}$$

Zener diode has 3 states

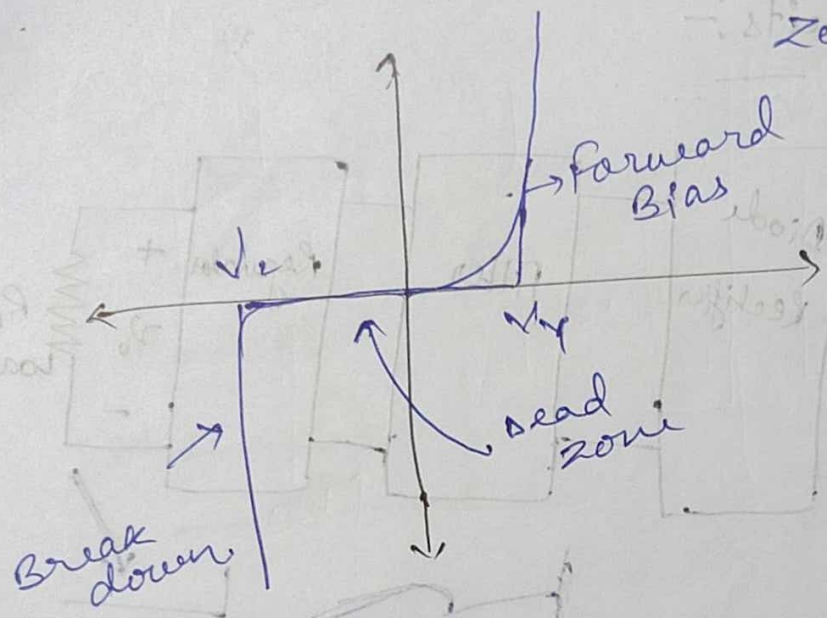

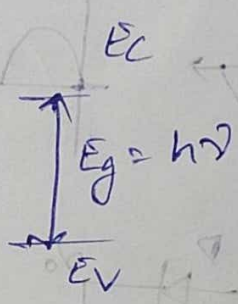
Photodiode - Reverse Bias
LED - Forward Bias




center tap
 $V_{peak} = V_{max} + V_f$

Bridged
 $V_{peak} = V_{max} + 2V_f$


$V_{p(max)} = V_s + V_b$

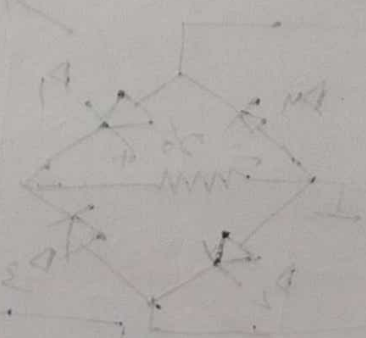


* Clippers *

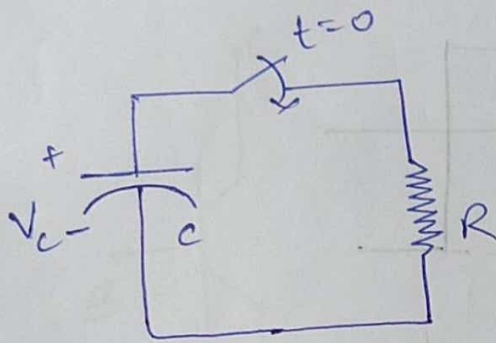


$$V_R(t) = V_C e^{-t/RC} \quad R = \infty$$

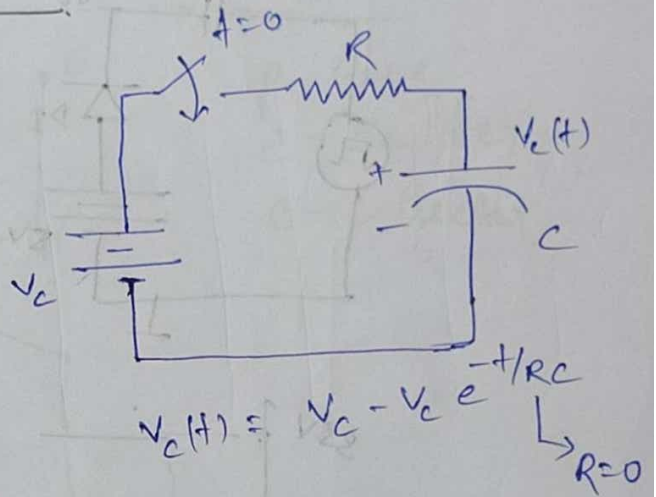

Circuit 1

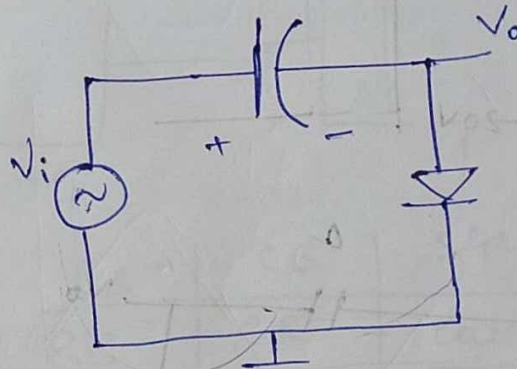




$$V_i = V_A \sin(\omega t)$$

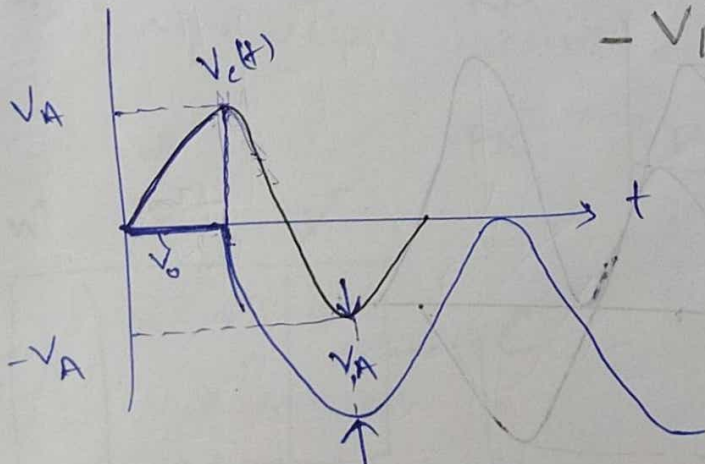



$$-V_i + V_C$$

$$V_C = V_i$$



Circuit-2 $V_{pp} = 8V$

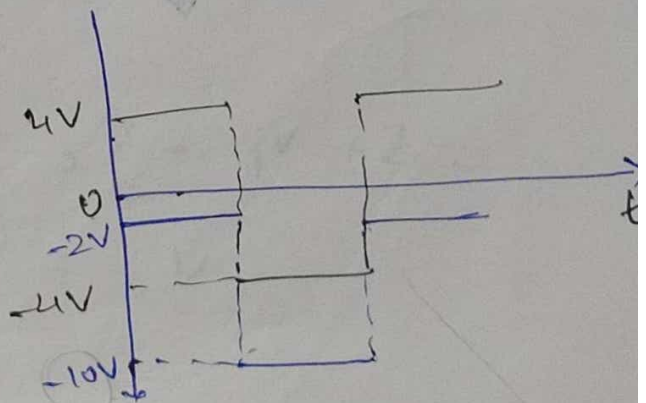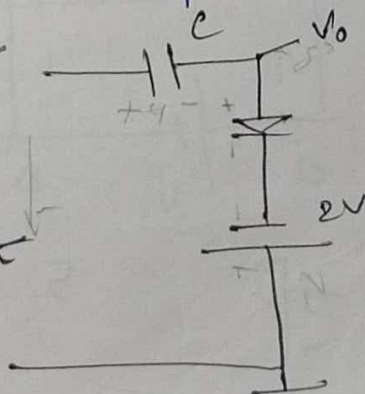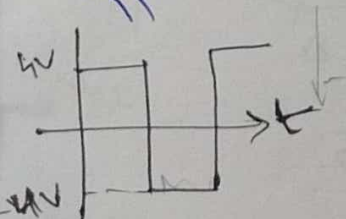

Circuit-3

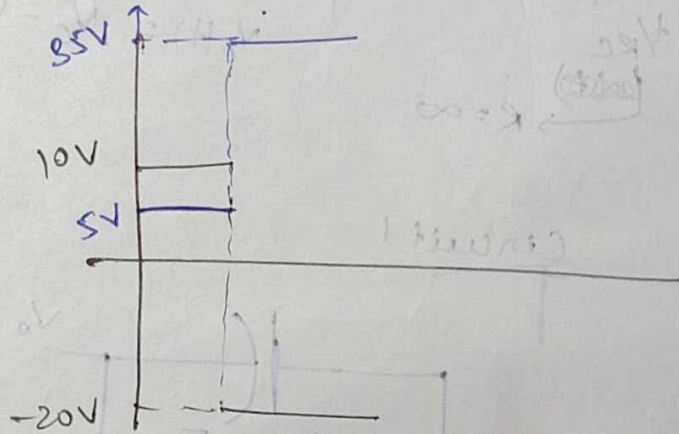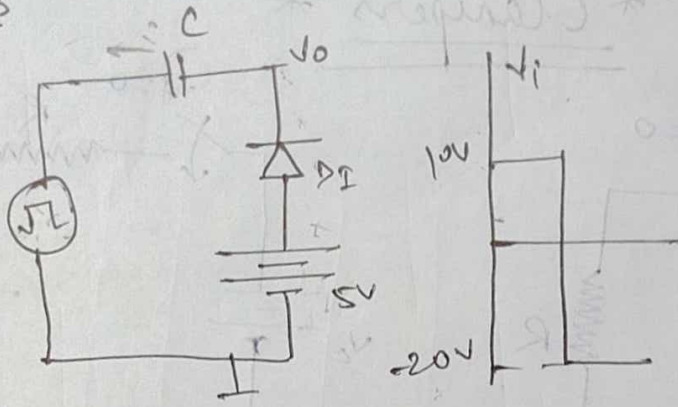



Circuit-4

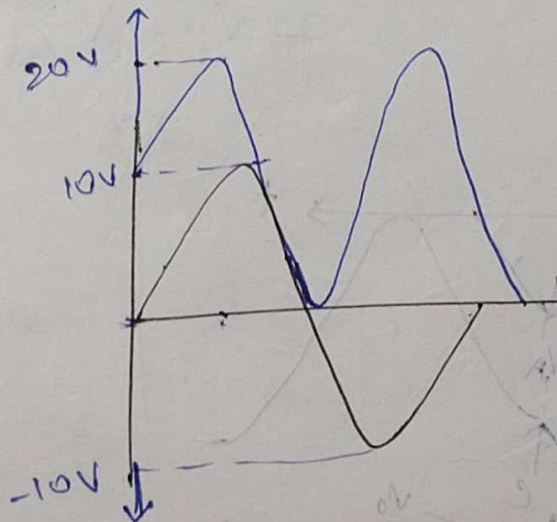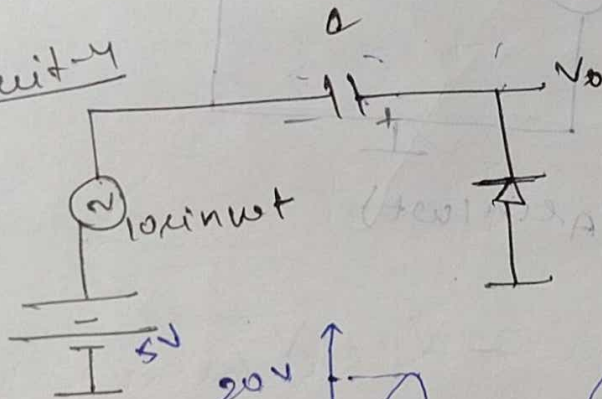



$$-5 + V_i - V_c = 0$$

$$V_c = V_i - 5 = 5$$

* Bipolar Junction Transistors (BJTs)

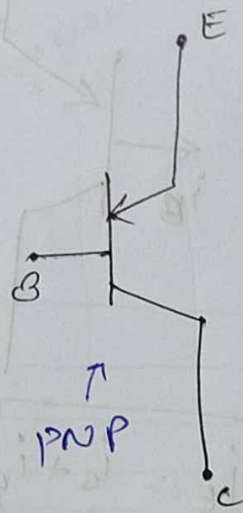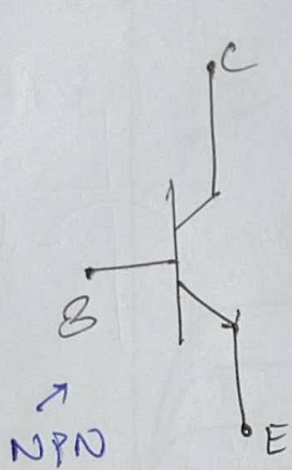




B - Base
E - Emitter
C - Collector

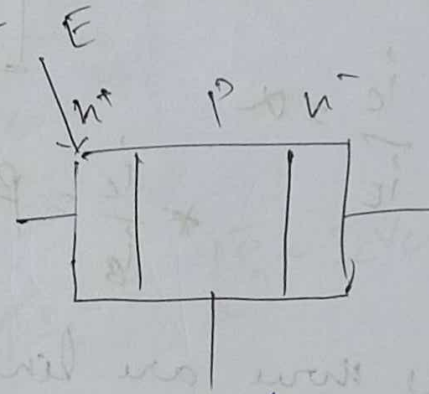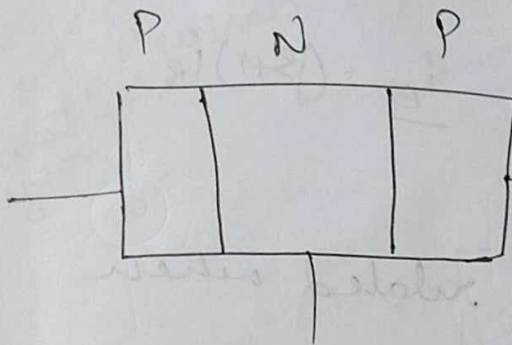

$$I_E = I_{E_{exp}} \left(\frac{V_{BE}}{V_T} \right)$$

EB	CB	SE
RB	RB	cutoff
FB	RB	Forward active region / mode
RB	FB	Reverse active region / mode
FB	FB	Saturation Region

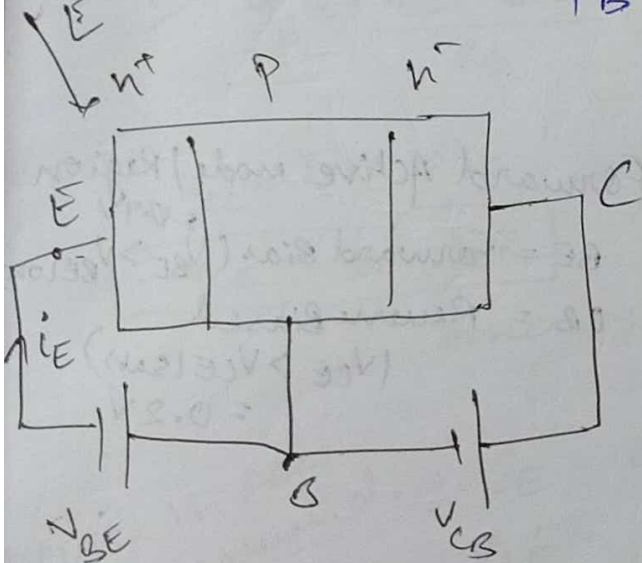

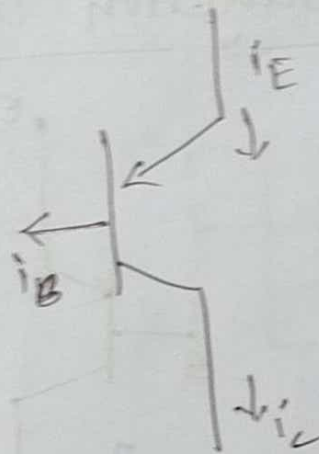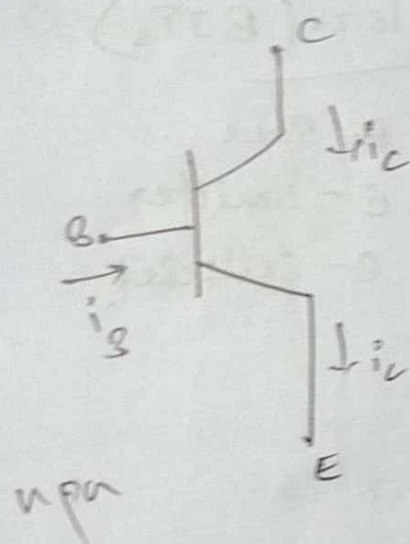

$$i_E = i_C + i_B$$

$$\alpha = \frac{i_C}{i_E}$$

$$\beta = \frac{i_C}{i_B}$$


$$i_E = (\beta + 1) i_B$$

These are linearly related when device in FB.

$$\alpha = \frac{\beta}{\beta + 1}, \quad \beta = \frac{\alpha}{1 - \alpha}$$

We can make faster device using npn BJT than pnp BJT

BJT Characteristics:-

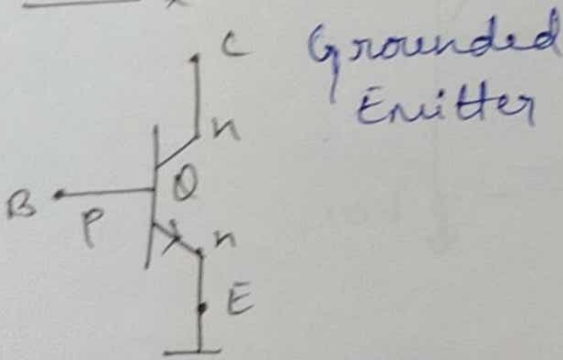

Grounded Emitter

$$V_{BE} > V_{BE(on)} = 0.7V$$


Forward Active mode / Region

BE = Forward Bias ($V_{BE} > V_{BE(on)}$)


CB = Reverse Biased ($V_{CE} > V_{CE(sat)}$)

$$= 0.2V$$

- output characteristics :-

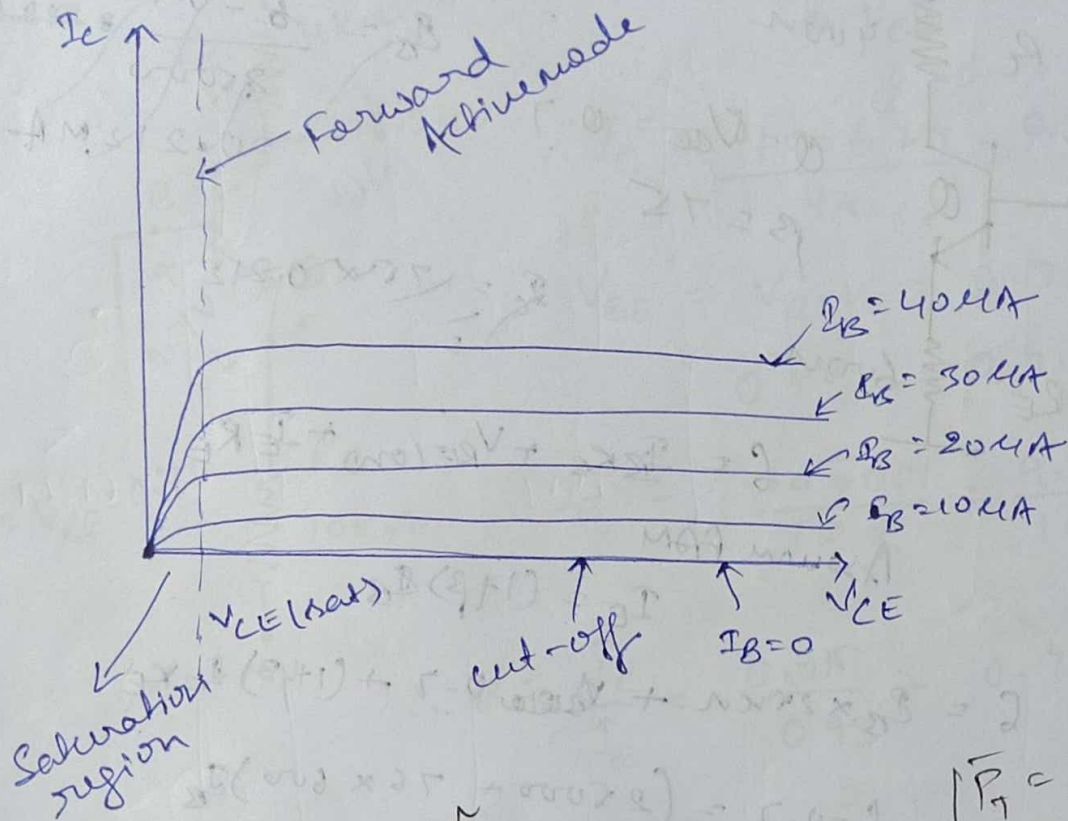

$$P_T = I_C V_{CE}$$

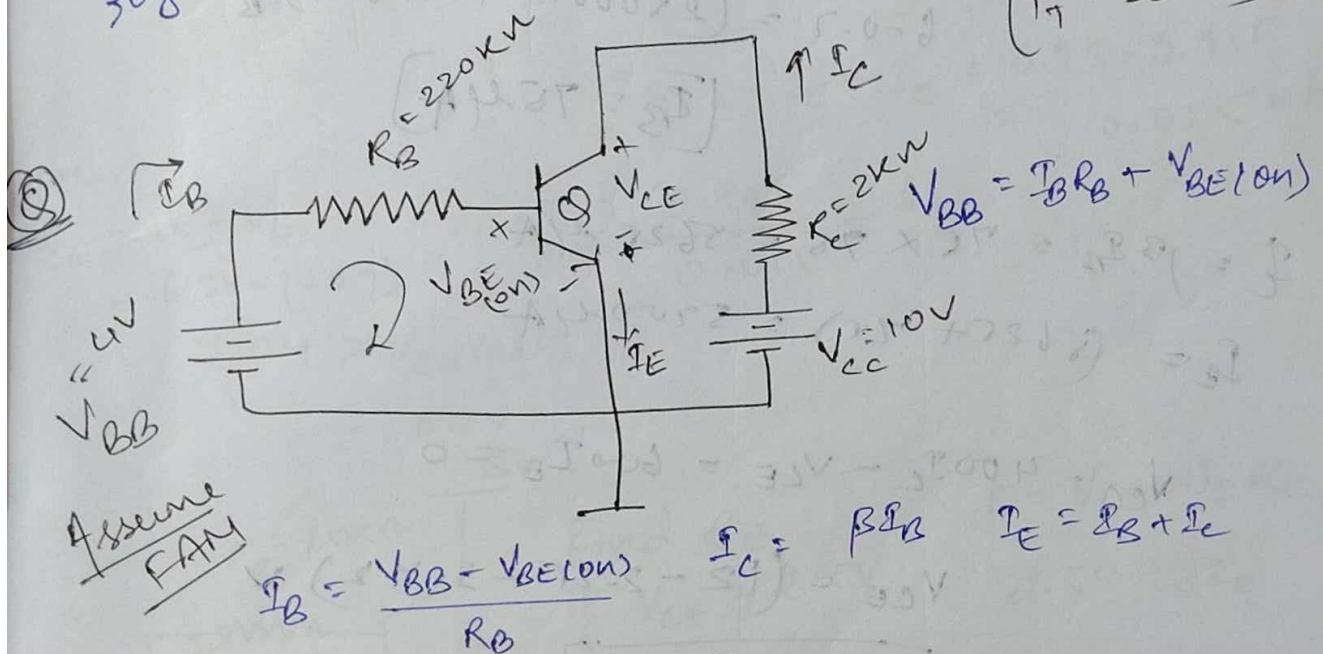

Assume FAM

$$I_B = \frac{V_{BB} - V_{BE(on)}}{R_B}$$

$$I_C = \beta I_B \quad I_E = I_B + I_C$$

now $V_{CC} = I_C R_C + V_{CE}$

$$\therefore V_{CE} = V_{CC} - I_C R_C$$

Assume FAM

$$I_C = 3mA$$


$$I_E = 5.01mA$$

$$V_{CE} = 10 - 3 \times 2 \times 10^{-3} = 4V$$

$$P_T = 12mW$$

Device in FAM
as assumed.

⑧

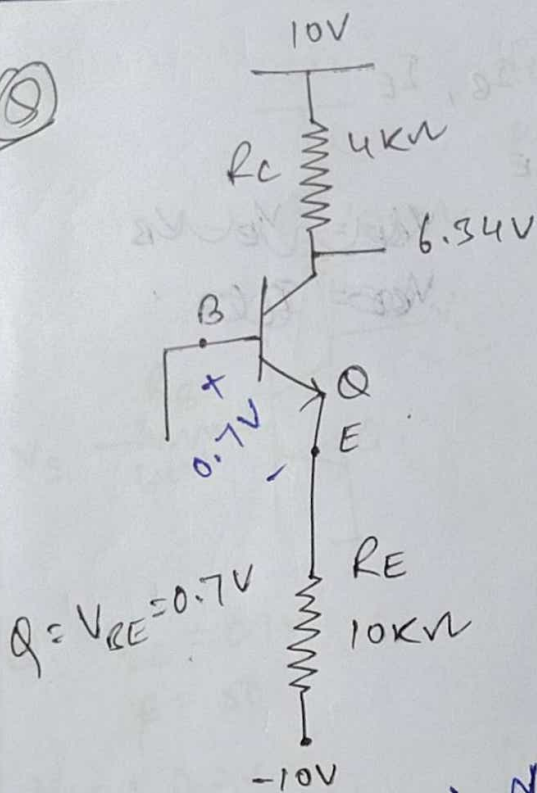

Find I_B, I_C, I_E & V_{CE}

$$I_C = \frac{10 - 6.34}{4k} = 0.915 \text{ mA}$$

$$V_{BE} = V_B - V_E = 0.7 \text{ V}$$

$$0 + V_E = -0.7 \text{ V}$$

$$I_E = \frac{+10 - 0.7}{10k} = \frac{9.3}{10000} = 0.93 \text{ mA}$$

$$\therefore \alpha = \frac{I_C}{I_E} = \frac{0.915}{0.93} = 0.98$$


$$I_B = I_E - I_C = 0.93 - 0.915 = 0.015 \text{ mA}$$

Here

$$V_{CE} = V_C - V_E = 6.34 - (-0.7)$$

$$= 7.04 > V_{CE(\text{sat})}$$

$$= 0.2 \text{ V}$$

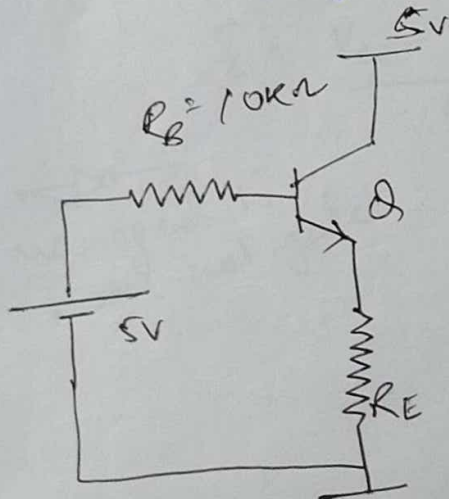

Find R_E
if $V_{CE} = 2.5 \text{ V}$

$$\alpha : \beta = 100$$

$$V_{BE} = 0.7 \text{ V}$$

$$I_E = 10k \times 0.018 = 18.18 \mu\text{A}$$

$$V = V_{CE} + I_E R_E$$

$$2.5 = I_E R_E$$

$$5 = I_B \times 10 + 0.7 + 2.5$$

$$2.5 - 0.7 = I_B \times 10k$$


$$I_B = \frac{1.8}{10k}$$

$$I_B = 0.18 \text{ mA}$$

$$\therefore \frac{2.5}{18.18} = R_E = 0.1375 = 137.5 \Omega$$

Ans

Q

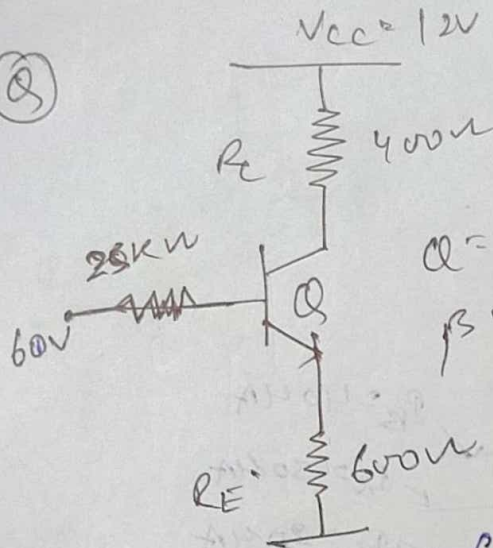

$$I_B = \frac{6 - 0.7}{25000} = 0.212mA$$

$$I_E = 75 \times 0.212$$

$$6 = I_B R_B + V_{BE(ON)} + I_E R_E$$

Assume FAM

$$I_E = (1 + \beta) I_B$$

$$6 = I_B \times 25k\Omega + 0.7 + (1 + \beta) I_B R_E$$

$$6 - 0.7 = (25000 + 76 \times 600) I_B$$

$$[I_B = 754\mu A]$$

$$I_C = \beta I_B = 75 \times 75 = 5625\mu A$$

$$I_E = (5625 + 75) = 5700\mu A$$


$$V_{CC} - 400I_C - V_{CE} - 600I_E = 0$$

$$V_{CE} = (12 - 2.25 - 3.42) V$$

$$[V_{CE} = 6.33 V]$$

*Device in FAM as assumed

Q

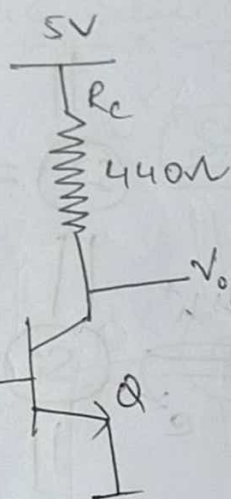

find I_B , I_C & V_o

when


i) $V_i = 0.2V = \text{logic 0}$

ii) $V_i = 3.6V = \text{logic 1}$

Here, i) $V_i = 0.2V$

$I_B = 0$ $I_C = 0$

$V_o = 5V$

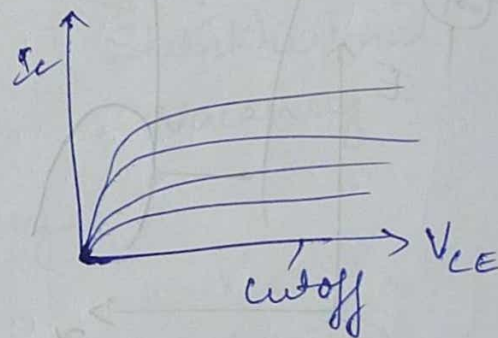

Q: $V_{BE} = 0.7V$

$\beta = 50$

$V_{CE} = 0.2V$

ii) $V_i = 3.6V$

$I_B = \frac{3.6 - 0.7}{640} = 4.53mA$

$I_C = \beta I_B = 0.226A$

$V_o = V_{CC} - I_C R_C = 5 - 0.226 \times 440 = 0.2V$

EB	CB	Mode
FB	RB	PAM
RB	RB	cut-off ←
FB	FB	Saturation
RB	FB	Inverse Active

Saturation

Force $V_{CE} = V_{CE(sat)}$


$I_C = \frac{V_{CC} - V_{CE(sat)}}{R_C} = 10.91mA$

we managed to make not-gate

generation of holes

P-type

holes get recombined with electrons

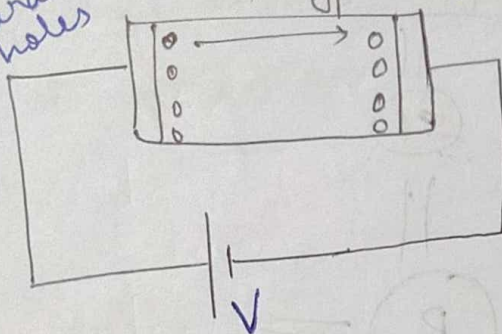

Drift velocity $\rightarrow 400 \text{ cm/s}$

$$v_{\text{drift } p} = \mu_p E$$

mobility

$$\left[\frac{1}{\mu} = \frac{1}{\mu_n} + \frac{1}{\mu_p} \right]$$

$$v_{\text{drift } n} = \mu_n E$$

$$1350 \text{ cm}^2/\text{Vs}$$


$$\left[J_n = q n v_{\text{drift } n} = q n \mu_n E \right]$$

$$\left[J_{p, \text{drift}} = \cancel{q p \mu_p E} q p \mu_p E \right]$$


$$J_{\text{drift}} = J_{n, \text{drift}} + J_{p, \text{drift}}$$

$$= q (n \mu_n + p \mu_p) E \quad (A/\text{cm}^2)$$

Diffusion:-

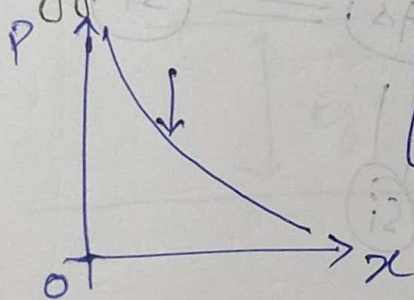
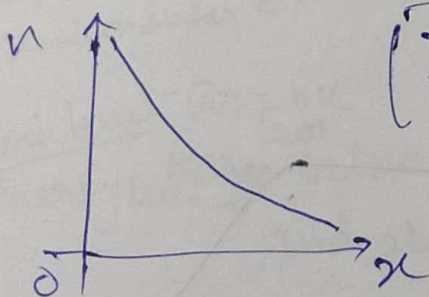
$$\left[J_{\text{diff } p} = -q D_p \frac{dp}{dx} \right]$$





$$\left[J_{\text{diff } n} = q D_n \frac{dn}{dx} \right]$$

$$\left[J = J_{\text{diff}} + J_{\text{drift}} \right]$$

$$\left[\frac{D_n}{\mu_n} = \frac{kT}{q} = \frac{D_p}{\mu_p} \right]$$

Einstein's relation

-(BJT - Biasing) -

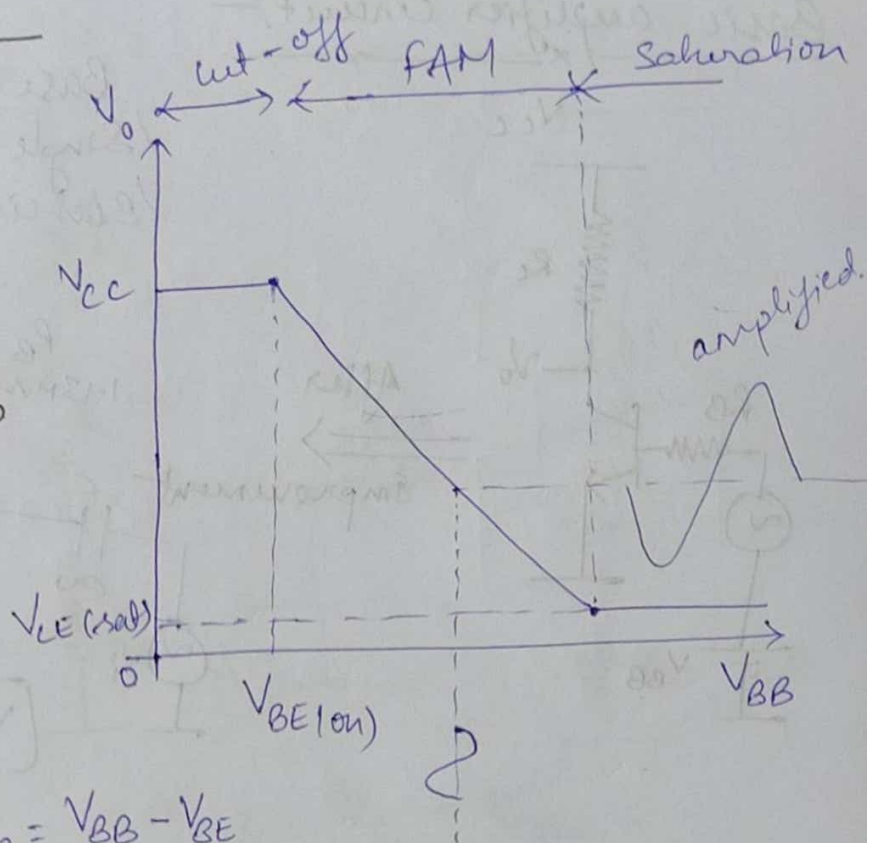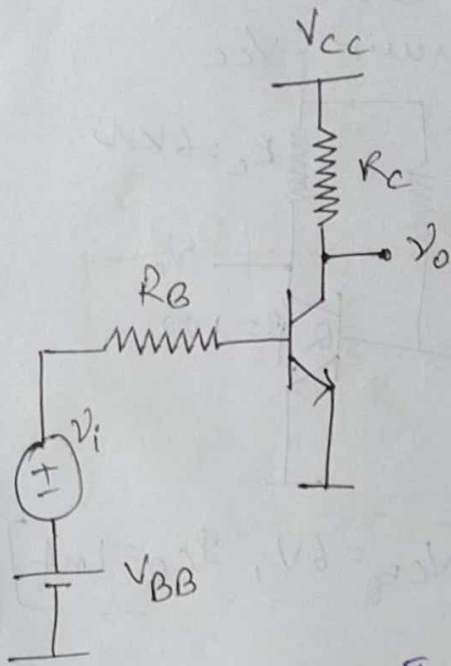


$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

$$I_C = \frac{\beta I_B}{R_B} = \beta \left(\frac{V_{BB} - V_{BE}}{R_B} \right)$$

(V_{CE}, I_C)
 operating point
 Quiescent point

$$V_O = V_{CC} - I_C R_C$$

$$V_O \propto V_{BB}$$

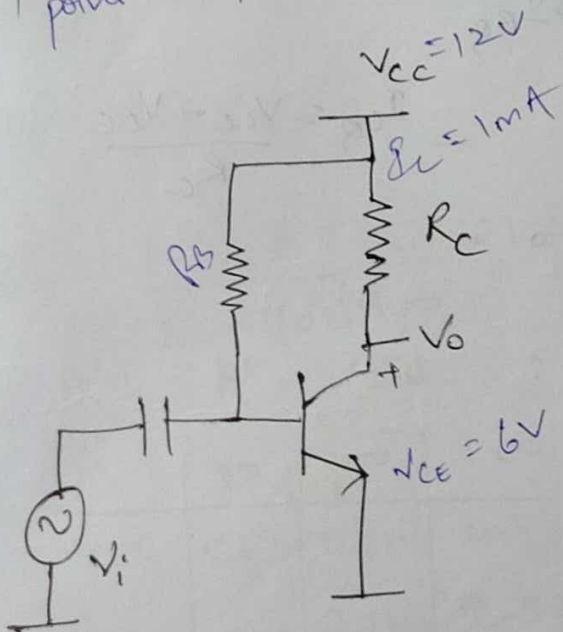


$$I_B = \frac{V_{CC} - V_{BE(on)}}{R_B}$$

$$I_C = \beta I_B$$


$$V_{CE} = V_{CC} - I_C R_C$$

Basic amplifier circuit

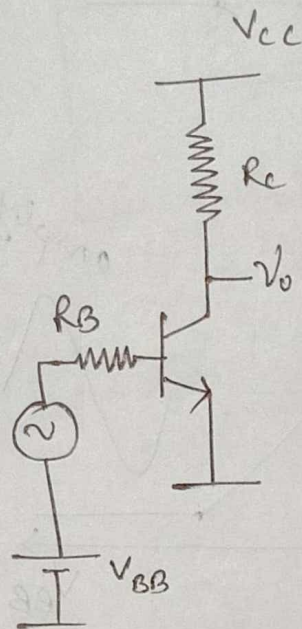

After
Improvement

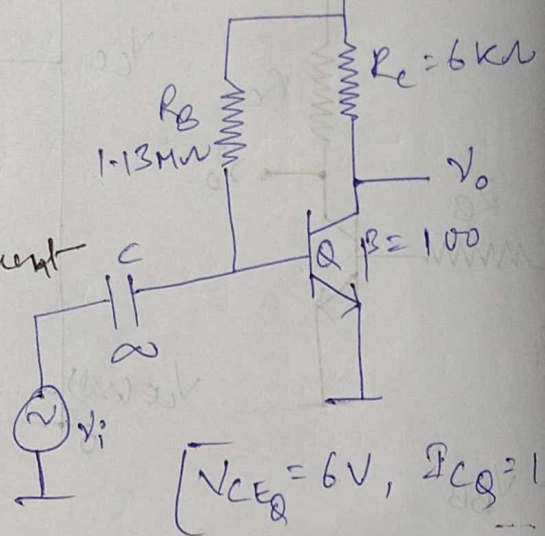Base Bias circuit
/ Single Base Resistor
/ Bias circuit




$$[V_{CEQ} = 6V, I_{CQ} = 1mA]$$

β	50	100	150
V_{CEQ}	9V	6V	3V
I_{CQ}	0.5mA	1mA	1.5mA

$$I_B = \frac{V_{CC} - V_{BE(on)}}{R_B}$$



$$V_{CE} = V_{CC} - I_{CQ} R_C$$
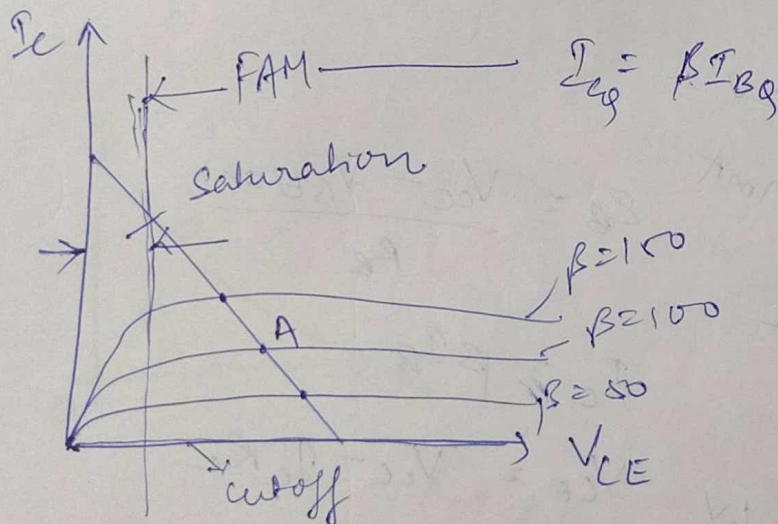
$$I_{BQ} = \frac{V_{CC} - V_{BE(on)}}{R_B} = 104\mu A$$



$$I_{CQ} = \frac{V_{CC} - V_{CE}}{R_C}$$

Voltage divider Bias circuit:-

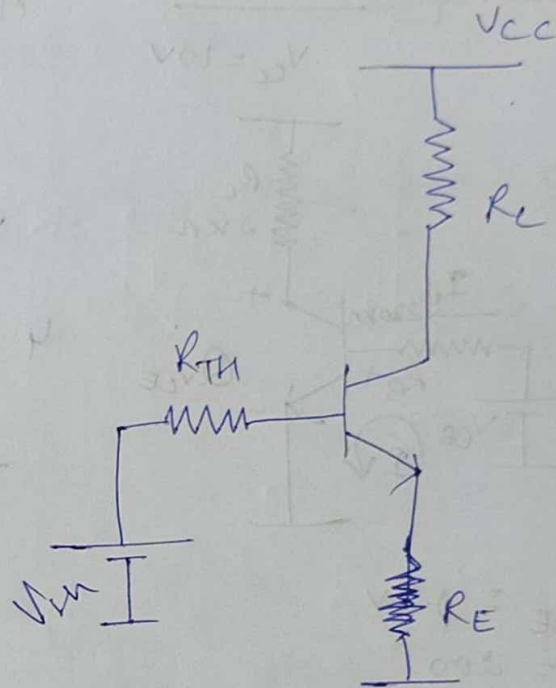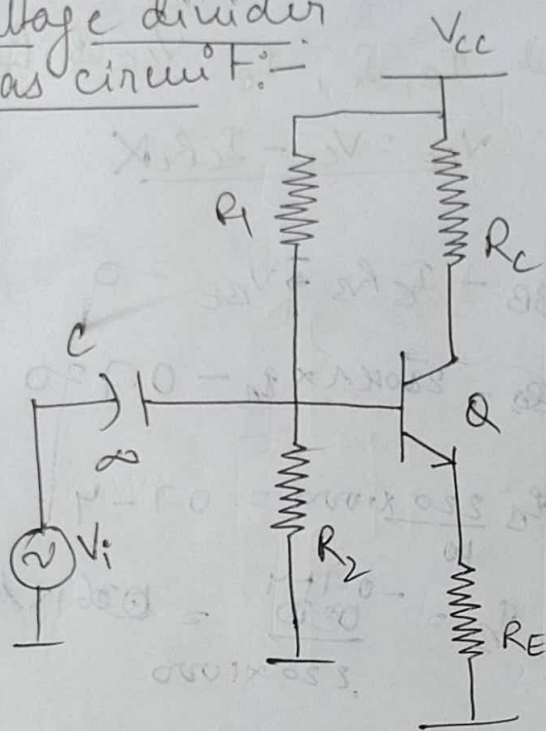

$$R_{TH} = R_1 || R_2$$

$$I_B = \frac{V_{TH} - V_{BE(on)}}{R_{TH} + (1 + \beta)R_E}$$

$$V_{TH} = \frac{V_{CC} R_2}{R_1 + R_2}$$

$$I_{CQ} = \beta I_{BQ}$$

$$V_{CEQ} = V_{CC} - I_{CQ} R_C - I_{EQ} R_E$$

$$R_{TH} = 100 \text{ k}\Omega$$

$$V_{CE} = 10 - I_C R_C - I_E R_E$$

$$\beta = 100$$


$$V_{TH} = 1.7 \text{ V}$$

$$= 10 - (100 \times 21.42 \mu\text{A} \times 2 \text{ k}\Omega) - (1 + \beta) 21.42 \mu\text{A} \times 400$$

$$= 4.85 \text{ V}$$

$$I_B = \frac{1.7 - 0.7}{100 + (101) 400} = 21.42 \mu\text{A}$$


β	80	100	150
V_{CEQ}	5.69	4.81V	4.4
I_{CQ}	1.8mA	2.16mA	2.32mA

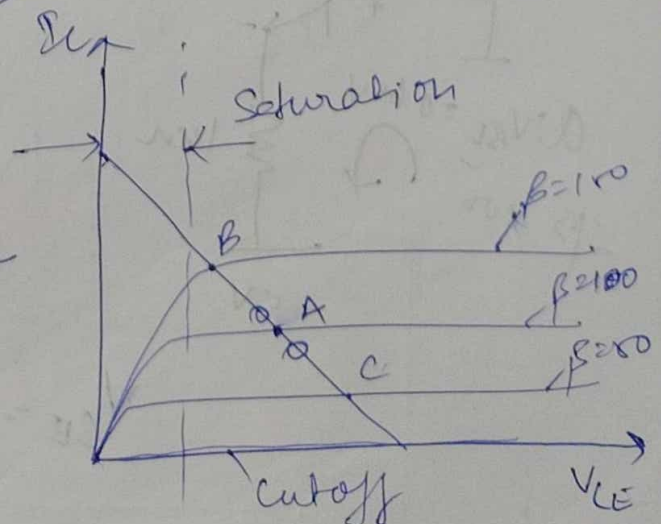

Revision: BJT DC

$$V_{CC} = 10V$$

Q

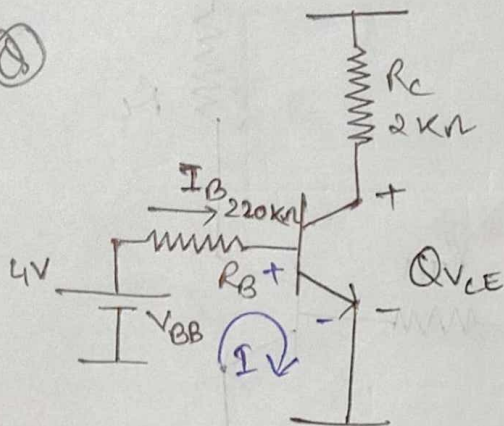

$$V_{BE} = 0.7V$$

$$\beta = 200$$

Find I_B , I_C , I_E , V_{CE} & P_T

$$V_{CE} = V_{CC} - I_C R_C$$

$$V_{BB} - I_B R_B - V_{BE} = 0$$

$$4 - 220k\Omega \times I_B - 0.7 = 0$$

$$-I_B \frac{220 \times 1000}{10} = 0.7 - 4$$

$$I_B = \frac{-0.7 + 4}{220 \times 1000} = 0.015 \text{ mA}$$

$$I_C = \beta I_B$$


$$I_C = 200 \times 0.015 \text{ mA}$$

$$= 3 \text{ mA}$$

$$V_{CE} = 10 - 3 \text{ mA} \times 2k\Omega$$

$$V_{CE} = 4$$

Q

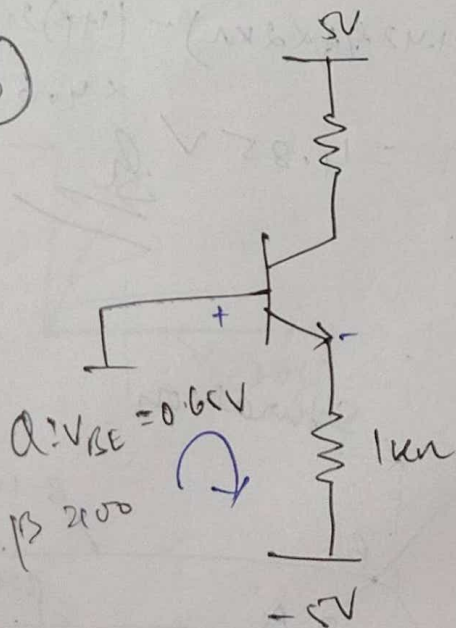

$$V_{BE} = 0.65V$$

$$\beta = 200$$

$$V_{BE} - 0.65 - I_E (1k\Omega) + 5 = 0$$

$$I_E = \frac{5 + 0.65}{1000}$$

$$I_E = 4.31 \text{ mA}$$

$$I_C = 4.31 \text{ mA}$$



$$I_B = 43.1 \mu\text{A}$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E + 5$$


$$5 - 1000 \times 4.31 \text{ mA} - 4.35$$

$$= -4.35 \text{ V}$$

FET-DC

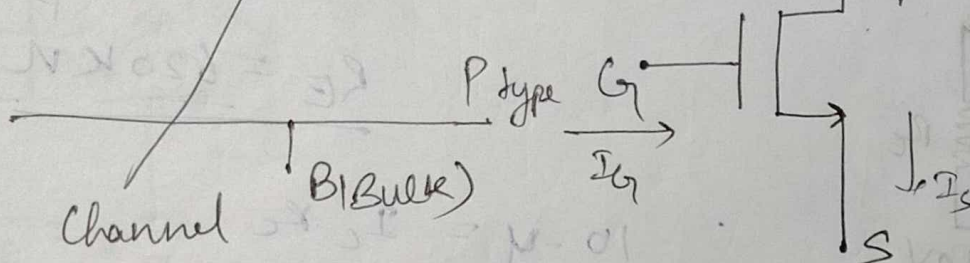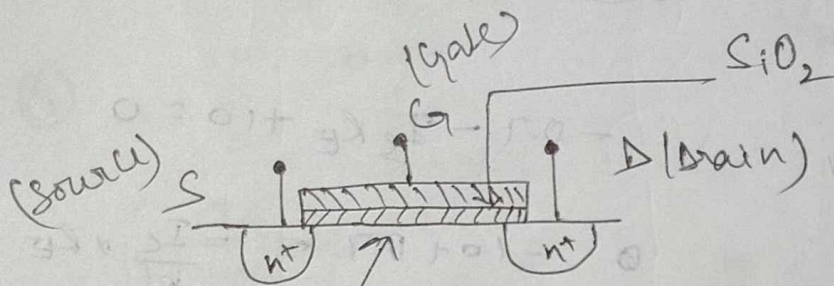

n-channel E-mode MOSFET

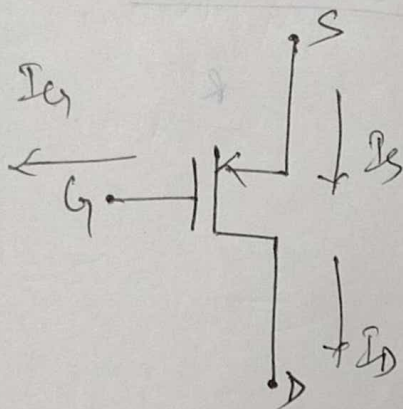

p-channel E-MOSFET


$\mu_n \gg \mu_p$

$I_D = I_S$ (any channel device)


cutoff $V_{GS} > V_{TH}$ (threshold voltage)
 $I_D = 0 \leftarrow$ cutoff

Triode Region $\begin{cases} V_{GS} > V_{TH}; V_{DS} \leq V_{GS} - V_{TH} \\ I_D = K_n [2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2] \end{cases}$

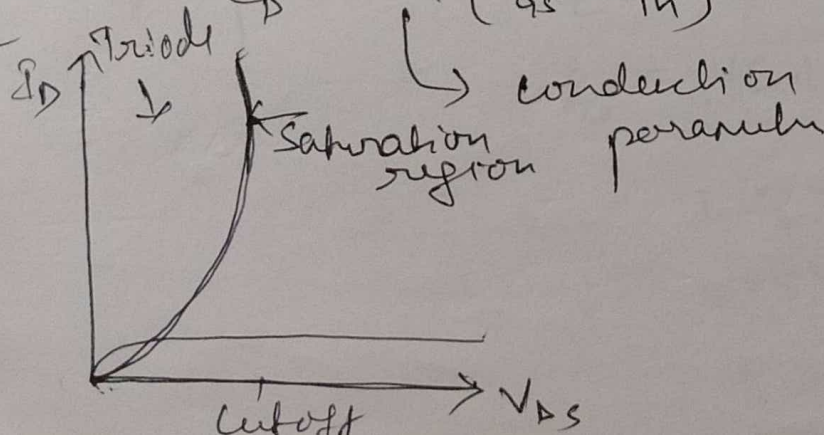Saturation region $\begin{cases} V_{GS} > V_{TH}; V_{DS} \geq V_{GS} - V_{TH} \end{cases} \xrightarrow{\text{condition for saturation}} I_D = K_n (V_{GS} - V_{TH})^2$



~~*~~

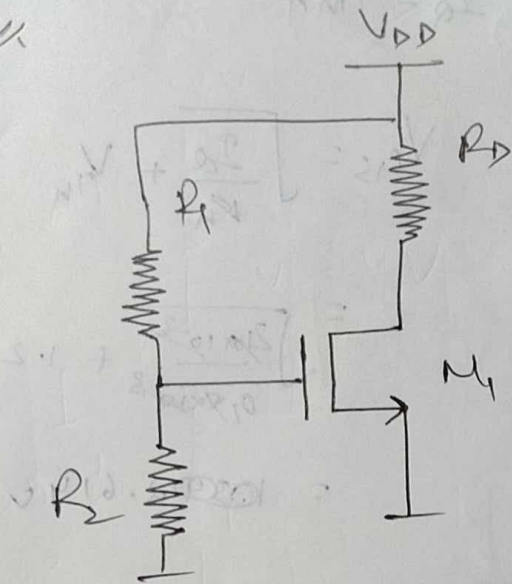

$$* V_{G1} = \frac{V_{DD} R_2}{R_1 + R_2} = V_{GS}$$

$$* I_D = K_n (V_{GS} - V_{TH})^2$$

$$* V_{DD} - I_D R_D = V_{DS}$$

$$* P_T = V_{DS} I_D$$

⑧

$$V_{TH} = 1V$$

$$K_n = 0.1 mA/V^2$$

$$V_{DD} = 5V$$

$$R_D = 20k\Omega$$

$$R_1 = 30k\Omega \quad R_2 = 20k\Omega$$

$V_{GS} = 2V$
 $V_{DS} = 3V$
 $V_{DS} = 3V$
 $V_{DS} = 3V$
 $V_{DS} = 3V$
 $V_{DS} = 3V$

$I_D = 0.02mA$
 $I_D = 0.02mA$
 $I_D = 0.02mA$
 $I_D = 0.02mA$
 $I_D = 0.02mA$
 $I_D = 0.02mA$
 $I_D = 0.02mA$
 $I_D = 0.02mA$
 $I_D = 0.02mA$
 $I_D = 0.02mA$

