



School of Electronics Engineering

CAT II

Programme Name & Branch: B.Tech - ECE

Circuit Theory (BECE 203L)

Winter Semester 22-23


Slot: D2+TD2+TDD2

Exam Duration: 90 mins

Maximum Marks: 50

Answer all the questions

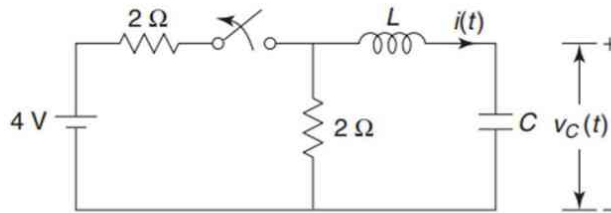
- Q1. The switch in the network of Figure 1 is opened at $t = 0$. Find $i(t)$ for $t > 0$, if $L = \frac{1}{2} H$ and $C = 1 F$.



10 M

Figure 1

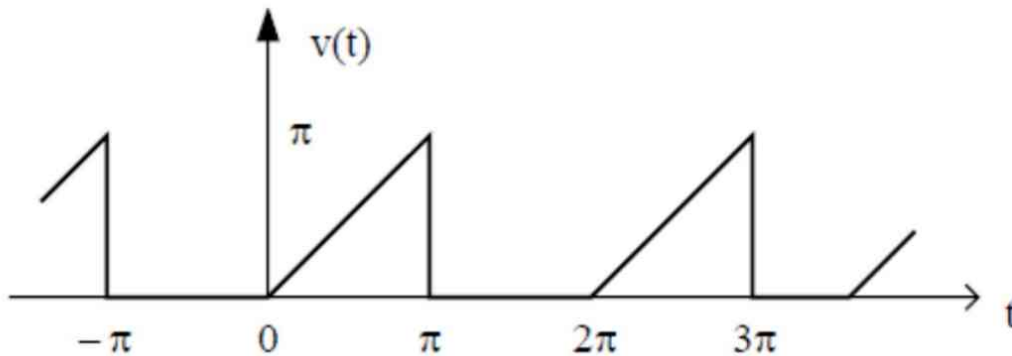
- Q2. Find the trigonometric Fourier series of the periodic waveform in Figure 2.



10 M

Figure 2

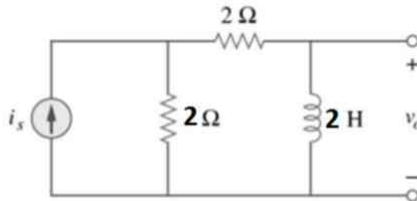
- Q3. Let $i_s(t) = 2 + \sum_{k=1}^{\infty} \frac{4}{n\pi} \sin(n\pi t)$, $n = 2k - 1$ is applied to the circuit in Figure 3. Find v_o using Fourier series approach.



10 M

Figure 3

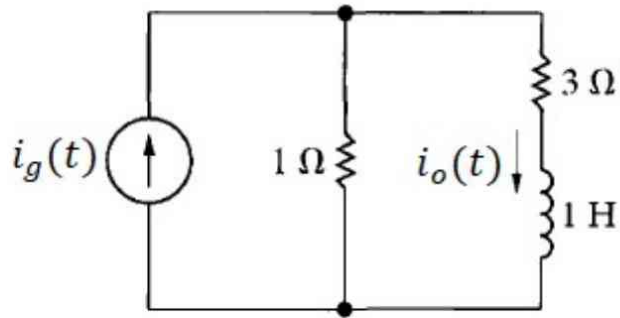
- Q4. Use the Fourier transform to find $i_o(t)$ in the circuit shown in Figure 4. The current source $i_g(t)$ is the signum function $20 \operatorname{sgn}(t)$ A.



10 M

Figure 4

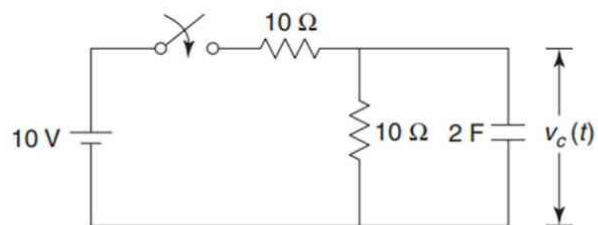- Q5. The switch in the network shown in Figure 5 is closed at $t = 0$. Determine the voltage across the capacitor using Laplace transform. Assume zero initial conditions.



10 M

Figure 5

Question 1

Solution At $t = 0^-$, the network has attained steady-state condition. Hence, the inductor acts as a short circuit and the capacitor acts as an open circuit.

$$v_C(0^-) = 4 \times \frac{2}{2+2} = 2 \text{ V}$$

$$i(0^-) = 0$$

Since current through the inductor and voltage across the capacitor cannot change instantaneously,

$$v_C(0^+) = 2 \text{ V}$$

$$i(0^+) = 0$$

Case I When $R = 2 \Omega$, $L = \frac{1}{2} \text{ H}$, $C = 1 \text{ F}$

$$\alpha = \frac{R}{2L} = \frac{2}{2 \times \frac{1}{2}} = 2$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{1}{2} \times 1}} = \frac{1}{\sqrt{0.5}} = 1.414$$

$$\alpha > \omega_0$$

This indicates an overdamped case.

$$i(t) = A_1 e^{s_1 t} - A_2 e^{s_2 t}$$

where,

$$s_1 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -2 - \sqrt{4 - 2} = -2 - \sqrt{2} = -3.414$$

and

$$s_2 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -2 + \sqrt{2} = -0.586$$

$$i(t) = k_1 e^{-3.414t} + k_2 e^{-0.586t}$$

At $t = 0$, $i(0) = 0$

$$k_1 + k_2 = 0 \quad \dots(i)$$

Also $v_L(0^+) + v_C(0^+) + v_R(0^+) = 0$

$$v_L(0^+) = -v_R(0^+) - v_C(0^+) = -2i(0^+) - v_C(0^+) = -2 \text{ V} \quad \dots(ii)$$

$$v_L(0^+) = L \frac{di}{dt}(0^+)$$

$$\frac{di}{dt}(0^+) = \frac{v_L(0^+)}{L} = -\frac{2}{0.5} = -4 \text{ A/s}$$

Differentiating the equation of $i(t)$ and putting the condition at $t = 0$,

$$-3.414 k_1 - 0.586 k_2 = -4 \quad \dots(iii)$$

Solving Eqs (i) and (iii), we get

$$k_1 = 1.414 \quad \text{and} \quad k_2 = -1.414$$

$$i(t) = 1.414(e^{-3.414t} - e^{-0.586t}) \quad \text{for } t > 0$$

Question 2

Since the waveform does not exhibit any symmetry, we will have to determine the coefficients a_0 , a_n and b_n . The a_0 coefficient is

$$a_0 = \frac{1}{2\pi} \int_{-\pi}^{\pi} v(t) dt$$

where, of course, $v(t) = t$ in the interval $0 \leq t \leq \pi$ and zero elsewhere and $\omega_0 = \frac{2\pi}{T}$

$$\begin{aligned} a_0 &= \frac{1}{2\pi} \int_0^{\pi} t dt \\ &= \frac{1}{2\pi} \left(\frac{t^2}{2} \right) \Big|_0^{\pi} = \frac{\pi}{4} \end{aligned} \quad a_0 = \pi/4$$

The a_n coefficient is

$$a_n = \frac{2}{2\pi} \int_0^{\pi} t \cos nt dt$$

Using a table of integrals, we find that

$$a_n = \frac{1}{\pi} \left[\frac{1}{n^2} \cos nt + \frac{1}{n} t \sin nt \right]_0^{\pi}$$

The second term is zero at $t = \pi$ and 0 and the first term can be written as

$$a_n = \frac{1}{\pi n^2} [(-1)^n - 1]$$

since the cosine term will be +1 or -1 depending upon the value of n . Thus

$$a_n = \frac{(-1)^n - 1}{\pi n^2}$$

In addition,

$$b_n = \frac{2}{2\pi} \int_0^{\pi} t \sin t dt$$

Once again, using a set of integral tables we find that

$$b_n = \frac{1}{\pi} \left[\frac{1}{n^2} \sin nt - \frac{1}{n} t \cos nt \right]_0^{\pi}$$


The first term will be zero at each limit, but the second term is nonzero at the upper and thus

$$\begin{aligned} b_n &= \frac{-\pi}{n\pi} (-1)^n \\ &= \frac{-(-1)^n}{n} \end{aligned}$$

Therefore, the Fourier series expansion is

$$v(t) = \frac{\pi}{4} + \sum_{n=1}^{\infty} \left[\frac{(-1)^n - 1}{\pi n^2} \cos nt - \frac{(-1)^n}{n} \sin nt \right]$$

Question 3

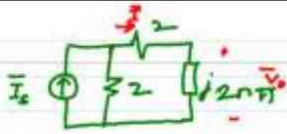

$$\bar{I} = \frac{\bar{I}_s(2)}{4 + j2n\pi}$$

$$\bar{V}_o = j2n\pi \bar{I}$$

$$\bar{V}_o = \frac{j2n\pi \bar{I}_s(2)}{4 + j2n\pi} = \frac{j4n\pi \bar{I}_s}{4 + j2n\pi} \rightarrow 2(2 + jn\pi)$$

DC $n=0$ $\bar{I}_s = 2$

$$\bar{V}_o = 0$$

n^{th} harmonic, $n \geq 1$

$$\bar{I}_s = \frac{4}{n\pi} \angle -90^\circ$$

$$\bar{V}_o = \frac{\bar{I}_s 4n\pi \angle 90^\circ}{2\sqrt{4+n^2\pi^2} \angle \tan^{-1}\left(\frac{n\pi}{2}\right)}$$

$$\bar{V}_o = \frac{\left(\frac{4}{n\pi} \angle -90^\circ\right) 4n\pi \angle 90^\circ}{2\sqrt{4+n^2\pi^2} \angle \tan^{-1}\left(\frac{n\pi}{2}\right)}$$

$$= \frac{8}{\sqrt{4+n^2\pi^2}} \angle -\tan^{-1}\left(\frac{n\pi}{2}\right)$$

$$V_o(t) = \sum_{k=1}^{\infty} \frac{8}{\sqrt{4+n^2\pi^2}} \cos(n\pi t - \tan^{-1}\left(\frac{n\pi}{2}\right)),$$

$n = 2k-1$

Question 4

The Fourier transform of the driving source is

$$\begin{aligned} I_g(\omega) &= \mathcal{F}\{20 \operatorname{sgn}(t)\} \\ &= 20 \left(\frac{2}{j\omega} \right) \\ &= \frac{40}{j\omega}. \end{aligned}$$

The transfer function of the circuit is the ratio of I_o to I_g ; so

$$H(\omega) = \frac{I_o}{I_g} = \frac{1}{4 + j\omega}.$$

The Fourier transform of $i_o(t)$ is

$$\begin{aligned} I_o(\omega) &= I_g(\omega)H(\omega) \\ &= \frac{40}{j\omega(4 + j\omega)}. \end{aligned}$$

Expanding $I_o(\omega)$ into a sum of partial fractions yields

$$I_o(\omega) = \frac{K_1}{j\omega} + \frac{K_2}{4 + j\omega}.$$

Evaluating K_1 and K_2 gives

$$\begin{aligned} K_1 &= \frac{40}{4} = 10, \\ K_2 &= \frac{40}{-4} = -10. \end{aligned}$$

Therefore

$$I_o(\omega) = \frac{10}{j\omega} - \frac{10}{4 + j\omega}.$$

The response is

$$\begin{aligned} i_o(t) &= \mathcal{F}^{-1}[I_o(\omega)] \\ &= 5 \operatorname{sgn}(t) - 10e^{-4t}u(t). \end{aligned}$$

Question 5

Solution At $t = 0^-$, the capacitor is uncharged.

$$v_c(0^-) = 0$$

Since the voltage across the capacitor cannot change instantaneously,

$$v_c(0^+) = 0$$

For $t > 0$, the transformed network is shown in Fig. 7.35.

Applying KCL at the node for $t > 0$,

$$\frac{V_c(s) - \frac{10}{s}}{10} + \frac{V_c(s)}{10} + \frac{V_c(s)}{\frac{1}{2s}} = 0$$

$$2sV_c(s) + 0.2V_c(s) = \frac{1}{s}$$

$$V_c(s) = \frac{1}{s(2s+0.2)} = \frac{0.5}{s(s+0.1)}$$

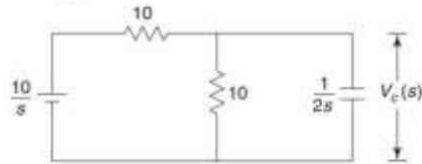


Fig. 7.35

By partial-fraction expansion,

$$V_c(s) = \frac{A}{s} + \frac{B}{s+0.1}$$

$$A = sV_c(s) \Big|_{s=0} = \frac{0.5}{s+0.1} \Big|_{s=0} = \frac{0.5}{0.1} = 5$$

$$B = (s+0.1)V_c(s) \Big|_{s=-0.1} = \frac{0.5}{s} \Big|_{s=-0.1} = -\frac{0.5}{0.1} = -5$$

$$V_c(s) = \frac{5}{s} - \frac{5}{s+0.1}$$

Taking inverse Laplace transform,

$$v_c(t) = 5 - 5e^{-0.1t} \quad \text{for } t > 0$$