

Applications of Linear Differential Equations with Constant Coeff's. (LDWCC) (1)

Electrical circuit

The formation of Differential Equation for an electric circuit depends upon the following laws.

(i) $i = \frac{dq}{dt}$

(ii) Voltage drop across resistance (R) = Ri

(iii) Voltage drop across inductance (L) = $L \frac{di}{dt}$


(iv) Voltage drop across Capacitance (C) = $\frac{q}{C}$

Kirchoff's Law

Voltage Law : The algebraic sum of the voltage drop around any closed circuit is equal to the resultant electromotive force in the circuit.


Current Law ; At a junction (or) nodes,
Current coming is equal to current going.

L-R Series circuit

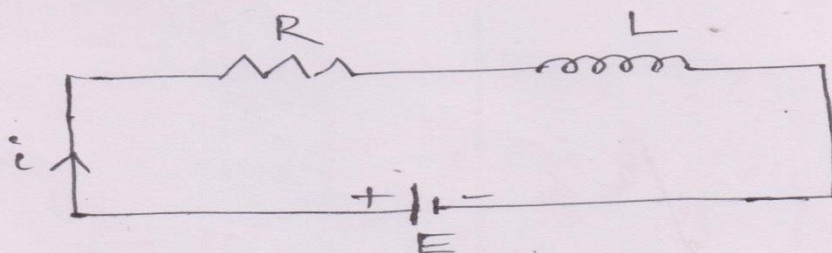

by voltage law, $Ri + L \frac{di}{dt} = E$

L-R-C circuit

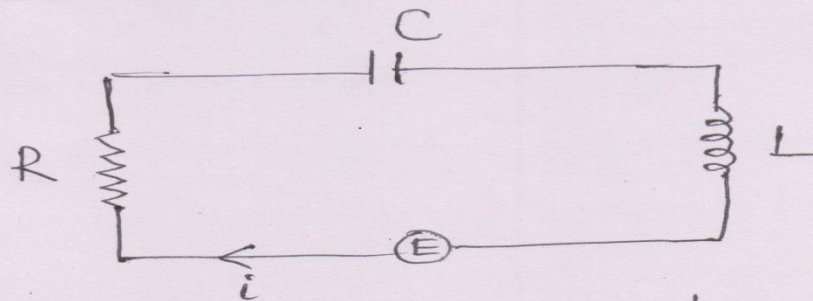

by voltage law, $Ri + L \frac{di}{dt} + \frac{q}{C} = E$

(or) $L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{q}{C} = E$ ($\because i = \frac{dq}{dt}$)

① An electric circuit consists of an inductance 0.1 henry, a resistance of 20 ohms and a Condenser of capacitance 25 micro-farads. Find the charge q and the current i at any time 't', given that at $t=0$, $q=0.05$ coulomb, $i=0$ when $t=0$

③

Sol: Given $L = 0.1 \text{ h}$, $R = 20 \text{ } \Omega$,
 $C = 25 \text{ m.f} = 25 \times 10^{-6} \text{ farad}$

The D.E. for the given data is

$$L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{q}{C} = 0 \quad \text{--- ①}$$

It's operator form is $\left[D^2 + \left(\frac{R}{L}\right)D + \frac{1}{LC} \right] q = 0$ --- ②

$$\text{(or)} \left[D^2 + \left(\frac{20}{0.1}\right)D + \frac{1}{(0.1)(25 \times 10^{-6})} \right] q = 0$$

$$\text{Clearly } q_c = e^{-100t} \left[C_1 \cos(100\sqrt{39}t) + C_2 \sin(100\sqrt{39}t) \right]$$

$$\therefore q = q_c = e^{-100t} \left[C_1 \cos(100\sqrt{39}t) + C_2 \sin(100\sqrt{39}t) \right]$$

When $t=0$; $q=0.05$ & $i=0$, then $C_1 = 0.05$
 $C_2 = 0.008$

$$\therefore q = e^{-100t} \left[0.05 \cos(624.5t) + 0.08 \sin(624.5t) \right]$$

(2) An inductor of 2 henries, resistor of 16 ohms and capacitor of 0.02 farads are connected in series with a battery of electromotive force $E = 100 \sin 3t$. At $t=0$, the charge on the capacitor and current in the circuit are zero. Find the charge and current. (4)

Sol: Given $L = 2 \text{ h}$; $R = 16 \Omega$; $C = 0.02 \text{ farad}$
 $E = 100 \sin 3t$.

The D.E. for the given data is

$$L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{q}{C} = E$$

(or) It's operator form is $\left[D^2 + \frac{R}{L} D + \frac{1}{LC} \right] q = \frac{E}{L}$ (1)

$$(or) \left[D^2 + \left(\frac{16}{2} \right) D + \left(\frac{1}{2 \times 0.02} \right) \right] q = \frac{100 \sin 3t}{2}$$

Clearly $q_c = e^{-4t} [C_1 \cos 3t + C_2 \sin 3t]$

$$q_p = \frac{25}{52} [2 \sin 3t - 3 \cos 3t]$$

$$\therefore q = q_c + q_p = e^{-4t} [C_1 \cos 3t + C_2 \sin 3t] + \frac{25}{52} [2 \sin 3t - 3 \cos 3t]$$

(5)

$$\begin{aligned}
 i = \frac{dq}{dt} &= -4e^{-4t}(C_1 \cos 3t + C_2 \sin 3t) \\
 &\quad - 3e^{-4t}(C_1 \sin 3t - C_2 \cos 3t) \\
 &\quad + \frac{25}{52}(6 \cos 3t + 9 \sin 3t)
 \end{aligned}$$

when $t=0$, $q=0$ & $i=0$

$$\therefore C_1 = 75/52 \quad ; \quad C_2 = 50/52$$

$$\begin{aligned}
 \therefore q &= \frac{25}{52} e^{-4t} [3 \cos 3t + 2 \sin 3t] \\
 &\quad + \frac{25}{52} [2 \sin 3t - 3 \cos 3t]
 \end{aligned}$$

$$\begin{aligned}
 i &= \frac{75}{52} [2 \cos 3t + 3 \sin 3t] \\
 &\quad - \frac{25}{52} e^{-4t} [17 \sin 3t + 6 \cos 3t]
 \end{aligned}$$

Exercise :-

(6)

- ① For an electric circuit with $L = 0.05$ henry, $R = 20$ ohms and $C = 100 \times 10^{-6}$ farad, the applied e.m.f is 100 volts. prove that the charge q at time 't' is given by

$$q(t) = 0.01 - e^{-200t} [0.01 \cos(400t) + 0.02 \sin(400t)]$$

if initially $q=0$ and $i=0$

- ② An alternating E.M.F $E \sin pt$ is applied to a circuit at $t=0$. Given the equation for the current i as $L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = pE \cos pt$. Find the current i when $CR^2 > 4L$.