



BEEE203L

CIRCUIT THEORY

DR. P. VIJAYAPRIYA
PROFESSOR/ SELECT

MODULE – VII

TWO PORT NETWORKS

Contents

- ▶ Open circuit impedance parameters
- ▶ Short circuit admittance parameters
- ▶ Transmission parameters
- ▶ Hybrid parameters
- ▶ Relationship between parameter sets
- ▶ Interconnection of two port networks

Interconnection of 2-port networks

4


- ▶ There are various types of interconnections possible for two-port networks, namely, cascade, parallel, series, series-parallel and parallel-series.
- ▶ We will concentrate on the relation between the input and output quantities of the cascaded, series and parallel two-port networks only.

Cascaded connection

5

In the cascade connection, the output port of the first network becomes the input port of the second network. Since it is assumed that input and output currents are positive when they enter the network, we have

$$I_1' = -I_2$$

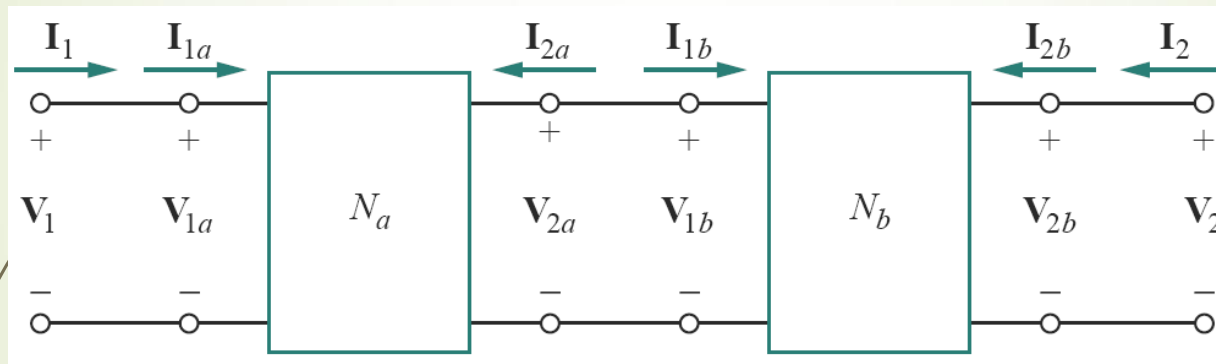

The ABCD parameters for the two networks are

$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix}$$

$$\begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix} = \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

6

From the diagram, $V_{1b} = V_{2a}$ and $I_1' = -I_2$, Substituting this in the matrix we get

$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_1 \end{bmatrix} = \begin{bmatrix} \mathbf{V}_{1a} \\ \mathbf{I}_{1a} \end{bmatrix}, \quad \begin{bmatrix} \mathbf{V}_{2a} \\ -\mathbf{I}_{2a} \end{bmatrix} = \begin{bmatrix} \mathbf{V}_{1b} \\ \mathbf{I}_{1b} \end{bmatrix}, \quad \begin{bmatrix} \mathbf{V}_{2b} \\ -\mathbf{I}_{2b} \end{bmatrix} = \begin{bmatrix} \mathbf{V}_2 \\ -\mathbf{I}_2 \end{bmatrix}$$

So

$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_1 \end{bmatrix} = \begin{bmatrix} \mathbf{A}_a & \mathbf{B}_a \\ \mathbf{C}_a & \mathbf{D}_a \end{bmatrix} \begin{bmatrix} \mathbf{A}_b & \mathbf{B}_b \\ \mathbf{C}_b & \mathbf{D}_b \end{bmatrix} \begin{bmatrix} \mathbf{V}_2 \\ -\mathbf{I}_2 \end{bmatrix}$$

If

$$\begin{bmatrix} \mathbf{A} & \mathbf{B} \\ \mathbf{C} & \mathbf{D} \end{bmatrix} = \begin{bmatrix} \mathbf{A}_a & \mathbf{B}_a \\ \mathbf{C}_a & \mathbf{D}_a \end{bmatrix} \begin{bmatrix} \mathbf{A}_b & \mathbf{B}_b \\ \mathbf{C}_b & \mathbf{D}_b \end{bmatrix}$$

Then

$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_1 \end{bmatrix} = \begin{bmatrix} \mathbf{A} & \mathbf{B} \\ \mathbf{C} & \mathbf{D} \end{bmatrix} \begin{bmatrix} \mathbf{V}_2 \\ -\mathbf{I}_2 \end{bmatrix}$$


Or

$$\boxed{[\mathbf{T}] = [\mathbf{T}_a][\mathbf{T}_b]}$$

Series connection

7

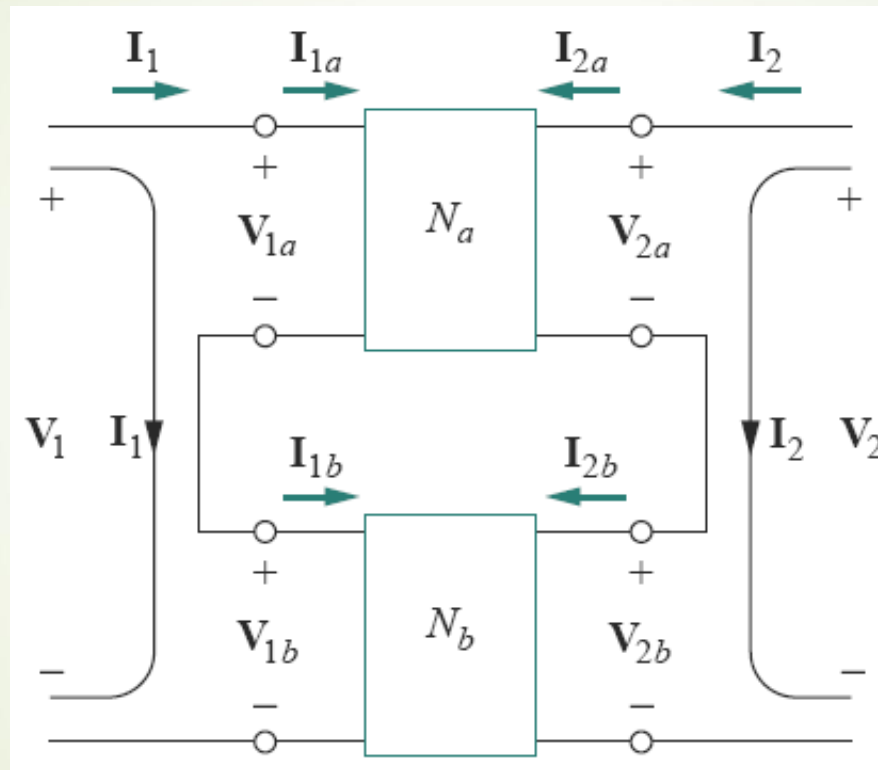- In a series connection, both the networks carry, the same input current and their output currents are also equal.



In this resultant Z-parameter matrix for the series-connected networks is the sum of Z matrices of each individual two-port network.

- For network N_a

$$\mathbf{V}_{1a} = \mathbf{z}_{11a}\mathbf{I}_{1a} + \mathbf{z}_{12a}\mathbf{I}_{2a}$$

$$\mathbf{V}_{2a} = \mathbf{z}_{21a}\mathbf{I}_{1a} + \mathbf{z}_{22a}\mathbf{I}_{2a}$$

- For network N_b

$$\mathbf{V}_{1b} = \mathbf{z}_{11b}\mathbf{I}_{1b} + \mathbf{z}_{12b}\mathbf{I}_{2b}$$

$$\mathbf{V}_{2b} = \mathbf{z}_{21b}\mathbf{I}_{1b} + \mathbf{z}_{22b}\mathbf{I}_{2b}$$


- Also the currents are equal i.e

$$\mathbf{I}_1 = \mathbf{I}_{1a} = \mathbf{I}_{1b}, \quad \mathbf{I}_2 = \mathbf{I}_{2a} = \mathbf{I}_{2b}$$

- For the combined network

$$\mathbf{V}_1 = \mathbf{V}_{1a} + \mathbf{V}_{1b} = (\mathbf{z}_{11a} + \mathbf{z}_{11b})\mathbf{I}_1 + (\mathbf{z}_{12a} + \mathbf{z}_{12b})\mathbf{I}_2$$
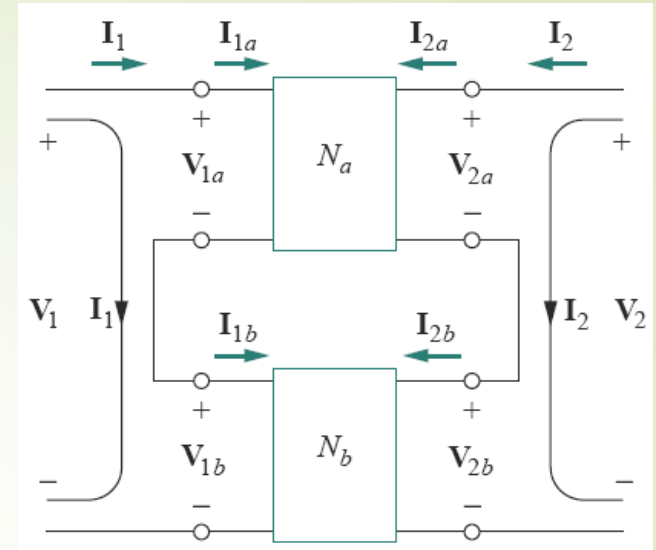
$$\mathbf{V}_2 = \mathbf{V}_{2a} + \mathbf{V}_{2b} = (\mathbf{z}_{21a} + \mathbf{z}_{21b})\mathbf{I}_1 + (\mathbf{z}_{22a} + \mathbf{z}_{22b})\mathbf{I}_2$$



- So for the combined network, the Z parameters are

$$\begin{bmatrix} \mathbf{z}_{11} & \mathbf{z}_{12} \\ \mathbf{z}_{21} & \mathbf{z}_{22} \end{bmatrix} = \begin{bmatrix} \mathbf{z}_{11a} + \mathbf{z}_{11b} & \mathbf{z}_{12a} + \mathbf{z}_{12b} \\ \mathbf{z}_{21a} + \mathbf{z}_{21b} & \mathbf{z}_{22a} + \mathbf{z}_{22b} \end{bmatrix}$$

- And hence

$$\begin{bmatrix} \mathbf{V}_1 \\ \mathbf{I}_1 \end{bmatrix} = \begin{bmatrix} \mathbf{z}_{11} & \mathbf{z}_{12} \\ \mathbf{z}_{21} & \mathbf{z}_{22} \end{bmatrix} \begin{bmatrix} \mathbf{V}_2 \\ \mathbf{I}_2 \end{bmatrix}$$


- Or for series network

$$[\mathbf{z}] = [\mathbf{z}_a] + [\mathbf{z}_b]$$


Parallel connection

10

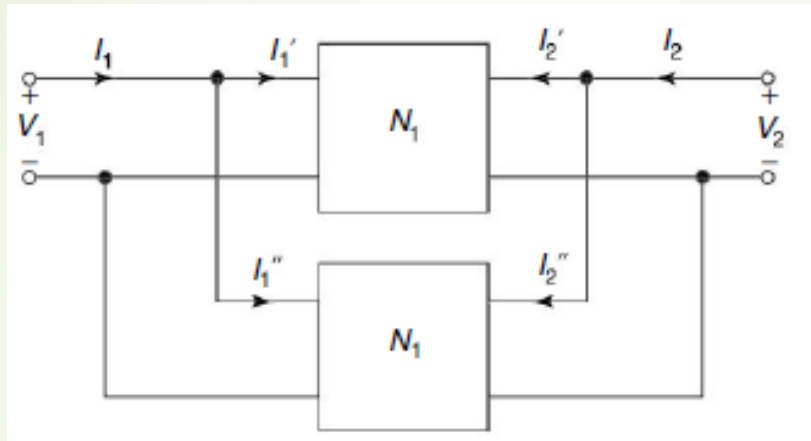- In the parallel connection, the two networks have the same input voltages and the same output voltages



- This can be redrawn as

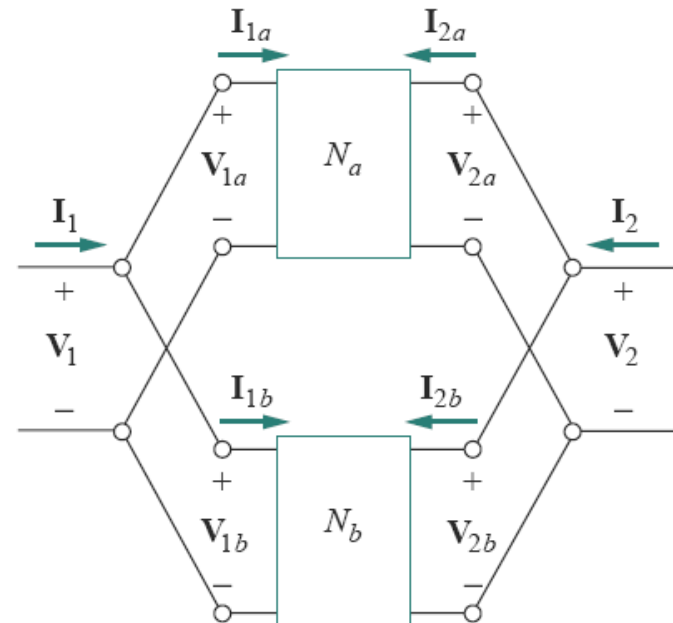

- For network N_a

$$\mathbf{I}_{1a} = \mathbf{y}_{11a} \mathbf{V}_{1a} + \mathbf{y}_{12a} \mathbf{V}_{2a}$$

$$\mathbf{I}_{2a} = \mathbf{y}_{21a} \mathbf{V}_{1a} + \mathbf{y}_{22a} \mathbf{V}_{2a}$$

- For network N_b

$$\mathbf{I}_{1b} = \mathbf{y}_{11b} \mathbf{V}_{1b} + \mathbf{y}_{12b} \mathbf{V}_{2b}$$

$$\mathbf{I}_{2a} = \mathbf{y}_{21b} \mathbf{V}_{1b} + \mathbf{y}_{22b} \mathbf{V}_{2b}$$

- Also the Voltages are equal and the total current is the sum of individual currents, i.e


$$\mathbf{V}_1 = \mathbf{V}_{1a} = \mathbf{V}_{1b}, \quad \mathbf{V}_2 = \mathbf{V}_{2a} = \mathbf{V}_{2b}$$

$$\mathbf{I}_1 = \mathbf{I}_{1a} + \mathbf{I}_{1b}, \quad \mathbf{I}_2 = \mathbf{I}_{2a} + \mathbf{I}_{2b}$$

- For the combined network

$$\mathbf{I}_1 = (\mathbf{y}_{11a} + \mathbf{y}_{11b}) \mathbf{V}_1 + (\mathbf{y}_{12a} + \mathbf{y}_{12b}) \mathbf{V}_2$$
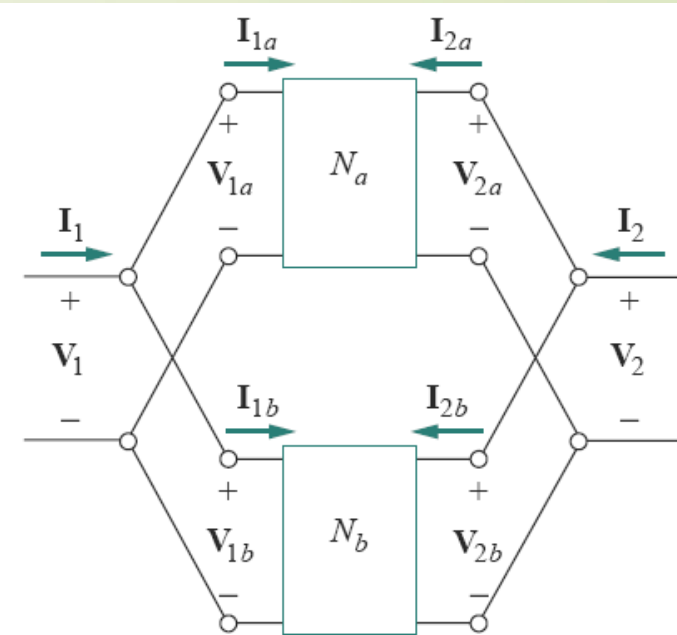
$$\mathbf{I}_2 = (\mathbf{y}_{21a} + \mathbf{y}_{21b}) \mathbf{V}_1 + (\mathbf{y}_{22a} + \mathbf{y}_{22b}) \mathbf{V}_2$$



- So for the combined network, the Y parameters are

$$\begin{bmatrix} \mathbf{y}_{11} & \mathbf{y}_{12} \\ \mathbf{y}_{21} & \mathbf{y}_{22} \end{bmatrix} = \begin{bmatrix} \mathbf{y}_{11a} + \mathbf{y}_{11b} & \mathbf{y}_{12a} + \mathbf{y}_{12b} \\ \mathbf{y}_{21a} + \mathbf{y}_{21b} & \mathbf{y}_{22a} + \mathbf{y}_{22b} \end{bmatrix}$$

- And hence


$$\begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} \mathbf{y}_{11} & \mathbf{y}_{12} \\ \mathbf{y}_{21} & \mathbf{y}_{22} \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix}$$

- Or for parallel network

$$[\mathbf{y}] = [\mathbf{y}_a] + [\mathbf{y}_b]$$

Three ways that two ports are interconnected:


* Cascade

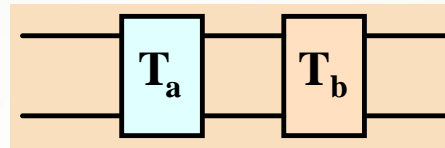

ABCD parameters

$$[T] = [T_a] [T_b]$$


* Series

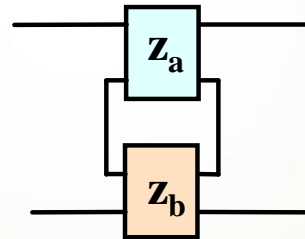

Z parameters

$$[z] = [z_a] + [z_b]$$

* Parallel

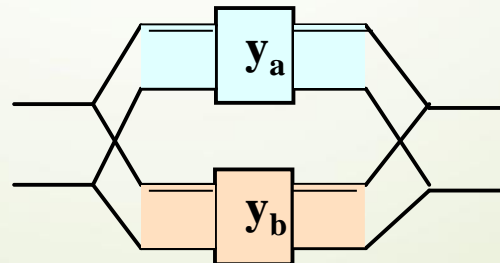


Y parameters

$$[y] = [y_a] + [y_b]$$

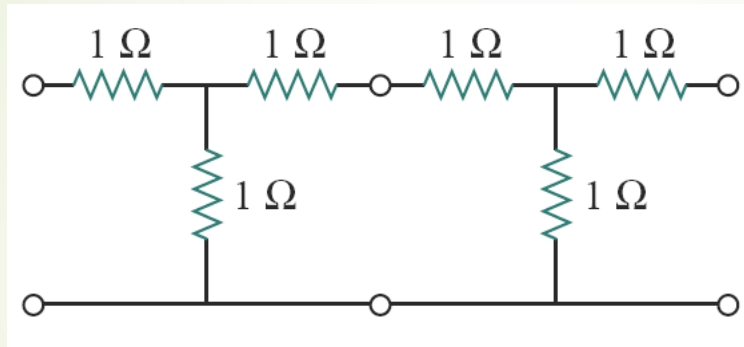Problems


14

P.7.21 Find the transmission parameters for the cascaded two-ports shown in Fig.




$$\begin{bmatrix} 7 & 12\ \Omega \\ 4\ \text{S} & 7 \end{bmatrix}$$

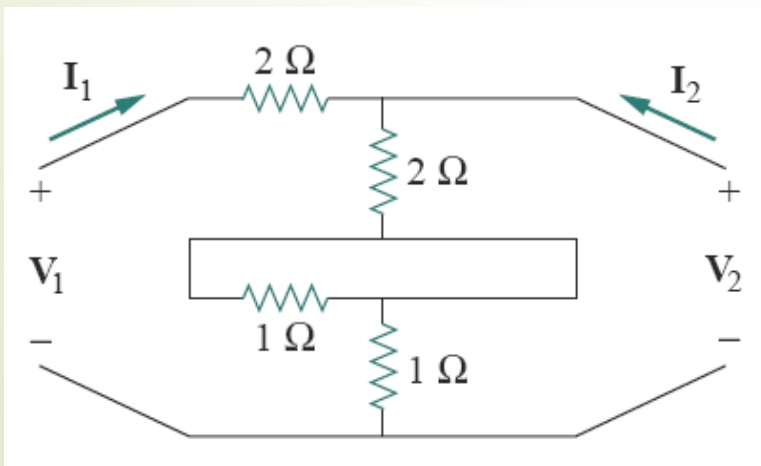P.7.22 Obtain z parameter presentation of the circuit in Fig.



$$[Z] = [Z_a] + [Z_b] = \begin{bmatrix} 4+2 & 2+1 \\ 2+1 & 2+1 \end{bmatrix} \Omega$$

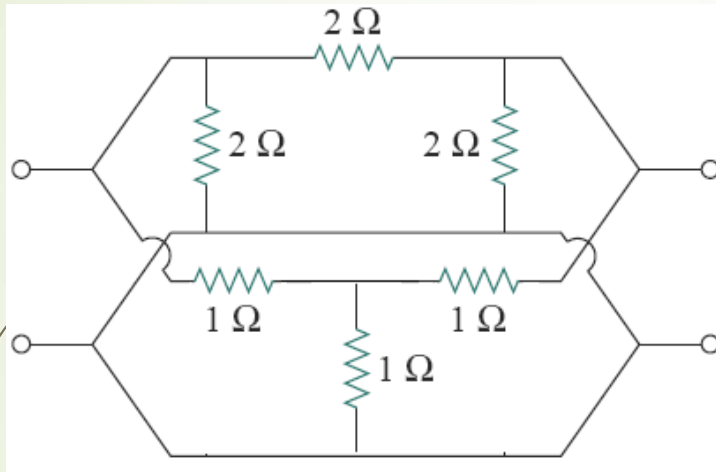P.7.23 Obtain y parameter presentation of the circuit in Fig.



$$[Y] = [Y_a] + [Y_b] = \begin{bmatrix} 1 + \frac{2}{3} & -\frac{1}{2} - \frac{1}{3} \\ -\frac{1}{2} - \frac{1}{3} & 1 + \frac{2}{3} \end{bmatrix} S$$