

NAND & NOR GATE IMPLEMENTATION

STEP TO GET NAND- NAND LOGIC

- STEP 1: Draw the **logic circuit using AND, OR and NOT GATES** for the given/ Obtained B.E.
- STEP 2: Put Bubbles at **input of OR** and at the **output of AND**.
- Step 3: Insert **Inverter (NOT GATE) for each bubbles**. (i.e. before NOR and After NAND)
- Step 4: Remove **double NOT gates / two NOT gates** connected in series (adjacent), if any
- Step 5: Replace **bubbled OR, Inverter** by NAND.

STEP TO GET NOR- NOR LOGIC

- STEP 1: Draw the **logic circuit using AND, OR and NOT GATES** for the given/ Obtained B.E
- STEP 2: Put Bubbles at **input of AND** and at the **output of OR**.
- Step 3: Insert **Inverter (NOT GATE) for each bubbles**. (i.e. before NOR and After NAND)
- Step 4: Remove **double NOT gates / two NOT gates** connected in series (adjacent), if any
- Step 5: Replace **bubbled AND, Inverter** by **NOR**.