



VIT

Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)

REG.NO.: 26BEE0497

SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - I
FALL SEMESTER 2026-2027



SLOT: C1+TC1+TCC1

Programme Name & Branch : B.Tech ECE, BVD, BLC
Course Code and Course Name : BAECE103 & Network Theory
Faculty Name(s) : DHARANI BAIG, VIJAY KUMAR, NITHISH KUMAR V, NAVEEN MISHRA, SHANIDUL HOQUE, MOHIUL ISLAM, HENRIDASS, SUDIPTA KUMAR SARKAR
Class Number(s) : VL2026270105286/5293/5313/5291/5296/5299/5315/5288
Date of Examination : 11.08.2026
Exam Duration : 90 minutes (9.30 AM – 11.00 AM) Maximum Marks: 50
General instruction(s):

- Answer All Questions
- M - Max mark; CO – Course Outcome; BL – Blooms Taxonomy Level
(1 – Remember, 2 – Understand, 3 – Apply, 4 – Analyse, 5 – Evaluate, 6 – Create)

Course Outcomes are:




1. Compute DC circuit parameters using circuit laws and theorems
2. Determine the natural and step responses of RC, RL, and RLC circuits
3. Apply appropriate techniques and theorems for sinusoidal steady-state analysis
4. Apply the Laplace transform to circuits for steady-state and transient analysis
5. Compute two-port network parameters and network graph matrices for circuit analysis

  Q. No.	Question	CO	BL	Marks
1.	Apply appropriate circuit reduction techniques to determine the <u>equivalent resistance</u> seen by the source in the circuit shown in Figure 1. 	1	BL3	10
2.	Calculate all the <u>node voltages</u> in the circuit shown in Figure 2 using <u>nodal analysis</u> . 	1	BL3	10



SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - I
FALL SEMESTER 2026-2027

SLOT: C1+TC1+TCC1

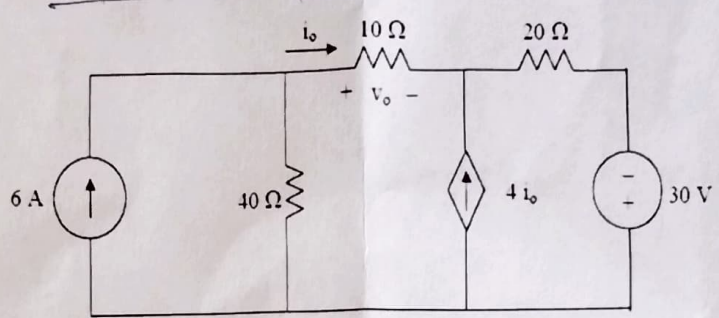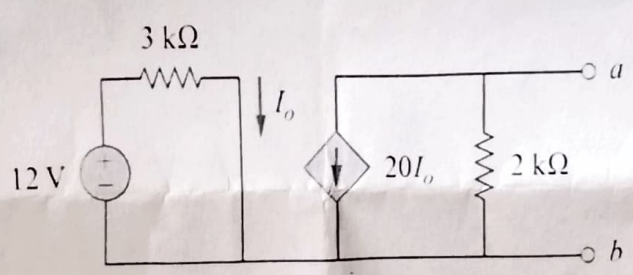 Figure 2				
3.	Use the superposition principle to find i_o in the circuit shown in Figure 3. 	1	BL3	10
4.	Find the Thevenin equivalent circuit between terminals $a-b$ of the circuit shown in Figure 4. 	1	BL3	10
5.	Compute the value of R that results in maximum power transfer to the 10Ω resistor in the circuit shown in Figure 5. 	1	BL3	10
