



VIT[®]

Slot: A2+TA2+TAA2

Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)

SCHOOL OF ELECTRONICS ENGINEERING (SENSE)
CONTINUOUS ASSESSMENT TEST- II

Winter Semester: 2022-23

Programme Name & Branch: B.Tech & ECE

Class Number: VL2022230506379

Course Code: BECE203L

Course Title : Circuit Theory



Faculty Name: Dr. Shanidul Hoque




Date: 07/05/2023

Exam Duration: 90 Minutes



Maximum Marks: 50

Answer all the following questions

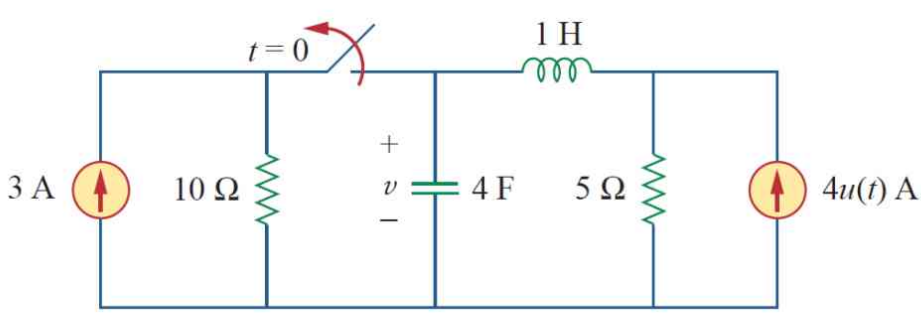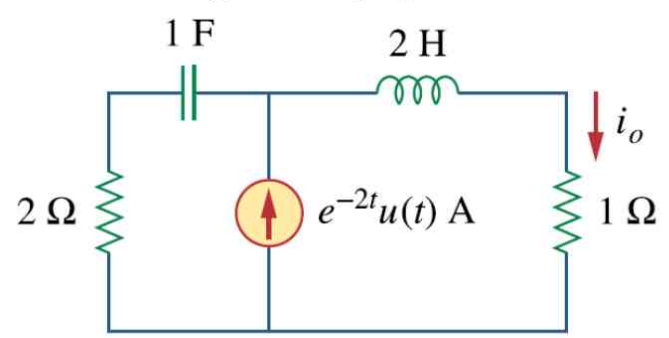S. No	Questions	Marks
1	(a) Find the voltage $v(t)$ for $t > 0$ in the circuit of Figure 1. What type of response will it produce?  Figure 1	10
2	(a) Find the Laplace transform of the function $f(t) = (e^{-at} - e^{-bt})u(t)$. (b) Find $i_o(t)$ in the circuit of Figure 2 using Laplace transform method.  Figure 2	3 7

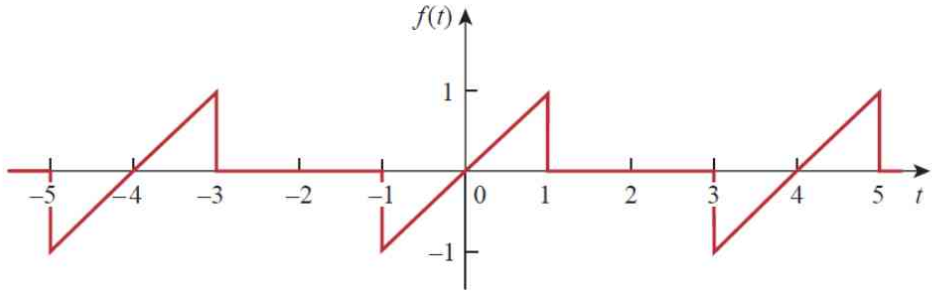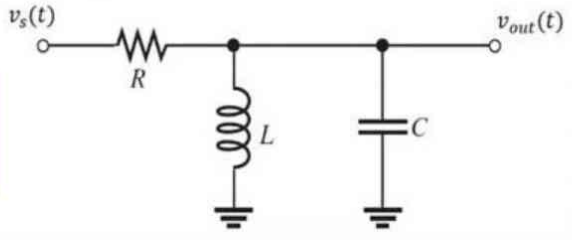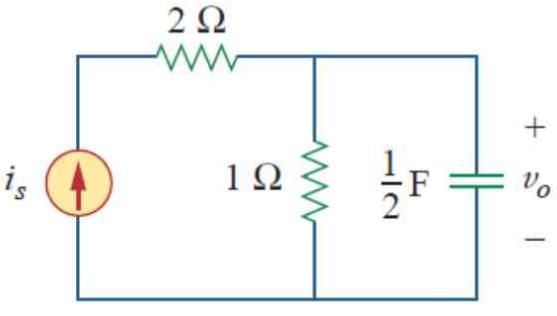3	For the waveform shown in Figure 3, (i) Specify the type of symmetry it has, (ii) Find Fourier series expansion of $f(t)$ and calculate a_3 & b_3, (iii) Find the RMS value using the first five non-zero harmonics.  Figure 3	10
4	Determine the output voltage $v_{out}(t)$ in the given circuit of Figure 4 if $R= 10\ \Omega$, $L=2\text{ H}$, $C=0.25\text{ F}$ and the input voltage $v_s(t)$ given by the Fourier series $v_s(t) = 3 + \frac{4}{\pi} \sum_{n=1}^{\infty} \frac{\sin(n\pi t)}{n} \text{ V}$  Figure 4 Also plot the amplitude spectrum and phase spectrum for $n=1, 2, 3$.	10
5	Find the voltage $v_o(t)$ and current $i_o(t)$ using Fourier transform method in the circuit of Figure 5 considering $i_s(t) = 8e^{-t}u(t)\text{ A}$.  Figure 5	10

Answer:

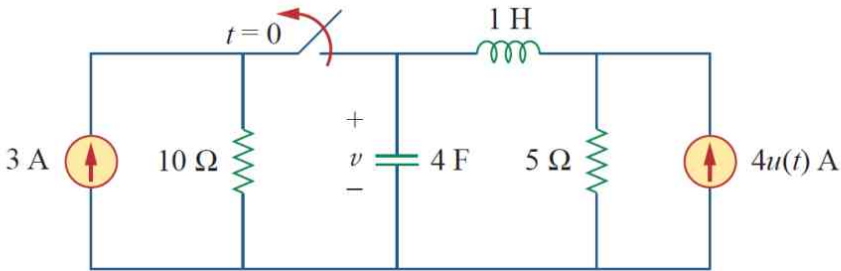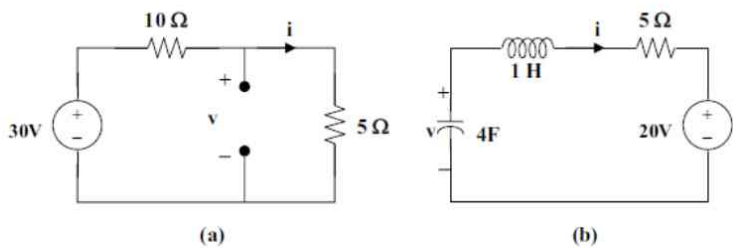S. No	Questions	Marks
1	Find the voltage $v(t)$ for $t > 0$ in the circuit of Figure 1. What type of response will it produce?  Figure 1 We may transform the current sources to voltage sources. For $t = 0^-$, the equivalent circuit is shown in Figure (a).  (a) (b) $i(0) = 30/15 = 2 \text{ A}, v(0) = 5 \times 30/15 = 10 \text{ V}$ For $t > 0$, we have a series RLC circuit, shown in (b). $\alpha = R/(2L) = 5/2 = 2.5$ $\omega_o = 1/\sqrt{LC} = 1/\sqrt{4} = 0.5, \text{ clearly } \alpha > \omega_o \text{ (overdamped response)}$ $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_o^2} = -2.5 \pm \sqrt{6.25 - 0.25} = -4.95, -0.0505$ $v(t) = V_s + [A_1 e^{-4.95t} + A_2 e^{-0.0505t}], V_s = 20.$ $v(0) = 10 = 20 + A_1 + A_2 \text{ or } A_2 = -10 - A_1 \quad (1)$ $i(0) = C dv(0)/dt \text{ or } dv(0)/dt = 2/4 = 1/2$ Hence, $0.5 = -4.95A_1 - 0.0505A_2 \quad (2)$ From (1) and (2), $0.5 = -4.95A_1 + 0.505(10 + A_1) \text{ or } -4.445A_1 = -0.005$ $A_1 = 0.001125, A_2 = -10.001$ $v(t) = \underline{[20 + 0.001125e^{-4.95t} - 10.001e^{-0.0505t}] \text{ V}}$	10
2	(a) Find the Laplace transform of the function $f(t) = (e^{-at} - e^{-bt})u(t)$. $F(s) = (b-a)/(s+a)(s+b)$	3

(b) Find $i_o(t)$ in the circuit of Figure 2 using Laplace transform method.

7


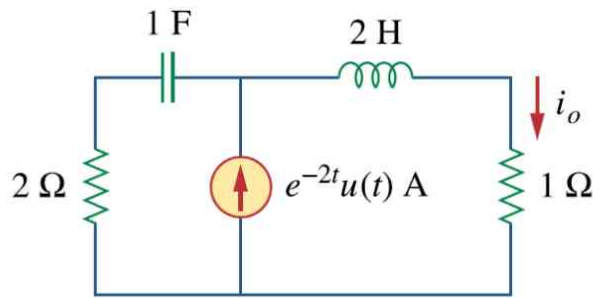


Figure 2

Consider the following circuit.

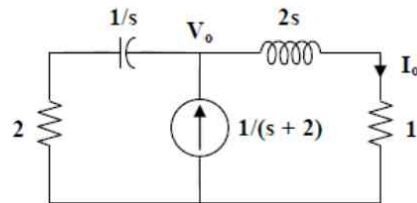

Applying KCL at node o,

$$\frac{1}{s+2} = \frac{V_o}{2s+1} + \frac{V_o}{2+1/s} = \frac{s+1}{2s+1} V_o$$

$$V_o = \frac{2s+1}{(s+1)(s+2)}$$

$$I_o = \frac{V_o}{2s+1} = \frac{1}{(s+1)(s+2)} = \frac{A}{s+1} + \frac{B}{s+2}$$

$$A = 1, \quad B = -1$$

$$I_o = \frac{1}{s+1} - \frac{1}{s+2}$$

$$i_o(t) = \underline{(e^{-t} - e^{-2t})u(t) \text{ A}}$$

3

For the waveform shown in Figure 3,

- Specify the type of symmetry it has,
- Find Fourier series expansion of $f(t)$ and calculate a_3 & b_3 ,
- Find the RMS value using the first five non-zero harmonics.

10

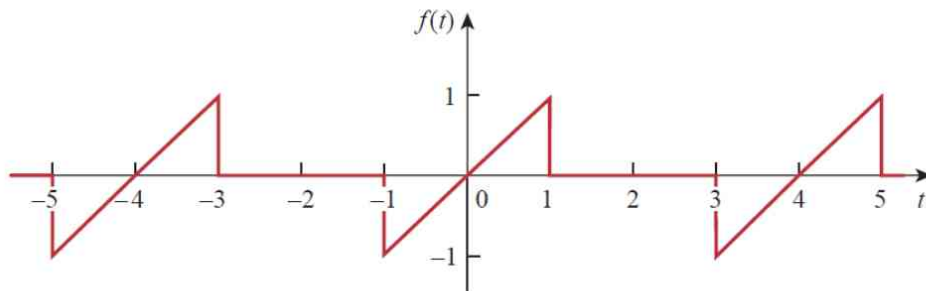
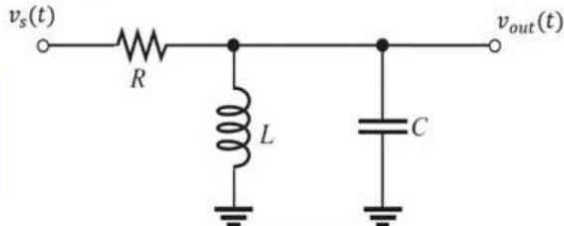


Figure 3

	(a) Odd symmetry (b) $a_0 = 0 = a_n, T = 4, \omega_0 = 2\pi/T = \pi/2$ $f(t) = t, \quad 0 < t < 1$ $= 0, \quad 1 < t < 2$ $b_n = \frac{4}{4} \int_0^1 t \sin \frac{n\pi t}{2} dt = \left[\frac{4}{n^2 \pi^2} \sin \frac{n\pi t}{2} - \frac{2t}{n\pi} \cos \frac{n\pi t}{2} \right]_0^1$ $= \frac{4}{n^2 \pi^2} \sin \frac{n\pi}{2} - \frac{2}{n\pi} \cos \frac{n\pi}{2} - 0$ $= 4(-1)^{(n-1)/2} / (n^2 \pi^2), \quad n = \text{odd}$ $-2(-1)^{n/2} / (n\pi), \quad n = \text{even}$ $a_3 = 0, b_3 = 4(-1)/(9\pi^2) = \underline{-0.04503}$ (c) $b_1 = 4/\pi^2, b_2 = 1/\pi, b_3 = -4/(9\pi^2), b_4 = -1/(2\pi), b_5 = 4/(25\pi^2)$ $F_{rms} = \sqrt{a_0^2 + \frac{1}{2} \sum (a_n^2 + b_n^2)}$ $F_{rms}^2 = 0.5 \sum b_n^2 = [1/(2\pi^2)][(16/\pi^2) + 1 + (16/(81\pi^2)) + (1/4) + (16/(625\pi^2))]$ $= (1/19.729)(2.6211 + 0.27 + 0.00259)$ $F_{rms} = \sqrt{0.14667} = \underline{0.383}$ Compare this with the exact value of $F_{rms} = \sqrt{\frac{2}{T} \int_0^1 t^2 dt} = \sqrt{1/6} = 0.4082$ or	
4	Determine the output voltage $v_{out}(t)$ in the given circuit of Figure 4 if $R=10 \Omega$, $L=2 \text{ H}$, $C=0.25 \text{ F}$ and the input voltage $v_s(t)$ given by the Fourier series $v_s(t) = 3 + \frac{4}{\pi} \sum_{n=1}^{\infty} \frac{\sin(n\pi t)}{n} \text{ V}$  Figure 4 Also plot the amplitude spectrum and phase spectrum for $n=1, 2, 3$.	10

Solutions:

The radian frequency is given by $\omega_n = n\omega_0 = n\pi$ rad/sec. Using phasors, we get for the output voltage:

$$V_{out}(j\omega) = \frac{X_C || X_L}{R + X_C || X_L} V_s(j\omega) = \frac{\left(\frac{1}{j\omega_n L} \cdot \frac{1}{j\omega_n C} \right)}{R + \left(\frac{1}{j\omega_n L} + \frac{1}{j\omega_n C} \right)} V_s(j\omega) = \frac{\left(\frac{j\omega_n L}{-\omega_n^2 LC + 1} \right)}{R + \left(\frac{j\omega_n L}{-\omega_n^2 LC + 1} \right)} V_s(j\omega)$$

$$V_{out}(j\omega) = \frac{j\omega_n L}{R - \omega_n^2 LC + 1 + j\omega_n L} V_s(j\omega)$$

$$V_{out}(j\omega) = \frac{jn\pi \cdot 2}{10 - (n\pi)^2 \cdot 2 \cdot 0.25 + 1 + jn\pi \cdot 2} V_s(j\omega)$$

$$V_{out}(j\omega) = \frac{jn\pi}{5 - 2.5n^2\pi^2 + jn\pi} V_s(j\omega)$$

$$V_{out}(j\omega) = \frac{jn\pi}{5 - 2.5n^2\pi^2 + jn\pi} \cdot \frac{-j4}{n\pi} = \frac{4}{5 - 2.5n^2\pi^2 + jn\pi} \text{ V}$$

The real term $5 - 2.5n^2\pi^2 < 0$ for $n \geq 1$, thus $5 - 2.5n^2\pi^2 + jn\pi$ is in the 2nd quadrant.


The phase of the denominator $5 - 2.5n^2\pi^2 + jn\pi$ is given by $180^\circ - \arctan\left(\frac{n\pi}{5 - 2.5n^2\pi^2}\right)$.

The phase of $V_{out}(j\omega)$ is given by

$$\theta_n = 0^\circ - \left[180^\circ - \arctan\left(\frac{n\pi}{5 - 2.5n^2\pi^2}\right) \right] \Rightarrow \theta_n = -180^\circ + \arctan\left(\frac{n\pi}{5 - 2.5n^2\pi^2}\right)$$

The magnitude of $V_{out}(j\omega)$ is given by
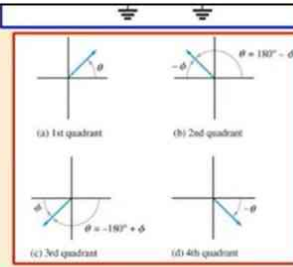
$$A_n = \frac{4}{\sqrt{(5 - 2.5n^2\pi^2)^2 + (n\pi)^2}}$$



For DC ($n = 0$ or $\omega_n = 0$), we have:

$$V_s = 3 \text{ V} \Rightarrow V_{out} = 0 \text{ V (Inductor is short for DC)}$$

For AC (n^{th} harmonic), we have:

$$\left. \begin{aligned} \theta_n &= -180^\circ + \arctan\left(\frac{n\pi}{5 - 2.5n^2\pi^2}\right) \\ A_n &= \frac{4}{\sqrt{(5 - 2.5n^2\pi^2)^2 + (n\pi)^2}} \end{aligned} \right\} \begin{aligned} V_{out} &= A_n \angle \theta_n \text{ V} \\ V_{out} &= \frac{4}{\sqrt{(5 - 2.5n^2\pi^2)^2 + (n\pi)^2}} \angle \left(-180^\circ + \arctan\left(\frac{n\pi}{5 - 2.5n^2\pi^2}\right) \right) \text{ V} \end{aligned}$$

Time domain:

$$v_{out}(t) = \sum_{n=1}^{\infty} A_n \cos(n\pi t + \theta_n) = \sum_{n=1}^{\infty} \frac{4}{\sqrt{(5 - 2.5n^2\pi^2)^2 + (n\pi)^2}} \cos\left(n\pi t - 180^\circ + \arctan\left(\frac{n\pi}{5 - 2.5n^2\pi^2}\right)\right)$$

Using $\cos(x - 180^\circ) = -\cos(x)$, we get

$$v_{out}(t) = - \sum_{n=1}^{\infty} \frac{4}{\sqrt{(5 - 2.5n^2\pi^2)^2 + (n\pi)^2}} \cos\left(n\pi t + \arctan\left(\frac{n\pi}{5 - 2.5n^2\pi^2}\right)\right)$$

The first four terms ($n = 1, 2, 3, 4$) of the harmonics are:

$$n = 1: v_{out1}(t) = \frac{-4}{\sqrt{(5 - 2.5 \cdot 1^2 \cdot \pi^2)^2 + (1\pi)^2}} \cos\left(1\pi t - \arctan\left(\frac{1\pi}{5 - 2.5 \cdot 1^2 \cdot \pi^2}\right)\right) = -0.201 \cos(1\pi t - 9.07^\circ) \text{ V}$$


$$n = 2: v_{out2}(t) = \frac{-4}{\sqrt{(5 - 2.5 \cdot 2^2 \cdot \pi^2)^2 + (2\pi)^2}} \cos\left(2\pi t - \arctan\left(\frac{2\pi}{5 - 2.5 \cdot 2^2 \cdot \pi^2}\right)\right) = -0.043 \cos(2\pi t - 3.84^\circ) \text{ V}$$

$$n = 3: v_{out3}(t) = \frac{-4}{\sqrt{(5 - 2.5 \cdot 3^2 \cdot \pi^2)^2 + (3\pi)^2}} \cos\left(3\pi t - \arctan\left(\frac{3\pi}{5 - 2.5 \cdot 3^2 \cdot \pi^2}\right)\right) = -0.018 \cos(3\pi t - 2.49^\circ) \text{ V}$$

$$n = 4: v_{out4}(t) = \frac{-4}{\sqrt{(5 - 2.5 \cdot 4^2 \cdot \pi^2)^2 + (4\pi)^2}} \cos\left(4\pi t - \arctan\left(\frac{4\pi}{5 - 2.5 \cdot 4^2 \cdot \pi^2}\right)\right) = -0.010 \cos(4\pi t - 1.85^\circ) \text{ V}$$

Output Signal Spectrum
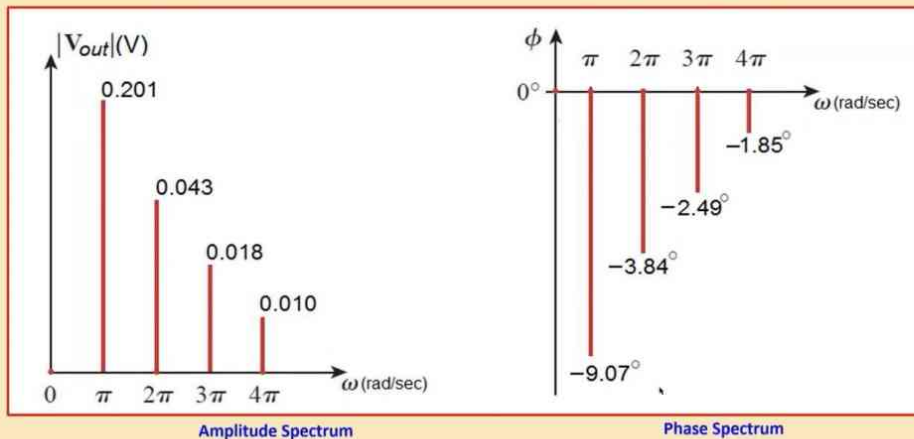
$$v_{out}(t) = -0.201 \cos(\pi t - 9.07^\circ) - 0.043 \cos(2\pi t - 3.84^\circ) - 0.018 \cos(3\pi t - 2.49^\circ) - 0.010 \cos(4\pi t - 1.85^\circ) + \dots \text{ V}$$



5

Find the voltage $v_o(t)$ and current $i_o(t)$ using Fourier transform method in the circuit of Figure 5 considering $i_s(t) = 8e^{-t}u(t)$ A.

10

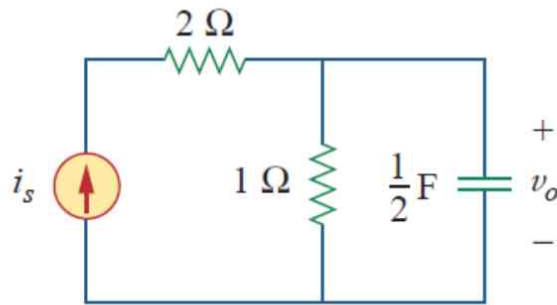


Figure 5

$$\frac{1}{2}F \longrightarrow \frac{1}{j\omega C} = \frac{2}{j\omega}$$

$$I_o = \frac{1}{1 + \frac{2}{j\omega}} I_s$$

$$V_o = \frac{2}{j\omega} I_o = \frac{\frac{2}{j\omega}}{1 + \frac{2}{j\omega}} I_s = \frac{2}{2 + j\omega} \frac{8}{1 + j\omega}$$

$$= \frac{16}{(s+1)(s+2)}, s = j\omega$$

$$= \frac{A}{s+1} + \frac{B}{s+2}$$

where $A = 16/1 = 16$, $B = 16/(-1) = -16$

Thus,

$$v_o(t) = \underline{16(e^{-t} - e^{-2t})u(t)} \text{ V.}$$

$$i_o(t) = Cdv(t)$$