

Course: BECE102L - Digital Systems Design

Class NBR(s): 4252 / 4256 / 4262 / 4264 / 4266 / 4269  
/ 4271 / 4273 / 4276 / 4278 / 4280 / 4284  
/ 4287 / 4292 / 4293 / 4297 / 4299 / 4310  
/ 4311

Slot: E1+TE1

Max. Marks: 100

Time: Three Hours

- KEEPING MOBILE PHONE/ANY ELECTRONIC GADGETS, EVEN IN 'OFF' POSITION IS TREATED AS EXAM MALPRACTICE
- DON'T WRITE ANYTHING ON THE QUESTION PAPER

Answer ALL Questions  
(10 X 10 = 100 Marks)

1. Simplify the following using Boolean Algebra and draw the circuit using CMOS logic.

$$F = [A\bar{B}(C + BD) + \bar{A}B]C$$

2. i) Simplify the following to POS using K – Map. [5]

$$Y(A, B, C, D) = \sum m(1,5,7,9,13,14) + d(2,4,10,11,12,15)$$

ii) Redraw the following circuit shown in Figure 1 using only NAND gates [5] without losing the functionality.

 


Figure 1

3. Derive the truth table and draw the circuit for the below Verilog HDL code

```

module fat3(in,out);
  input [2:0]in;
  output [2:0]out;
  reg [2:0]out;
  always @ (in)
  begin
    case (in)
      0 : out = 0;
    
```

```
1 : out = 1;
2 : out = 3;
3 : out = 2;
4 : out = 6;
5 : out = 7;
6 : out = 5;
7 : out = 4;
```

```
endcase
```

```
end
```

```
endmodule
```

4. **Scenario:** Design a traffic light control system for a two-way intersection, where each direction has a red, yellow, and green light.

**Inputs:**

- **A:** Sensor for Direction 1 (1 if a vehicle is present, 0 otherwise)
- **B:** Sensor for Direction 2 (1 if a vehicle is present, 0 otherwise)
- **C:** Emergency Vehicle Signal (1 if an emergency vehicle is approaching, 0 otherwise)

**Tasks:**

- Design a truth table** for the traffic light system, specifying the output signals for each light (R1, G1, Y1 for Direction 1 and R2, G2, Y2 for Direction 2).
- Derive the logic expressions** for each output using AND, OR, and NOT gates based on the truth table.
- Implement the logic expressions** using basic gates and draw the circuit diagram.
- Write the gate level HDL.

5. Design the full adder using PAL and write down the logical expression of Adder.

6. Design a circuit that compares two binary numbers X and Y, each having two bits ( $X = X_2 X_1$ ;  $Y = Y_1 Y_2$ ). It has two outputs A and C.

(i) A is supposed to be 1 when  $X > Y$

(ii) C is 1 when  $X = Y$ .

Do not use adders/subtractor for this design; instead use a fundamental design process. Draw the minimum sum-of-products circuit. Assume complemented inputs are NOT available, but multiple input gates can be considered.

- (i) Construct a state table for the circuit shown in Figure 2. Obtain the equation for the next value of the output Q in terms of Q, A and B. write the dataflow HDL. [5]

 


Figure 2


- (ii) Convert D- Flip Flop to T – Flip Flop. [5]

8. Design a synchronous MOD-12 counter using D - FF. Write behavioral Verilog code and the test bench to verify the design.

9. (a) Design a Moore Sequential Circuit whose output is 1, whenever the input sequence ends with 1001. Design the circuit using JK – FF.

OR

 9. (b) Analyse the given circuit and draw the state diagram and state table



10. (a) Implement the following function using only one 4:1 Digital Switch and external logic gates. Where P and R are selection lines.

$$F(PQRS) = P\bar{Q}\bar{R} + \bar{P}QR + PQRS + \overline{(Q+R+S)}$$

OR

10. (b) Design a circuit using Decoder to convert 8421 code to Gray code.

⇔⇔⇔ E/L/TX ⇔⇔⇔