

School of Computer Science Engineering and Information Systems

Fall Semester 2023-2024

Continuous Assessment Test – II

Programme Name & Branch: BTECH CSE (BCB, BCE, BCI, BCT, BDS, BKT)


Course Name & code: BECE102L Digital Systems Design

Slot: B2+TB2

Exam Duration: 90 Min.

Maximum Marks: 50

General instruction(s): Answer all the questions

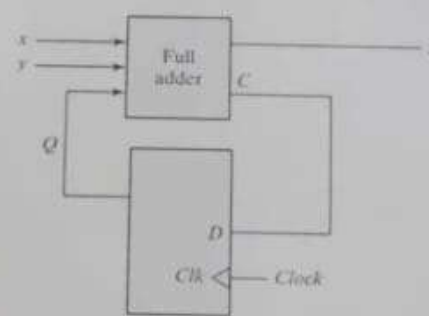Q. No	Question	Max Marks
1.	Obtain the Boolean expressions ($A > B$, $A = B$ and $A < B$) for 3-bit magnitude comparator. Based on the comparison, develop a control network to perform the following operation in block diagram level. a. If $A = B$, Perform array multiplication b. If $A > B$, Perform two complement subtraction c. If $A < B$, Perform binary addition.	10
2.	A sequential circuit has one flip-flop Q, two inputs x and y, and one output S. It consists of a full-adder circuit connected to a D flip-flop, as shown in Figure 3. Derive the state table and state diagram of the sequential circuit. 	10
3.	A new clocked X-Y flip-flop is defined with two inputs, X and Y in addition to the clocked input. The flip flop functions as follows: If $XY = 01$, the flip flop state (Q) becomes 1 at the next clock pulse If $XY = 10$, the flip flop state (Q) becomes 0 at the next clock pulse. If $X = Y$, the flip flop toggles its state (Q) at the next clock pulse. i. Provide the truth table for the X-Y flip flop ii. Provide the characteristics table iii. Provide the Excitation table for the X-Y flip flop iv. Implement X-Y flip flop using a J-K flip flop v. Write the Verilog code for final implemented circuit using behavioral modeling.	10

5/10 / 5/5

4.	Design a four-bit shift register with parallel load using D flip-flops. There are two control inputs: shift and load. When shift = 1, the content of the register is shifted by one position. New data are transferred into the register when load = 1 and shift = 0. If both control inputs are equal to 0, the content of the register does not change.	10
5.	Design a synchronous counter for the count sequence 0-3-5-7-2-1-0 using positive edge triggered D flip-flop. Write the Verilog code for the designed flip flop.	10

(3)