



**School of Electrical Engineering
B.Tech – EEE
Continuous Assessment Test I – Fall Semester 2024-2025**

Course code: BEEE102L

Course Name: Basic Electrical and Electronics Engineering

Time Duration: 90 min.



Max.Marks:50

Faculty in charge: Dr.S.Prabhakar Karthikeyan, Dr.I.Jacob Raglend and Dr. Anusuya Bhattacharyya

Answer all Questions

Assumptions can be made wherever necessary

Sl. No	Questions	Max Marks
1.	<p style="text-align: center;">Figure 1</p> <p>Find the branch currents and mesh currents using mesh analysis for the circuit shown in figure 1.</p>	<p>[10]</p> <p style="text-align: center;">4</p>
2.	<p style="text-align: center;">Figure 2</p> <p>Calculate the value of load resistance R_L such that maximum power transfer occurs from source to the load. Also calculate the maximum power?</p>	<p>[10]</p> <p style="text-align: center;">4</p>

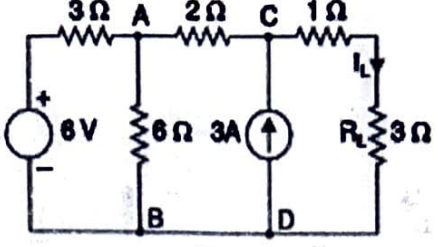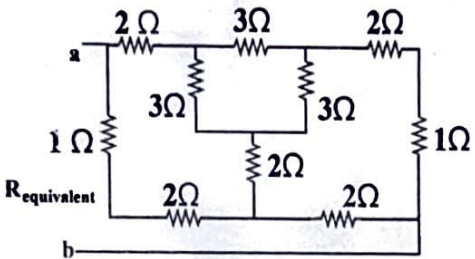3 ✓	 <p style="text-align: center;">Figure 3</p> <p>From figure 3, verify super position theorem and hence find the current I_L?</p>	<p>[10]</p> <p style="text-align: center;">4</p>
4	<p>A 10 ohms resistor is connected in series with a 100micro Farad capacitor to a 230 V, 50 Hz supply. Find (a) the impedance, (b) current, (c) power factor, (d) phase angle, (e) voltage across the resistor and the capacitor.</p>	<p>[10]</p> <p style="text-align: center;">3</p>
5	<p>Determine the resistance between the point a and b of the network shown in Figure 4</p>  <p style="text-align: center;">Figure 4</p>	<p>[10]</p> <p style="text-align: center;">7</p>