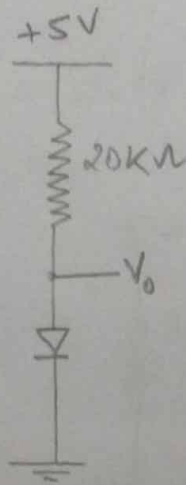


① Find voltage V_o and current through diodes:-

①



here, diode in forward bias get short


$$\therefore V_o = 0V \quad \underline{\underline{\text{Ans}}}$$

Now, current

$$i = \frac{5V}{20k\Omega} = 250\mu A \text{ or } 0.25mA$$

$$i = 0.25mA \quad \underline{\underline{\text{Ans}}}$$

②

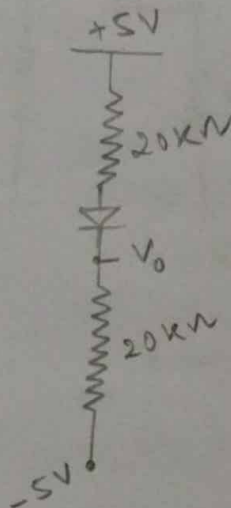

here, diode in forward bias get short

$$i = \frac{5 - (-5)}{40 \times 10^3} A$$

$$= \frac{10}{40 \times 10^3} = 0.25mA \quad \underline{\underline{\text{Ans}}}$$

$$i = 0.25mA$$


Now, voltage across $20k\Omega$

$$5 - V_o = i \times 20k\Omega$$

$$\Rightarrow 5 - V_o = 0.25 \times 20 \times 10^{-3} \times 10^3$$

$$\Rightarrow 5 - V_o = 5 \quad \therefore V_o = 0V \quad \underline{\underline{\text{Ans}}}$$

③

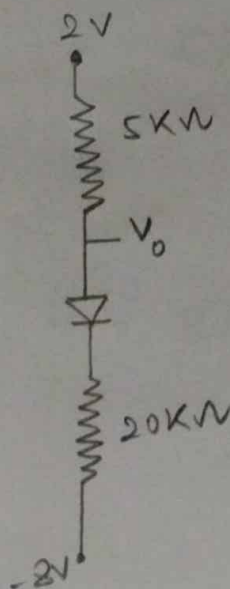

here, diode in forward bias get short

$$i = \frac{2 - (-2)}{25 \times 10^3} = \frac{4}{25 \times 10^3} = 0.16mA$$

$$\therefore i = 0.16mA \quad \underline{\underline{\text{Ans}}}$$


Now, voltage across $5k\Omega$

$$\Rightarrow 2 - V_o = i \times 5k\Omega$$


$$\Rightarrow 2 - V_o = 0.16 \times 5 \times 10^{-3} \times 10^3$$

$$\Rightarrow 2 - V_o = 0.8 \quad \therefore V_o = 1.2V \quad \underline{\underline{\text{Ans}}}$$

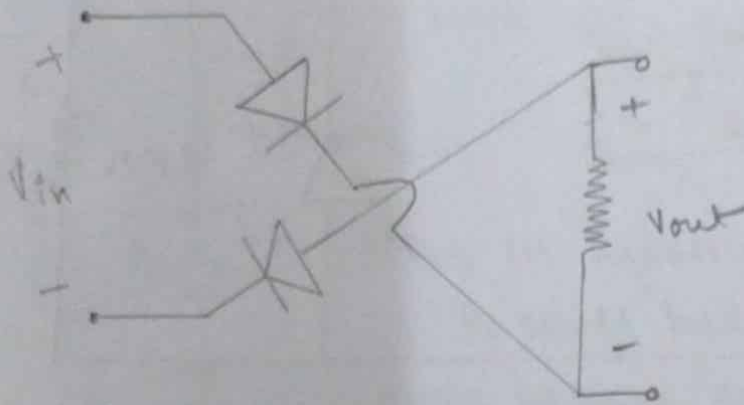- ② 10 V peak-to-peak sine wave of frequency 1 kHz
draw input and resulting output




Can be redrawn as

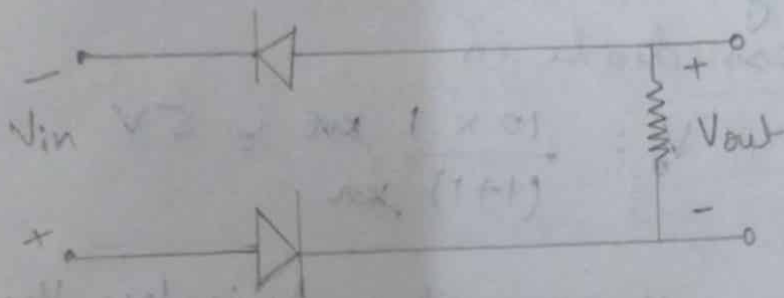


Here, in positive half cycle both the diodes are in forward bias
applying KVL, $-V_{out} - V_{in} = 0 \therefore V_{in} = -V_{out}$

During, negative half-cycle, both the diodes in reverse bias.

$$V_{out} = 0V$$

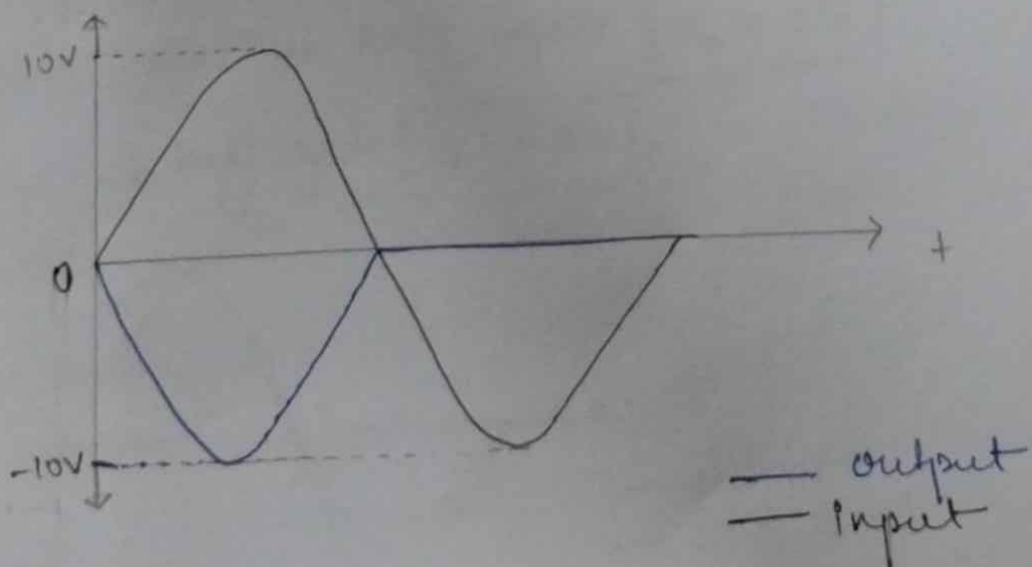

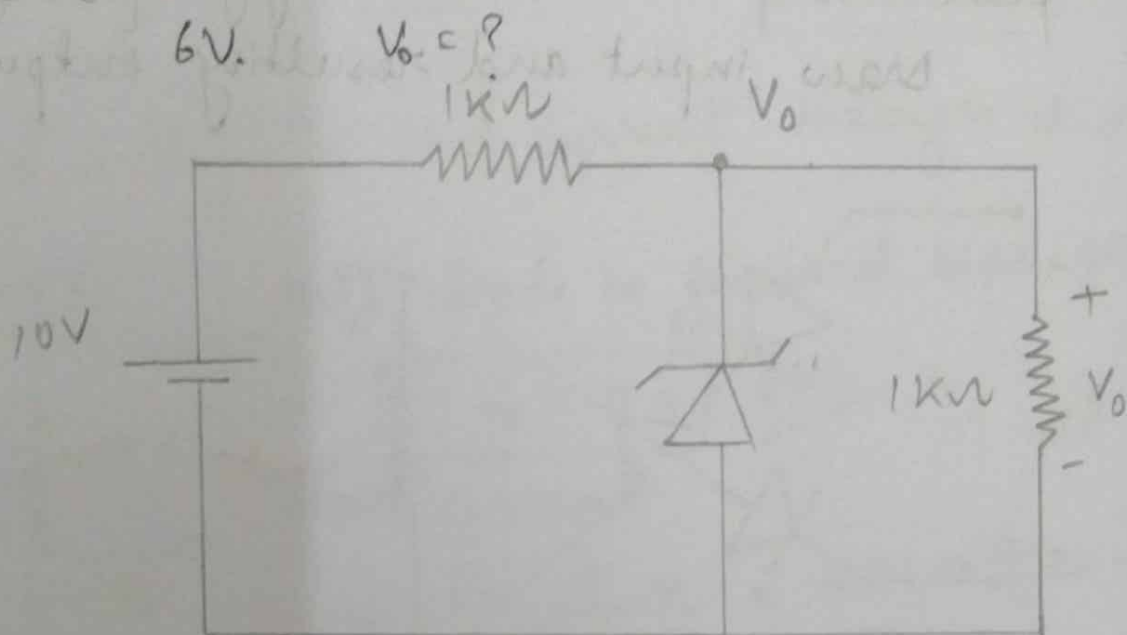③ Zener diode is ideal with zener breakdown voltage 6V. $V_0 = ?$



Here, assuming Zener diode is OFF
Voltage across diode is


$$V_0 = \frac{10 \times 1 \text{ k}\Omega}{(1+1) \text{ k}\Omega} = 5 \text{ V}$$

Since, voltage $V_0 = 5 \text{ V}$ at node is less than
Zener breakdown voltage i.e 6V

Therefore, Zener diode will be open and
output voltage $V_0 = 5 \text{ V}$ will be fixed

Ans.

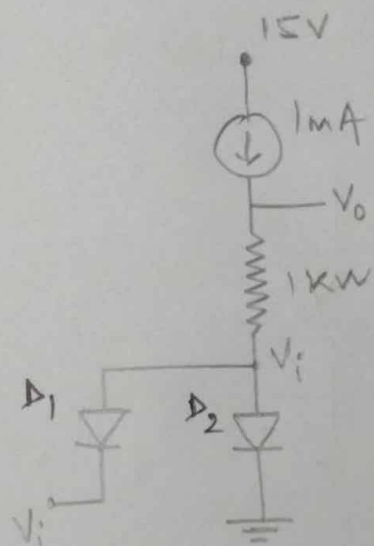④ $V_i = \text{Sinusoid } 10V \text{ \& frequency } 1kHz$



Here, In positive half cycle

D_2 will become short

Now, $V_o = 1mA \times 1k\Omega$

$V_o = 1V$ for +ve half cycle

Now, in negative half cycle

D_1 will become short


Now, voltage across $1k\Omega$

$V_o - V_i = 1V$

$\therefore V_o = 1 + V_i = 1 - 10 = -9V$

$\therefore V_o = -9V$


in -ve half cycle.

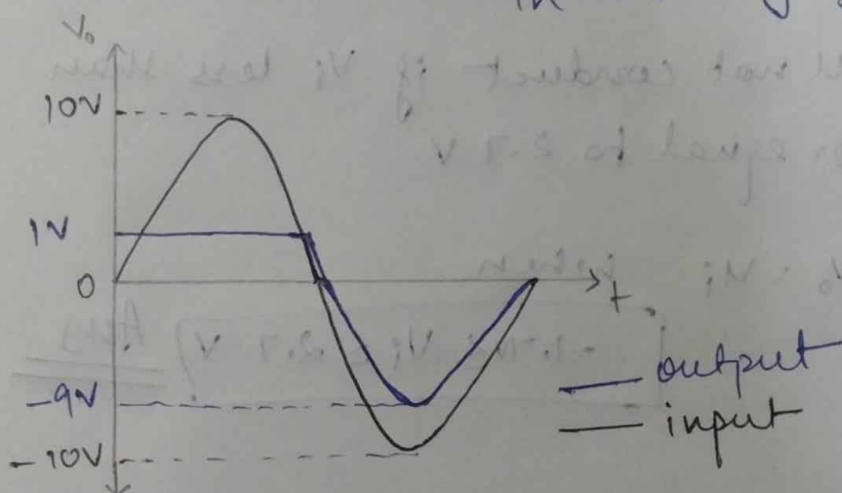


Replace $1k\Omega$ with $2k\Omega$ then,

for, positive half cycle $V_o = 2V$

in, negative half cycle $V_o = -8V$

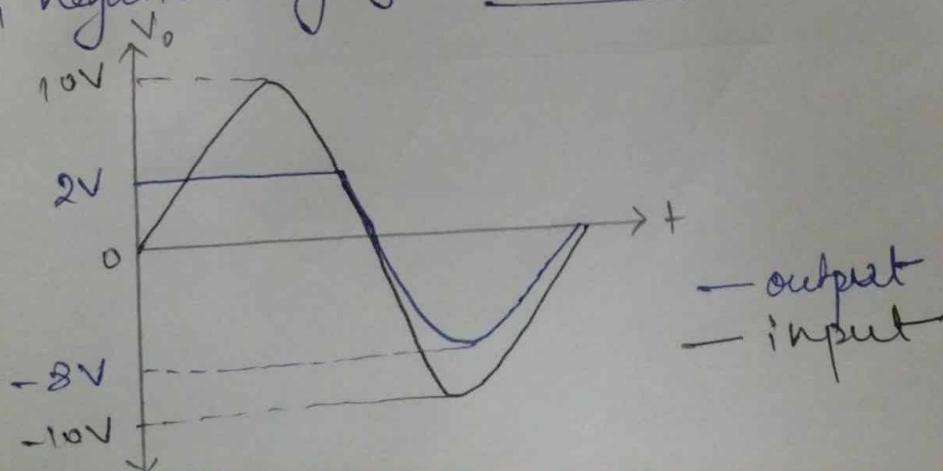

⑤ D_1 & D_2 silicon diode of 0.7V

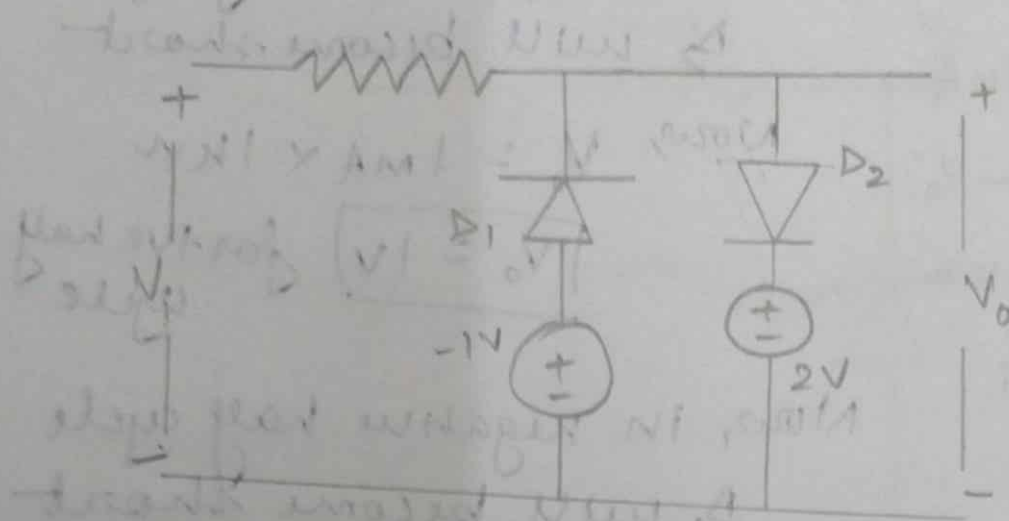

Solⁿ Range of voltage for which $V_o = V_i$

Case-I D_1 will not conduct if V_i is greater or equal $-1.7V$

Case-II D_2 will not conduct if V_i less than or equal to $2.7V$

$\therefore$ for $V_o = V_i$ when

$$\boxed{-1.7V \leq V_i \leq 2.7V} \quad \underline{\underline{\text{Ans}}}$$