

Roll No.: 23BDS0055

Name: yash Hirani

Experiment No.:4

Date:31 Jan 2024

Sinusoidal steady state response of RLC series circuit

4.1 Aim

To find the steady state response of the single phase AC circuits with Series RC, RL, and RLC load and resonance frequency of a RLC circuit using OrCAD tool

4.2 Apparatus/ Tool Required



S. No.	Components / Part	Value / Type	Keyword
1.	AC Voltage Source	V	VAC
2.	Ground	0 / Source	GND
3.	Resistors	Ω	R
4.	Inductor	H	L
5.	Capacitor	F	C


Analysis type: AC sweep/ Primary Sweep/ Global Parameters/ Linear

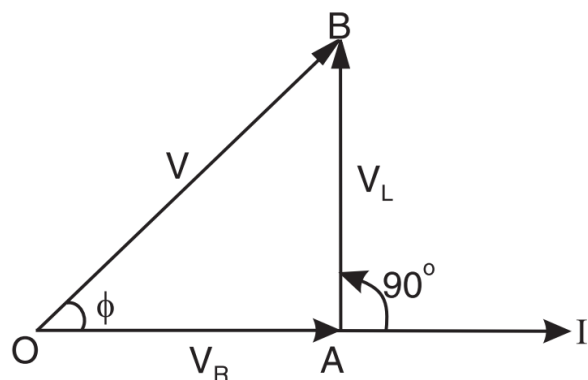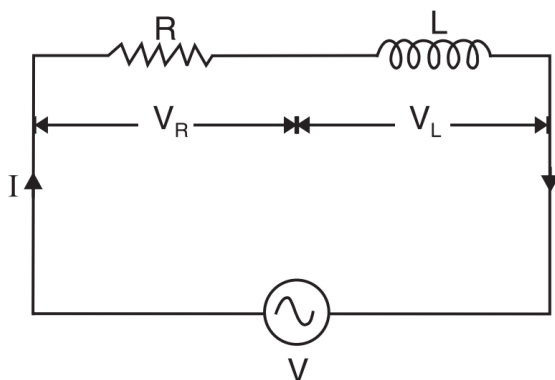4.3 Theory

R-L Series AC Circuit:

A circuit is considered with a pure resistance of $R = 7 \Omega$ in series with a coil of pure inductance $L = 31.8 \text{ mH}$ connected across a single phase AC voltage source of 230 V, 50 Hz.





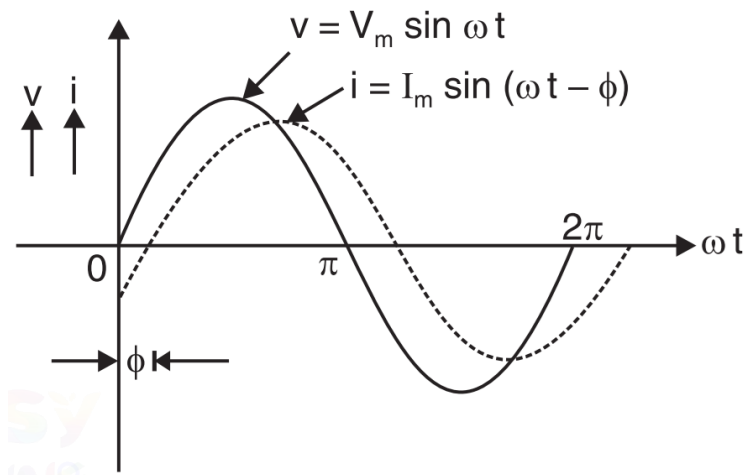

$$\tan \phi = \frac{V_L}{V_R} = \frac{IX_L}{IR} = \frac{X_L}{R}$$

R-C Series AC Circuit:

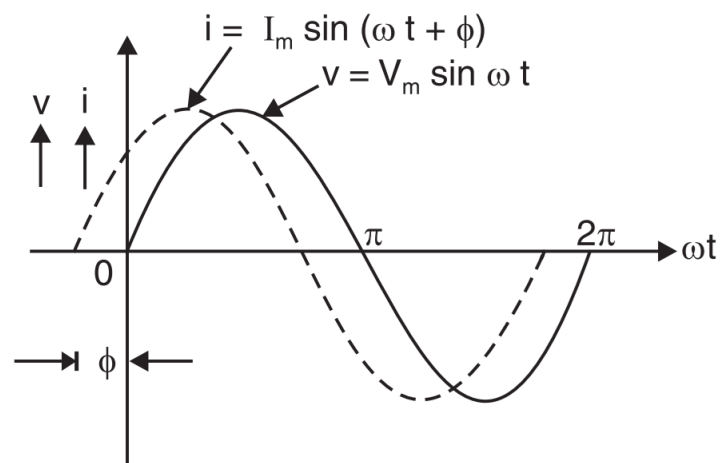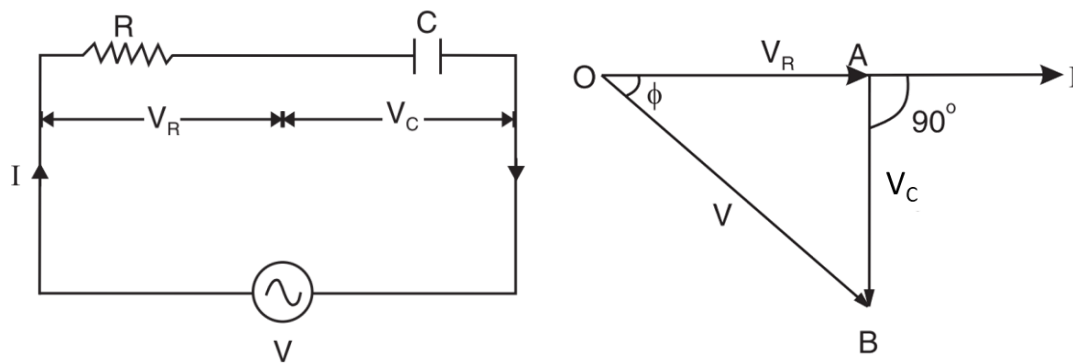
A circuit is considered with a pure resistance of $R = 30 \, \Omega$ in series with a pure capacitance $C = 79.5 \, \mu\text{F}$ connected across a single phase AC voltage source of 100 V, 50 Hz.



$$\tan \phi = \frac{V_C}{V_R} = \frac{IX_C}{IR} = \frac{X_C}{R}$$

R-L-C Series AC Circuit:

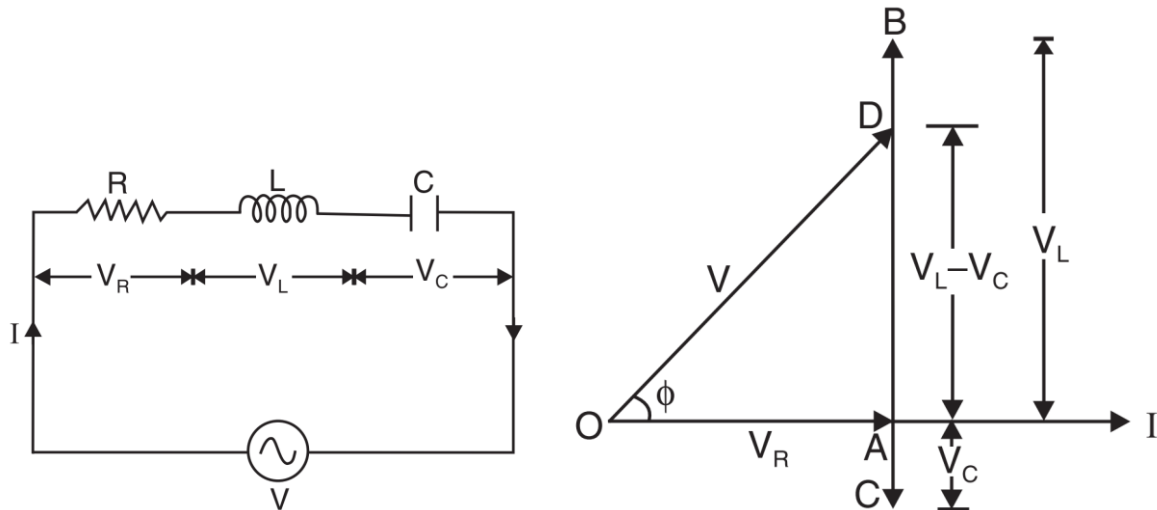A circuit is considered with a pure resistance of $R = 2.5 \Omega$ in series with a pure capacitance $C = 6.8 \mu\text{F}$ and pure Inductor $L = 0.066 \text{ H}$ connected across a single phase AC voltage source of 230 V , 50 Hz .




For an RLC circuit, $Z = \sqrt{R^2 + (X_L - X_C)^2}$

When $X_L = X_C$; Z is minimum.


$I = \frac{V}{Z}$ is maximum

The frequency found when $X_L = X_C$ is called resonance frequency.

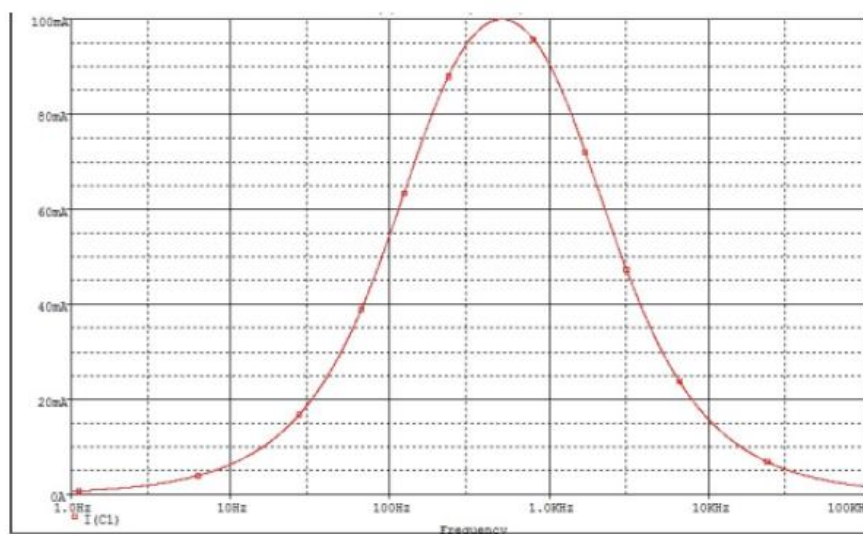Formulae:
$$f = \frac{1}{2\pi\sqrt{LC}}$$



4.4 Simulation Model

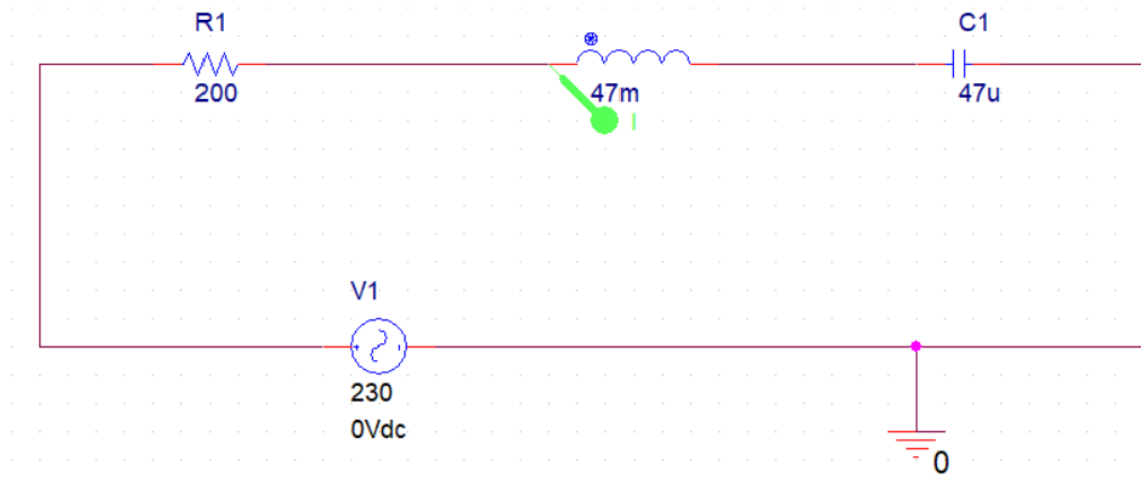

4.5 Procedure

- 1) Open orCAD Tool and create new project.
- 2) Draw the circuits using the tools: R analog, L analog, C analog, VAC/source, connecting wire
and a ground potential.
- 3) Enter the values in R, L, V and C.
- 4) Go to PSpice and create a new simulation profile.
- 5) In the simulation settings dialogue box, chose analysis type as AC Sweep. Under AC sweep
type, enter start frequency=0.1, end frequency=100000 and points/decade=100. Now enter
APPLY and OK.
- 6) Take the current marker and place at the point between wire and the inductor.
- 7) Now click Run PSpice
- 8) A different window with a bell-shaped curve opens up with its peak giving us the resonance
frequency (x coordinate) and resonance current (y coordinate).
- 9) Compare the values to the manually calculated values and write the result.

4.6 Result:

Result:-

$$\begin{aligned}\text{Calculated Resonance frequency} &= f = \frac{1}{2\pi\sqrt{LC}} \\ &= \frac{1}{2\pi\sqrt{47m \times 10^{-6}}} \\ &= 107.083\end{aligned}$$

stimulated Resonance frequency: $f = 107.152$

Inference - we studied the sinusoidal steady state response of an RLC circuit & found the resonance frequency using a simulated RLC circuit

