



**SCHOOL OF ELECTRICAL ENGINEERING**  
**CONTINUOUS ASSESSMENT TEST - I**  
**WINTER SEMESTER 2022-2023 (Freshers)**

Programme Name & Branch: **EE Freshers (B. Tech)**

Course Code: **EEEE1001**

Course Name: **Basic Electrical and Electronic Engineering**

Faculty Name(s): **Tapan Prakash**



Emp. No(s): **17094**

Class Number(s): **EE-202214000479**

Exam Duration: **90 minutes**


Maximum Marks: **50**

General Instruction(s): **Answer all questions. Assume suitable data if necessary.**

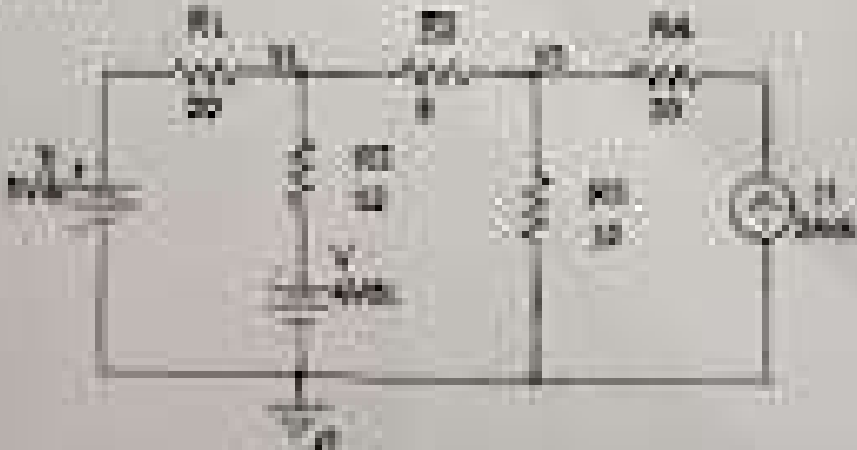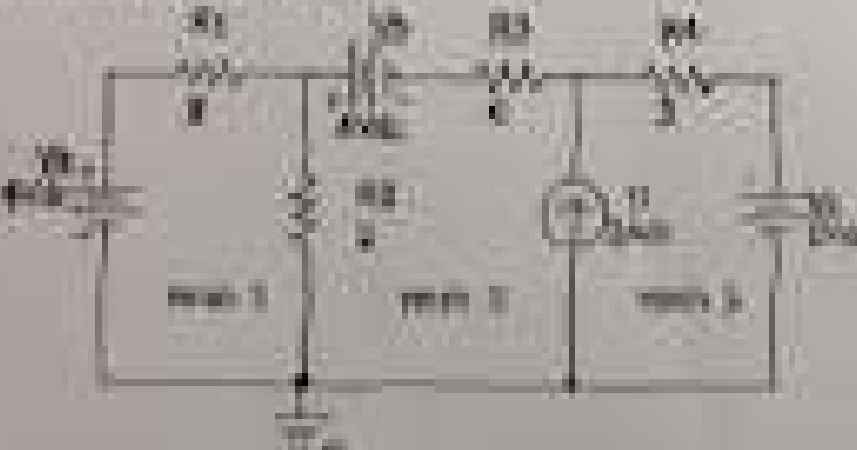Q.No	Question	Marks
1	<p>Analyze circuit given below by node analysis and find the voltages <math>V_1</math> and <math>V_2</math>. Assume values are in ohms.</p> 	10
2	<p>Find the branch currents through resistances <math>R_1</math>, <math>R_2</math>, <math>R_3</math> and <math>R_4</math> using mesh current analysis. Assume values are in ohms.</p> 	10

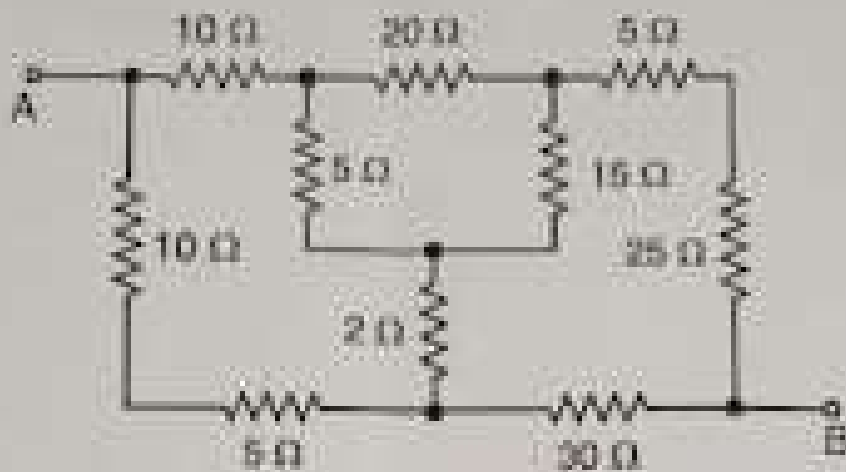1.


Apply star-delta transformation to determine equivalent resistance between terminals A and B.



10

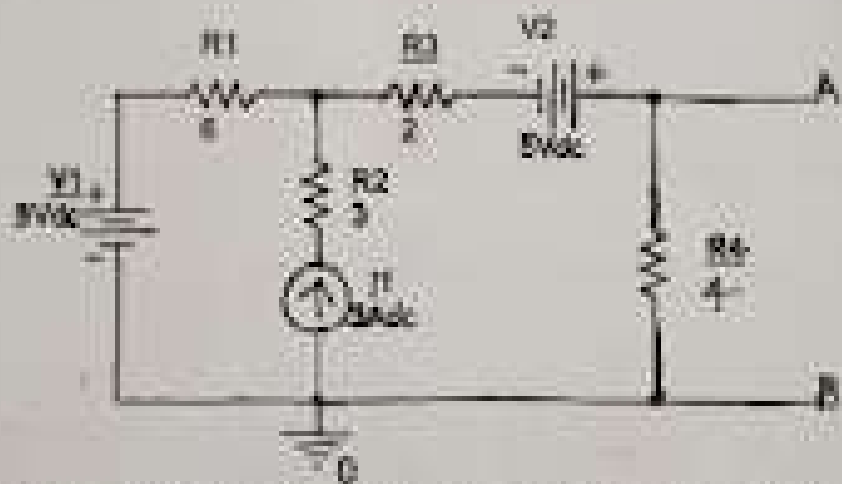4.

Find the maximum power that can be transferred through terminal AB. Resistances are in ohms.



10

3.

A resistance of 20 Ω, an inductance of 0.2 H and a capacitance of 100 μF are connected in series across 220-V, 50-Hz mains. Determine the following (a) impedance (b) current (c) voltage across R, L, and C. Draw the phasor diagram.

10