



**SCHOOL OF ELECTRICAL ENGINEERING**  
**WINTER SEMESTER 2025-2026**  
**CONTINUOUS ASSESSMENT TEST - II**

Programme Name & Branch : B.Tech. Electrical and Computer Science Engineering  
 Course Code and Course Name : BECS201L - Semiconductor Devices and Circuits  
 Faculty Name(s) : Dr. Arunkumar G  
 Class Number(s) : VL2025260506454  
 Date of Examination : 15/03/2026, 09.30 to 11.00 AM  
 Exam Duration : 90 minutes Maximum Marks: 50

**General instruction(s):**

- Answer All Questions
- Rough work should not be done on question paper. It will be treated as malpractice.
- M - Max mark; CO - Course Outcome; BL - Blooms Taxonomy Level (1 - Remember, 2 - Understand, 3 - Apply, 4 - Analyse, 5 - Evaluate, 6 - Create)

**Course Outcomes Statements:**

CO. 3: Comprehend design aspects of amplifier circuits

CO. 4: Analyze the performance characteristics and applications of Op-Amp

| Q. No | Question                                                                                                                                                                                                                                                                                                                                                   | M  | CO | BL |
|-------|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----|----|----|
| 1.    | In a BJT CE voltage-divider bias (VDB) amplifier circuit, $V_{CC} = 22\text{ V}$ , $R_1 = 15\text{ k}\Omega$ , $R_2 = 4.7\text{ k}\Omega$ , $R_C = 2.2\text{ k}\Omega$ , $R_E = 1\text{ k}\Omega$ , $\beta = 200$ , $V_s = 10\text{ mV}$ , $R_L = 10\text{ k}\Omega$ , $R_S = 5\text{ }\Omega$ . Determine, $Z_i$ , $Z_o$ , $A_v$ and $V_o$ .              | 10 | 3  | 3  |
| 2.    | In a E-MOSFET CS voltage-divider bias (VDB) amplifier circuit, $V_{DD} = 40\text{ V}$ , $R_1 = 22\text{ M}\Omega$ , $R_2 = 18\text{ M}\Omega$ , $R_D = 3\text{ k}\Omega$ , $R_S = 0.82\text{ k}\Omega$ , $k = 0.12\text{ mA/V}^2$ , $V_{th} = 5\text{ V}$ , $V_s = 5\text{ mV}$ , $R_L = 10\text{ k}\Omega$ . Determine, $Z_i$ , $Z_o$ , $A_v$ and $V_o$ . | 10 | 3  | 3  |
| 3.    | a) In a BJT CE Class A Power Amplifier circuit, $V_{CC} = 15\text{ V}$ , $I_{CQ} = 64.1\text{ mA}$ , $V_{CEQ} = 5.756\text{ V}$ , $V_{Orms} = 2.07\text{ V}$ , $R_L = 100\text{ }\Omega$ . Determine the efficiency of the circuit.                                                                                                                        | 5  | 3  | 3  |
|       | b) In a CE Differential Amplifier circuit, $V_{CC} = 15\text{ V}$ , $V_{EE} = -15\text{ V}$ , $R_C = 5\text{ k}\Omega$ , $R_E = 7.5\text{ k}\Omega$ . Use the second-approximation method to determine $I_T$ , $I_E$ , $V_{C1}$ and $V_{C2}$ .                                                                                                             | 5  |    |    |
| 4.    | a) Design an Op-Amp inverting summer circuit to produce $V_o = -(3V_1 + 5V_2)$                                                                                                                                                                                                                                                                             | 5  | 4  | 3  |
|       | b) Design an Op-Amp practical integrator with a DC gain of 20 to integrate a square wave of 10 kHz.                                                                                                                                                                                                                                                        | 5  |    |    |
| 5.    | Construct six cases of comparator circuits using an Op-Amp, with an input sine-wave of 5V, 3V as reference voltage. Sketch the necessary wave forms.                                                                                                                                                                                                       | 10 | 4  | 3  |