



VIT[®]

Vellore Institute of Technology
(Deemed to be University under section 3 of UGE Act, 1956)

School of Electronics Engineering

CAT I

BECE 102L- Digital Systems Design

Programme & Branch: B. Tech. ECE

Slot: C1+TC1

Duration: 90 minutes

Marks: 50

Class Numbers: VL2022230503275, 3276, 3278

Faculty: Dr Rajesh N, Dr Niroj Kumar Sahu , Dr Sathya P

Answer ALL the Questions

S.No	Question	CO	BTL	Mark
1	(i) Simplify the Boolean function by Boolean algebra $F = AB + (AC)' + AB'C (AB+C)$ (ii) Obtain the canonical POS of the expression $F = A+B'C$	1	2	5 5
2	Realize the function using (a). AOI logic , (b). NAND only logic (c). NOR only logic $F = A'B' + A'C' + B'C'$	1	2	10
3	Obtain the (a). minimum SOP and (b). minimum POS of the function $F(A,B,C,D) = \sum m(0,1,2,5,8,9,10)$ using 4 variable K – Map	1	3	10
4	Write a gate level modelling program for Full Subtractor.	2	1	10
5	(1) Consider the following inputs to solve the expressions. $a = 4'b1011, b = 4'b0110, c = 4'b10xx, d = 4'b10x1, e = 4'b10zz$	2	3	5

$y1 = (a \& e)$


$y2 = (a != b)$

$y3 = (b == c)$

$y4 = (a \wedge b)$

$y5 = \{2\{a\}, \{b\}\}$

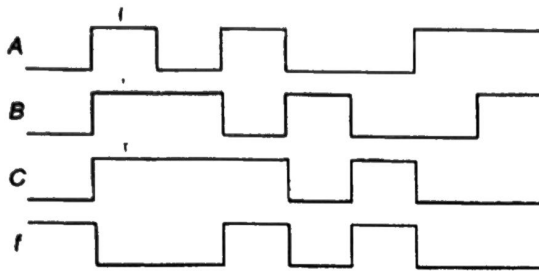(ii) Given the timing diagram of a function. Find the displayed function as sum of minterm in simplified form. Consider A, B, C are the inputs and f is the output.



5