 


**VIT**Vellore Institute of Technology
(Deemed to be University under section 3 of U.C. Act, 1956)**School of Computer Science and Engineering****Fall Semester 2022-2023****Continuous Assessment Test – II****Programme Name & Branch : BTECH CSE****SLOT: D1+TD1****Course Name & code: Digital Systems Design BECE102L****Class Number (-):** VL2022230104432, VL2022230104433, VL2022230104434,
VL2022230104441, VL2022230104438, VL2022230104437, VL2022230104441,
VL2022230104442, VL2022230104446, VL2022230104442, VL2022230104574**Faculty Name (s):** JAYAKRISHNAN P, SHWETA B THOMAS, MANGAIYARKARASI R,
DEBASHIS MAJI, SUMIT KUMAR JINDAL, RAJESH G, DEBASHISH DASH, ANJU
THOMAS, VIKAS VIJAYVARGIYA, KUMARANARAYANA SWAMY C, DINAH ANN
VARUGHESE**Exam Duration: 90 Min.****Maximum Marks: 50****General instruction(s):**

Mention the question number outside the margin clearly. Answer in sequential order with clarity.
Draw the diagrams neatly using appropriate pencil and scale.

Q.N o.	Questions	Max Marks
✓ 1.	i. Implement the following Boolean function using a multiplexer. $F(A,B,C,D) = \sum(0,1,5,6,9,11,12,13,14)$ ii. For the above design, write a verilog code using conditional operator.	5 5
✓ 2.	Implement a 2-bit magnitude comparator using 4to16 decoder	10
✓ 3.	i. Consider a data transmission system used to transmit 4-bit data. The system uses odd parity to detect the error in transmission. Design a system that generates the parity bit at the transmitter side and checks the parity at receiver side. ii. Write a Verilog code for the above design.	5 5

4.	i. Design a D-Flip flop using T Flip Flop ii. Write a verilog code for the above design using structural modelling.	5 5
5.	In the sequential circuit using JK Flip Flop given below, assume that the initial value of $Q_1 = 0$ & $Q_2 = 1$ and give the function table and draw the wave sequences of the outputs Q_1 and Q_2 for 6 positive edge clock cycles. 	10

$$(A=B) = D_0 + D_5 + D_{10} + D_{15}$$

$$(A>B) = D_4 + D_8 + D_9 + D_{12} + D_{13} + D_{14}$$

$$(A<B) = D_1 + D_2 + D_3 + D_6 + D_7 + D_{11}$$