



Vellore – 632014, Tamil Nadu, India
SCHOOL OF ELECTRICAL ENGINEERING
FALL SEMESTER 2023-2024
CAT-II

SLOT: D1

Programme Name & Branch : B.Tech (EEE & EIE)

Course Code: BEEE205L

Course Name : Electronic Devices & Circuits

Faculty Members : Dr. M.N. Venkataraman, Dr. P. Uma Sathyakam, Dr. R. Gnanavignesh

Class Number(s) : VL2023240103145


Date of the Examination : 18-October-2023



Duration : 90 minutes


Max. Marks : 50

General instruction(s): Use calculator to the numerical with three decimal points.

Answer ALL Questions

 Q. No.	Question	Max. Marks	CO	BL
1.	Figure 1 depicts a partially bypassed common emitter amplifier. Find the following metrics for the amplifier if $\beta = 100$ and $V_{BE,ON} = 0.7$ V. a) DC operating conditions (2.5 marks) b) Input impedance (2.5 marks) c) Overall voltage gain (2.5 marks) d) Output impedance (2.5 marks)	10	2	L3
 Figure 1				

  2.	For the amplifier depicted in Figure 2, the input signal source v_s is a sinusoid of frequency 50 Hz and amplitude of 5 mV. The output load is denoted by R_L. With the given parameters $\alpha = 0.98$ and $V_{BE,ON} = 0.7$ V, determine the following - Input impedance (2.5 marks) - Overall voltage gain (2.5 marks) - Output impedance (2.5 marks) - Output voltage amplitude in mV (2.5 marks)  Figure 2	10	2	L4
3.	For the emitter follower shown in Figure 3, $\beta = 100$ and $V_{BE,ON} = 0.7$ V. Obtain the following: - Input impedance (2 marks) - Voltage gain (2 marks) - Output impedance (3 marks) - Proof that the device small signal voltage gain is always less than 1. (3 marks)  Figure 3	10	2	L5

 4.	Explain with appropriate diagrams, the working principle of a n-channel enhancement MOSFET.	10	2	L2
5.	Find V_{GS}, I_D and V_{DS} for the following circuit shown in Figure 4. The given parameters for the n-channel enhancement MOSFET are $V_{TN} = 5 \text{ V}$, $K = 0.12 \text{ mA/V}^2$.  Figure 4	10	2	L5