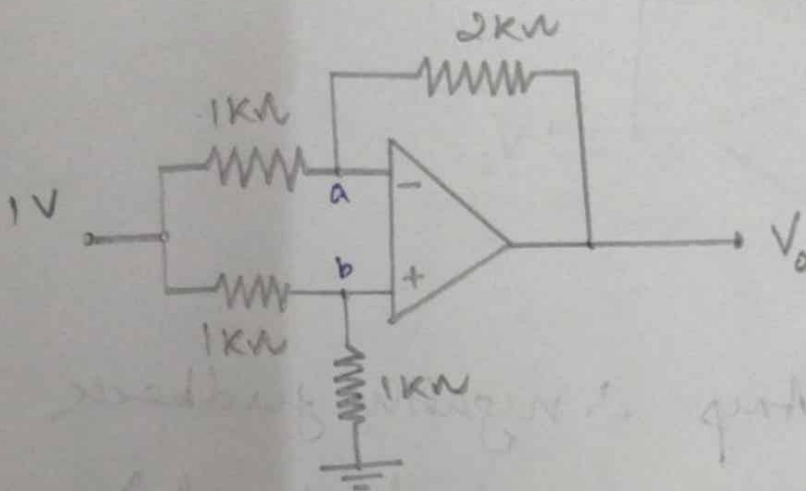


① the ideal op Amp is used. $V_o = \underline{\hspace{2cm}}?$



Solⁿ: Here, Op Amp in negative feedback

$\therefore V^+ = V^-$ (Virtual short)

$$\therefore V_b = \frac{1 \times 1 \text{ k}\Omega}{(1+1) \text{ k}\Omega} = 0.5 \text{ V} \quad \left(\begin{array}{l} \text{voltage division} \\ \text{across two } 1 \text{ k}\Omega \\ \text{resistances} \end{array} \right)$$

$$\therefore V^+ = V^- = 0.5 \text{ V}$$

Now, at node a, nodal analysis,

$$\frac{-V_a + 1}{1 \text{ k}\Omega} = \frac{V_a - V_o}{2 \text{ k}\Omega} \quad \left(\because V_a = V^- = 0.5 \text{ V} \right)$$


$$\Rightarrow 2(-0.5 + 1) = 0.5 - V_o$$

$$\Rightarrow 1 - 0.5 = -V_o$$

$$\therefore V_o = -0.5 \text{ V}$$

Ans

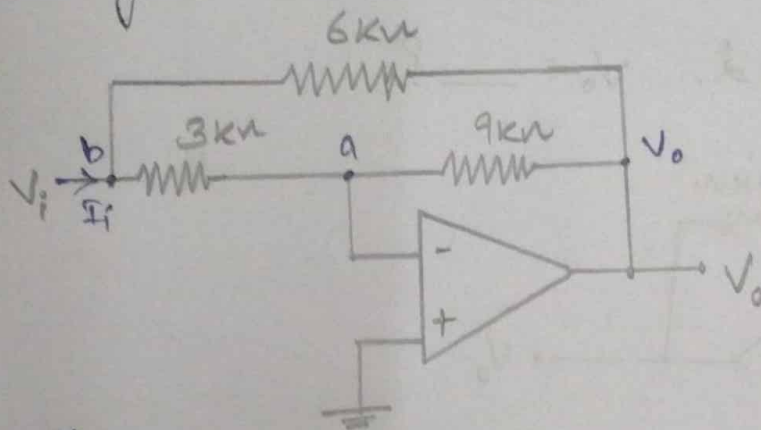Q2 Assume OpAmp to be ideal. The input resistance of the circuit is ____



Solⁿ Here, ideal opAmp $\therefore$ negative feedback

$$V^+ = V^- = 0V \text{ (virtual short)}$$

$$\boxed{V_a = 0V} \text{ (1)}$$

Assume, I_i input current

Now, current across $3k\Omega$ & $9k\Omega$ will be same as they are in series.

$$\therefore \frac{V_i - V_a}{3k\Omega} = \frac{V_a - V_o}{9k\Omega} \Rightarrow 3V_i = -V_o$$

$$\boxed{\therefore V_o = -3V_i} \text{ (2)}$$

Now, Applying KCL at node 'b',

$$I_i = \frac{V_i - V_a}{3k\Omega} + \frac{V_i - V_o}{6k\Omega} \quad \text{(substituting values of (2))}$$

$$\Rightarrow I_i = \frac{V_i - 0}{3k\Omega} + \frac{V_i + 3V_i}{6k\Omega}$$


$$\Rightarrow I_i = \frac{V_i}{3k\Omega} + \frac{4V_i}{6k\Omega} \Rightarrow I_i = \frac{6V_i}{6k\Omega}$$

$$\Rightarrow \frac{V_i}{I_i} = 1k\Omega \text{ i.e. } \boxed{R_i = 1k\Omega} \text{ Ans}$$

Input resistance is $1k\Omega$

Ans

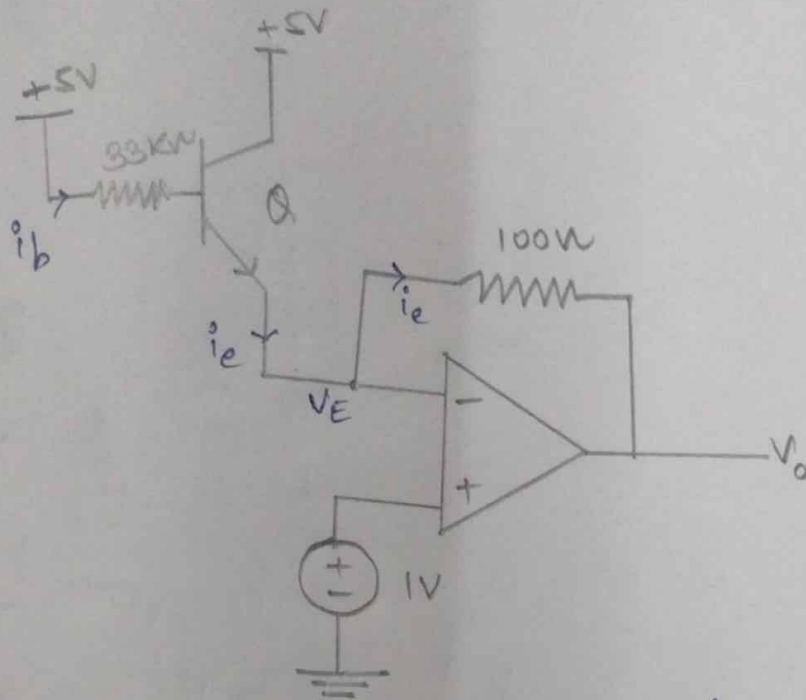Q3) Assuming $V_{BE} = 0.7V$ & $\beta = 99$ of transistor Q.
output voltage V_o in ideal opAmp circuit
is _____.



Solⁿ: Here, opAmp in negative feedback
 $\therefore V^+ = V^- = 1V = V_E$ (Virtual short)

Therefore
On BJT,

$$i_b = \frac{V_{BB} - V_{BE} - V_E}{R_B} = \frac{5 - 0.7 - 1}{33k\Omega}$$

$$\boxed{i_b = 0.10 \text{ mA}}$$

$$\text{Now, } i_e = (1 + \beta) i_b$$

$$= 100 i_b = 10 \text{ mA}$$

$$\boxed{\therefore i_e = 10 \text{ mA}}$$

Now, this i_e will flow through 100Ω resistance

$$\therefore \text{we can say, } \frac{V_E - V_o}{100\Omega} = 10 \text{ mA}$$

$$\Rightarrow 1 - V_o = \frac{10}{1000} \times 1000 \Rightarrow 1 - V_o = 1$$

$$\boxed{\therefore V_o = 0V}$$

Hence output will be 0V.

Ans