
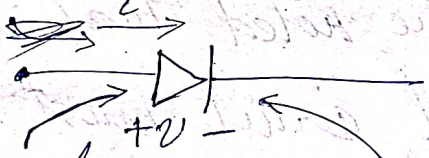
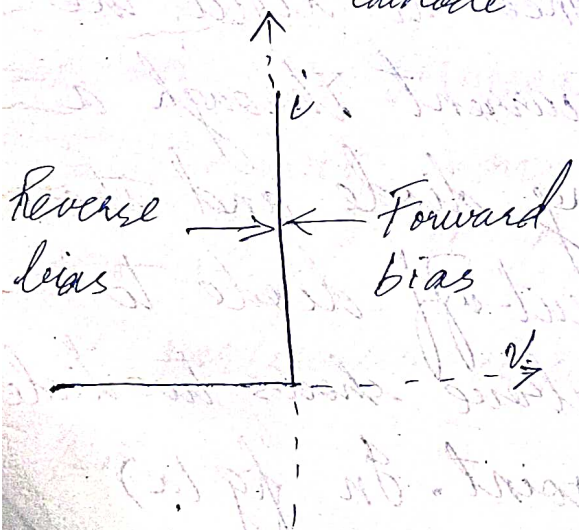



Diodes

The simplest and most fundamental non-linear circuit element is the diode. Just like a resistor, the diode has two terminals; but unlike the resistor which has a straight line relationship between the current flowing through it and the voltage appearing across it, the diode has a non-linear characteristic.

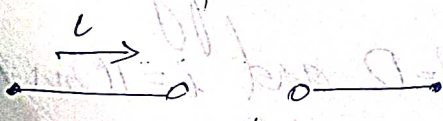The Ideal Diode: The ideal diode may be considered the most nonlinear circuit element. It is a two-terminal device having the circuit symbol  as shown in adjacent figure as well as the IV characteristic shown. The terminal characteristics of the ideal diode can be interpreted as follows: If a negative voltage is applied to the diode,





 $v < 0 \Rightarrow i = 0$

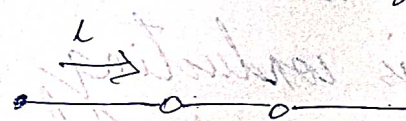

 $i > 0 \Rightarrow v = 0$

no current flows and the diode behaves as an open circuit. Diodes operated in this mode are said to be reverse biased, or operated in the reverse direction and is said to be cut-off or simply off.

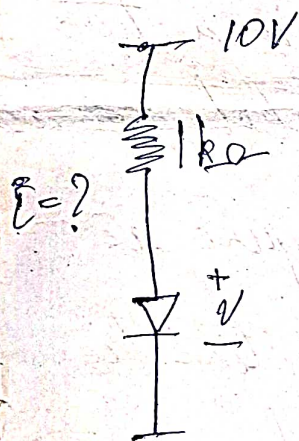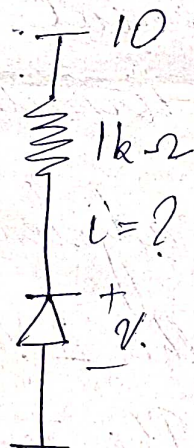On the other hand, if a positive current is applied to the ideal diode, zero voltage appears across the diode. In other words the ideal diode behaves as a short circuit in the forward direction, it passes any current with zero voltage drop. A forward biased diode is said to be turned on or simply on.



FB diode
ckt (a)



RB diode
ckt (b)

From the above description it should be noted that the external circuit must be designed to limit the forward current through a conducting diode and the

reverse voltage ~~across~~ across a cut-off diode to predetermined values. Figure above shows two diode circuits that illustrate this point. In fig (a) the diode is conducting and $V=0$ and $i=10\text{mA}$. For the reverse biased diode is cut off i.e. $V=10\text{V}$ and $i=0\text{A}$.





The positive terminal of the diode is called the anode and the negative terminal the cathode.

The $i-v$ characteristic of the ideal diode should explain this choice of its arrow-like circuit symbol.






The $i-v$ characteristic of the ideal diode is highly non-linear; although it consists of two straight line segments, they are of 90° to each other. A non linear curve that consists of straight-line segments is said to be piecewise linear. If a device having a piecewise linear characteristic is used in a particular application in such a way that the signal ~~is~~ across its terminals swings along only one of the linear segments then the device can be considered a linear ~~use~~ circuit element as far as particular circuit application is concerned.







Q.E.D.



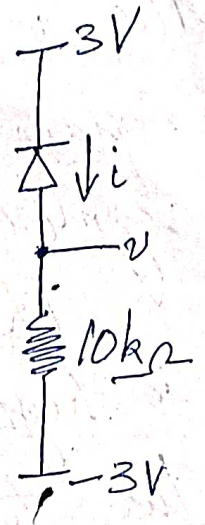
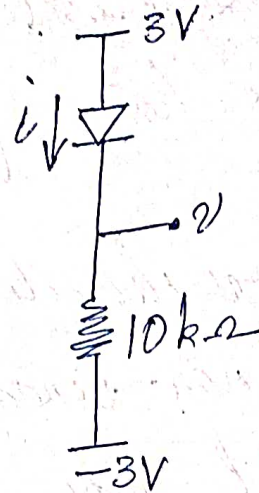
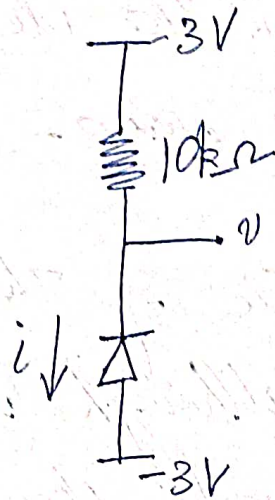
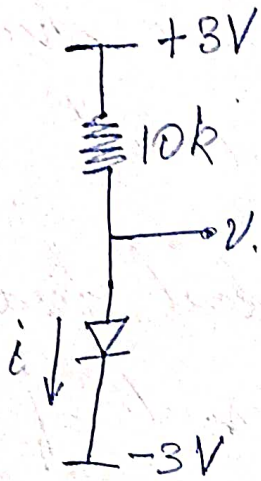
Prob: For the circuits shown in figure ~~below~~ using ideal ~~resistors~~ diodes find the voltages and currents indicated.



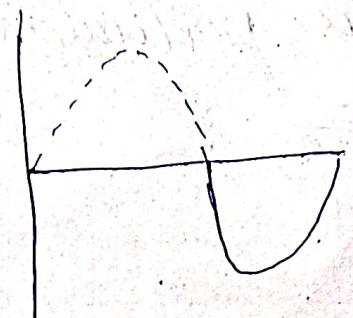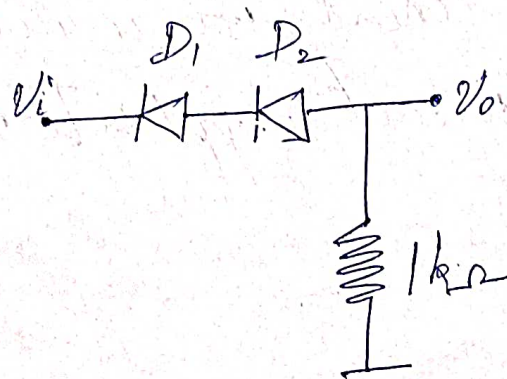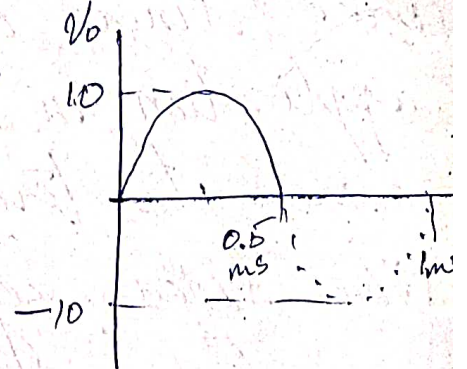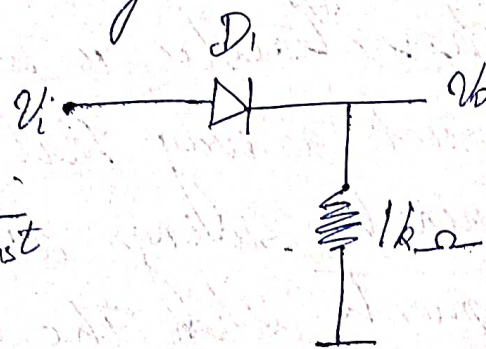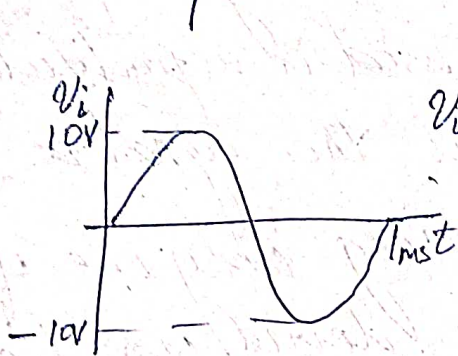Prob # In each of the diode circuits shown in figure v_i is 1kHz , 10V peak sine wave. Sketch the waveform resulting at v_o .




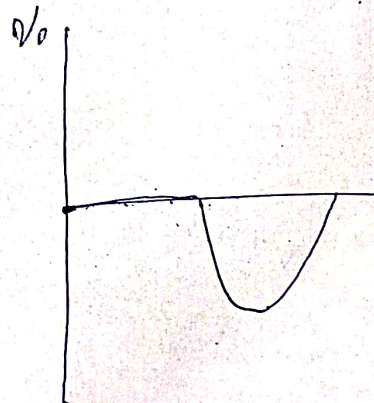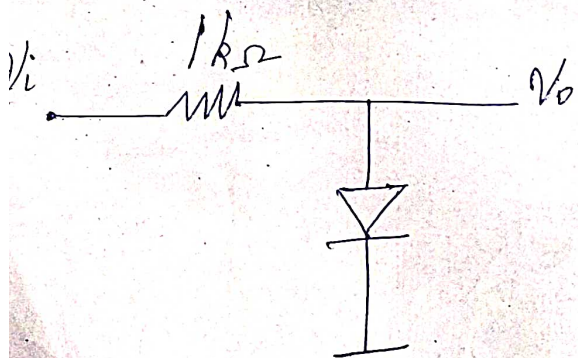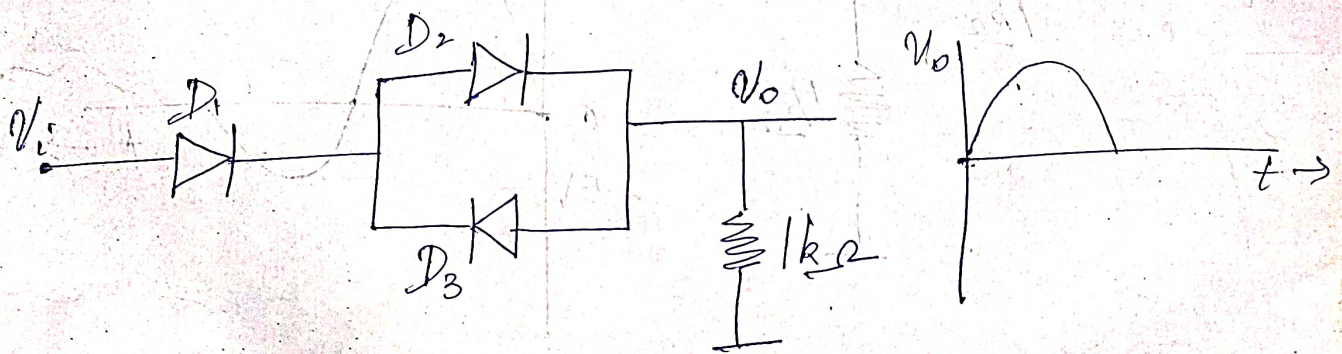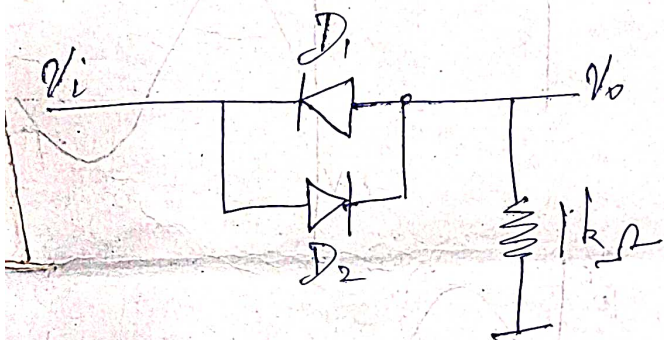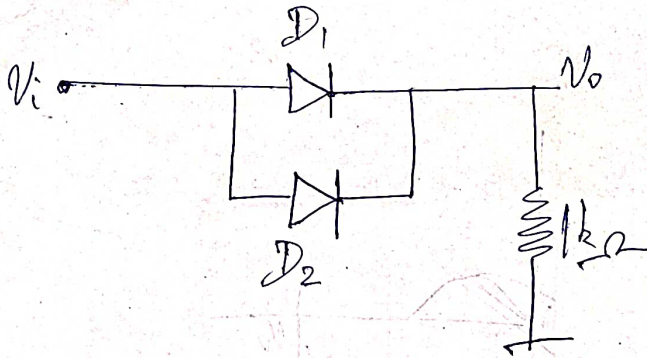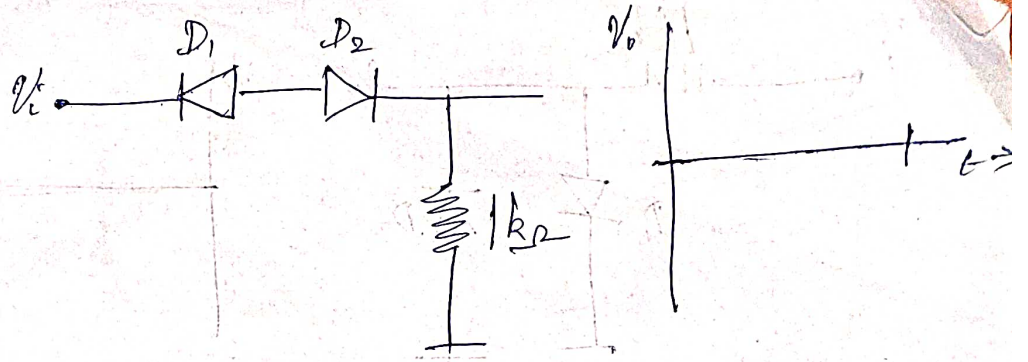

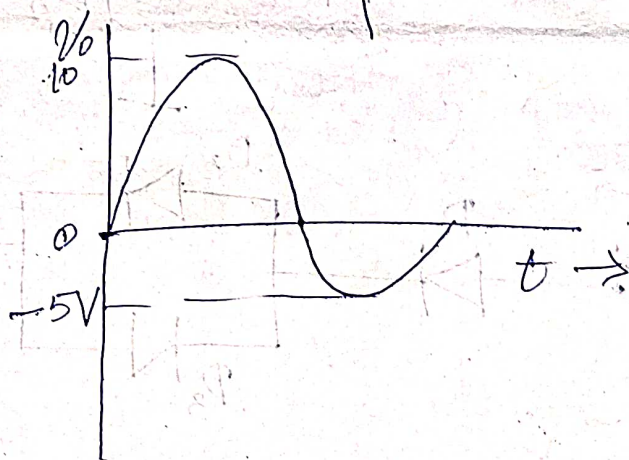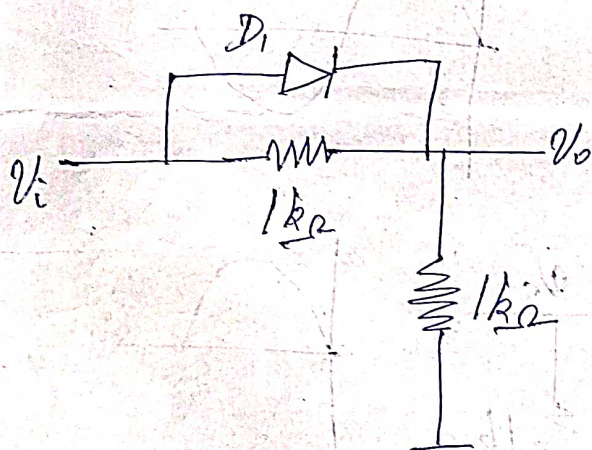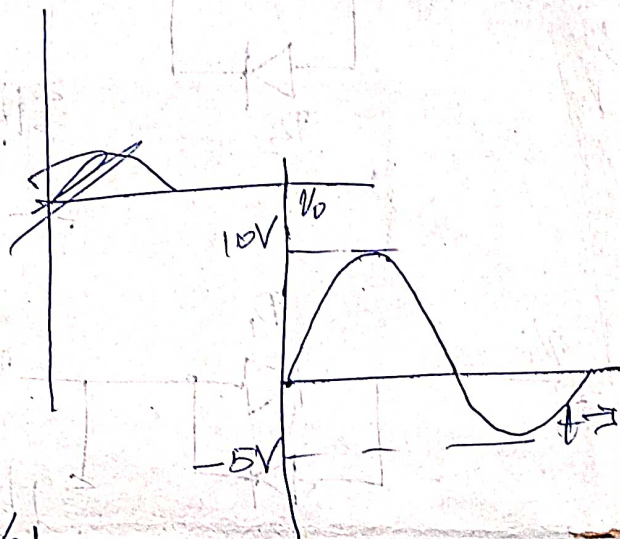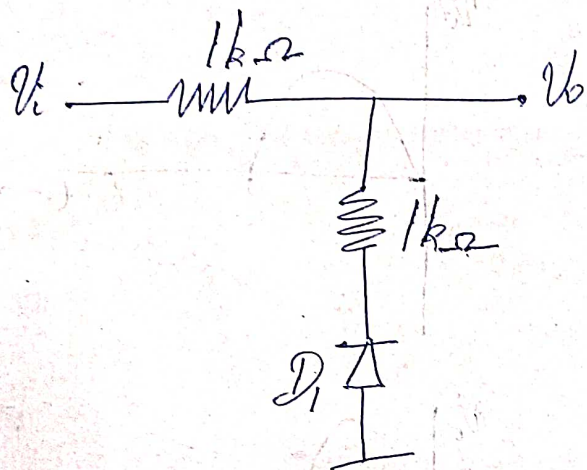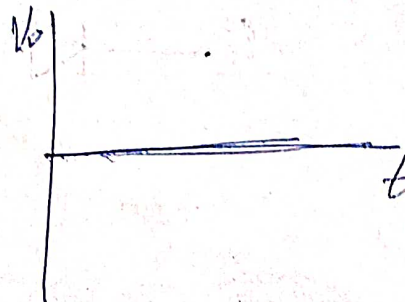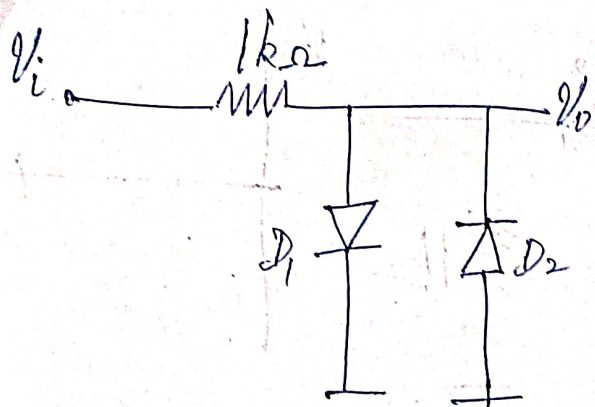


Real diodes (Practical Diodes) as Ideal diodes Extension.

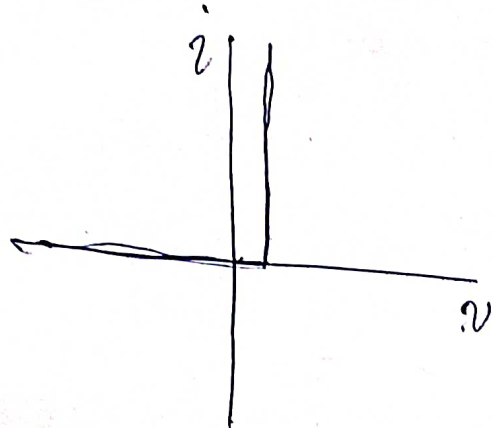
If the applied voltages are large the practical diode characteristics can be approximated as



practical diode

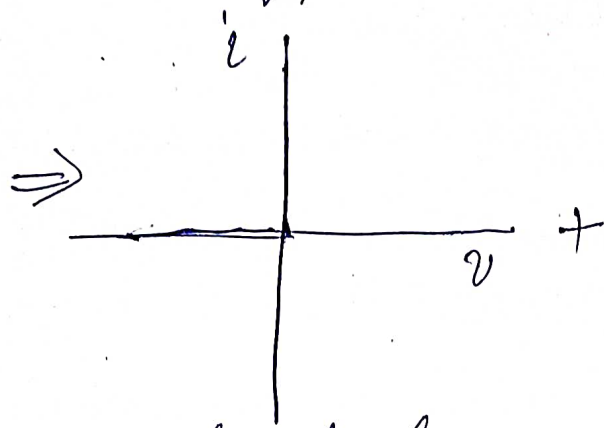


ideal diode

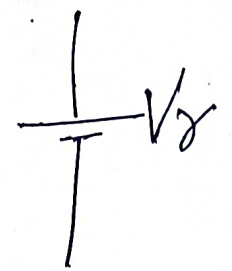

battery of voltage V_s

Practical diode replacement:

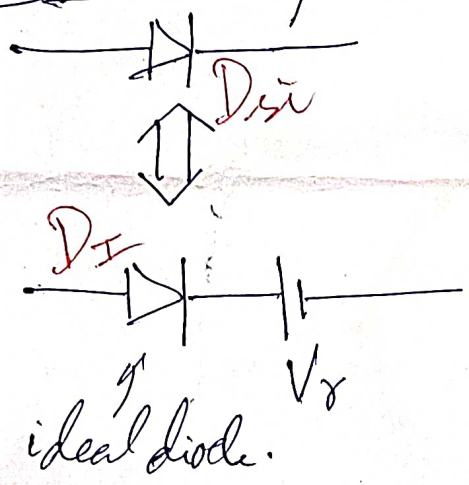

ideal diode.