

DECODER

- A binary decoder is a combinational logic circuit that converts binary information from the n coded inputs to a maximum of 2^n unique outputs.
- We have following types of decoders $2 \times 4, 3 \times 8, 4 \times 16, \dots$

2x4 decoder

 


Fig 1: Block diagram


| Inputs | | Output | | | |
|--------|---|----------------|----------------|----------------|----------------|
| A | B | D ₀ | D ₁ | D ₂ | D ₃ |
| 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |

Fig 2: Truth table

DECODERS


Higher order decoder implementation using lower order:

Ex: 4x16 decoder using 3x8 decoders

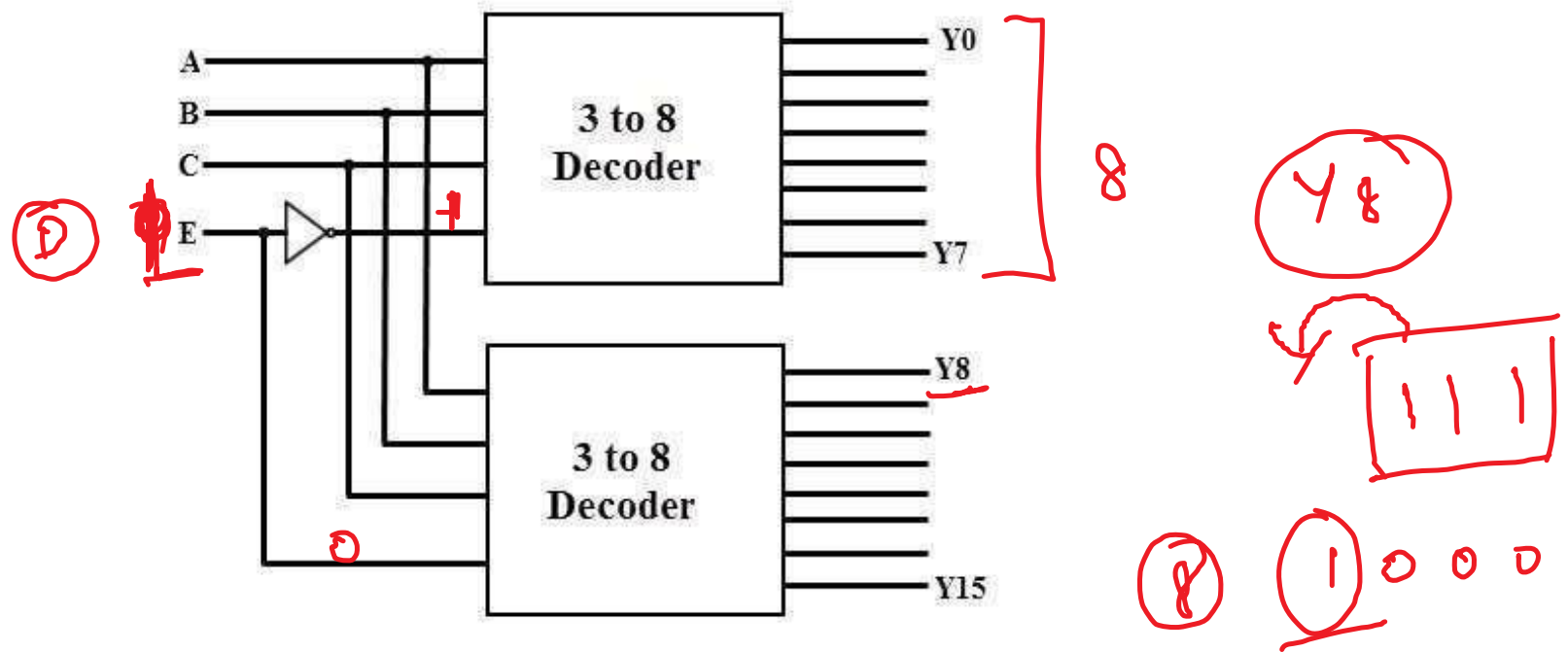


Decoders

Demux

 


 - The decoder is called **n-to-m-line decoder**, where $m \leq 2^n$.




- The decoder is also used in conjunction with other code converters such as a **BCD-to-seven-segment decoder**.

 - 3-to-8 line decoder: For each possible input combination, there are seven outputs that are equal to 0 and only one that is equal to 1.



Binary decoder

n -data

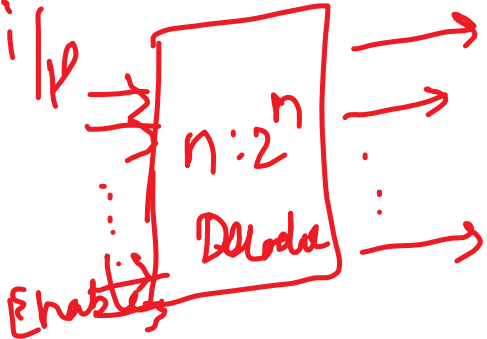

possible
 2^n
o/p.


Transmitter n
ip. $\rightarrow 2^n$

ip

En ip
- - - - -

(2) ip
A 2^1
B 2^0

$2^n = 4$ / o/p
3 Y_3
2 Y_2
1 Y_1
 Y_0

 


00
01
10
11
ip

o/p
Decoder

o/p
seven
segment
display

BCD
(0-9)

Seven
segment
display

 


$n \rightarrow 2^n$

$2 \rightarrow 2^4 = 2 \text{ to } 4 \text{ decoder.}$


→ A decoder which has a n -bit binary 'i/p' code and a one activated o/p out of 2^n o/p code is called binary decoder.





| En | A | B | Y_3 | Y_2 | Y_1 | Y_0 |
|----|---|---|-------|-------|-------|-------|
| 0 | X | X | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 | 0 | 0 |

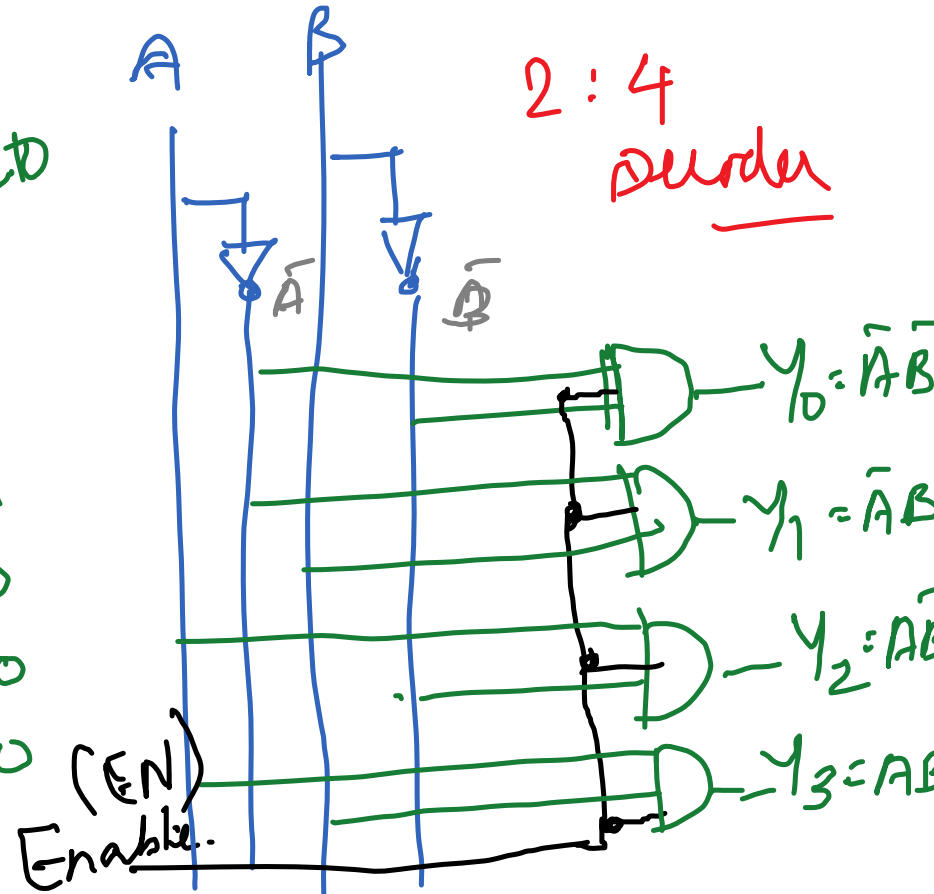


2 to 4 Decoder IC 74x138
3 to 8 Decoder IC 74x138

0

 

    

BCD
 0 000
 1 001
 2 010
 3 011

 


3 to 8 pin (line) decoder.

| <u>En</u> | A | B | C | Y_7 | Y_6 | Y_5 | Y_4 | Y_3 | Y_2 | Y_1 | Y_0 | |
|-----------|---|---|---|-------|-------|-------|-------|-------|-------|-------|-------|---|
| 0 | X | X | X | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |

A B C

3 to 8 Decoder

 

$Y_0 = \bar{A}\bar{B}\bar{C}$

$Y_1 = \bar{A}\bar{B}C$

$Y_2 = \bar{A}B\bar{C}$

$Y_3 = \bar{A}BC$

$Y_4 = A\bar{B}\bar{C}$

$A\bar{B}C$

$\bar{A}B\bar{C}$

ABC

4.2.2 The 74X138 3-to-8 Decoder

 


Fig. 4.9 Logic symbol

The 74X138 is a commercially available 3-to-8 decoder. It accepts three binary inputs (A, B, C) and when enabled, provides individual active low outputs ($Y_0 - Y_7$). The device has three enable inputs: two low ($\overline{G}_{2A}, \overline{G}_{2B}$) and one active high (G_1). Fig. 4.9 and Table 4.4 show logic symbol and function table respectively.

| Inputs | | | | | | Outputs | | | | | | | |
|----------|----------|-------|---|---|---|------------------|------------------|------------------|------------------|------------------|------------------|------------------|------------------|
| G_{2B} | G_{2A} | G_1 | C | B | A | \overline{Y}_7 | \overline{Y}_6 | \overline{Y}_5 | \overline{Y}_4 | \overline{Y}_3 | \overline{Y}_2 | \overline{Y}_1 | \overline{Y}_0 |
| 1 | X | X | X | X | X | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| X | 1 | X | X | X | X | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| X | X | 0 | X | X | X | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 |
| 0 | 0 | 1 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 |
| 0 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |

Table 4.4 Function table

2 to 4 Decoder using IC 74x139

74x138 3 to 8

Per decoder

74x139 2 to 4

Decoder

4.2.3 The 74X139 Dual 2-to-4 Decoder

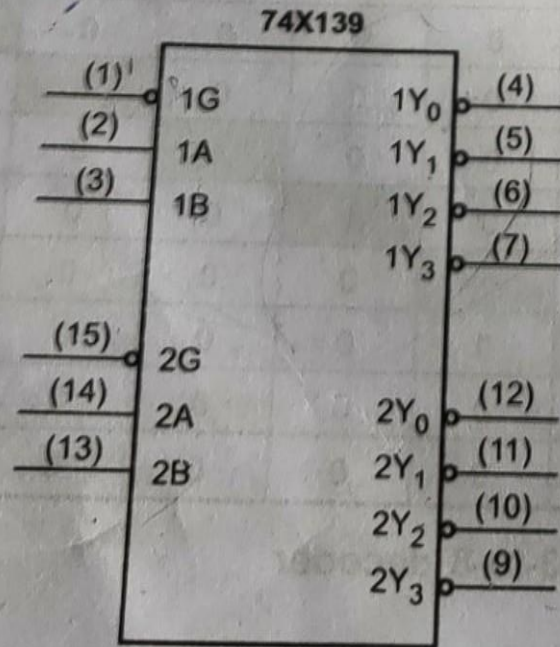


Fig. 4.10 Logic symbol for IC 74X139

The 74X139 consists of two independent and identical decoders. The enable inputs and of IC 74X139 are active low. shows the logic symbol and shows the function table for IC The Table 4.5 shows the truth one half of a 74X139 dual 2-to The truth table for other half first half.

nOnePlus

$$G = 0$$

$$\overline{Y} = 1$$

$$Y_0 = Y_0'$$

0

| INPUT | | | OUTPUT | | | |
|----------------|---|---|------------------|------------------|------------------|------------------|
| G bar | B | A | Y3 bar | Y2 bar | Y1 bar | Y0 bar |
| \overline{G} | | | $\overline{Y_3}$ | $\overline{Y_2}$ | $\overline{Y_1}$ | $\overline{Y_0}$ |
| 1 | X | X | 1 | 1 | 1 | 1 |
| 0 | 0 | 0 | 1 | 1 | 1 | 0 |
| 0 | 0 | 1 | 1 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 | 1 | 1 |

$G = 1$

0

$Y_0 = 1$

$Y_1 = 1$

$Y_2 = 1$


$Y_3 = 0$

Anode

Cathode

Decoder with enable input

 - Some decoders are constructed with NAND gates, it becomes more economical to generate the decoder minterms in their complemented form.
- As indicated by the truth table, only one output can be equal to 0 at any given time, all other outputs are equal to 1.



(a) Logic diagram

E 1

| <u>E</u> | <u>A</u> | <u>B</u> | <u>D₀</u> | <u>D₁</u> | <u>D₂</u> | <u>D₃</u> |
|----------|----------|----------|----------------------|----------------------|----------------------|----------------------|
| 1 | X | X | 1 | 1 | 1 | 1 |
| 0 | 0 | 0 | 0 | 1 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 | 1 | 0 |

(b) Truth table

Fig. 4-19 2-to-4-Line Decoder with Enable Input

2.4 Cascading Binary Decoders

Binary decoder circuits can be connected together to form a larger decoder. Fig. 4.11 shows the 4 × 16 decoder using two 3 × 8 decoders.

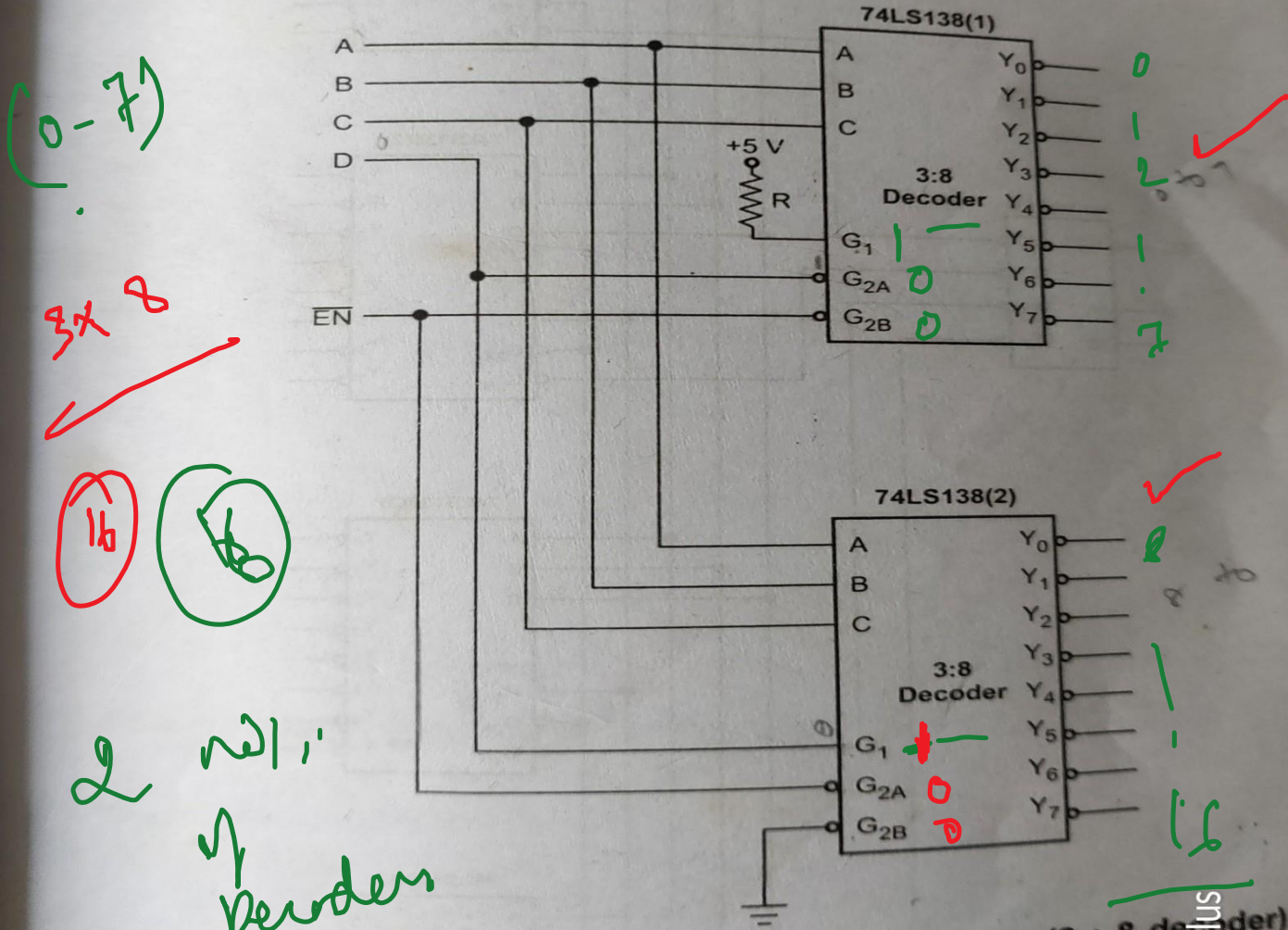



Fig. 4.11 4:16 decoder using two 74LS138 ICs (3 : 8 decoder)

Here, one input line (D) is used to enable/disable the decoders. When D is enabled and the other is disabled. Thus the bottom decoder outputs the top eight outputs generate minterms 0 0 0 0 to 0 1 1 1. When D =

Example 4.4 : Design 5-to-32 decoder using one 2-to-4 and four 3-to-8 decoder ICs.

Solution : The Fig. 4.12 shows the construction of 5-to-32 decoder using four 74LS138, half 74LS139. The half section of 74LS139 IC is used as a 2-to-4 decoder to decode the higher order inputs, D and E. The four outputs of this decoder are used to enable one

5x41 smaller
 1 24D
 5 32D
 5x32 decoder

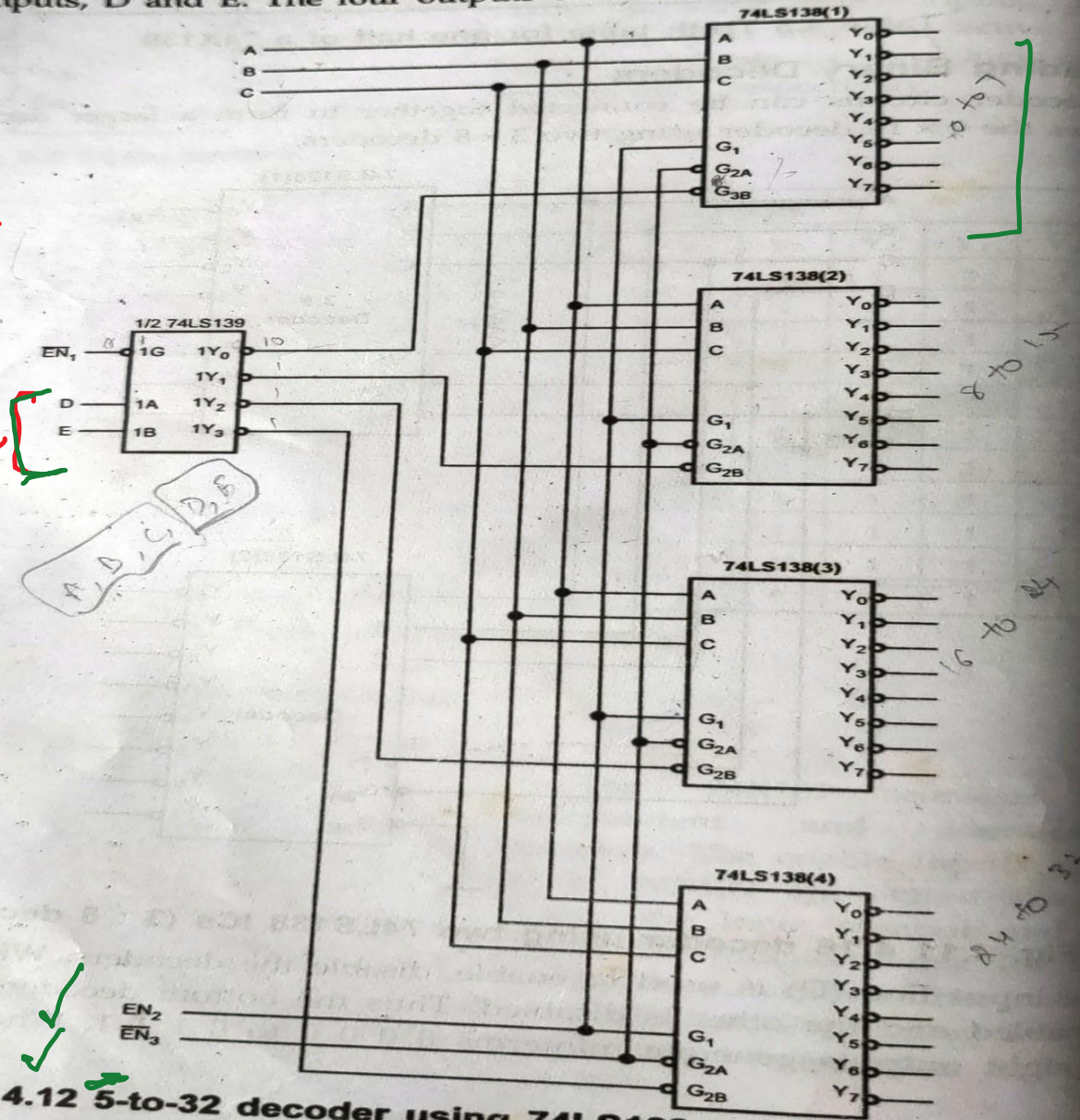

40
 0-7
 8-15
 16-24
 24-31
 32


Fig. 4.12 5-to-32 decoder using 74LS138 and 74LS139

Demultiplexer


= Decoder X } 0/1's are same

A decoder with an enable input is referred to as a decoder/demultiplexer.

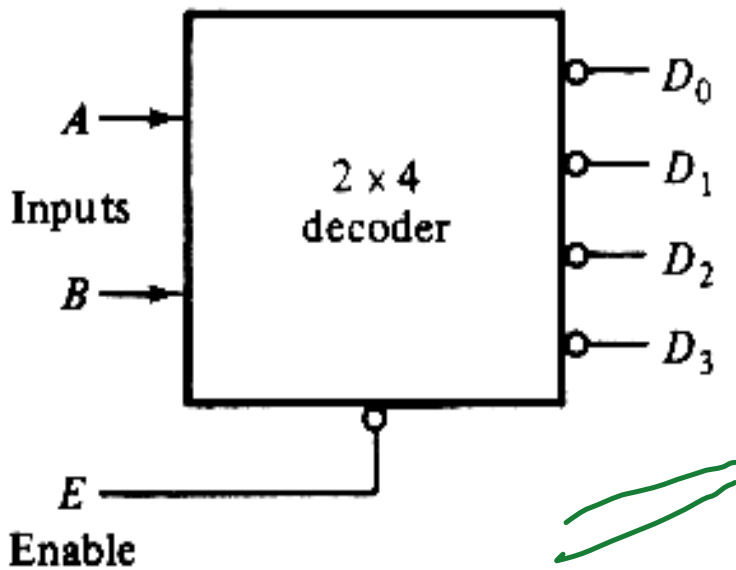The truth table of demultiplexer is the same with decoder.



E=0 XX
(a) Decoder with enable

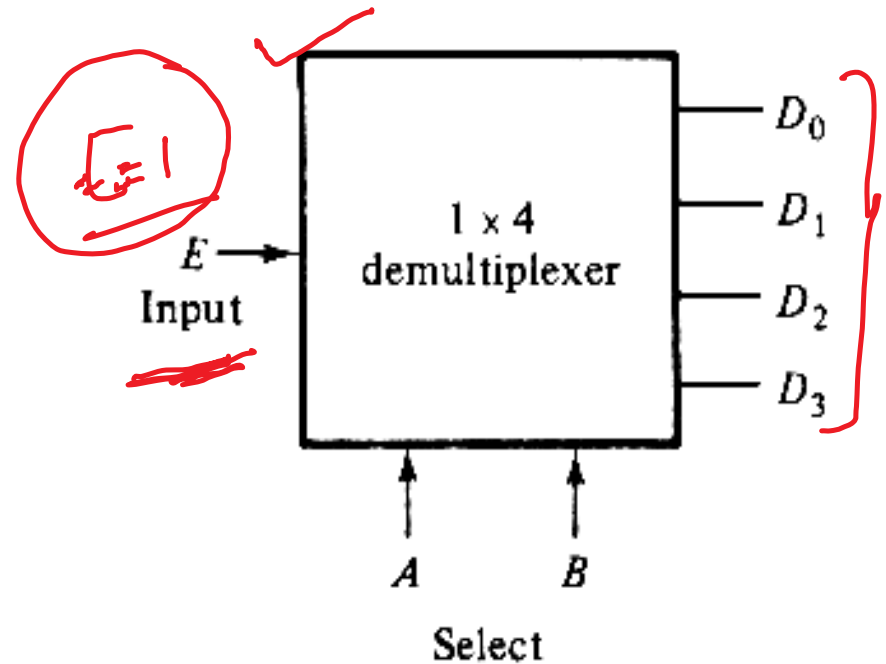

(b) Demultiplexer

3-to-8 decoder with enable implement the 4-to-16 decoder


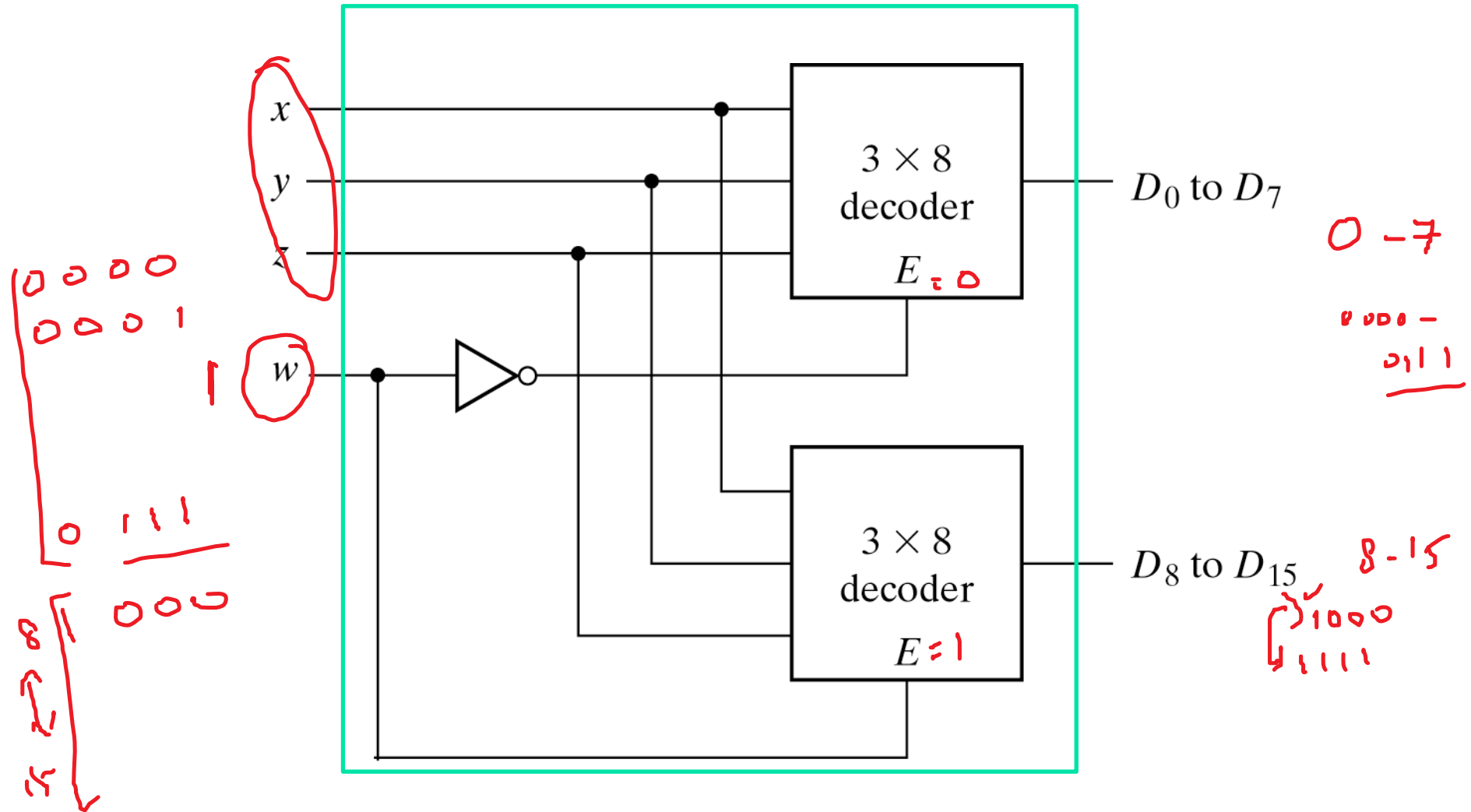


Fig. 4-20 4 × 16 Decoder Constructed with Two 3 × 8 Decoders

Cascading binary decoders


(4*16 Decoder using 3*8 decoder)

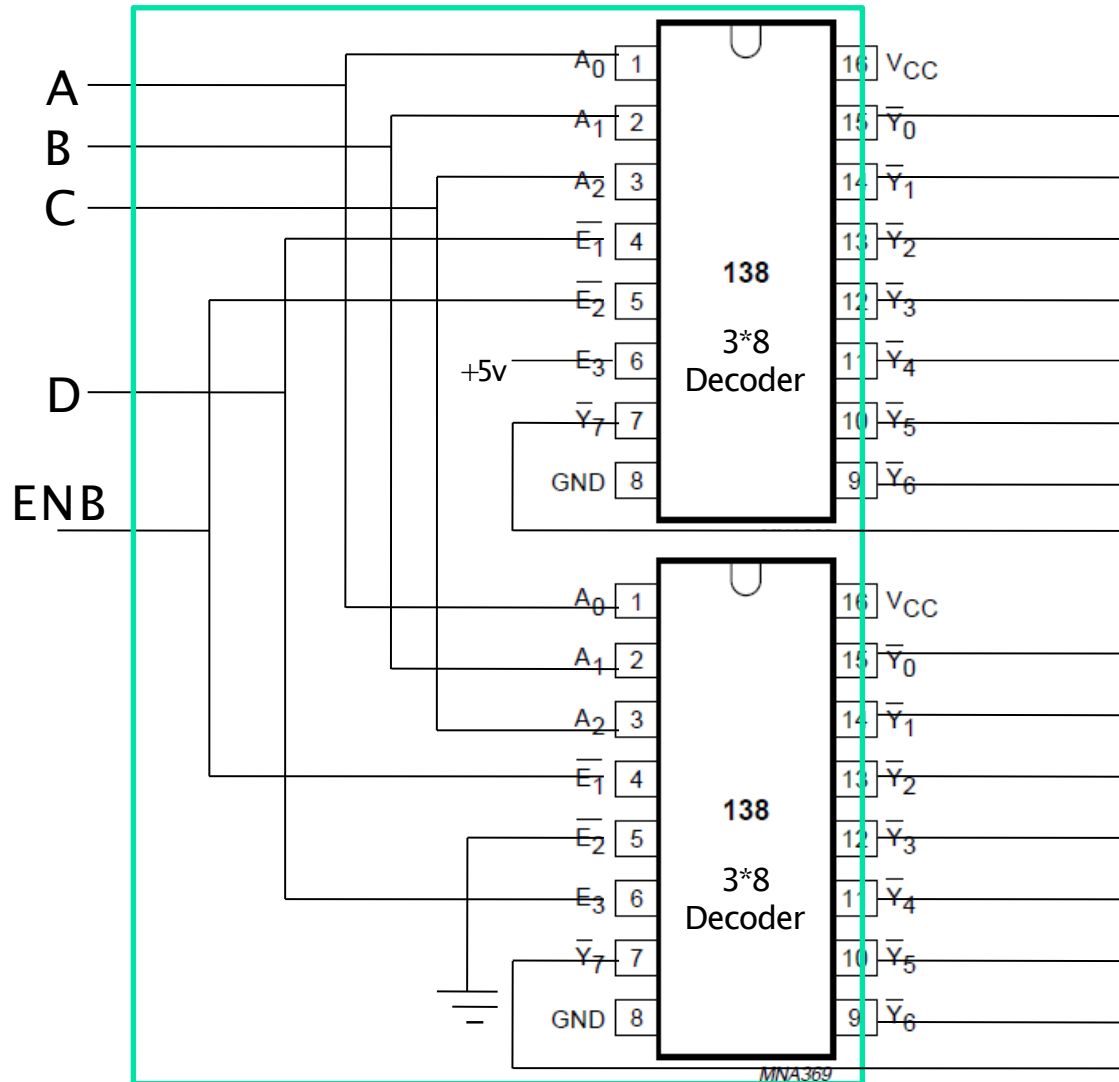

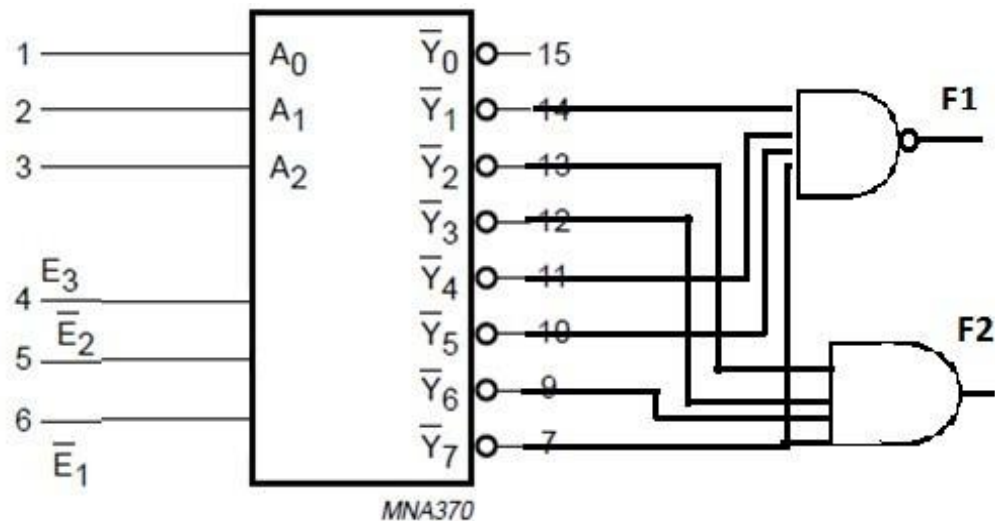Example

Implement the following multiple output function using 74LS138 and external gates. $F_1(A,B,C) = \sum m(1,4,5,7)$ & $F_2(A,B,C) = \prod m(2,3,6,7)$

74LS138 is a 3*8 decoder. The outputs of this ic have active Low, i.e in SOP form for F_1 using NAND gate and POS function for F_2 using AND gate.



Implementation of a Full Adder with a Decoder

- From table 4-4, we obtain the functions for the combinational circuit in sum of minterms:

$$S(x, y, z) = \sum(1, 2, 4, 7)$$

$$C(x, y, z) = \sum(3, 5, 6, 7)$$

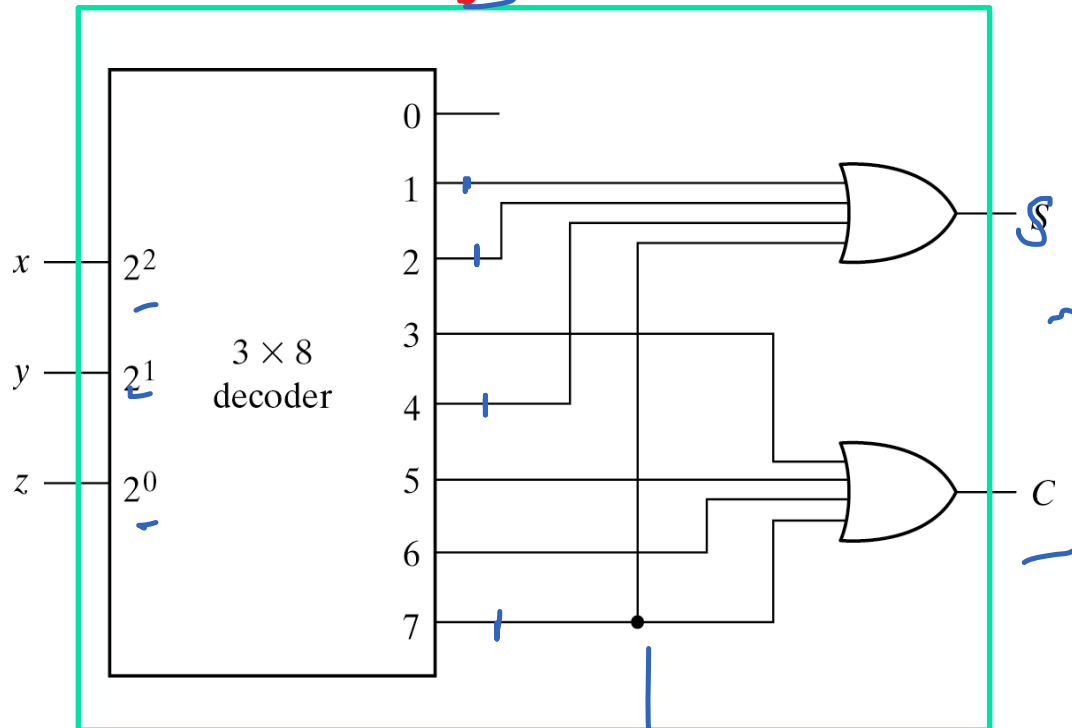


Fig. 4-21 Implementation of a Full Adder with a Decoder

Handwritten notes for the decoder inputs:
 $x = 2^2$
 $y = 2^1$
 $z = 2^0$

Handwritten notes for the sum function:
 $0-7$
 3×8
 $D. (0-7)$


Handwritten notes for the carry function:
 $\Sigma = OR$
 Decoder
 $(8-16)$
 decoder cascaded.

$$n \rightarrow 2^n$$


Decoder




DeMUX Multiplexer.

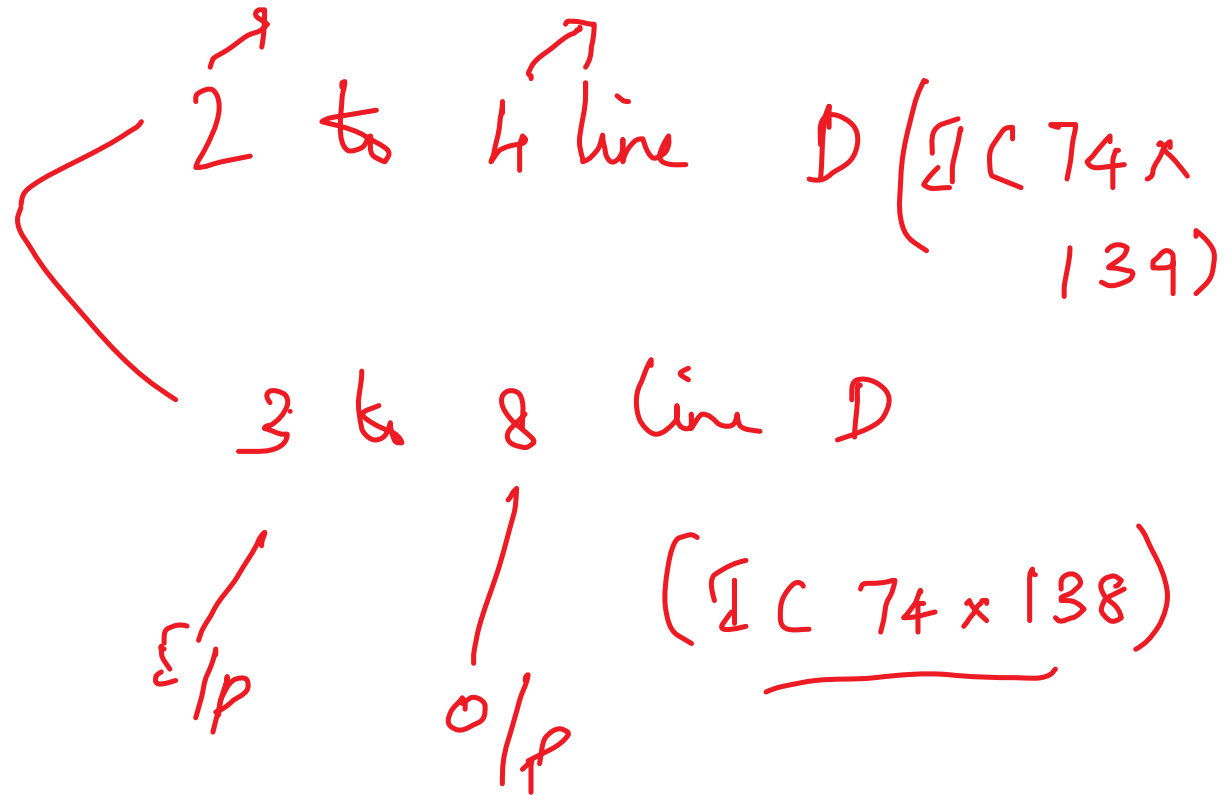

3 bit

 

IC 74x139 (2 to 4 line Decoder)

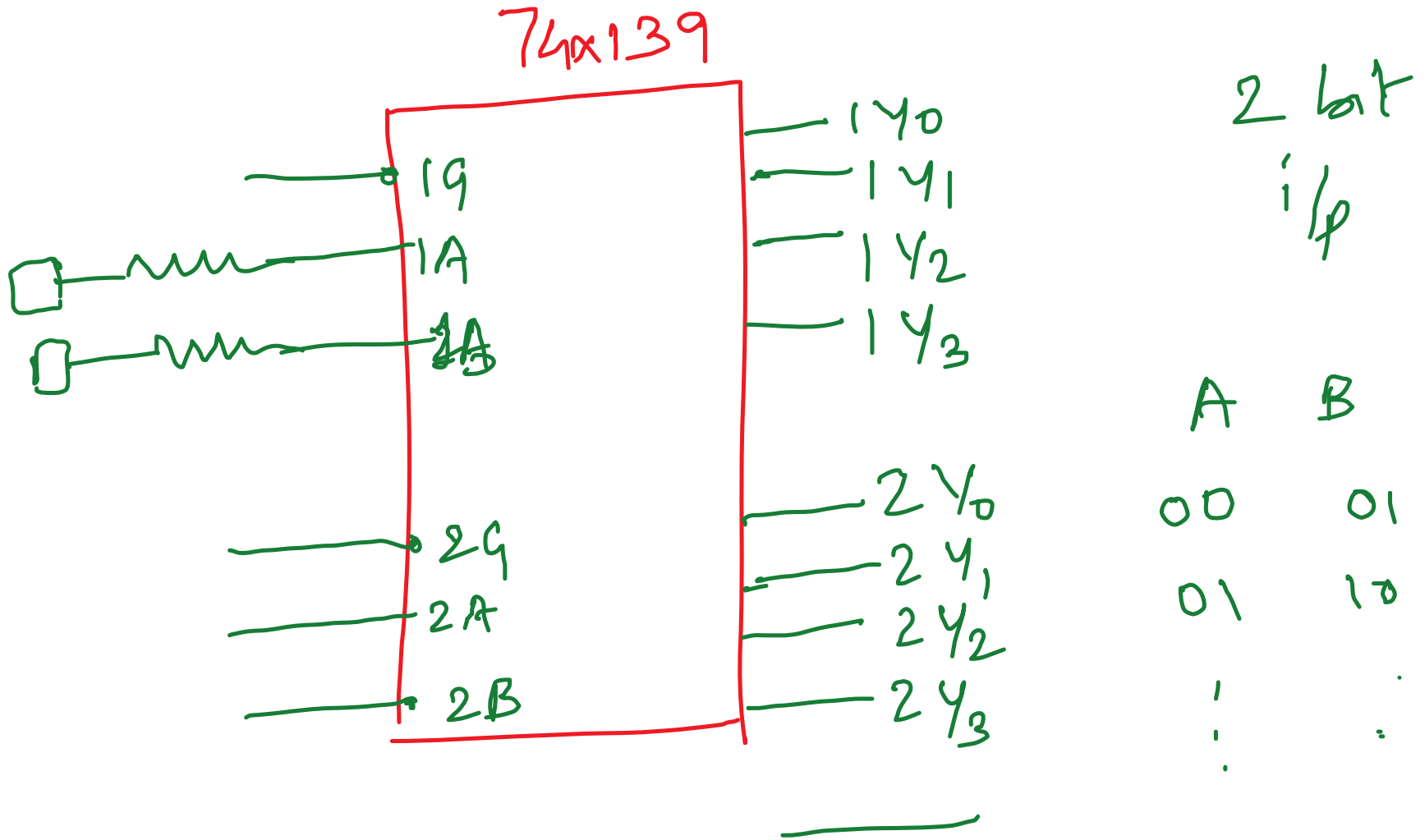

G_1 B A γ_3 γ_2 γ_1 γ_0 $G \rightarrow 1$
 $\overline{G} \rightarrow 0$

$-1G_0$
 $-2G_0$


$\frac{1}{p}$

$\frac{0/p}{\overline{\quad}}$

| G | \overline{G} | B | A | γ_3 | γ_2 | γ_1 | γ_0 |
|-----|----------------|---|---|------------|------------|------------|------------|
| 0 | 1 | X | X | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 | 1 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 | 1 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 0 | 1 | 1 | 1 |

IC 74x138


3 to 8 line Decoder

 

B → 0 (G_{2B})




A = 0 (G_{2A})

A B C
0 0 1

 


0-9 →

BCD to 7 segment Display Decoder

   

| | Inputs | | | | Outputs | | | | | | |
|----------|--------|---|---|---|----------|----------|----------|----------|----------|----------|----------|
| Digit | A | B | C | D | a | b | c | d | e | f | g |
| <u>0</u> | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | <u>1</u> | <u>1</u> | 0 | 0 | 0 | 0 |
| 2 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 |
| 3 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 1 |
| 4 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 5 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 |
| <u>6</u> | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| 7 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |
| <u>8</u> | 1 | 0 | 0 | 0 | <u>1</u> | <u>1</u> | <u>1</u> | <u>1</u> | <u>1</u> | <u>1</u> | <u>1</u> |
| 9 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 |





 

Common Cathode

17
11

a, b, c, d, e, f

  

Common anode =


Reverse of
common
cathode

$g = 1$


$a, b, c, d, e, f = 0$

$= 1 \quad g = 0$

DC 9V

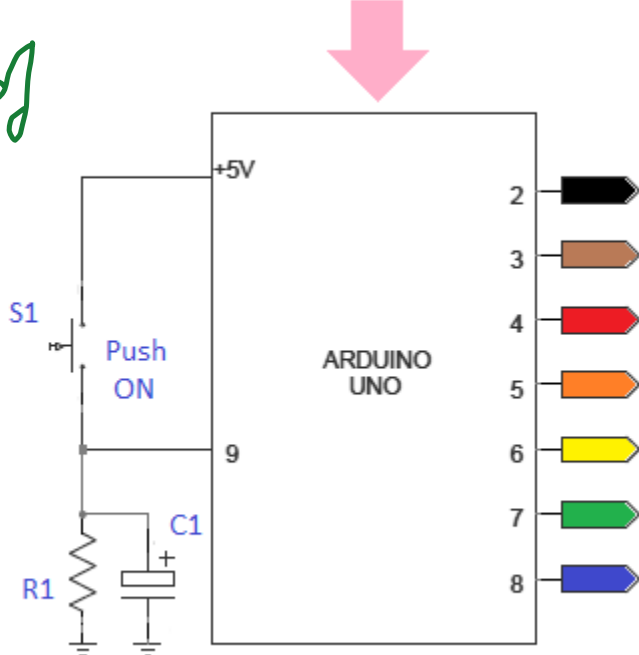

R1: 10K C1: 10uF/16V

 


R2: 330 R

Digit

A B C D



[✓]a [✓]b [✓]c [✓]d [✓]e [✓]f [✓]g

| | | | | | | | | | | | |
|---|---|---|---|---|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 2 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 |
| 3 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 1 |
| 4 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 5 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 |
| 6 | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| 7 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |
| 8 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 9 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 |

 

(0-9) ← BCD to Common Cathode 7-Segment Decoder

K-map for a

 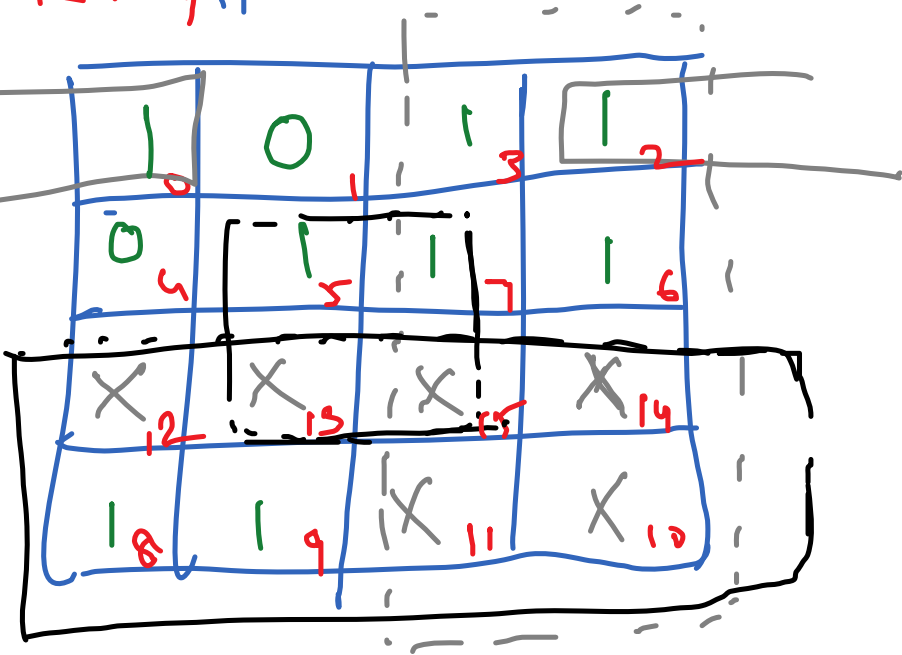

$$10 - 15 = \text{"X"}$$

$$a = A + C + BD + \overline{B}\overline{D}$$

Plot the same K-map for b, c, d, e, f, g

$$b = \overline{B} + \overline{C}\overline{D} + CD$$

$$c = B\overline{C} + D$$

$$d = \overline{B}\overline{D} + \overline{C}\overline{D} + B\overline{C}D + \overline{B}C + A$$

$$e = \overline{B}\overline{D} + \overline{C}\overline{D}$$

$$f = A + \overline{C}\overline{D} + B\overline{C} + B\overline{D}$$

$$g = A + B\overline{C} + \overline{B}C + C\overline{D}$$


logic diagrams for the values a, f, g

for common anode


| Digits | A | B | C | D |
|--------|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 2 | 0 | 0 | 1 | 0 |
| 3 | 0 | 0 | 1 | 1 |
| 4 | 0 | 1 | 0 | 0 |
| 5 | 0 | 1 | 0 | 1 |
| 6 | 0 | 1 | 1 | 0 |
| 7 | 0 | 1 | 1 | 1 |
| 8 | 1 | 0 | 0 | 0 |
| 9 | 1 | 0 | 0 | 1 |

| a | b | c | d | e | f | g |
|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 | 1 | 1 |
| 2 | 0 | 1 | 0 | 0 | 1 | 0 |
| 3 | 0 | 0 | 0 | 0 | 1 | 1 |
| 4 | 1 | 0 | 0 | 1 | 1 | 0 |
| 5 | 0 | 1 | 0 | 0 | 1 | 0 |
| 6 | 0 | 1 | 0 | 0 | 0 | 0 |
| 7 | 0 | 0 | 0 | 1 | 1 | 1 |
| 8 | 0 | 0 | 0 | 0 | 0 | 0 |
| 9 | 0 | 0 | 0 | 0 | 0 | 1 |

Display Decoder

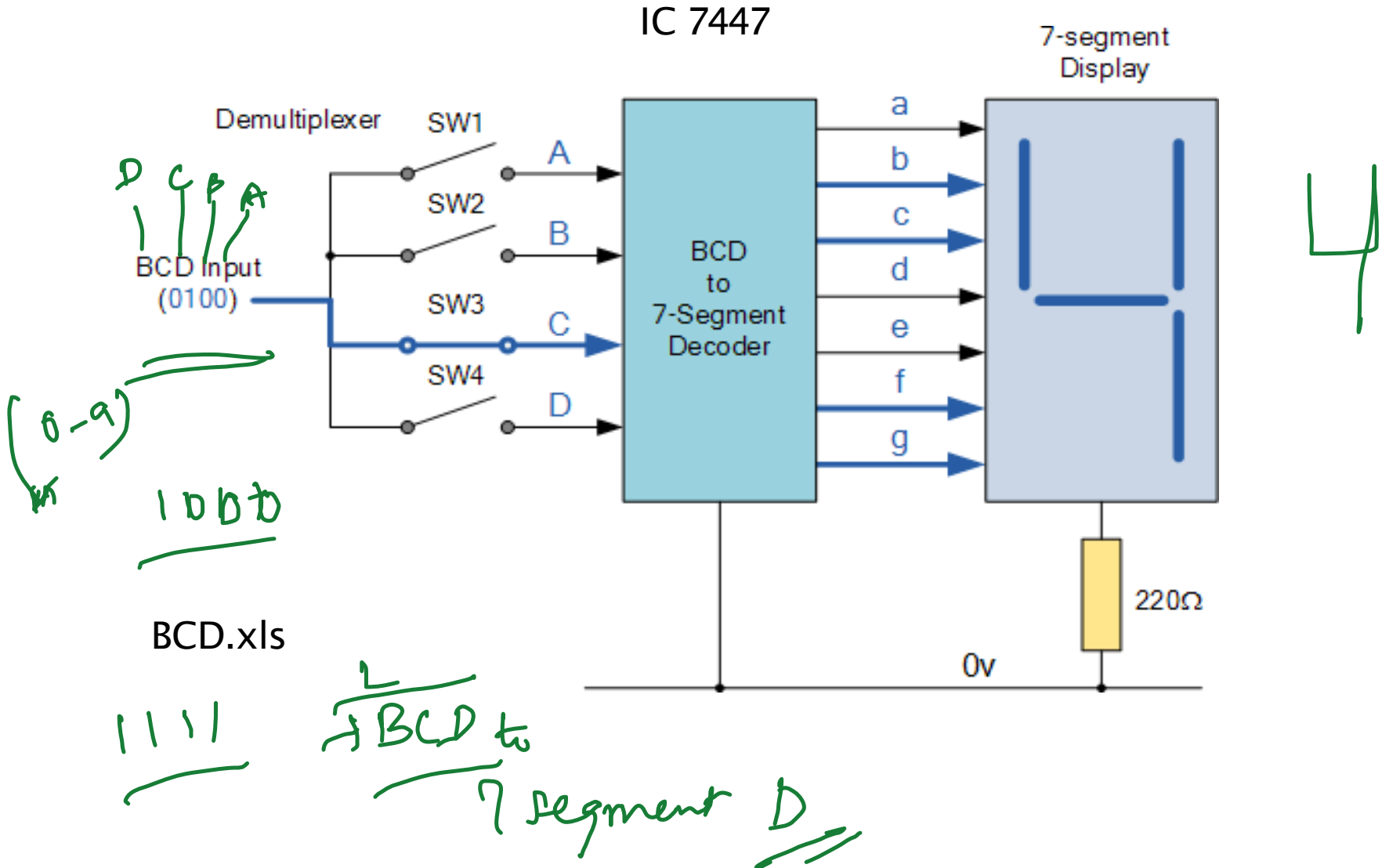

Common Anode LED Display

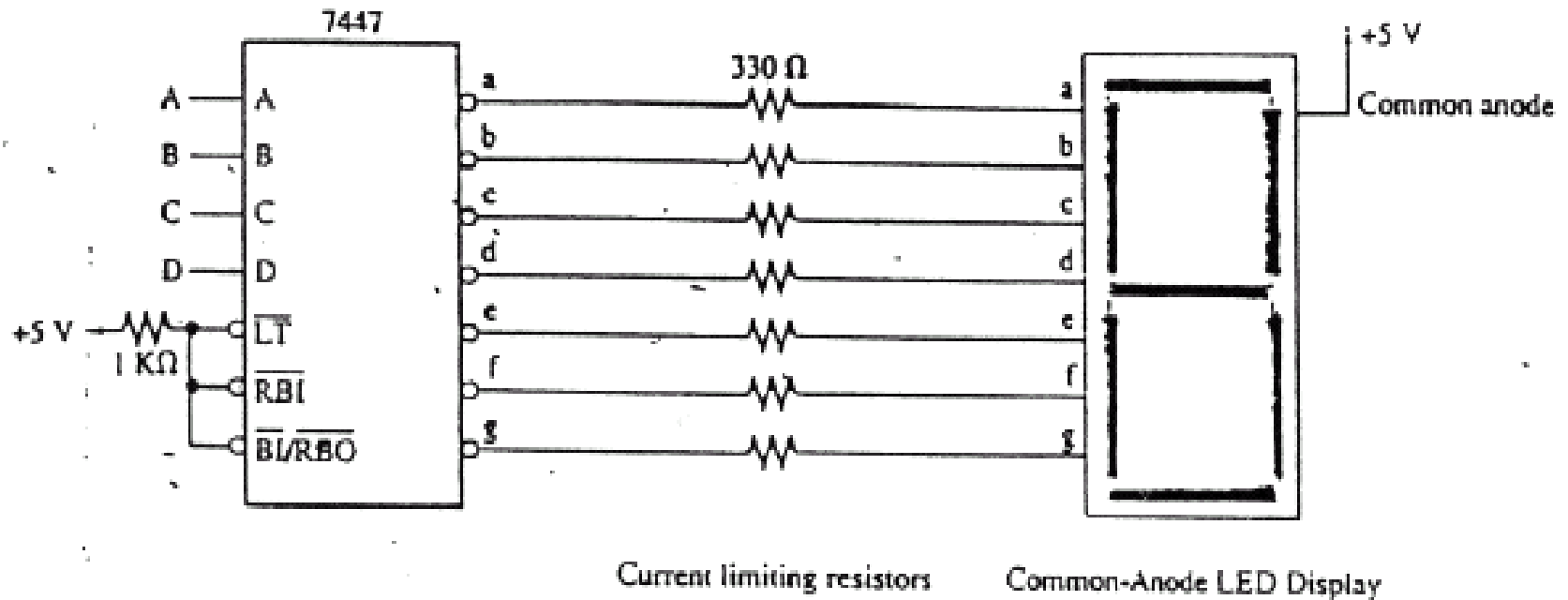

ENCODERS

- An Encoder is a combinational circuit that performs the reverse operation of Decoder. It has maximum of 2^n input lines and 'n' output lines.
- It will produce a binary code equivalent to the input, which is active High.

 


Fig 1: block diagram of 4x2 encoder

ENCODERS

Octal to binary encoder

| Octal digits | Binary | | |
|----------------|----------------|----------------|----------------|
| | A ₂ | A ₁ | A ₀ |
| D ₀ | 0 | 0 | 0 |
| D ₁ | 1 | 0 | 1 |
| D ₂ | 2 | 0 | 1 |
| D ₃ | 3 | 0 | 1 |
| D ₄ | 4 | 1 | 0 |
| D ₅ | 5 | 1 | 0 |
| D ₆ | 6 | 1 | 1 |
| D ₇ | 7 | 1 | 1 |

Fig 2: Truth table

 


Fig 3: Logic diagram

ENCODER

Priority encoder

A 4 to 2 priority encoder has four inputs Y_3 , Y_2 , Y_1 & Y_0 and two outputs A_1 & A_0 . Here, the input, Y_3 has the highest priority, whereas the input, Y_0 has the lowest priority.

| Inputs | | | | Outputs | | |
|--------|-------|-------|-------|---------|-------|-----|
| Y_3 | Y_2 | Y_1 | Y_0 | A_1 | A_0 | V |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | x | 0 | 1 | 1 |
| 0 | 1 | x | x | 1 | 0 | 1 |
| 1 | x | x | x | 1 | 1 | 1 |

Fig 4: Truth table

Encoders

4-to-2 Bit Binary Encoder

$$2^n \rightarrow n \text{ O/P}$$

$$4 \rightarrow 2 \text{ O/P}$$



$$8 \rightarrow 3 \text{ O/P}$$

— —

(1) (2)

01
10

01

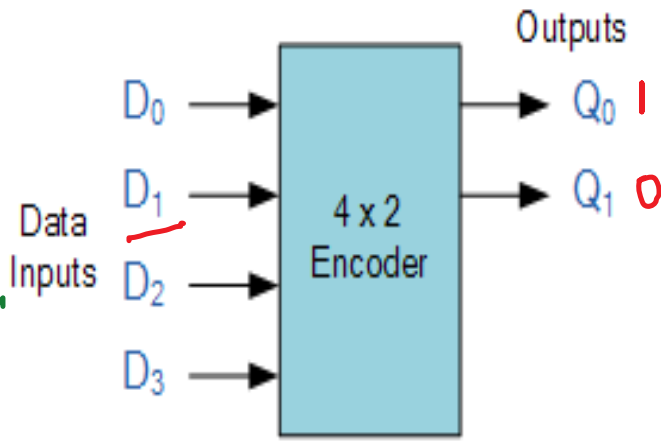 

| Inputs | | | | Outputs | |
|----------------|----------------|----------------|----------------|----------------|----------------|
| D ₃ | D ₂ | D ₁ | D ₀ | Q ₁ | Q ₀ |
| 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 0 | 0 | X | X |

> One of the main disadvantages of standard digital encoders is that they can generate the wrong output code when there is more than one input present at logic level "1". For example, if we make inputs D₁ and D₂ HIGH at logic "1" both at the same time, the resulting output is neither at "01" or at "10" but will be at "11" which is an output binary number that is ~~different to the actual input present~~.

Decoders

3x8 D

74x138

2x4 D

74x139



74 LS 138

ⓐ 74 LS 139

Encoders



Decimal to BCD Encoder

74xx147



9 x 4 (BCD O/P)

I/p.

74xx148




priority
encoder

04 to 2 bit p.e

~~2, 3, 4~~

8-to-3 Bit Priority Encoder

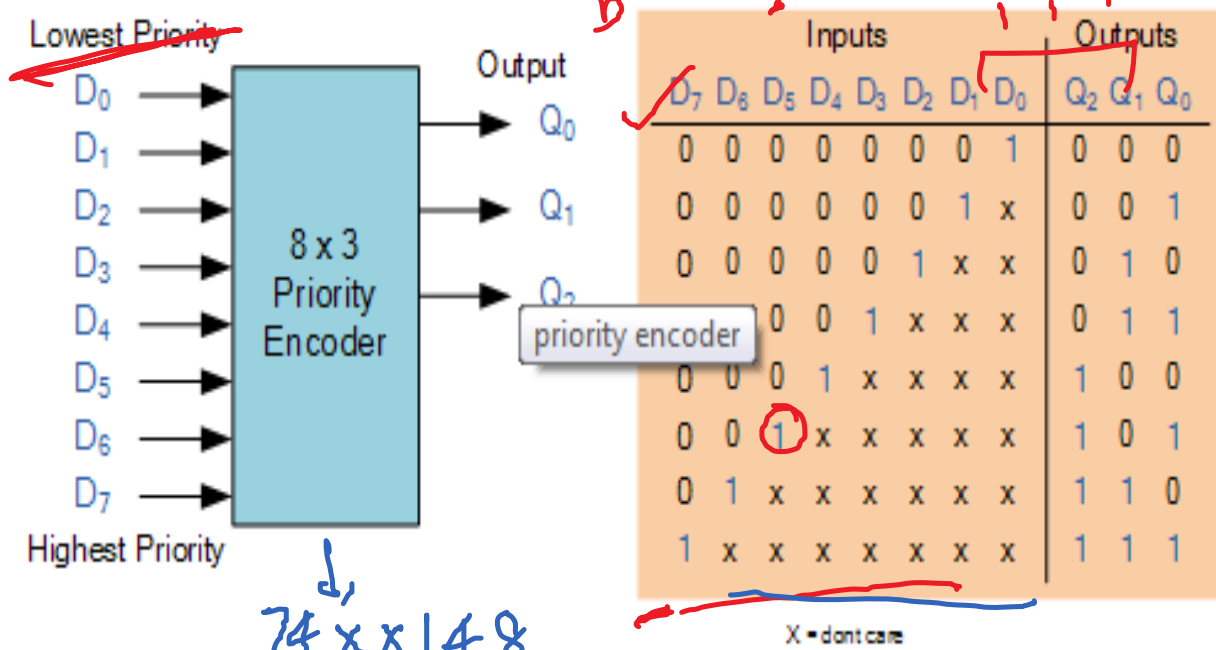

74xx148

10
 .
 01

 10 xi
 01

➤ Priority encoders output the highest order input first for example, if input lines “D2“, “D3” and “D5” are applied simultaneously the output code would be for input “D5” (“101”) as this has the highest order out of the 3 inputs. Once input “D5” had been removed the next highest output code would be for input “D3” (“011”), and so on.

- An **encoder** is the **inverse operation of a decoder**.
- We can derive the Boolean functions by table 4-7

$$z = D_1 + D_3 + D_5 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$

$$x = D_4 + D_5 + D_6 + D_7$$

→ 0-7 (8 i/p lines)

8 to 3 line encoder

Table 4-7
Truth Table of Octal-to-Binary Encoder

| Inputs | | | | | | | | Outputs | | |
|--------|-------|-------|-------|-------|-------|-------|-------|---------|-----|-----|
| D_0 | D_1 | D_2 | D_3 | D_4 | D_5 | D_6 | D_7 | x | y | z |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |


0-7

0-7

Encoder

ENC PC

◆ An implementation

 

■ limitations

- ◆ illegal input: e.g. $D_3 = D_6 = 1$
- ◆ the output = 111 ('13 and '16)

Priority encoder

- If two inputs are active simultaneously, the output produces an undefined combination. We can establish an input **priority** to ensure that only one input is encoded.
- **Another ambiguity** in the octal-to-binary encoder is that an **output with all 0's** is generated when **all the inputs are 0**; the output is the same as when D_0 is equal to 1.
- The discrepancy tables on Table 4-7 and Table 4-8 can **resolve aforesaid condition by providing one more output** to indicate that at least one input is equal to 1.

Priority encoder

$V=0$ • no valid inputs

$V=1$ • valid inputs

X 's in output columns represent don't-care conditions

X 's in the input columns are useful for representing a truth table in condensed form.

Instead of listing all 16 minterms of four variables.

4 x 2 encoder

Table 4-8

Truth Table of a Priority Encoder

| Inputs | | | | Outputs | | |
|--------|-------|-------|-------|---------|-----|-----|
| D_0 | D_1 | D_2 | D_3 | x | y | V |
| 0 | 0 | 0 | 0 | X | X | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| X | 1 | 0 | 0 | 0 | 1 | 1 |
| X | X | 1 | 0 | 1 | 0 | 1 |
| X | X | X | 1 | 1 | 1 | 1 |

$V_{in} = 0$ off (0)
 $V_{in} = 1$ (on)

Priority Encoder

- Resolve the ambiguity of illegal inputs
- Only one of the input is encoded

Truth Table of a Priority Encoder

| Inputs | | | | Outputs | | |
|--------|-------|-------|-------|---------|-----|-----|
| D_0 | D_1 | D_2 | D_3 | x | y | V |
| 0 | 0 | 0 | 0 | X | X | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| X | 1 | 0 | 0 | 0 | 1 | 1 |
| X | X | 1 | 0 | 1 | 0 | 1 |
| X | X | X | 1 | 1 | 1 | 1 |

- D_3 has the highest priority
- D_0 has the lowest priority
- X: don't-care conditions ≈ 1
- V: valid output indicator

Priority Encoder

4x2 line
P.E.

x

y

| | | D_2 | | | |
|----------|----|------------|---------------|---------------|---------------|
| | | D_2D_3 | 00 | 01 | 11 |
| D_0D_1 | 00 | m_0 X | m_1 1 | m_3 1 | m_2 1 |
| | 01 | m_4 | m_5 1 | m_7 1 | m_6 1 |
| D_0 | 11 | m_{12} | m_{13} 1 | m_{15} 1 | m_{14} 1 |
| | 10 | m_8 | m_9 1 | m_{11} 1 | m_{10} 1 |

D_3

$$x = D_2 + D_3$$


| | | D_2 | | | |
|----------|----|---------------|---------------|---------------|----------|
| | | D_2D_3 | 00 | 01 | 11 |
| D_0D_1 | 00 | m_0 X | m_1 1 | m_3 1 | m_2 |
| | 01 | m_4 1 | m_5 1 | m_7 1 | m_6 |
| D_0 | 11 | m_{12} 1 | m_{13} 1 | m_{15} 1 | m_{14} |
| | 10 | m_8 | m_9 1 | m_{11} 1 | m_{10} |

D_3

$$y = D_3 + D_1D'_2$$

$V_i = 0$
(00) (00)

Priority Encoder

 


$$x = D_2 + D_3$$

$$y = D_3 + D_1 D_2'$$

$$V = D_0 + D_1 + D_2 + D_3$$

IC 74LS 348 8 TO 3 PRIORITY ENCODER

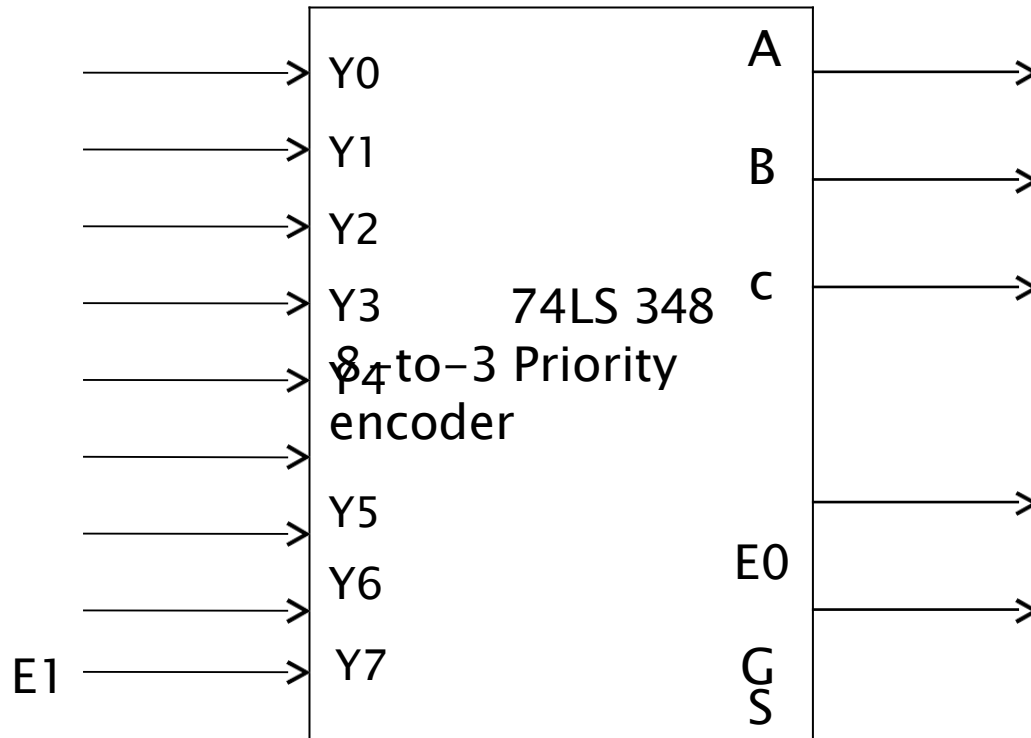

FUNCTION TABLE

| INPUTS | | | | | | | | | OUTPUTS | | | | |
|--------|---|---|---|---|---|---|---|---|---------|----|----|----|----|
| EI | 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 | A2 | A1 | A0 | GS | EO |
| H | X | X | X | X | X | X | X | X | Z | Z | Z | H | H |
| L | H | H | H | H | H | H | H | H | Z | Z | Z | H | L |
| L | X | X | X | X | X | X | X | L | L | L | L | L | H |
| L | X | X | X | X | X | X | L | H | L | L | H | L | H |
| L | X | X | X | X | X | L | H | H | L | H | L | L | H |
| L | X | X | X | L | H | H | H | H | L | H | L | L | H |
| L | X | X | L | H | H | H | H | H | H | L | H | L | H |
| L | X | L | H | H | H | H | H | H | H | H | L | L | H |
| L | L | H | H | H | H | H | H | H | H | H | H | L | H |

H = high logic level, L = low logic level, X = irrelevant
 Z = high-impedance state

MULTIPLEXERS ^{4x1} → encoder ^{4x2}

- Multiplexer is a combinational circuit that has maximum of 2^n data inputs, 'n' selection lines and single output line. One of these data inputs will be connected to the output based on the values of selection lines.
- We have different types of multiplexers $2 \times 1, 4 \times 1, 8 \times 1, 16 \times 1, 32 \times 1, \dots$

 



Fig 1: Block diagram

SOP form
 D
 D
 D

| Selection Lines | | Output |
|-----------------|-------|--------|
| S_1 | S_0 | Y |
| 0 | 0 | I_0 |
| 0 | 1 | I_1 |
| 1 | 0 | I_2 |
| 1 | 1 | I_3 |

Fig 2: Truth table

MULTIPLEXERS

 


| s_1 | s_0 | Y |
|-------|-------|-------|
| 0 | 0 | I_0 |
| 0 | 1 | I_1 |
| 1 | 0 | I_2 |
| 1 | 1 | I_3 |

Fig 3: Logic diagram

- Now let us implement the higher-order Multiplexer using lower-order Multiplexers.

MULTIPLEXERS

- Ex: 8x1 Multiplexer

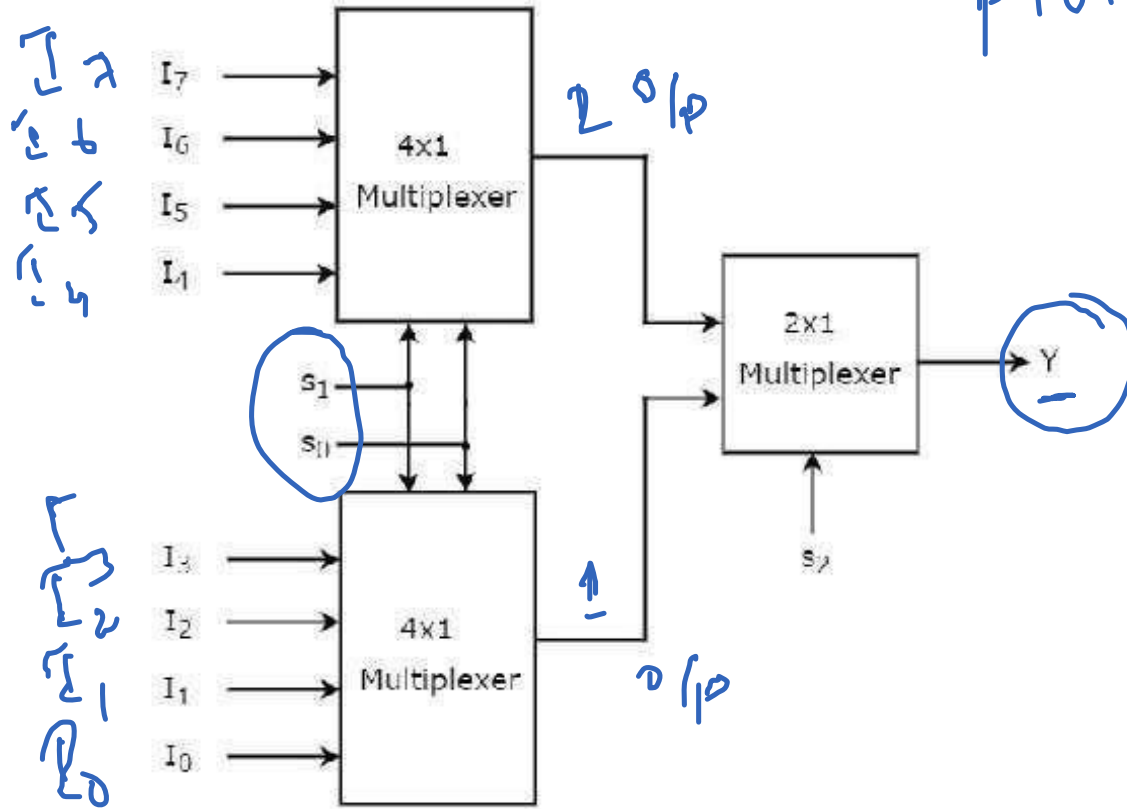

$\left. \begin{matrix} 7 \\ 6 \\ 5 \\ 4 \end{matrix} \right\} 2^0/p$

$\left. \begin{matrix} 3 \\ 2 \\ 1 \\ 0 \end{matrix} \right\} 2^1/p$

Plot

8x1 MUX

Unit

2

4x1 MUX.

1


2x1

MUX

Fig 3: 8x1 Multiplexer diagram

MULTIPLEXERS

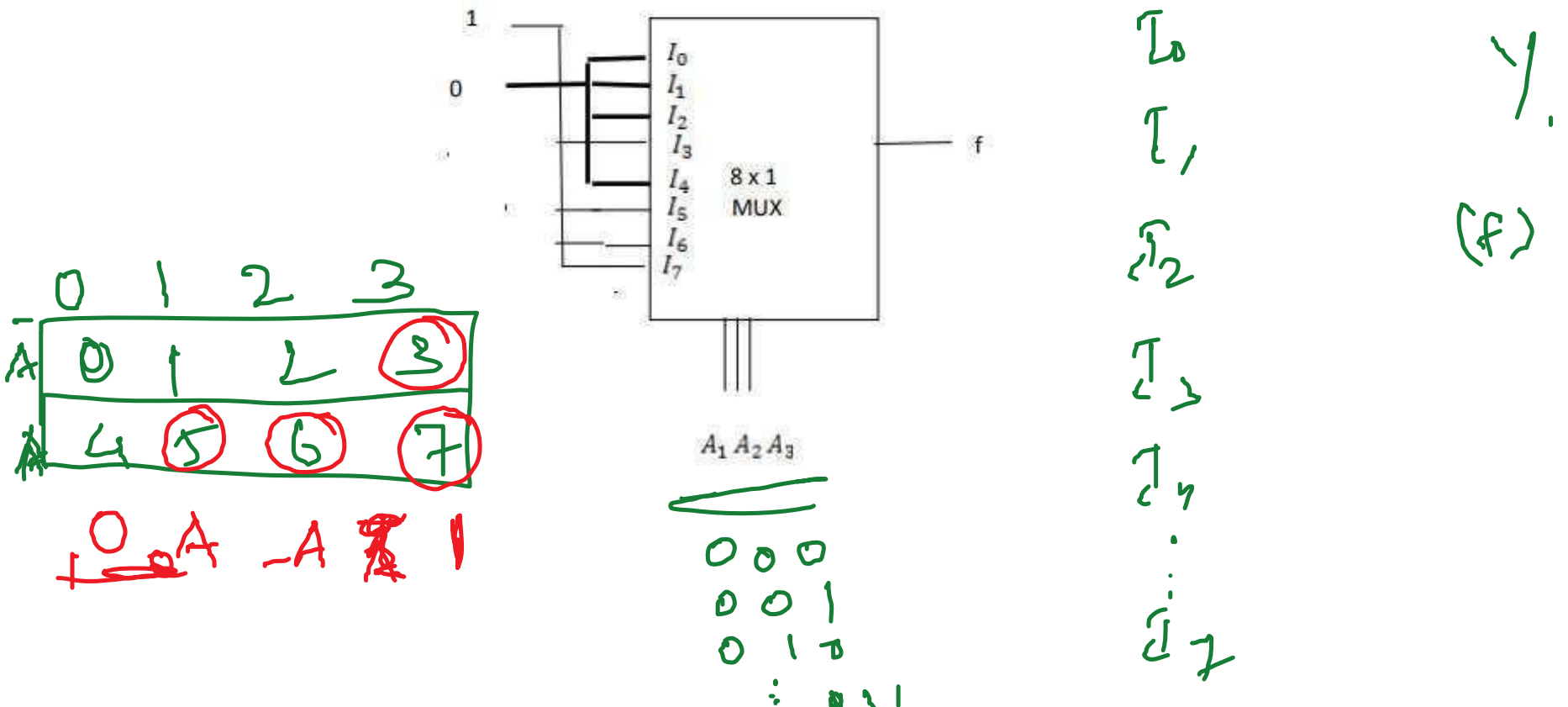- Implementation of Boolean function using multiplexer
- $f(A_1, A_2, A_3) = \Sigma(3, 5, 6, 7)$ implementation using 8x1 mux




MULTIPLEXERS

$f(A_1, A_2, A_3) = \Sigma(3, 5, 6, 7)$ implementation using 4x1 mux

Method:1


| Minterms | A_1 | A_2 | A_3 | f |
|----------|-------|-------|-------|-----|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 2 | 0 | 1 | 0 | 0 |
| 3 | 0 | 1 | 1 | 1 |
| 4 | 1 | 0 | 0 | 0 |
| 5 | 1 | 0 | 1 | 1 |
| 6 | 1 | 1 | 0 | 1 |
| 7 | 1 | 1 | 1 | 1 |

 

MULTIPLEXERS


Method:2

| Minterm | A_1 | A_2 | A_3 | f | |
|---------|-------|-------|-------|-----|---------------|
| 0 | 0 | 0 | 0 | 0 | |
| 1 | 0 | 0 | 1 | 0 | $f=0$ I_0 |
| 2 | 0 | 1 | 0 | 0 | |
| 3 | 0 | 1 | 1 | 1 | $f=A_3$ I_1 |
| 4 | 1 | 0 | 0 | 0 | |
| 5 | 1 | 0 | 1 | 1 | $f=A_3$ I_2 |
| 6 | 1 | 1 | 0 | 1 | |
| 7 | 1 | 1 | 1 | 1 | $f=1$ I_3 |

 


Multiplexer

 - ◆ Select binary information from one of many input lines and direct it to a single output line
- ◆ 2 input lines, n selection lines and one output line
- ◆ E.g.: 2-to-1-line multiplexer




(a) Logic diagram

 

(b) Block diagram

Two-to-one-line multiplexer

4-to-1-Line Multiplexer

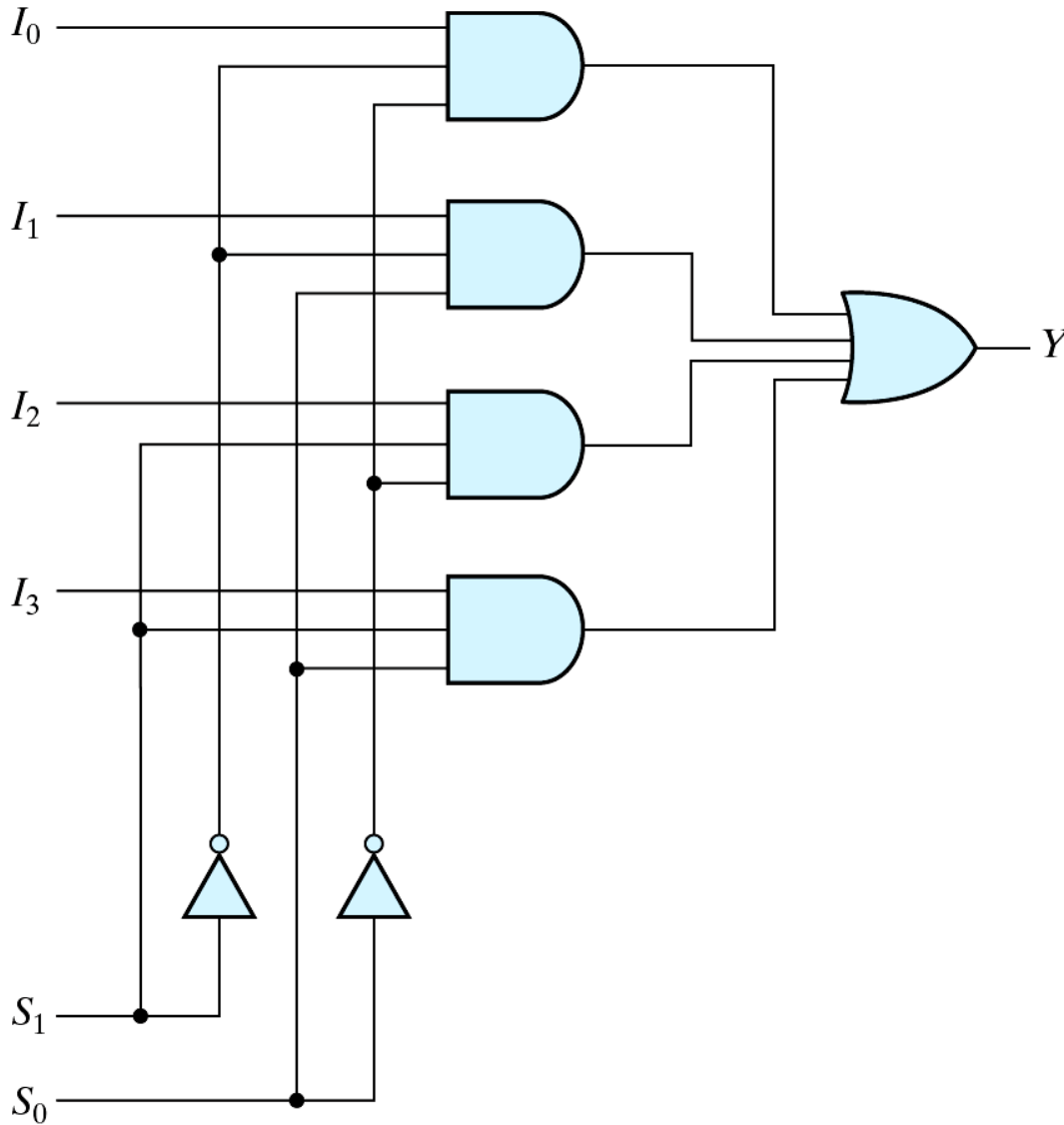


(a) Logic diagram

| S_1 | S_0 | Y |
|-------|-------|-------|
| 0 | 0 | I_0 |
| 0 | 1 | I_1 |
| 1 | 0 | I_2 |
| 1 | 1 | I_3 |

(b) Function table

8 to 1 Multiplexer using IC 74LS 151

 

TRUTH TABLE

| E | S ₂ | S ₁ | S ₀ | I ₀ | I ₁ | I ₂ | I ₃ | I ₄ | I ₅ | I ₆ | I ₇ | Z | Z |
|---|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|---|---|
| H | X | X | X | X | X | X | X | X | X | X | X | H | L |
| L | L | L | L | L | X | X | X | X | X | X | X | H | L |
| L | L | L | L | H | X | X | X | X | X | X | X | L | H |
| L | L | L | H | X | L | X | X | X | X | X | X | H | L |
| L | L | L | H | X | H | X | X | X | X | X | X | L | H |
| L | L | H | L | X | X | L | X | X | X | X | X | H | L |
| L | L | H | L | X | X | H | X | X | X | X | X | L | H |
| L | L | H | H | X | X | X | L | X | X | X | X | H | L |
| L | L | H | H | X | X | X | H | X | X | X | X | L | H |
| L | H | L | L | X | X | X | X | L | X | X | X | H | L |
| L | H | L | L | X | X | X | X | H | X | X | X | L | H |
| L | H | L | H | X | X | X | X | X | L | X | X | H | L |
| L | H | L | H | X | X | X | X | X | H | X | X | L | H |
| L | H | H | L | X | X | X | X | X | X | L | X | H | L |
| L | H | H | L | X | X | X | X | X | X | H | X | L | H |
| L | H | H | H | X | X | X | X | X | X | X | L | H | L |
| L | H | H | H | X | X | X | X | X | X | X | H | L | H |

H = HIGH Voltage Level
 L = LOW Voltage Level
 X = Don't Care

- For **Dual 4 to 1 Multiplexer** we are using IC 74LS153. it has two set of input 4 Lines and with two set of Enables with two set of output lines.
- For **16 to 1 Multiplexer** we are using IC 74LS150. It has 16 input lines with 4 Select lines along with one Enable Active low and one output

Boolean Function Implementation Using MUX

- ◆ MUX: a decoder + an OR gate
- ◆ 2^n -to-1 MUX can implement any Boolean function of n input variable.
- ◆ Procedure:
 - assign an ordering sequence of the input variable
 - the rightmost variable (D) will be used for the input lines
 - assign the remaining $n-1$ variables to the selection lines w.r.t. their corresponding sequence
 - construct the truth table
 - consider a pair of consecutive minterms starting from m_0
 - determine the input lines

DEMULTIPLEXER

- A demultiplexer is a device that takes a single input line and routes it to one of several digital output lines.
- A demultiplexer of 2^n outputs has n select lines, which are used to select which output line to send the input.
- We have $1 \times 2, 1 \times 4, 1 \times 8, \dots$ Demultiplexers.

Handwritten notes: $1 \times 4, 1 \times 8, 1 \times 2, \dots$

 


Fig:1 Block diagram

| Selection Inputs | | Outputs | | | |
|------------------|-------|---------|-------|-------|-------|
| S_1 | S_0 | Y_3 | Y_2 | Y_1 | Y_0 |
| 0 | 0 | 0 | 0 | 0 | I |
| 0 | 1 | 0 | 0 | I | 0 |
| 1 | 0 | 0 | I | 0 | 0 |
| 1 | 1 | I | 0 | 0 | 0 |

Fig :2 Truth table

DEMULTIPLEXER

Boolean functions for each output as

$$Y_3 = s_1 s_0 I$$

$$Y_2 = s_1 s_0' I$$

$$Y_1 = s_1' s_0 I$$

$$Y_0 = s_1' s_0' I$$

 


Fig:3 Logic diagram

BOOLEAN FUNCTION IMPLEMENTATION USING MULTIPLEXERS

- $F(A, B, C, D) = \sum(1, 3, 4, 11, 12, 13, 14, 15)$
- This function can be implemented using multiplexer of various sizes
- 16×1 – A, B, C, D are selection lines
- 8×1
 - A as input line and B, C, D as selection lines
 - B as input line and A, C, D as selection lines
 - C as input line and A, B, D as selection lines
 - D as input line and A, B, C as selection lines
- 4×1
 - A, B as input lines and C, D as selection lines and vice-versa
 - A, C as input lines and B, D as selection lines and vice-versa
 - A, D as input lines and B, C as selection lines and vice-versa

Implementation using Multiplexer

$F(A, B, C, D) = \sum(1, 3, 4, 11, 12, 13, 14, 15)$
using 16 x 1 Multiplexer

