



SCHOOL OF ELECTRICAL ENGINEERING
FALL SEMESTER 2022-2023
CAT-I

SLOT: G1

Programme Name & Branch: B.Tech (CSE, ECE, CSB)

Course Code: EEE102L





Course Name : Basic Electrical and Electronics Engineering

Date of the Examination : 12.11.2022

Duration : 90 minutes

Max. Marks : 50

	Question	Mark
1.	Find the node voltages V_1, V_2, and V_3. Also Find the current i_1, i_2 and i_3 At Node 1 $\frac{V_1 - V_2}{8} + \frac{V_1}{4} - 5 + \frac{V_1 - V_3}{2} + 3 = 0$ $V_1 - V_2 + 2V_1 - 40 + 4V_1 - 4V_3 + 24 = 0$ $7V_1 - V_2 - 4V_3 = 16 \quad \text{--- (1)}$ At Node 2 $\frac{V_2 - V_1}{8} + \frac{V_2 - V_3}{4} + \frac{V_2}{2} = 0$ $V_2 - V_1 + 2V_2 - 2V_3 + 4V_2 = 0$ $-V_1 + 7V_2 - 2V_3 = 0$	1.5 1.5

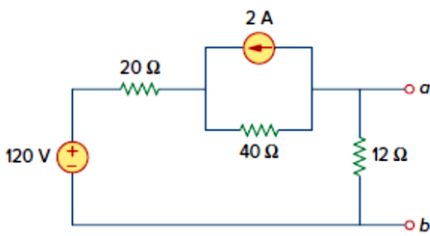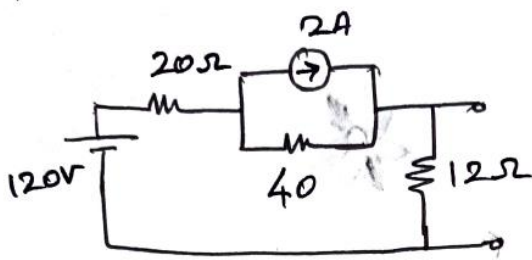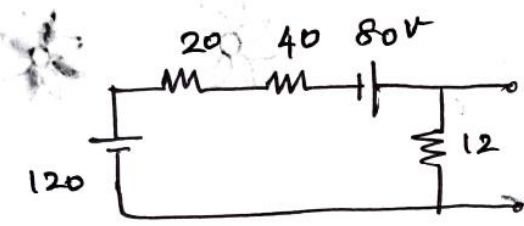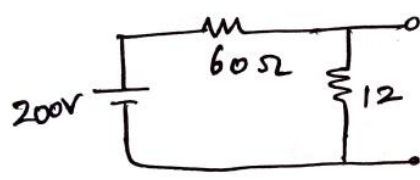	At Node 3 $\frac{V_3 - 12}{8} + \frac{V_3 - V_2}{4} + \frac{V_3 - V_1}{2} - 3 = 0$ $V_3 - 12 + 2V_3 - 2V_2 + 4V_3 - 4V_1 - 24 = 0$ $-4V_1 - 2V_2 + 7V_3 = 36$ Solving $V_1 = 1.37 \text{ V} \quad V_2 = 5.882 \text{ V} \quad V_3 = 13.164 \text{ V}$ $i_1 = \frac{V_1 - V_2}{8} = 0.634$ $i_2 = \frac{V_2 - V_3}{4} = -1.935$ $i_3 = \frac{V_3 - 0}{2} = 6.582$	1.5 1.5 +3 +1 for units
2.	Find the value of maximum power that can be transferred across the terminals a-b using Maximum Power Transfer Theorem.     $V_{12} = I \times 12 = \frac{200}{72} \times 12 = 33.33 \text{ V}$	4

	$R_{th} = 20 + 40 \parallel 12 \Omega$ $= 60 \parallel 12 \Omega$ $= 10 \Omega$ $\therefore$ Thevenin eqt ckt is: & for P_{max} $R_L = 10 \Omega$ $P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{33.33^2}{4 \times 10} = 27.77 \text{ W}$	3 1 2
3.	a) Obtain the equivalent resistance at the terminals $a-b$ for the circuit shown below. Also find the current in 30Ω resistor if a voltage of 100V is applied across the terminals $a-b$. $R_{ab} = 9.23$ $I_{30} = I \times \frac{13.3}{43.3} \quad I = 100/9.23 = 10.84 \text{ A}, \quad I_{30} = 3.328 \text{ A}$	2 2 2 2,2
4.	Below figure shows a load being fed by a voltage source through a transmission line. The impedance of the line is $(4+j2) \Omega$ and the load is $(15 - j10) \Omega$. Find the current, real and reactive power absorbed by each of these impedances. Also calculate the system power factor and the value of L & C at a supply frequency of 50Hz.	

		units
--	--	-------