



Continuous Assessment Test – I

Programme Name & Branch: B.Tech, ECE

Course Name & Code: Analog Circuits-BECE 206L

Semester: Fall-2023-24

Slot: G1



Exam Duration: 90 Min



Maximum Marks: 50

General instruction(s):

Assume constants whenever it is needed

Answer all Questions

  S.No.	Question	Marks	CO	BL
1.	Determine the Q point, DC load line and all the nodal voltages for the circuit shown in Fig.1. Given $V_{tn} = 1V$ and $K_n'(W/L) = 1 \text{ mA/V}^2$.  Fig.1	10	1	L3
2.	Derive the expressions for the mid band gain A_M and the upper 3-dB frequency f_H of the Common Emitter amplifier circuit shown in Fig.2 at high frequency using hybrid π model.  Fig.2	10	1	L3

  3.	For the circuit shown in Fig.3, $V_{CC} = 5V$, $R_{sig} = 10\text{ k}\Omega$, $R_1 = 68\text{ k}\Omega$, $R_2 = 27\text{ k}\Omega$, $R_E = 2.2\text{ k}\Omega$, $R_C = 4.7\text{ k}\Omega$, $R_L = 10\text{ k}\Omega$ and $\beta = 200$. The collector current is 0.8 mA, $f_T = 1\text{ GHz}$ and $C_\mu = 0.8\text{ pF}$. Find the midband gain and the upper 3-dB frequency.  Fig.3	10	1	L3
4.	For the CS amplifier circuit given in Fig.4. The circuit is biased to have $g_m = 1\text{ mA/V}$. Find A_M, f_{p1}, f_{p2}, f_{p3}, f_L.  Fig.4	10	1	L3
5	A class A Power amplifier is designed with $V_{DD} = 15\text{ V}$ and $R_D = 7\text{ k}\Omega$ and $K_n'(W/L) = 4\text{ mA/V}^2$, $V_{TN} = 1\text{ V}$, and $\lambda = 0$. Assume the output voltage swing is limited to the range between the transition point and $V_{DS} = 9\text{ V}$, to minimize nonlinear distortion. Determine the saturation point and V_{DSQ}. Also calculate the input power, output power and the efficiency.	10	2	L3

