



# VIT\*

Vellore Institute of Technology  
(Deemed to be University under section 3 of UGC Act, 1956)

Vellore – 632014, Tamil Nadu, India

**SLOT: A1+TA1**


**SCHOOL OF ELECTRICAL ENGINEERING  
FALL SEMESTER 2023-2024  
CAT-II**

Programme Name & Branch : B. Tech. Course Code: BEEE102L  
Course Name : Basic Electrical and Electronics Engineering  
Faculty Members : Dr Washima Tasnin, Dr. Raja Singh, Dr. Satyajit Das,  
Dr. Satyajit Mohanty, Dr. Kalaiselvan N  
Class Number(s) : 7767, 7761, 7773, 7857, 7878  
Date of the Examination : 15-10-2023

**Duration : 90 minutes**


**Max. Marks : 50**

**General instruction(s): Answer All the Questions**

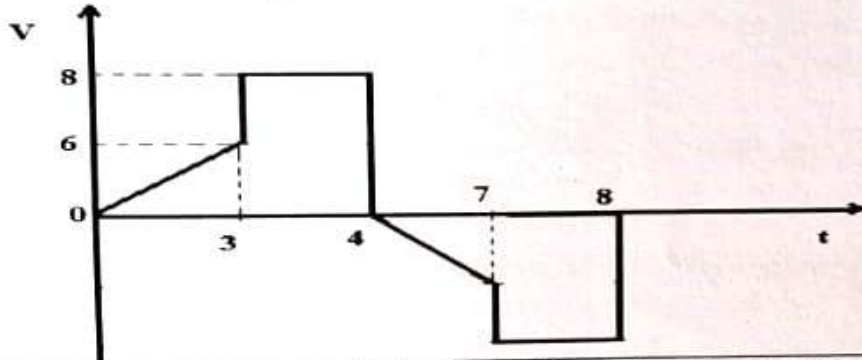Q. No	Question	Mark
1	<p>A voltage wave has variations as shown in Figure below. Find the average value, effective value, form factor and peak factor.</p> 	10
2	<p>A balanced star connected load of <math>(4+j3) \Omega</math> per phase is connected to a balanced 3-phase 400V supply. The phase current is 12 A. Find the (i) Total active power (ii) Reactive power (iii) Total apparent power</p>	10
3	<p>a. Determine <math>_{xx}</math> and reduce the following number system            (i) <math>(756)_{10} - (432)_8 + (4FA)_{xx} = (\quad)_2</math>            (ii) <math>(4DC)_{16} + (537)_2 + (523)_{16} = (\quad)_2</math></p> <p>b. Draw the logic circuits for the expression: <math>A'B + ABC' + AB'C' + AC</math></p>	10
4	<p>a. Reduce the Boolean expression using Boolean rules  <math>A'BC + AB'C' + A'B'C' + AB'C + ABC</math></p> <p>b. Minimize the following Boolean function using K-map  <math>F(A, B, C, D) = \sum m(0, 1, 2, 5, 7, 8, 9, 10, 13, 15)</math></p>	10
5	<p>Design a combinational circuit to add three-bit binary numbers namely A, B and C using K-map. Also, draw its logic diagram using AND and OR gates.</p>	10

class Number(s) : 7767, 7761

7773, 7857, 7878

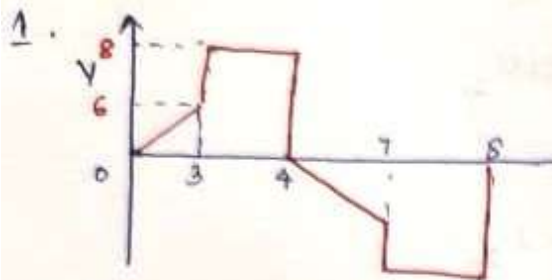

Average Value :  $\frac{\text{Area under the half cycle}}{\text{Period}}$

$$= \frac{(\text{Area of triangle} + \text{Area of Rectangle})}{\text{Period}}$$

$$= \left[ \frac{1}{2} \cdot bh + b \cdot h \right] / 4$$

$$= \frac{1}{2} (3 \times 6) + (1 \times 8) / 4$$

$$= 17/4 = 4.25 \text{ V}$$

Effective Value (RMS) :  $\sqrt{\frac{\text{Area under the Squared half the cycle}}{\text{Period}}}$

= Area under the Squared triangle Wave + Area under the Squared rectangle wave

$$= \sqrt{\frac{(\frac{1}{3} \times 6^2 \times 3) + (1 \times 8^2)}{4}}$$

$$= \sqrt{\frac{100}{4}} = 5 \text{ V}$$

Form factor =  $\frac{V_{RMS}}{V_{Avg}} = \frac{5}{4.25} = 1.176$

Peak factor =  $\frac{\text{Maximum Value}}{\text{RMS Value}} = \frac{8}{5} = 1.6$

2. Star Connected

$Z = 4 + 3j$  ;  $V = 400 \text{ V}$  Supply


$V_L = \sqrt{3} V_{ph}$  ;  $I_L = I_{ph} = 12 \text{ A}$

$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 231 \text{ V}$

$Z_{ph} = 4 + 3j = 5 \angle 36.86^\circ$

$\phi = 36.86^\circ \Rightarrow \cos(36.86^\circ) = \text{0.8}$

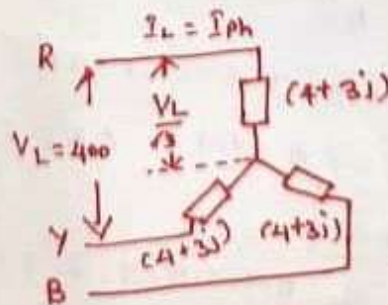(1) Total active power =  $\sqrt{3} V_L I_L \cos \phi$   
 $= \sqrt{3} \cdot 400 \cdot 12 \cdot \cos 36.86^\circ = 9.6 \text{ kW}$   
 $= 6.65 \text{ kW}$




(i)  $Q = \sqrt{3} V_L I_L \sin \phi$   
 $= \sqrt{3} \cdot (400) (12) \sin 36.86 = 4.9 \text{ kVAR}$

(ii)  $S = \sqrt{3} V_L I_L$   
 $= \sqrt{3} \cdot 400 \cdot 12 = 8.31 \text{ kVA}$

(3) (i)  $(756)_{10} - (432)_8 + (4FA)_{xx} = (-)_{2}$   
 $1011110100_2 - 100011010_2 + 10011111010_2$   
 $= 0110110100_2$

(ii)  $(ADC)_{16} + (537)_2 + (523)_{16} = (-)_{2}$   
 $010011011100_2 + 1000011001_2 + 10100100011_2$   
 $= 0110000011000_2$

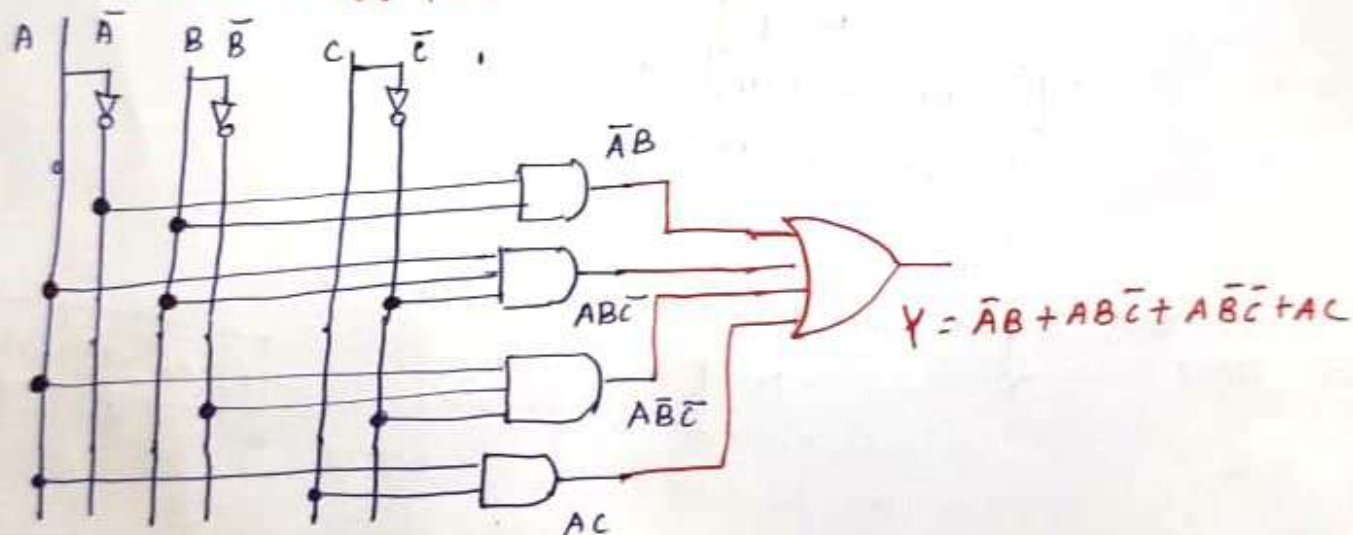(b)  $\bar{A}B + AB\bar{C} + A\bar{B}\bar{C} + AC$



④ Reduce the Boolean Expression using boolean Rules

①  $\bar{A}BC + A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + A\bar{B}C + ABC$

$\bar{A}BC + A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + A\bar{B}C + ABC$

$B C [\bar{A} + A] + \bar{B}\bar{C}$

$\bar{A}BC + ABC + \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + A\bar{B}C + ABC$

$B C (\bar{A} + A) + \bar{B}\bar{C} (\bar{A} + A) + A\bar{B} (C + \bar{C})$

$B C + \bar{B}\bar{C} + A\bar{B}$

$[\because A\bar{B}\bar{C} = A\bar{B}\bar{C} + A\bar{B}C]$

$\because A + \bar{A} = 1$   
 $C + \bar{C} = 1$

②  $F(A, B, C, D) = \sum m(0, 1, 2, 5, 7, 8, 9, 10, 13, 15)$


$Y = \bar{B}\bar{D} + BD + \bar{B}\bar{C}$

	00	01	11	10
AB	1 <sup>0</sup>	1 <sup>1</sup>		1 <sup>2</sup>
00		1 <sup>3</sup>	1 <sup>4</sup>	
01		1 <sup>5</sup>	1 <sup>6</sup>	
11		1 <sup>7</sup>	1 <sup>8</sup>	
10	1 <sup>9</sup>	1 <sup>10</sup>		1 <sup>11</sup>

⑤ Three bit Full Adder

[WON Combination with 3 min term]


# B. Full Adder

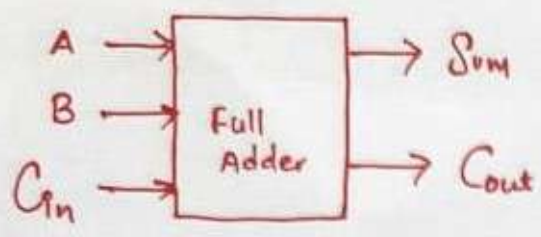

Truth Table


Input			Output	
A	B	C <sub>in</sub>	Sum	C <sub>out</sub>
0	0	0	0	0
1	0	0	1	0
2	0	1	1	0
3	0	1	0	1
4	1	0	1	0
5	1	1	0	1
6	1	0	0	1
7	1	1	1	1

Logical Expression For Sum

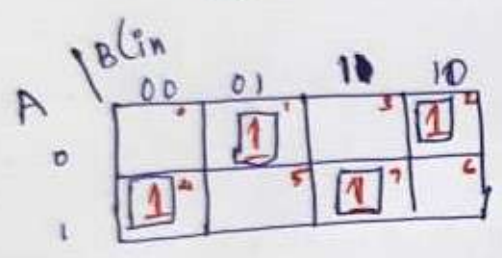

$$S = \bar{A}\bar{B}C_{in} + \bar{A}B\bar{C}_{in} + A\bar{B}\bar{C}_{in} + ABC_{in}$$

Logical expression for Carry

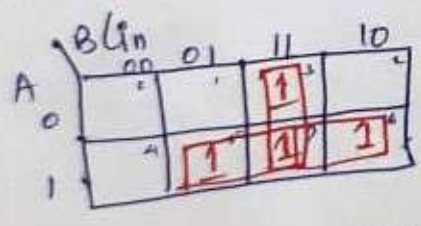

$$C = AC_{in} + AB + BC_{in}$$

