



VIT

Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)

Vellore – 632014, Tamil Nadu, India
SCHOOL OF ELECTRICAL ENGINEERING
FALL SEMESTER 2023-2024
CAT-I

SLOT: A1+TA1

Programme Name & Branch : B.Tech. Course Code: BEEE102L

Course Name : Basic Electrical and Electronics Engineering

Faculty Members : Dr Washima Tasnin, Dr. Raja Singh, Dr. Satyajit Das,
Dr. Satyajit Mohanty, Dr. Kalaiselvan N

Class Number(s) : 7773, 7857, 7761, 7878, 7767




Date of the Examination : 10th August 2023


Duration : 90 minutes

Max. Marks : 50

General instruction(s):

Q	Question	Marks
1	Apply Node analysis and find the voltage drop V_{ab} for the circuit shown in Fig. 1. Fig. 1	10
2	Find the power delivered by the 10 V source by applying mesh analysis in the circuit shown in Fig. 2.	10

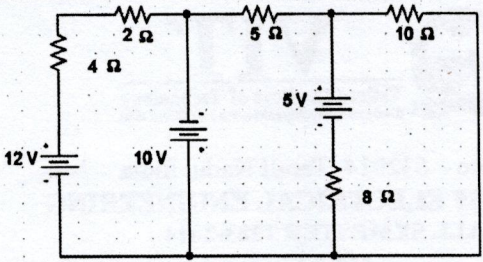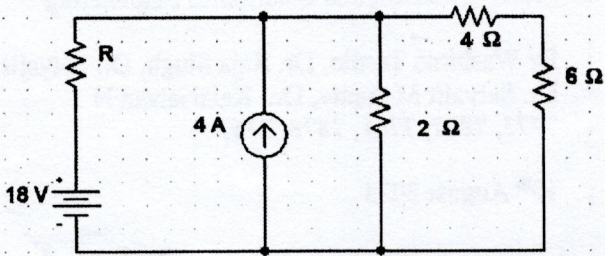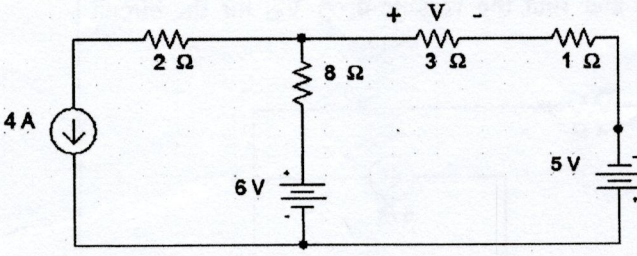	 <p style="text-align: center;">Fig. 2</p>	
3	<p>In the circuit shown in Fig. 3, find the value of R for which maximum power transfer takes place. Also, find the value of maximum power?</p>  <p style="text-align: center;">Fig. 3</p>	10
4	<p>Applying Superposition theorem, determine the current in 2 ohm resistor and voltage drop in 3 ohm resistor in the circuit shown in Fig. 4.</p>  <p style="text-align: center;">Fig. 4</p>	10
5	<p>A voltage $V(t) = 50 \sin 314 t$ is applied to series circuit consisting of 5 ohm resistance and a inductor 20 mH. Calculate</p> <ol style="list-style-type: none"> 1. expression for $i(t)$ 2. phase angle between voltage and current 3. power factor 4. active power consumed reactive power consumed by inductor 	10

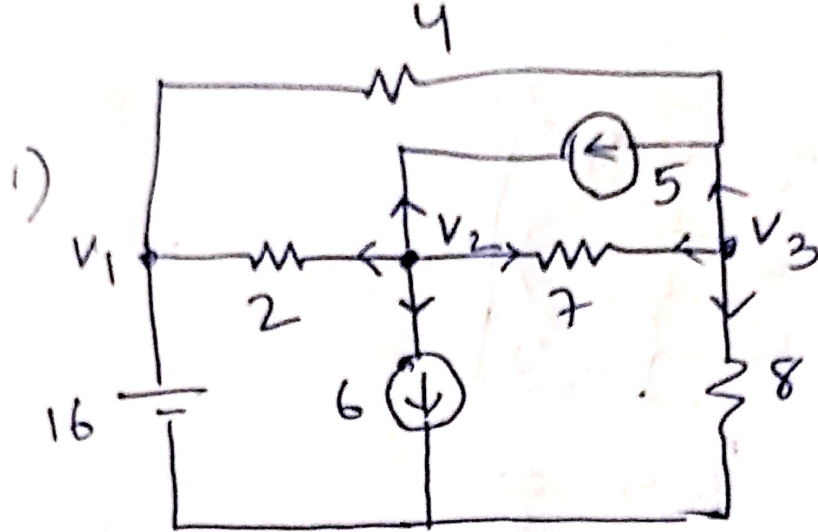

$$V_1 = 16$$

$$\frac{V_2 - V_1}{2} + 6 + \frac{V_2 - V_3}{7} + (-5) = 0$$

$$7(V_2 - 16) + 84 + 2V_2 - 2V_3 - 70 = 0$$

$$\Rightarrow 9V_2 - 2V_3 = 98$$


$$\frac{V_3}{8} + \frac{V_3 - V_2}{7} + 5 + \frac{V_3 - V_1}{4} = 0$$

$$7V_3 + 8(V_3 - V_2) + 280 + 14(V_3 - V_1) = 0$$

$$29V_3 - 8V_2 - 14V_1 + 280 = 0$$

$$2 \quad -8V_2 + 29V_3 = -56$$
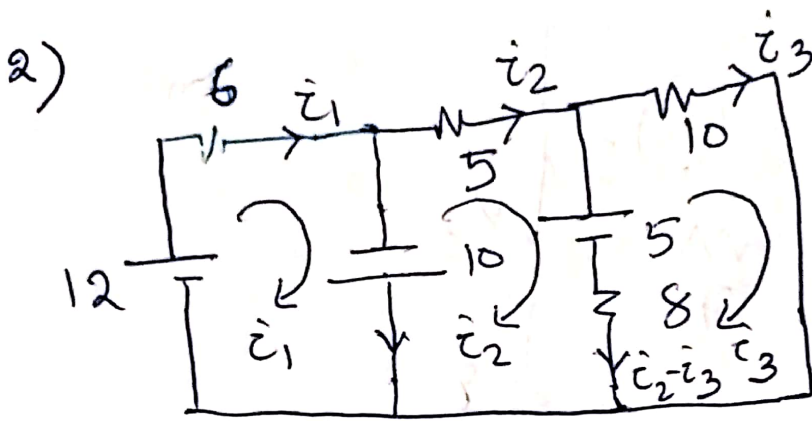
$$V_2 = 11.14V, \quad V_3 = 11.142V, \quad V_1 = 16V$$



$$6i_1 - 10 - 12 = 0 \Rightarrow i_1 = \frac{22}{6}$$

$$5i_2 + 5 + 8(i_2 - i_3) + 10 = 0$$

$$13i_2 - 8i_3 = -15 \quad \text{--- ①}$$

$$10i_3 - 8(i_2 - i_3) - 5 = 0$$

$$-8i_2 + 18i_3 = 5 \quad \text{--- ②}$$

Solving ① and ②

$$i_2 = -1.35 \text{ A}$$

$$i_3 = -0.323 \text{ A}$$



P delivered ~~by 10V~~
by 10V source

$$= 10 \times (i_1 - i_2)$$

$$= 10(3.66 + 1.35)$$

$$= 10 \times 5.02 = 50.2 \text{ W}$$

3)

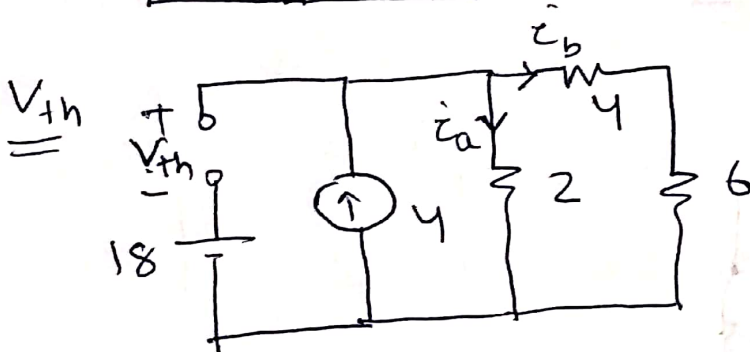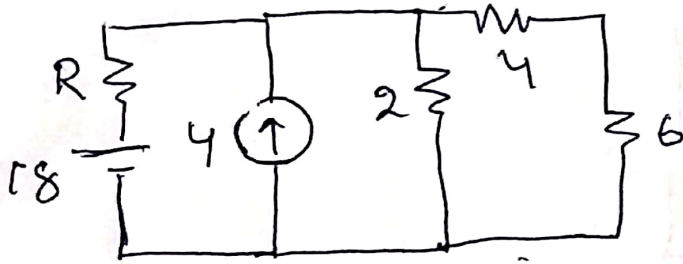


$$i_a = 4 \times \frac{10}{12} = \frac{10}{3} = 3.33 ; V_{th} = 2i_a - 18$$

$$= 2 \times 3.33 - 18$$

$$= 11.34 \text{ V}$$


R_{th}

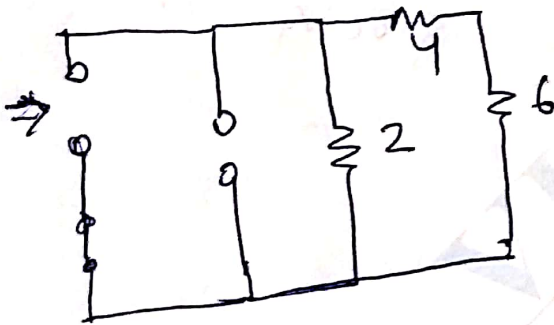


$$R_{th} = \frac{10 \times 2}{10 + 2} = \frac{20}{12}$$

$$= 1.66 \Omega$$


Thevenin equivalent circuit:

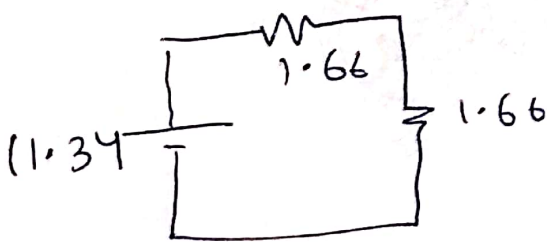
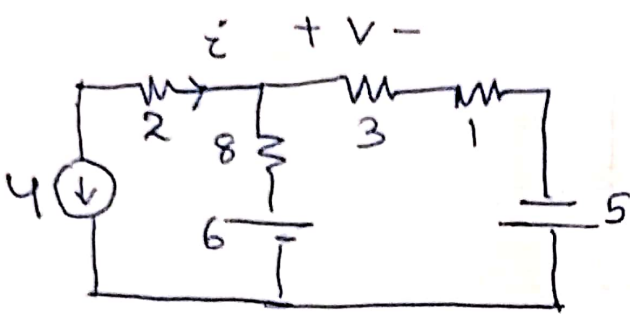
$$P_{max} = i^2 R = \left(\frac{11.34}{2 \times 1.66} \right)^2 \cdot 1.66 = \cancel{3.44} \cdot 1.66 = 19.36 \text{ W}$$



4A source active

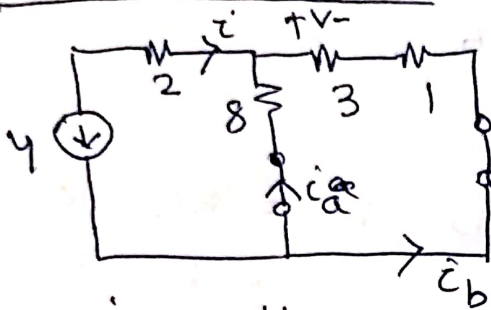


$$i_4 = 4$$

$$i_b = 4 \times \frac{8}{4+8} = 4 \times \frac{8}{12} = 2.66 \text{ A}$$

$$V_4 = -3 i_b = 8 \text{ V}$$


6V source active.

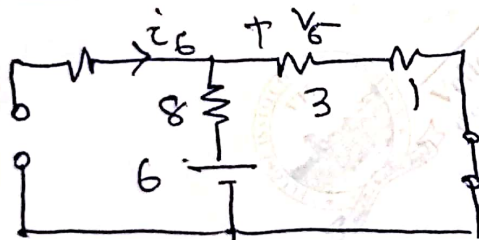

$$i_6 = 0$$

$$V_6 = 3 \times \frac{6}{12} = 1.5 \text{ V}$$

5V source active

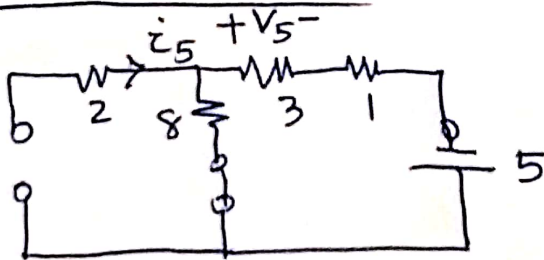

$$i_5 = 0$$

$$V_5 = 3 \times \frac{5}{12} = 1.25 \text{ V}$$

$$\text{Total current } i = -4 \text{ A}$$

$$V = 2 + 1.5 + 1.25 = 4.75 \text{ V}$$

$$v(t) = 50 \sin 314t = \frac{50}{\sqrt{2}} \angle 0^\circ$$

$$R = 5, \quad L = 20 \text{ mH}$$

$$\omega = 314, \quad X_L = \omega L = 314 \times 20 \times 10^{-3} = 6.28 \Omega$$

$$Z = R + j\omega L = 5 + j6.28 = 8.0 \angle 51.47^\circ \Omega$$

$$\tilde{i}(t) = \frac{50}{\sqrt{2}} \angle 0^\circ / 8.0 \angle 51.47^\circ = \frac{6.25}{\sqrt{2}} \angle -51.47^\circ \text{ A}$$

$$a) \tilde{i}(t) = 6.25 \sin(314t - 51.47^\circ) \text{ A}$$

b) phase angle between voltage and current 51.47° lagging

$$c) \text{ power factor} = \cos 51.47^\circ = 0.622 \text{ lagging}$$

$$d) P = \tilde{i}_{\text{rms}}^2 R = \left(\frac{6.25}{\sqrt{2}} \right)^2 5 = (4.42)^2 \times 5 = 97.5 \text{ W}$$

$$e) Q = \tilde{i}_{\text{rms}}^2 X_L = \left(\frac{6.25}{\sqrt{2}} \right)^2 6.28 = 19.53 \times 6.28 = 121.875 \text{ VAR}$$



Vellore Institute of Technology
VIT
Vellore Institute of Technology
Vellore Institute of Technology