







Vellore – 632014, Tamil Nadu, India  
**SCHOOL OF ELECTRICAL ENGINEERING**  
**FALL SEMESTER 2023-2024**  
**CAT-I**

**SLOT: E1+TE1**

Programme Name & Branch: **Fall Semester** Course Code: **BEEE102L**  
Course Name : **Basic Electrical and Electronics Engineering**  
Faculty Members: **Dr. M.Chilukuri, Dr. Mukul Chankaya, Dr. Thirumurugan C**  
Class Number(s):  
Date of the Examination:  
**Duration: 90 minutes** **Max. Marks : 50**


**General instruction(s):**

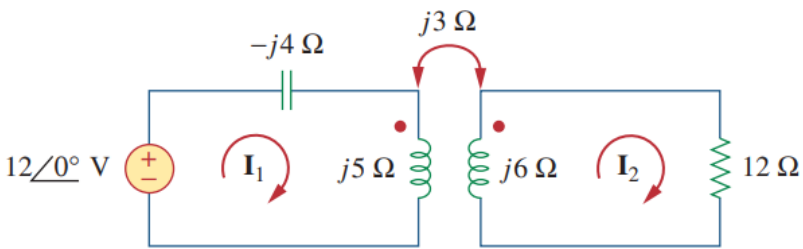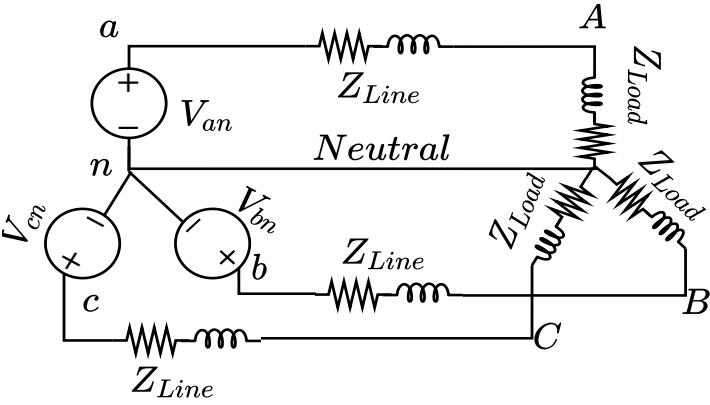Q. No	Question	Marks	CO	BL
1.	<p>Calculate the phasors currents <math>I_1</math> and <math>I_2</math> in circuit below. Also draw the electrical equivalent circuit for the same,</p>  <p style="text-align: center;">Fig. 1.</p>	10	3	5
2.	<p>In a balanced 3-phase Star-Star connection having phase 'a' voltage <math>V_{an} = 100\angle 0^\circ</math>, each phase line and load impedances is <math>Z_{Line} = 5 - 2j</math>, and <math>Z_{Load} = 10 + 8j</math> respectively. Consider the 'acb' phase sequence and calculate phase voltages, line voltages, and phase currents on both the generator and load sides.</p>  <p style="text-align: center;">Fig. 2.</p>	10	2	5

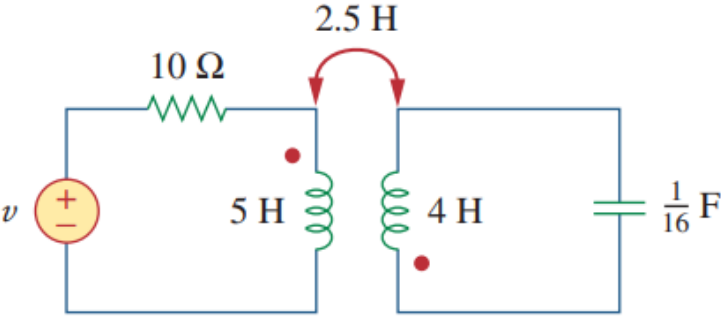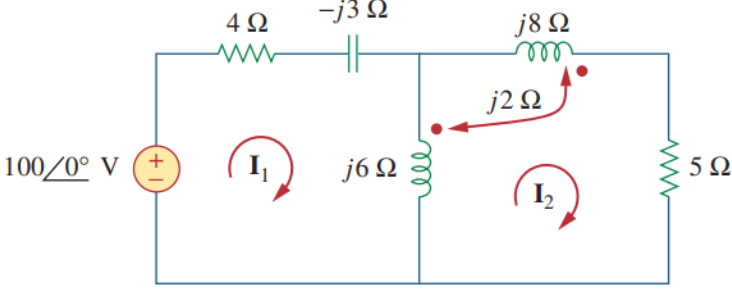3.	 <p style="text-align: center;">Fig 3.</p> <p>Calculate energy stored in the coupled inductors at a time <math>t=1s</math>, if <math>v = 60\cos(4t+30^\circ)</math> V. Also find the coupling coefficient.</p>	10	3	5
4.	<p>A transformer with 1000 primary turns and 400 secondary turns is supplied from a 220 V AC supply. Calculate the secondary side voltage and volts per turn ?</p>	10	4	3
5.	 <p style="text-align: center;">Fig 4.</p> <p>Calculate the mesh currents in circuit shown (Fig 4.) above.</p>	10	3	5

**Solution**

**Answer1:**

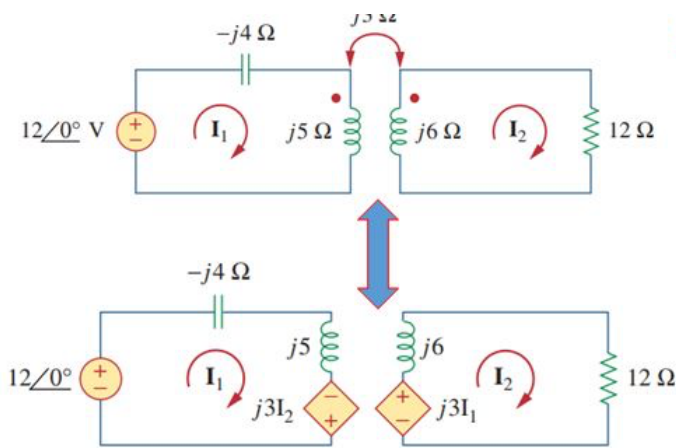

**Solution:** For loop 1, KVL gives

$$-12 + (-j4 + j5)\mathbf{I}_1 - j3\mathbf{I}_2 = 0$$

$$\text{or } j\mathbf{I}_1 - j3\mathbf{I}_2 = 12$$

For loop 2, KVL gives

$$-j3\mathbf{I}_1 + (12 + j6)\mathbf{I}_2 = 0$$


$$\mathbf{I}_1 = \frac{(12 + j6)\mathbf{I}_2}{j3} = (2 - j4)\mathbf{I}_2$$

$$\mathbf{I}_2 = \frac{12}{4 - j} = 2.91 \angle 14.04^\circ \text{ A}$$

$$\mathbf{I}_1 = (2 - j4)\mathbf{I}_2 = (4.472 \angle -63.43^\circ)(2.91 \angle 14.04^\circ)$$

$$\mathbf{I}_1 = 13.01 \angle -49.39^\circ \text{ A}$$

**Answer2:**

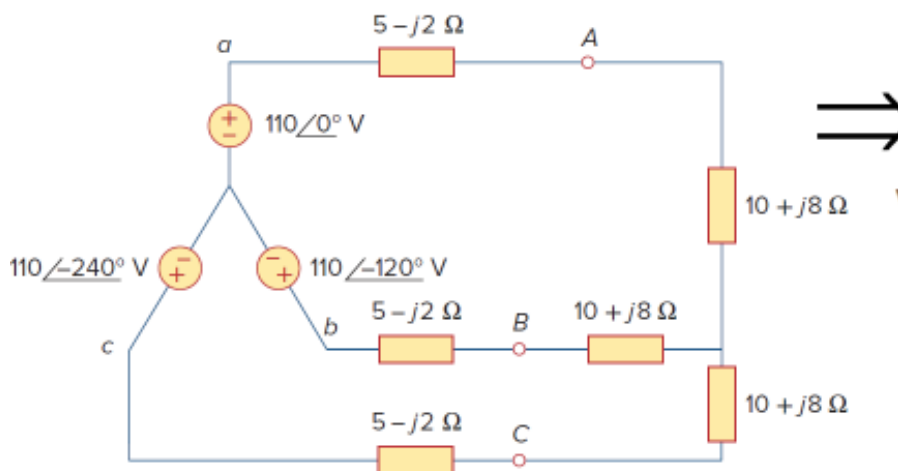


$$Z_Y = (5 - j2) + (10 + j8) = (15 + j6) \\ = 16.155 \angle 21.8^\circ$$

$$I_a = \frac{110 \angle 0^\circ}{16.155 \angle 21.8^\circ} = 6.81 \angle -21.8^\circ \text{ A}$$


ch as the source voltages in Fig. 1 are also in positive sequence:

$$I_b = I_a \angle -120^\circ = 6.81 \angle -141.8^\circ \text{ A}$$

$$I_c = I_a \angle -240^\circ = 6.81 \angle 98.2^\circ \text{ A}$$

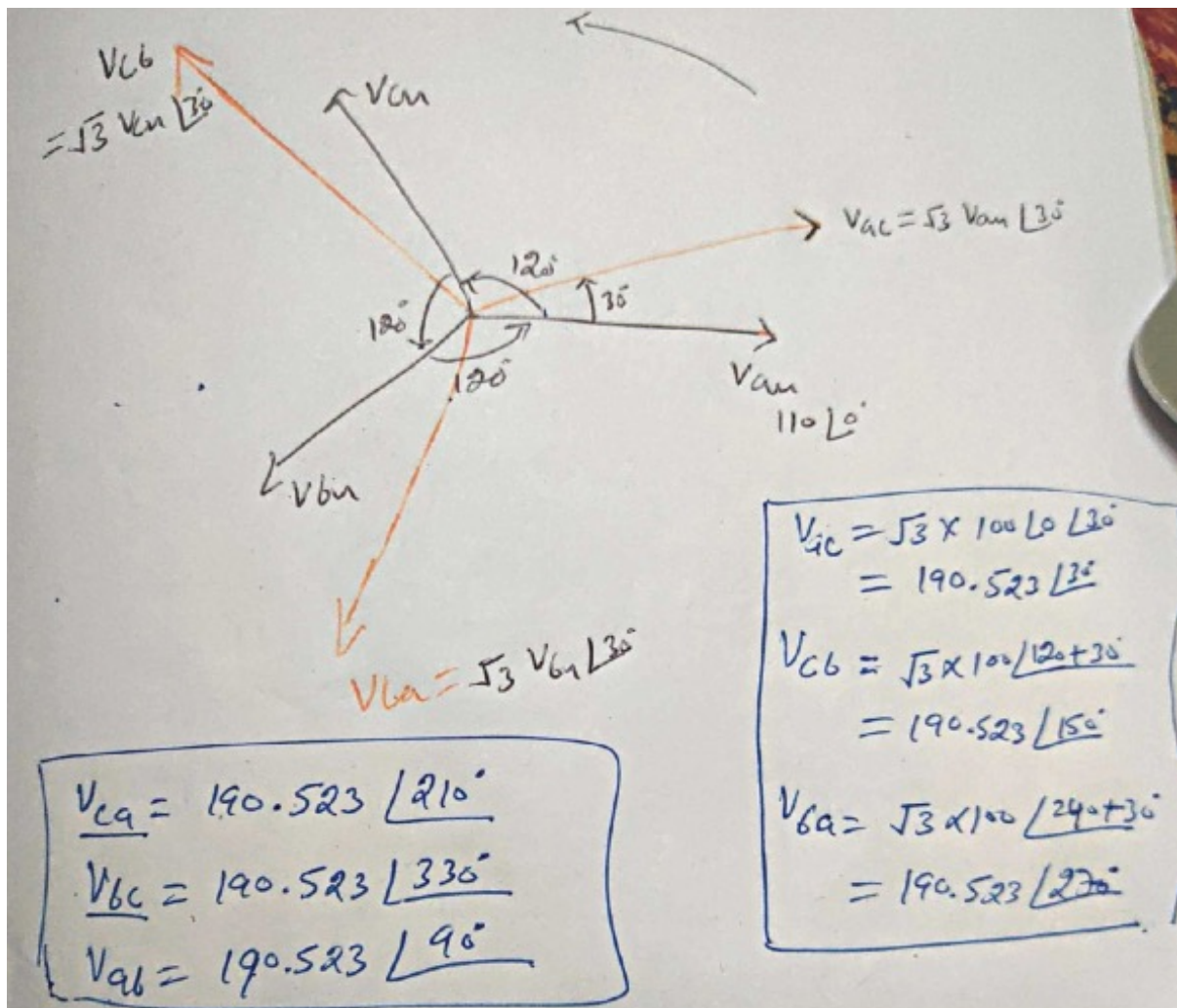

Answer 3:


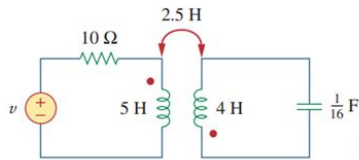


**Solution:** The coupling coefficient is

$$k = \frac{M}{\sqrt{L_1 L_2}} = \frac{2.5}{\sqrt{20}} = 0.56$$

we need to obtain the frequency-domain equivalent of the circuit.
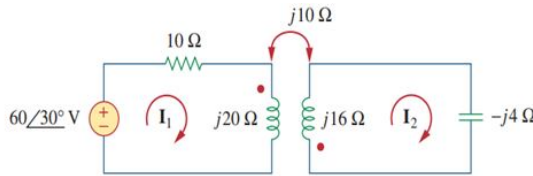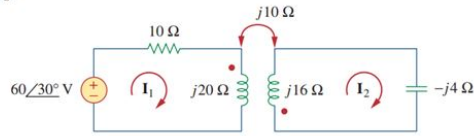
$$\begin{aligned} 60 \cos(4t + 30^\circ) &\Rightarrow 60 \angle 30^\circ, \quad \omega = 4 \text{ rad/s} \\ 5 \text{ H} &\Rightarrow j\omega L_1 = j20 \Omega \\ 2.5 \text{ H} &\Rightarrow j\omega M = j10 \Omega \\ 4 \text{ H} &\Rightarrow j\omega L_2 = j16 \Omega \\ \frac{1}{16} \text{ F} &\Rightarrow \frac{1}{j\omega C} = -j4 \Omega \end{aligned}$$



For mesh 1,

$$(10 + j20)\mathbf{I}_1 + j10\mathbf{I}_2 = 60 \angle 30^\circ$$

For mesh 2,

$$j10\mathbf{I}_1 + (j16 - j4)\mathbf{I}_2 = 0$$

$$\text{or } \mathbf{I}_1 = -1.2\mathbf{I}_2$$

**Substituting this into above equation**

$$\mathbf{I}_2(-12 - j14) = 60 \angle 30^\circ \Rightarrow \mathbf{I}_2 = 3.254 \angle 160.6^\circ \text{ A} \quad \text{and} \quad \mathbf{I}_1 = -1.2\mathbf{I}_2 = 3.905 \angle -19.4^\circ \text{ A}$$

In the time-domain,  $i_2 = 3.254 \cos(4t + 160.6^\circ)$  and  $i_1 = 3.905 \cos(4t - 19.4^\circ)$ .

At time  $t = 1 \text{ s}$ ,  $4t = 4 \text{ rad} = 229.2^\circ$ .  $i_2 = 3.254 \cos(229.2^\circ + 160.6^\circ) = 2.824 \text{ A}$

$i_1 = 3.905 \cos(229.2^\circ - 19.4^\circ) = -3.389 \text{ A}$

$$w = \frac{1}{2}L_1 i_1^2 + \frac{1}{2}L_2 i_2^2 + M i_1 i_2$$

$$w = \frac{1}{2}(5)(-3.389)^2 + \frac{1}{2}(4)(2.824)^2 + 2.5(-3.389)(2.824) = 20.73 \text{ J}$$

Answer 4;

A transformer with 1000 primary turns and 400 secondary turns is supplied from a 220 V AC supply. Calculate the secondary voltage and the volts per turn.

### Solution

Given data,

$$N_1 = 1000 \text{ and } N_2 = 400$$

$$V_1 = 220 \text{ V}$$

The turns ratio of transformer is,

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$\Rightarrow V_2 = V_1 \times \frac{N_2}{N_1} = 220 \times \frac{400}{1000}$$

$$\therefore V_2 = 88 \text{ Volts}$$


The volts per turn is given by,

$$\text{For primary winding} = \frac{V_1}{N_1} = \frac{220}{1000} = 0.22 \text{ Volts}$$

$$\text{For Secondary winding} = \frac{V_2}{N_2} = \frac{88}{400} = 0.22 \text{ Volts}$$


Hence, from this example, it is clear that the volts per turn for a transformer remain the same on both primary and secondary windings.

Answer 5.

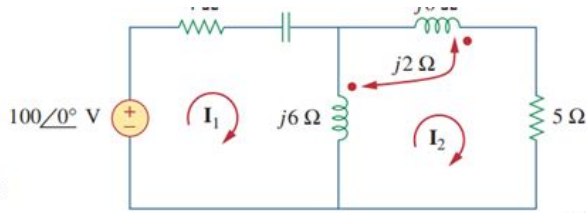

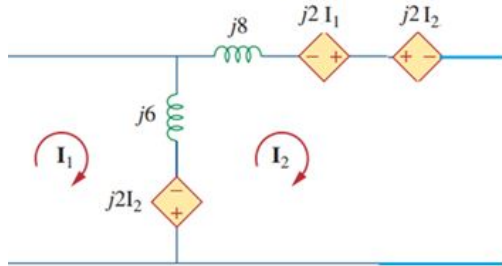**olution:**

Model showing the polarity of the induced voltages.



for mesh 1 KVL gives

$$-100 + \mathbf{I}_1(4 - j3 + j6) - j6\mathbf{I}_2 - j2\mathbf{I}_2 = 0$$

$$\text{or } 100 = (4 + j3)\mathbf{I}_1 - j8\mathbf{I}_2$$

for mesh 2, KVL gives

$$0 = -2j\mathbf{I}_1 - j6\mathbf{I}_1 + (j6 + j8 + j2 \times 2 + 5)\mathbf{I}_2$$

$$\text{or } 0 = -j8\mathbf{I}_1 + (5 + j18)\mathbf{I}_2$$

Putting **equations** in matrix form, we get

$$\begin{bmatrix} 100 \\ 0 \end{bmatrix} = \begin{bmatrix} 4 + j3 & -j8 \\ -j8 & 5 + j18 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 4 + j3 & -j8 \\ -j8 & 5 + j18 \end{vmatrix} = 30 + j87$$

$$\Delta_1 = \begin{vmatrix} 100 & -j8 \\ 0 & 5 + j18 \end{vmatrix} = 100(5 + j18) \quad \mathbf{I}_1 = \frac{\Delta_1}{\Delta} = \frac{100(5 + j18)}{30 + j87} = \frac{1,868.2/74.5^\circ}{92.03/71^\circ} = 20.3/3.5^\circ \text{ A}$$

$$\Delta_2 = \begin{vmatrix} 4 + j3 & 100 \\ -j8 & 0 \end{vmatrix} = j800 \quad \mathbf{I}_2 = \frac{\Delta_2}{\Delta} = \frac{j800}{30 + j87} = \frac{800/90^\circ}{92.03/71^\circ} = 8.693/19^\circ \text{ A}$$