



**VIT**  
Vellore Institute of Technology  
(Deemed to be University) established on 12/11/1984

**School of Electrical Engineering**

Fall Semester 2023-24

Continuous Assessment Test – 1

SLOT: G1+TG1

Programme Name & Branch : B.Tech & CSE

Course Name & code: Basic of Electrical and Electronics Engineering & BEEE102L

Class Numbers: VL2023240107487, VL2023240107785, VL2023240107779, VL2023240107494, VL2023240107791

Faculty Names: Dr. Suprava Chakraborty, Dr. Venkata Ramana Kasi, Dr. Jakeer Hussain, Dr. Monica Subashini M, Dr. Rajesh Kumar Lenka

Exam Duration: 90 Min.

Maximum Marks: 50


**General instruction:**

Answer all questions

Q.No.	Question	Max Marks
1.	<p>For the circuit in Fig. 1, find the branch current <math>I</math> using mesh current analysis.</p> <p>Fig.1</p>	10
2.	<p>Calculate the node voltage <math>V_x</math> in the circuit shown in Fig. 2, using node voltage analysis.</p> <p>Fig.2</p>	10

3.	<p>Calculate the value of <math>R_L</math> for maximum power transfer in the circuit of Fig. 3.          Compute the maximum power absorbed by the <math>R_L</math>.</p>	10
Fig.3		
4.	<p>Use Superposition theorem to find <math>v</math> in the circuit of Fig. 4.</p>	10
Fig.4		
5.	<p>A coil of inductance <math>125\text{ mH}</math> and negligible resistance is connected in series with a <math>5\ \Omega</math> resistor and <math>100\ \mu\text{F}</math> capacitor to a <math>300\text{ V}</math>, <math>50\text{ Hz}</math> supply.          Calculate</p> <ol style="list-style-type: none"> <li>Circuit impedance</li> <li>Circuit current</li> <li>Circuit phase angle</li> <li>Voltage across inductive coil</li> <li>Voltage across capacitor</li> </ol>	10

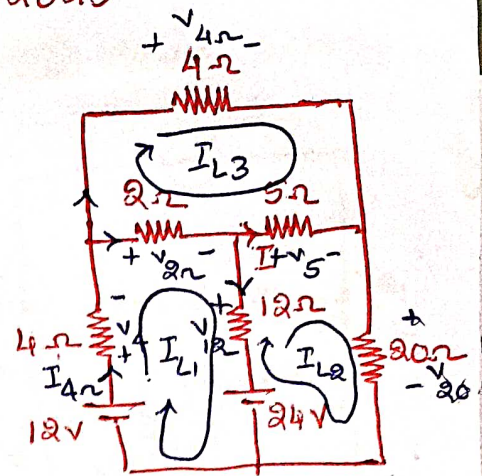1] Find branch current  $I$ , using mesh current analysis.



KVL @ loop-1 :

$$12 = V_{4\Omega} + V_{2\Omega} + V_{12\Omega} + 24$$

$$-12 = 4I_{L1} + 2(I_{L1} - I_{L3}) + 12(I_{L1} - I_{L2})$$

$$-12 = 18I_{L1} - 12I_{L2} - 2I_{L3} \quad \text{--- (1)}$$

KVL @ loop-2 :

$$24 + V_{12\Omega} = V_{5\Omega} + V_{20\Omega}$$

$$24 + 12(I_{L1} - I_{L2}) = 5(I_{L2} - I_{L3}) + 20I_{L2}$$

$$24 = -12I_{L1} + 37I_{L2} - 5I_{L3} \quad \text{--- (2)}$$

KVL @ loop-3 :

$$V_{5\Omega} + V_{2\Omega} = V_{4\Omega}$$

$$5(I_{L2} - I_{L3}) + 2(I_{L1} - I_{L3}) = 4I_{L3}$$

$$0 = -2I_{L1} - 5I_{L2} + 11I_{L3} \quad \text{--- (3)}$$

$\Rightarrow$  (1), (2), (3):

$$\begin{bmatrix} 18 & -12 & -2 \\ -12 & 37 & -5 \\ -2 & -5 & 11 \end{bmatrix} \begin{bmatrix} I_{L1} \\ I_{L2} \\ I_{L3} \end{bmatrix} = \begin{bmatrix} -12 \\ 24 \\ 0 \end{bmatrix}$$


$$Ax = B$$

$$x = A^{-1}B.$$

$$\Rightarrow \begin{bmatrix} I_{L1} \\ I_{L2} \\ I_{L3} \end{bmatrix} = \begin{bmatrix} -0.24 \\ 0.602 \\ 0.23 \end{bmatrix} //$$

$$\therefore I_{5\Omega} = I_{L2} - I_{L3} = 0.372 \text{ A} //$$

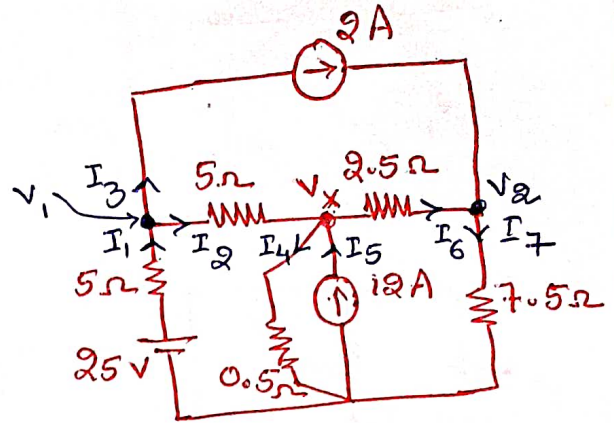(2) calculate the node voltage  $v_x$  using node voltage analysis:



KCL @ node-1:

$$I_1 = I_2 + I_3$$

$$\frac{25 - v_1}{5} = \frac{v_1 - v_x}{5} + 2$$

$$3 = 0.4 v_1 - 0.2 v_x \quad \text{--- ①}$$

KCL @ node-x:

$$I_2 + I_5 = I_4 + I_6$$

$$\frac{v_1 - v_x}{5} + 12 = \frac{v_x}{0.5} + \frac{v_x - v_2}{2.5}$$

$$12 = -0.2 v_1 + 2.6 v_x - 0.4 v_2 \quad \text{--- ②}$$

KCL @ node-2:

$$I_6 + I_3 = I_7$$

$$\frac{v_x - v_2}{2.5} + 2 = \frac{v_2}{7.5}$$

$$2 = -0.4 v_x + 0.534 v_2 \quad \text{--- ③}$$

$\Rightarrow$  ①, ②, ③:

$$\begin{bmatrix} 0.4 & -0.2 & 0 \\ -0.2 & 2.6 & -0.4 \\ 0 & -0.4 & 0.534 \end{bmatrix} \begin{bmatrix} v_1 \\ v_x \\ v_2 \end{bmatrix} = \begin{bmatrix} 3 \\ 12 \\ 2 \end{bmatrix}$$

$$A x = B$$

$$x = A^{-1} B$$

$$\therefore \begin{bmatrix} v_1 \\ v_x \\ v_2 \end{bmatrix} = \begin{bmatrix} 10.91 \\ 6.81 \\ 8.85 \end{bmatrix} //$$

$$\therefore v_x = 6.81 \text{ V} //$$

$$I_1 = \frac{25 - v_1}{5}$$

$$I_2 = \frac{v_1 - v_x}{5}$$

$$I_3 = 2 \text{ A}$$

$$I_4 = \frac{v_x}{0.5}$$

$$I_5 = 12 \text{ A}$$

$$I_6 = \frac{v_x - v_2}{2.5}$$

$$I_7 = \frac{v_2}{7.5}$$

3) Calculate  $R_{Lopt}$  for  $P_{RLmax}$ .


$V_{TH}$  calculation:  $V_{TH} = V_{ab} = V_a - V_b$ .

$$V_a = 60 \times \frac{20}{30} = 40 \text{ V}$$




$$V_b = 60 \times \frac{5}{30} = 10 \text{ V}$$

$$\therefore V_{TH} = V_{ab} = 30 \text{ V} \quad \text{--- (1)}$$

$R_{TH}$  calculation:

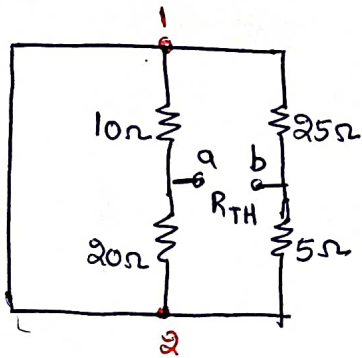

$\Rightarrow$

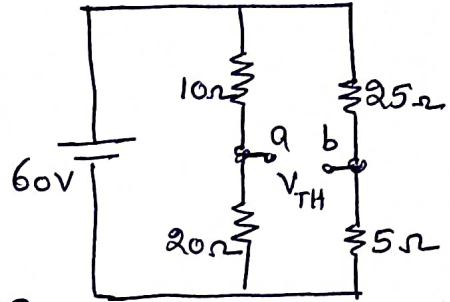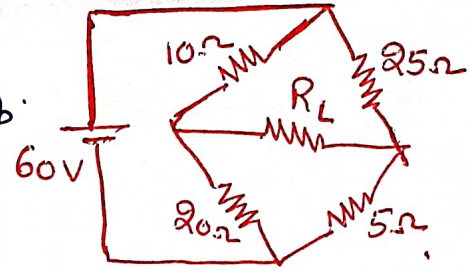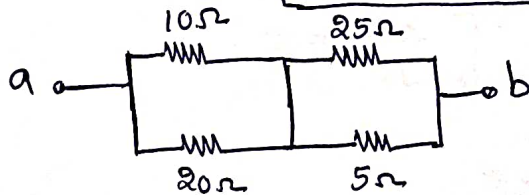


$$R_{TH} = R_{ab} = (10 \parallel 20) + (25 \parallel 5)$$

$$= 6.667 + 4.1667$$

$$= 10.83 \Omega \quad \text{--- (2)}$$

Thevenin ckt:

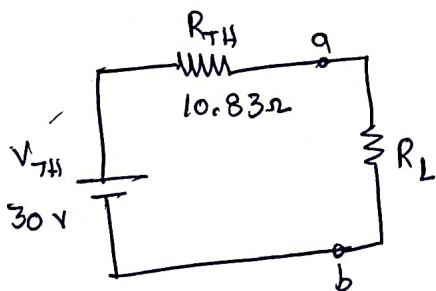

According to max power transfer theorem,


$R_{Lopt} = R_{TH}$  for  $P_{RLmax}$

$$\therefore R_{Lopt} = 10.83 \Omega //$$

$$P_{RLmax} = \frac{V_{TH}^2}{4 R_{TH}} = \frac{(30)^2}{4 (10.83)} = 20.77 \text{ W} //$$


[A] using superposition theorem, find  $V$ .

with 12V alone :

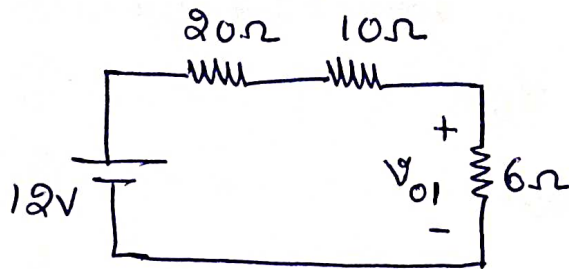


$$V_{o1} = 12 \times \frac{6}{20+10+6} = 2V \quad \text{--- (1)}$$

with 1.2A alone :

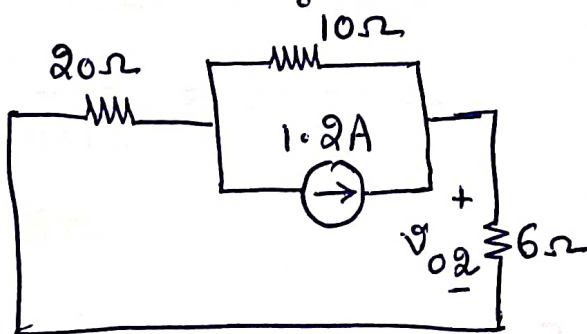

$\Rightarrow$

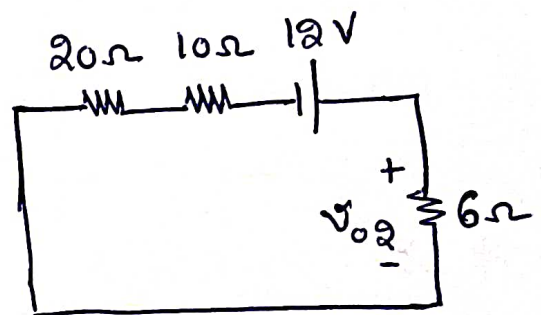

$$V_{o2} = 12 \times \frac{6}{20+10+6} = 2V \quad \text{--- (2)}$$

$$\therefore V_0 = V_{o1} + V_{o2} = 4V //$$

[5] Calculate


(a) Circuit impedance

(b) Circuit current

(c) Circuit phase angle

(d) voltage across inductive coil

(e) voltage across capacitor

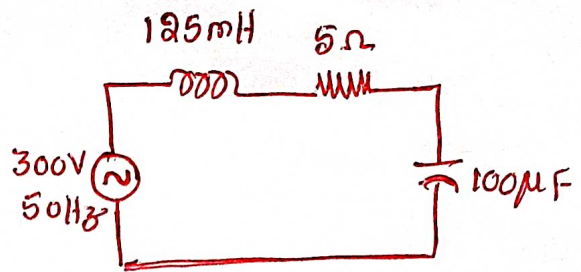

$$\bar{V}_s = 300\sqrt{2} \angle 0^\circ$$

$$X_L = 2\pi fL = 39.27 \Omega$$

$$X_C = \frac{1}{2\pi fC} = 31.83 \Omega$$

$$R = 5 \Omega$$

(a) Impedance :  $Z = R + j[X_L - X_C] = 5 + j7.44 = 8.96 \angle 56.1^\circ \Omega //$

(b) Circuit current :  $\bar{I} = \frac{\bar{V}}{Z} = \frac{300\sqrt{2} \angle 0^\circ}{8.96 \angle 56.1^\circ} = 47.35 \angle -56.1^\circ \text{ A} //$

$$I_{RMS} = \frac{47.35}{\sqrt{2}} = 33.48 \text{ A} //$$

(c) Circuit phase angle :  $\phi = -56.1^\circ //$

(d) voltage across inductive coil :  $V_L = I_L X_L$

$$= (47.35 \angle -56.1^\circ) (39.27 \angle 90^\circ)$$

$$= 1859.43 \angle 33.9^\circ \text{ V} //$$

(e) voltage across capacitive element :  $V_C = I_C X_C$

$$= (47.35 \angle -56.1^\circ) (31.83 \angle -90^\circ)$$

$$= 1507.1 \angle -146.1^\circ \text{ V} //$$