



School of Computer Science Engineering and Information Systems

Fall Semester 2023-2024

Continuous Assessment Test – I

Programme Name & Branch: BTECH CSE (BCB, BCE, BCI, BCT, BDS, BKT)

Course Name & code: BECE102L Digital Systems Design Slot: B2+TB2

Exam Duration: 90 Min.

Maximum Marks: 50

General instruction(s):

1. Answer all the questions

Q. No.	Question	Max Marks	CO	BL																								
1.	Simplify the Boolean function "F" using K-map and implement the function using only 2 input NAND gates $F = wxy'z + w'xz + wxyz$	10	CO1	BL3																								
2.	a) Reduce the following Boolean function "G" to three literals by Boolean laws/postulates/theorems $G = (x'y' + z)' + z + xy + wz$ b) Draw the schematic of (three literals function/simplified function) "G" using CMOS cells.	10	CO1	BL6																								
3.	<p>a. Find out errors in the following verilog program:</p> <table border="1"> <thead> <tr> <th>Line</th> <th>Error in code</th> </tr> </thead> <tbody> <tr><td>1</td><td>Module 1 mydesign (A,B,C);</td></tr> <tr><td>2</td><td>input a, b;</td></tr> <tr><td>3</td><td>output c;</td></tr> <tr><td>4</td><td>always (*)</td></tr> <tr><td>5</td><td>begin;</td></tr> <tr><td>6</td><td>if (a= 1'b01)</td></tr> <tr><td>7</td><td>assign c <= b;</td></tr> <tr><td>8</td><td>Else</td></tr> <tr><td>9</td><td>assign c = a;</td></tr> <tr><td>10</td><td>end</td></tr> <tr><td>11</td><td>end module;</td></tr> </tbody> </table> <p>b. Write a verilog code in dataflow level modeling for the following verilog program.</p> <pre> module test (in, En, Y); input [1:0] in; input En; output reg [3:0] Y; always @(*) begin if (En == 1'b1) begin case(in) 2'b00: Y = 4'b0001; </pre>	Line	Error in code	1	Module 1 mydesign (A,B,C);	2	input a, b;	3	output c;	4	always (*)	5	begin;	6	if (a= 1'b01)	7	assign c <= b;	8	Else	9	assign c = a;	10	end	11	end module;	10	CO2	BL3
Line	Error in code																											
1	Module 1 mydesign (A,B,C);																											
2	input a, b;																											
3	output c;																											
4	always (*)																											
5	begin;																											
6	if (a= 1'b01)																											
7	assign c <= b;																											
8	Else																											
9	assign c = a;																											
10	end																											
11	end module;																											


```

2'b01: Y = 4'b0010;
2'b10: Y = 4'b0100;
2'b11: Y = 4'b1000;
endcase
end
else
Y = 4'b0000;
end
endmodule

```

4. Find the Boolean functions from the below decoder circuit. Implement the function F1 using 8:1 MUX(s), F2 using 4:1 MUX(s), F3 using 2:1 MUX(s).

10 CO 3 BL6

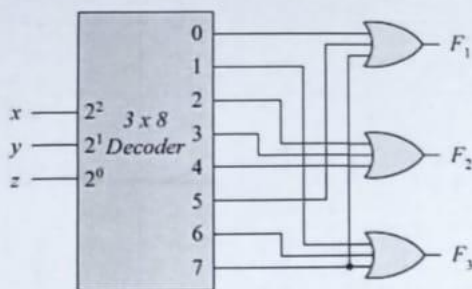

5. Design the combinational circuit with less number of logic gates for the input A, B, C and D as given in the truth table. Let Y and Z be the outputs of the design. Write the gate level/structural verilog code of the design along with its testbench code to verify it.


10 CO 3 BL6

A	B	C	D	Y	Z
0	0	0	0	1	1
0	0	0	1	1	0
0	0	1	0	1	1
0	0	1	1	0	X
0	1	0	0	0	0
0	1	0	1	0	1
0	1	1	0	1	0
0	1	1	1	0	X
1	0	0	0	1	1
1	0	0	1	1	0
1	0	1	0	1	1
1	0	1	1	0	X
1	1	0	0	0	0
1	1	0	1	0	1
1	1	1	0	0	0
1	1	1	1	X	X


B₂

BCEW2L - CAT1 - B2 - KEY.

 1) $F = wxy'z + w'xz + wxyz$
 01101 0101 1111
 0111 (3)



$F = xz$

 

w x y z
 0 1 0 1
 1 1 1 1

2) a) $G = (x'y' + z)' + z + xy + wz$

$= (x'y')'z' + z + xy + wz$

$= ((x') + (y'))z' + z + xy + wz$

$= (x + y)z' + z + xy + wz$

$= (x + y + z)(z + z') + xy + wz$

$= (x + y + z) + xy + wz$


$= z(1 + w) + x + y + xy$

$= z + x(1 + y) + y$ (5)

$z + x + y = x + y + z$

* Using $A + BC = (A + B)(A + C)$

b)

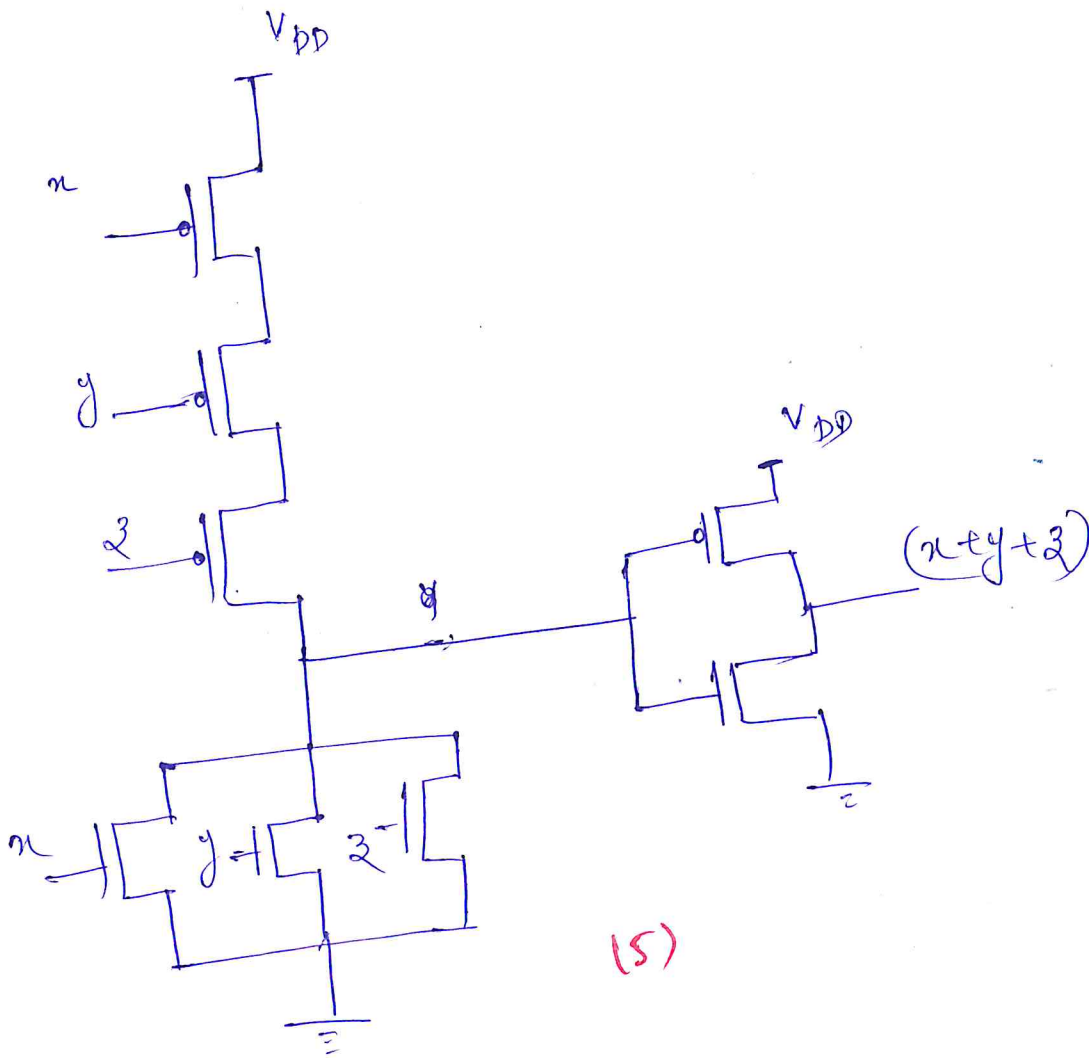

3. i) Module mydesign (A, B, C);

Error: Module → module (Capital M)
module name should start with a letter
not with a number.

2) input a, b;

Inputs are ~~not~~ defined in capital letters.

input a, b; → input A, B;

Colon to semi colon

3) output C;

C should be capital, neg is missing

output c; → output neg C;

4) always (*) → always @ (*)

@ is missing.

5) begin;

No need of Semicolon.

begin; → begin

6) if (a = 'b01') → ~~if (a = 'b01')~~ if (a == 'b01')

Defined as single bit, but two bits are there.
if (a) is enough.

7) assign c <= b;

~~no error~~ - can't use assign statement inside always @
c & b should be in caps.

8) Else → else

E should be small letter.

9) assign c = a;

~~no error~~ Can't use assign statement inside always @
c & a should be in caps

10) end

11) end module; → endmodule

There should not be any space b/w end and module.

No need of Semicolon.

3) b)


input is [1:0] in

Decoder. Let.

Each error (1/2)

Max. 10 errors

En. in[0] in[1]

 

```
module test (en, En, Y);  
input [1:0] in;  
input En;  
output reg [3:0] Y;  
assign Y[0] = En & ~ in[0] & ~ in[1];  
assign Y[1] = En & ~ in[0] & in[1];  
assign Y[2] = En & in[0] & ~ in[1];  
assign Y[3] = En & in[0] & in[1];  
endmodule.
```

15)

A) $F_1 = \Sigma(0, 5, 7)$


$F_2 = \Sigma(2, 3, 4)$

$F_3 = \Sigma(1, 6, 7)$


$F_1 \rightarrow 8:1$ MUX

x	y	z	F_1	F_2	F_3
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	1

 x, y as select lines. $\rightarrow F_2 \rightarrow 4:1$ MUX.




(2)

 

(4)

x	y	z	F ₃
0	0	0	0
0	0	1	1
0	1	0	0
0	0	0	0

$$F_3 = \bar{y}z$$

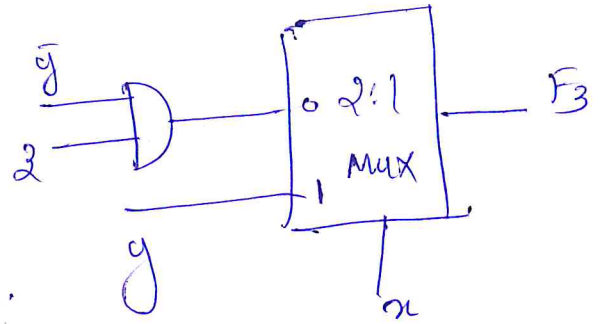


1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$F_3 = y\bar{z} + yz$$

$$= y(\bar{z} + z)$$


$$= y \cdot (1)$$

5)

 

$$Y = \bar{B}\bar{C} + \bar{B}\bar{D} + \bar{A}C\bar{D}$$


(2)

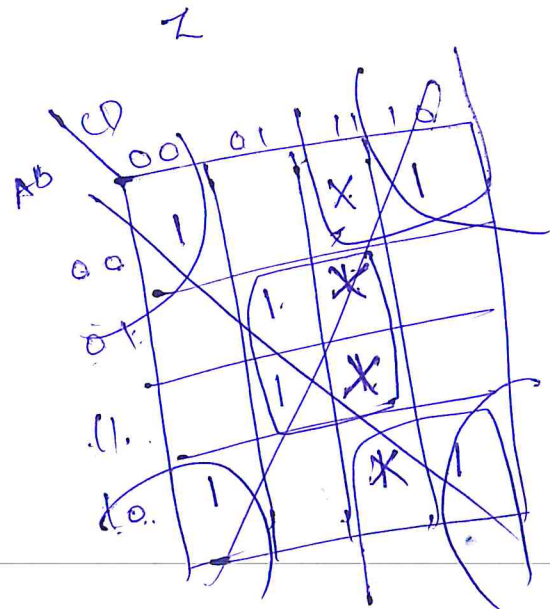

AB	CD
00	00
10	01
00	00
10	10
01	01
11	11
00	00
10	10

~~$$Z = BD + \bar{B}\bar{D} + \bar{B}C$$~~

00	11
10	10

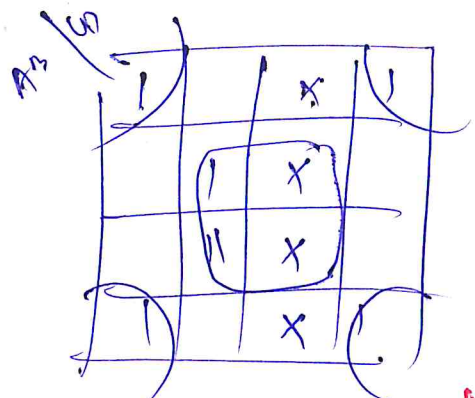

$$Z = BD + \bar{B}\bar{D}$$

(2)

```
module comb (A, B, C, D, Y, Z)
```

```
input A, B, C, D;
```

```
output Y, Z;
```

```
wire w1, w2, w3, w4, w5, w6, w7, w8;
```

```
not n1 (w1, A)
```

```
not n2 (w2, B)
```

```
not n3 (w3, C)
```

```
not n4 (w4, D);
```

```
and a1 (w5, w1, C, w4);
```

```
and a2 (w6, w2, w4);
```

```
and a3 (w7, w2, w3);
```

```
and a4 (w8, B, D);
```

```
or o1 (Y, w5, w6, w7);
```

```
or o2 (Z, w6, w8);
```

```
endmodule (3)
```

```
module testbench_comb;
```

```
reg A, B, C, D;
```

```
wire Y, Z;
```

```
integer i;
```

```
comb tb (A, B, C, D, Y, Z);
```

```
initial
```

begin

for (i=4'b0; i<16; i=i+1)

begin

{A, B, C, D} = i; #10;

end

{A, B, C, D} = 4'b0;

end

endmodule. (3)
