

Q1i)

$$AB + CD + A\bar{E}B$$

$$= ABC(C+\bar{C}) + CD(A+\bar{A}) + A\bar{E}B(C+\bar{C})$$

$$= ABC + AB\bar{C} + ACD + \bar{A}CD + A\bar{E}B\bar{C} + A\bar{E}BC$$

$$= ABC + AB\bar{C} + ACD + \bar{A}CD + A\bar{E}B\bar{C} + A\bar{E}BC$$

$$+ \bar{A}B\bar{C}D + \bar{A}BCD + \bar{A}\bar{E}BCD + \bar{A}EBCD + A\bar{E}B\bar{C}D + A\bar{E}BCD$$

$$= \boxed{\bar{A}B\bar{C}D + \bar{A}BCD + A\bar{E}B\bar{C}D + A\bar{E}BCD + A\bar{E}B\bar{C}D + A\bar{E}BCD}$$

Canonical SOP-form.

✓ POS Form

$$\frac{\sum m}{\text{POS Form}} = 1 - \frac{\sum \text{minterm terms}}{\text{SOP}}$$

$$= 1 - \frac{\sum (3, 8, 12, 13, 14, 15)}{\text{terms only}}$$

$$\text{POS} = \prod_{\text{max}} (0, 1, 2, 4, 5, 6, 7, 9, 10, 11)$$

$$= (A+B+C+D)(A+B+C+\bar{D})(A+B+\bar{C}+D)(A+\bar{B}+C+D)(A+\bar{B}+C+\bar{D})(A+\bar{B}+\bar{C}+D)(A+\bar{B}+\bar{C}+\bar{D})(\bar{A}+B+C+D)(\bar{A}+B+C+\bar{D})$$

(ii) $WX\bar{Y} + WX\bar{Z} + XY\bar{Z}$

$$= WX\bar{Y}(\bar{Z}+Z) + WX\bar{Z}(\bar{Y}+Y) + XY\bar{Z}(\bar{W}+W)$$

$$= \boxed{WX\bar{Y}\bar{Z} + WX\bar{Y}Z + WX\bar{Z}\bar{Y} + WX\bar{Z}Y + XY\bar{Z}\bar{W} + XY\bar{Z}W}$$

$$= WX\bar{Y}\bar{Z} + WX\bar{Y}Z + \bar{W}XY\bar{Z} + WXY\bar{Z} \text{ Canonical form in SOP.}$$

$$\text{POS form: } \frac{\sum M}{\text{POS}} = 1 - \frac{\sum \text{minterm terms}}{\text{SOP}}$$

$$= 1 - \frac{\sum \text{terms}}{\text{SOP}} (12, 13, 14, 6)$$


$$\prod_{\text{Max}} (0, 1, 2, 3, 4, 5, 7, 8, 9, 10, 11, 15)$$

$$= (W+X+Y+Z)(W+X+Y+\bar{Z})(W+X+\bar{Y}+Z)(W+X+\bar{Y}+\bar{Z})(W+\bar{X}+Y+Z)$$

$$(W+\bar{X}+Y+\bar{Z})(W+\bar{X}+\bar{Y}+Z)(\bar{W}+X+Y+Z)(\bar{W}+X+Y+\bar{Z})$$


$$(\bar{W}+X+\bar{Y}+Z)(\bar{W}+X+\bar{Y}+\bar{Z})(\bar{W}+X+Y+Z)$$

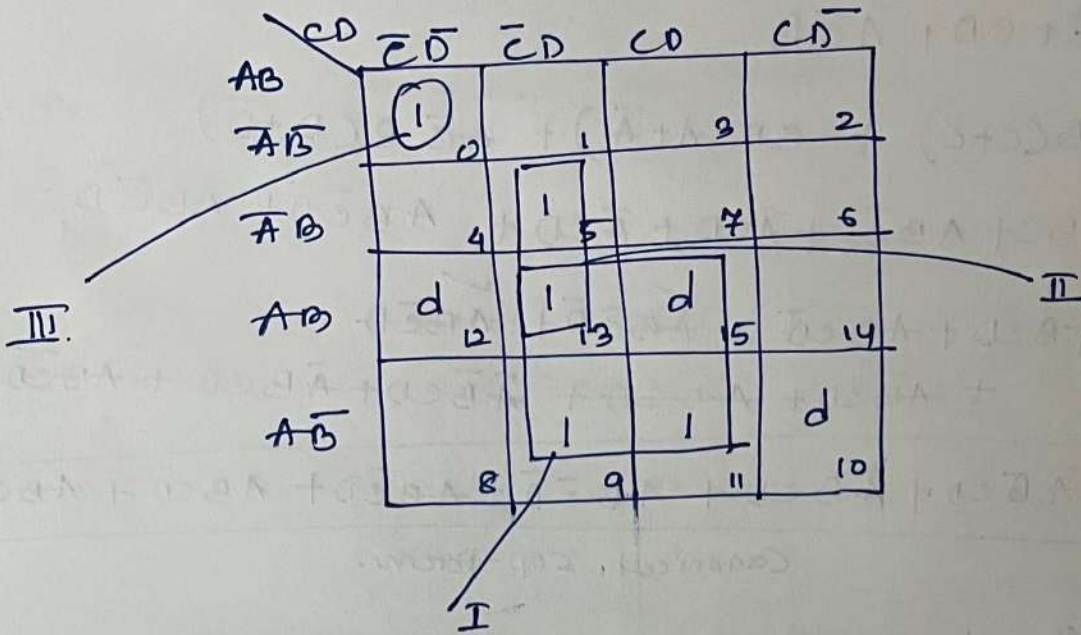2(i) $X(A, B, C, D) = \sum m(0, 5, 9, 11, 13) + d(10, 12, 15)$



$X(A, B, C, D) = \sum L I + L II + L III$
 $= \bar{A}\bar{B} + A\bar{B} + \bar{A}\bar{B}$

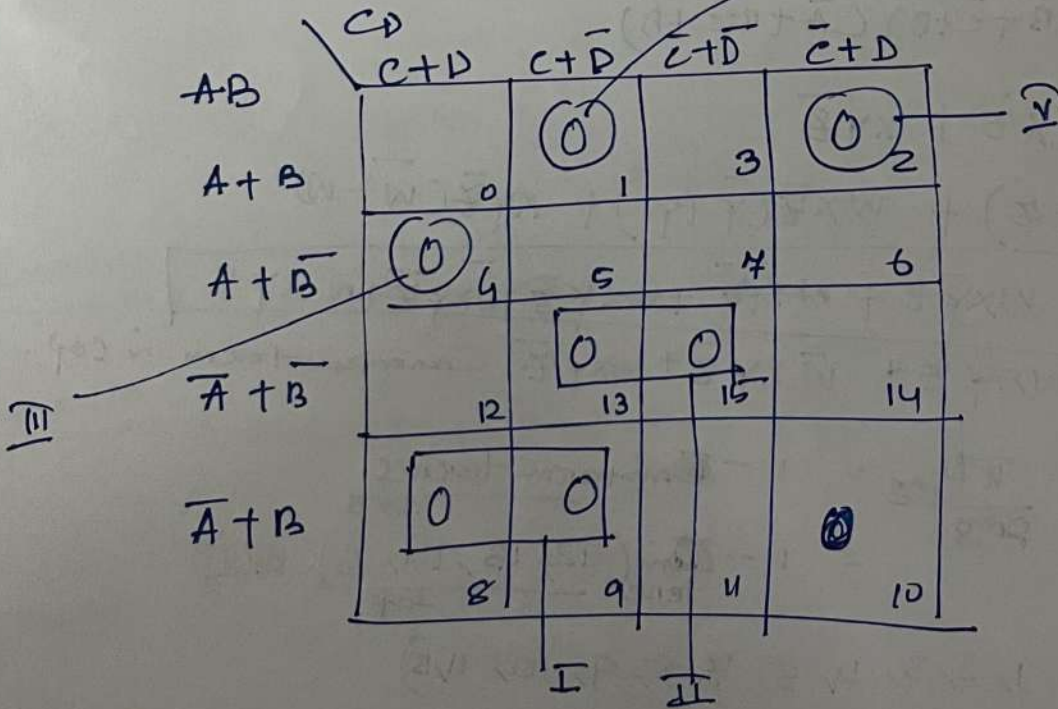2(ii) $Y(A, B, C, D) = \prod M(1, 2, 4, 8, 9, 13, 15)$



$Y(A, B, C, D) = (\bar{A} + \bar{B} + C)(\bar{A} + \bar{B} + \bar{D})(A + \bar{B} + C + D)(A + \bar{B} + \bar{C} + \bar{D})$

3(i)

line-1 module fig-1 (in A, B, C; out Y);

↳ capture should be in small caps

first output

then declare input

line-2

wires w1; w2; w3; w4; w5; w6; w7; w8; w9; w10;

no-s

Semicolon should be common

it should be semicolon.

line-3

not (w1-A); — semicolon (;)

↳ it should be ';

line-4

not (w2-C); — the output ~~should~~ input should be 'B'

↳ it should be ';

line-5

not (w3-B); — the input should be 'C'

↳ it should be ';

line-6

not (w4, A, w1); — 'B'

line-7

not (w5, B, w2); — 'A'

line-8

not (w6, w7, w2); — 'w1' small caps.

line-9

nand (w7, w3, w3); — 'w4'

line-10

nand (w8, w4, w5); — 'w' 'w2'

line-11

nand (w9, w6, w1); — 'w5' 'w6'

line-12

nand (w10, w2, w6); — 'e'

line-13

(w5, w3, w7, w6); — 'w5' 'w6'

line-14

end module — no space.

Finally the student here to write the error frame case separately for the structure.

4. (i) Full adder

A	B	e_{in}	S	C_o
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Sum


A \ B e_{in}	$B + e_{in}$	$A + \bar{e}_{in}$	$\bar{B} + e_{in}$	$\bar{B} + \bar{e}_{in}$
A	0 0	1 1	0 3	2 2
\bar{A}	4 4	0 5	7 7	0 6

Carry

A \ B e_{in}	$B + e_{in}$	$B + \bar{e}_{in}$	$\bar{B} + e_{in}$	$\bar{B} + \bar{e}_{in}$
A	0 0	1 1	0 3	2 2
\bar{A}	4 4	5 5	7 7	6 6

$$S = (A + B + e_{in}) (\bar{A} + \bar{B} + \bar{e}_{in}) + (\bar{A} + \bar{B} + e_{in}) (A + B + \bar{e}_{in})$$

$$C_o = A (B + e_{in})$$

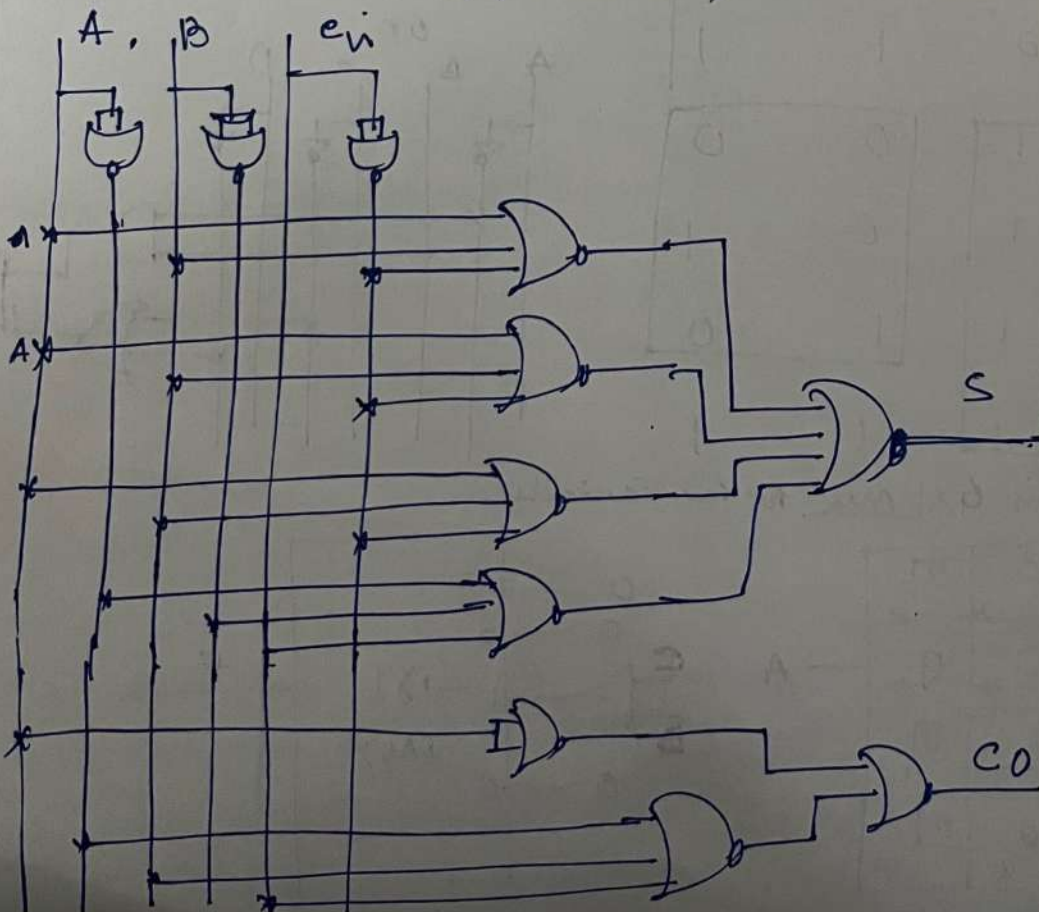

4 (b)

module fulladder (s, co, A, B, cin)






input A, B, cin;

output s, co;

assign s = (A | B | cin) & (A | B | ~cin) & (~A | B | ~cin) & (~A | ~B | cin)

assign co = A & (A | B | cin)

Extra work

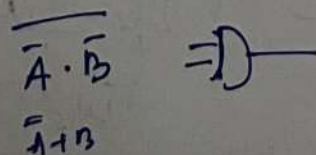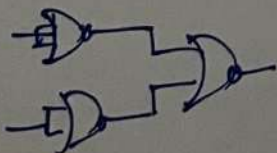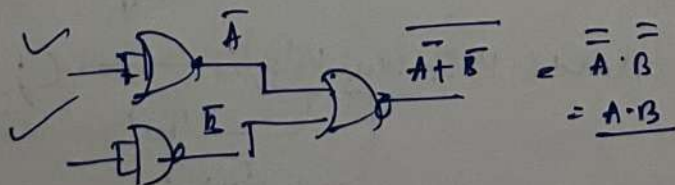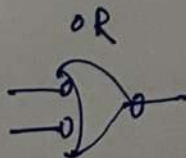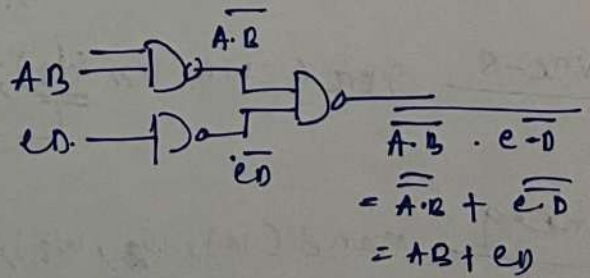

Design a combinational circuit

(5) (i)

$A + \bar{B} + cD = 0$ gives a set value

so $A \text{ must} = 0$
 $B \text{ must} = 1$



$C \cdot D = 0$, means $C=0, D=0$
 or $C \text{ or } D = 0$

A	B	C	D
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

$F = \bar{A} \bar{B} \bar{C} \bar{D} + \bar{A} \bar{B} \bar{C} D + \bar{A} \bar{B} C \bar{D}$
 $= \bar{A} \bar{B} \bar{C} + \bar{A} \bar{B} \bar{D}$
 $= \bar{A} \bar{B} (\bar{C} + \bar{D})$

only true

A B C D

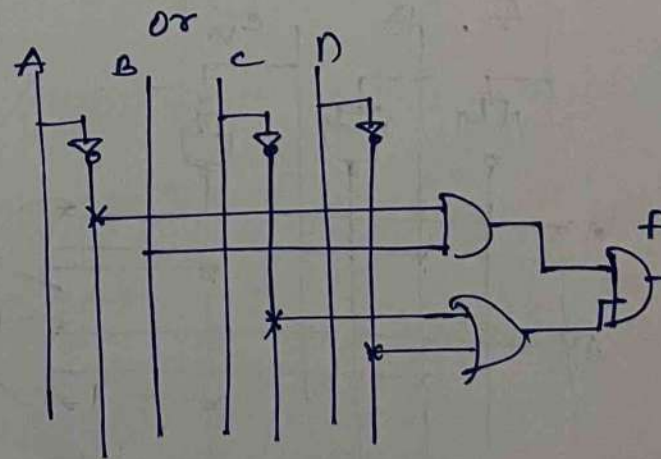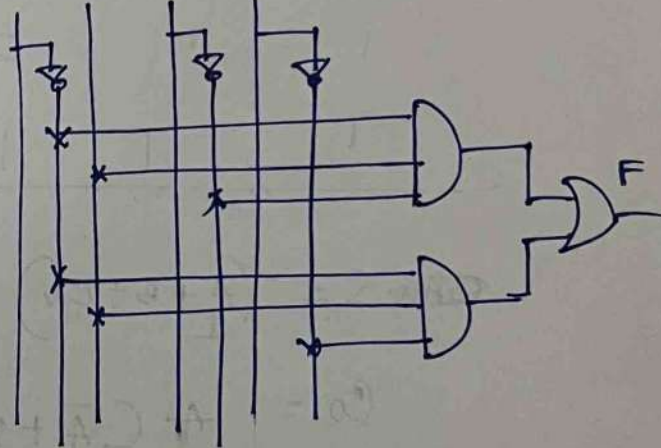

(b) $Z_m(4,5,6)$ using 4×1 mux for four variables

0	0	0	0
0	1	0	1
0	0	0	0
0	0	0	0

