



SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - I
WINTER SEMESTER 2024-2025

SLOT: D1

Programme Name & Branch : B. Tech - ECE
Course Code and Course Name : BECE305L – Antenna and Microwave Engineering
Faculty Name(s) : Dr. Shambavi K, Dr. Poonkuzhali R, Dr. Kannadassan D
Class Number(s) : VL2024250500657, 58, 59
Exam Duration : 90 minutes

Maximum Marks: 50

Answer All Questions

- BL – Blooms Taxonomy Level (1 – Remember, 2 – Understand, 3 – Apply, 4 – Analyse, 5 – Evaluate, 6 – Create)
- CO4: Design and analyze the passive components at microwave frequencies.
 - CO5: Design and analyze the various passive circuits at microwave frequencies.

Question		M	CO	BL																																																																																																																																				
The measured S matrix of a microwave network is given below. (i) Verify the matched, lossless, and reciprocal properties. (ii) Calculate the insertion loss between port-1 and 3, when all other ports are properly matched? (iii) What is the input reflection coefficient seen at port-1 when port-3 is short circuited and all other ports are matched.		10	4	3																																																																																																																																				
$[S] = \begin{bmatrix} 0.12\angle 90^\circ & 0.7\angle 45^\circ & 0.3\angle 45^\circ & 0 \\ 0.7\angle 45^\circ & 0 & 0 & 0.4\angle -45^\circ \\ 0.3\angle 45^\circ & 0 & 0 & 0.3\angle -45^\circ \\ 0 & 0.4\angle -45^\circ & 0.3\angle -45^\circ & 0 \end{bmatrix}$																																																																																																																																								
2.	(a) A circulator has following S-matrix at its operating frequency 5 GHz, calculate the insertion loss and isolation. $[S] = \begin{bmatrix} 0.001 & 0.95 & 0.097 \\ 0.097 & 0.001 & 0.95 \\ 0.95 & 0.097 & 0.001 \end{bmatrix}$ (b) A 30 W signal is fed into the collinear port 1 of a lossless H-plane tee junction. Calculate the power delivered through each port when other ports are terminated in matched load.	5	4	3																																																																																																																																				
3.	(a) A lossless T junction power divider has a source impedance of 50 Ω. Find the output characteristic impedances so that the input power is divided in 3:2 (P3:P2) ratio at 3 GHz. (b) Design a branch-line coupler to achieve 5 dB coupling for a system impedance of 45 Ohm and operating frequency of 6 GHz. Draw the typical layout of the coupler.	5	5	3																																																																																																																																				
4.	Design a 4 th order maximally flat low pass filter with open-circuited shunt stubs for cut-off frequency 3 GHz. The filter is connected between a load of 75 Ω and a generator with its internal impedance of 75 Ω. Draw the typical layout of the final filter circuit. [g1=1.6703; g2=1.1920; g3=2.3661; g4=0.8419]	10	5	3																																																																																																																																				
5.	Design a 50 Ω Chebyshev low pass filter with a cutoff frequency of 2 GHz, Insertion loss of at least 27 dB at 2.4 GHz and pass band ripple of 0.5 dB. Realize the filter circuit using stubs only. High and low impedances are 110 Ω and 20 Ω. Draw the typical layout of the final filter circuit.	10	5	3																																																																																																																																				
<table><tr><th>N</th><th>g1</th><th>g2</th><th>g3</th><th>g4</th><th>g5</th><th>g6</th><th>g7</th><th>g8</th><th>g9</th><th>g10</th><th>g11</th></tr><tr><td>1</td><td>0.6986</td><td>1.0000</td><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td></td></tr><tr><td>2</td><td>1.4029</td><td>0.7071</td><td>1.9841</td><td></td><td></td><td></td><td></td><td></td><td></td><td></td><td></td></tr><tr><td>3</td><td>1.5963</td><td>1.0967</td><td>1.5963</td><td>1.0000</td><td></td><td></td><td></td><td></td><td></td><td></td><td></td></tr><tr><td>4</td><td>1.6703</td><td>1.1926</td><td>2.3661</td><td>0.8419</td><td>1.9841</td><td></td><td></td><td></td><td></td><td></td><td></td></tr><tr><td>5</td><td>1.7058</td><td>1.2296</td><td>2.5408</td><td>1.2296</td><td>1.7058</td><td>1.0000</td><td></td><td></td><td></td><td></td><td></td></tr><tr><td>6</td><td>1.7254</td><td>1.2479</td><td>2.6064</td><td>1.3137</td><td>2.4758</td><td>0.8696</td><td>1.9841</td><td></td><td></td><td></td><td></td></tr><tr><td>7</td><td>1.7372</td><td>1.2583</td><td>2.6381</td><td>1.3444</td><td>2.6381</td><td>1.2583</td><td>1.7372</td><td>1.0000</td><td></td><td></td><td></td></tr><tr><td>8</td><td>1.7451</td><td>1.2647</td><td>2.6564</td><td>1.3590</td><td>2.6964</td><td>1.3389</td><td>2.5093</td><td>0.8796</td><td>1.9841</td><td></td><td></td></tr><tr><td>9</td><td>1.7504</td><td>1.2690</td><td>2.6678</td><td>1.3673</td><td>2.7239</td><td>1.3673</td><td>2.6678</td><td>1.2690</td><td>1.7504</td><td>1.0000</td><td></td></tr><tr><td>10</td><td>1.7543</td><td>1.2721</td><td>2.6754</td><td>1.3725</td><td>2.7392</td><td>1.3806</td><td>2.7231</td><td>1.3485</td><td>2.5239</td><td>0.8842</td><td>1.9841</td></tr></table>		N	g1	g2	g3	g4	g5	g6	g7	g8	g9	g10	g11	1	0.6986	1.0000										2	1.4029	0.7071	1.9841									3	1.5963	1.0967	1.5963	1.0000								4	1.6703	1.1926	2.3661	0.8419	1.9841							5	1.7058	1.2296	2.5408	1.2296	1.7058	1.0000						6	1.7254	1.2479	2.6064	1.3137	2.4758	0.8696	1.9841					7	1.7372	1.2583	2.6381	1.3444	2.6381	1.2583	1.7372	1.0000				8	1.7451	1.2647	2.6564	1.3590	2.6964	1.3389	2.5093	0.8796	1.9841			9	1.7504	1.2690	2.6678	1.3673	2.7239	1.3673	2.6678	1.2690	1.7504	1.0000		10	1.7543	1.2721	2.6754	1.3725	2.7392	1.3806	2.7231	1.3485	2.5239	0.8842	1.9841			
N	g1	g2	g3	g4	g5	g6	g7	g8	g9	g10	g11																																																																																																																													
1	0.6986	1.0000																																																																																																																																						
2	1.4029	0.7071	1.9841																																																																																																																																					
3	1.5963	1.0967	1.5963	1.0000																																																																																																																																				
4	1.6703	1.1926	2.3661	0.8419	1.9841																																																																																																																																			
5	1.7058	1.2296	2.5408	1.2296	1.7058	1.0000																																																																																																																																		
6	1.7254	1.2479	2.6064	1.3137	2.4758	0.8696	1.9841																																																																																																																																	
7	1.7372	1.2583	2.6381	1.3444	2.6381	1.2583	1.7372	1.0000																																																																																																																																
8	1.7451	1.2647	2.6564	1.3590	2.6964	1.3389	2.5093	0.8796	1.9841																																																																																																																															
9	1.7504	1.2690	2.6678	1.3673	2.7239	1.3673	2.6678	1.2690	1.7504	1.0000																																																																																																																														
10	1.7543	1.2721	2.6754	1.3725	2.7392	1.3806	2.7231	1.3485	2.5239	0.8842	1.9841																																																																																																																													