



SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - I
WINTER SEMESTER 2024-2025

SLOT: C1 +TC1+TCC1

Programme Name & Branch : B. Tech / ECE / BML / BVD
Course Code and Course Name : BECE203L – Circuit Theory
Faculty Name(s) : Dr. Sathya P, Dr. Dr.Velmurugan V, Dr.Venugopal P,
Dr.Vaegae Naveen Kumar, Dr.Kumaravel S, Dr. Avinash
Chandra, Dr.Abdul Majeed K
Class Number(s) : VL2024250500734, 0736, 0728, 0724, 0737, 0739, 0727, 0731
Date of Examination : 29.01.25
Exam Duration : 90 minutes **Maximum Marks: 50**

General instruction(s):

- Answer All Questions
- M - Max mark; CO – Course Outcome; BL – Blooms Taxonomy Level (1 – Remember, 2 – Understand, 3 – Apply, 4 – Analyse, 5 – Evaluate, 6 – Create)
- Course Outcomes:

CO1: Apply the knowledge of various circuit analysis techniques such as mesh analysis, nodal analysis, and network theorems to investigate the given network.

CO2: Analyse the resonance and transient response of the first order, second order circuits.




CO3: Able to solve the networks using graphical approach.

Q. No	Question	M	CO	BL
1.	Compute V_o in Fig. (a) using mesh analysis. Fig. (a)	10	1	3
2.	Construct both the Thevenin's and Norton's equivalent circuit at the terminals a-b in Fig. (b). Fig. (b)	10	1	3



SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - I
WINTER SEMESTER 2024-2025

SLOT: C1 +TC1+TCC1

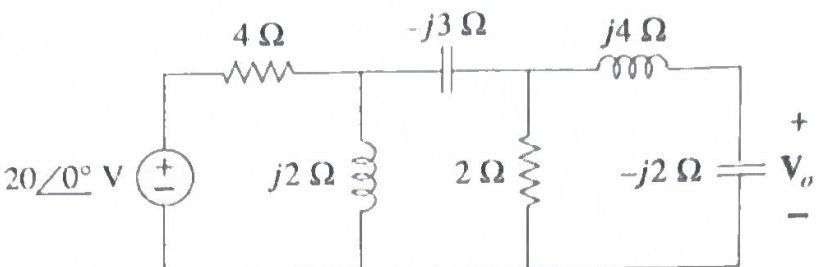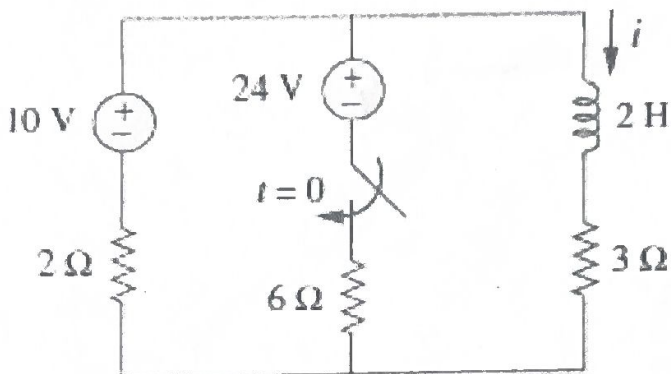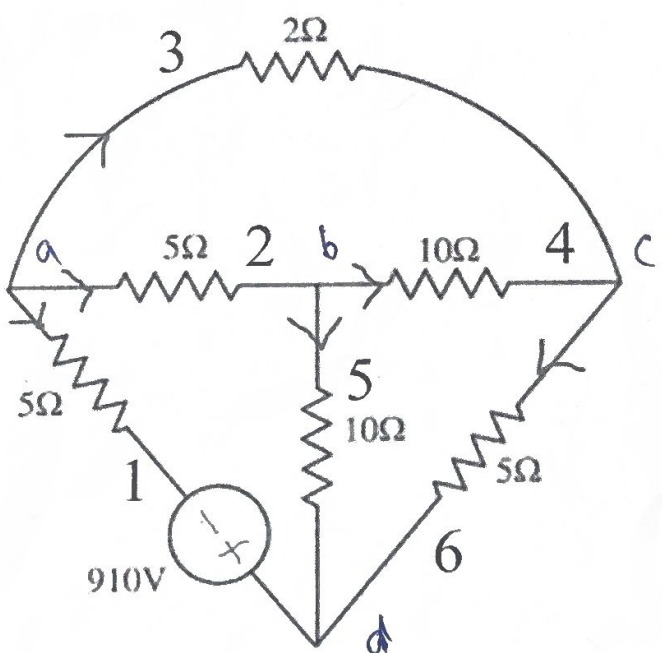3.	Apply the concept of source transformation to find V_o in Fig. (c).  Fig. (c)	10	1	3
4.	Calculate the inductor current $i(t)$ for $t > 0$ of the circuit shown in Fig. (d)  Fig. (d)	10	2	3
5.	Construct a network graph for given the circuit diagram as shown Fig. (e) . Find the incidence matrix and for a tree consisting of (1, 5, 6) (i) draw tie set matrix (ii) draw cut-set matrix.  Fig. (e)	10	3	3