



SCHOOL OF ELECTRICAL ENGINEERING (SELECT)
CONTINUOUS ASSESSMENT TEST - II
FALL SEMESTER 2024-2025

SLOT: C2+TC2

Programme Name & Branch : B.Tech (EEE, EIE & BEL)
Course Code and Course Name : BEEE206L and Digital Electronics
Faculty Name(s) : Vijayakumar D
Class Number(s) : 0102931
Date of Examination : 15th October 2024
Exam Duration : 90 minutes

Maximum Marks: 50

General instruction(s):

- Answer All Questions

Q. No	Question	M																																																										
1.	A device which is a combinational circuit that uses single input (1 port) that can be directed throughout several outputs (8 ports) design and write a Verilog code using behavioural level of modelling.	10																																																										
2.	Design a sequential circuit using T flip flops and state diagram from the given state transition table. <table><thead><tr><th colspan="2">Present State</th><th rowspan="2">Input</th><th colspan="2">Next State</th><th rowspan="2">Output</th></tr><tr><th>A</th><th>B</th><th>A</th><th>B</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>0</td><td>1</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td><td>1</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td><td>0</td><td>1</td></tr></tbody></table>	Present State		Input	Next State		Output	A	B	A	B	0	0	0	0	0	0	0	0	1	0	1	0	0	1	0	0	1	0	0	1	1	1	0	0	1	0	0	1	0	0	1	0	1	1	1	0	1	1	0	1	1	1	1	1	1	0	0	1	10
Present State		Input	Next State		Output																																																							
A	B		A	B																																																								
0	0	0	0	0	0																																																							
0	0	1	0	1	0																																																							
0	1	0	0	1	0																																																							
0	1	1	1	0	0																																																							
1	0	0	1	0	0																																																							
1	0	1	1	1	0																																																							
1	1	0	1	1	1																																																							
1	1	1	0	0	1																																																							
3.	Design a 2 bit binary counter using JK – flip flops, the state diagram shown below.																																																											






SCHOOL OF ELECTRICAL ENGINEERING (SELECT)
CONTINUOUS ASSESSMENT TEST - II
FALL SEMESTER 2024-2025

SLOT: C2+TC2

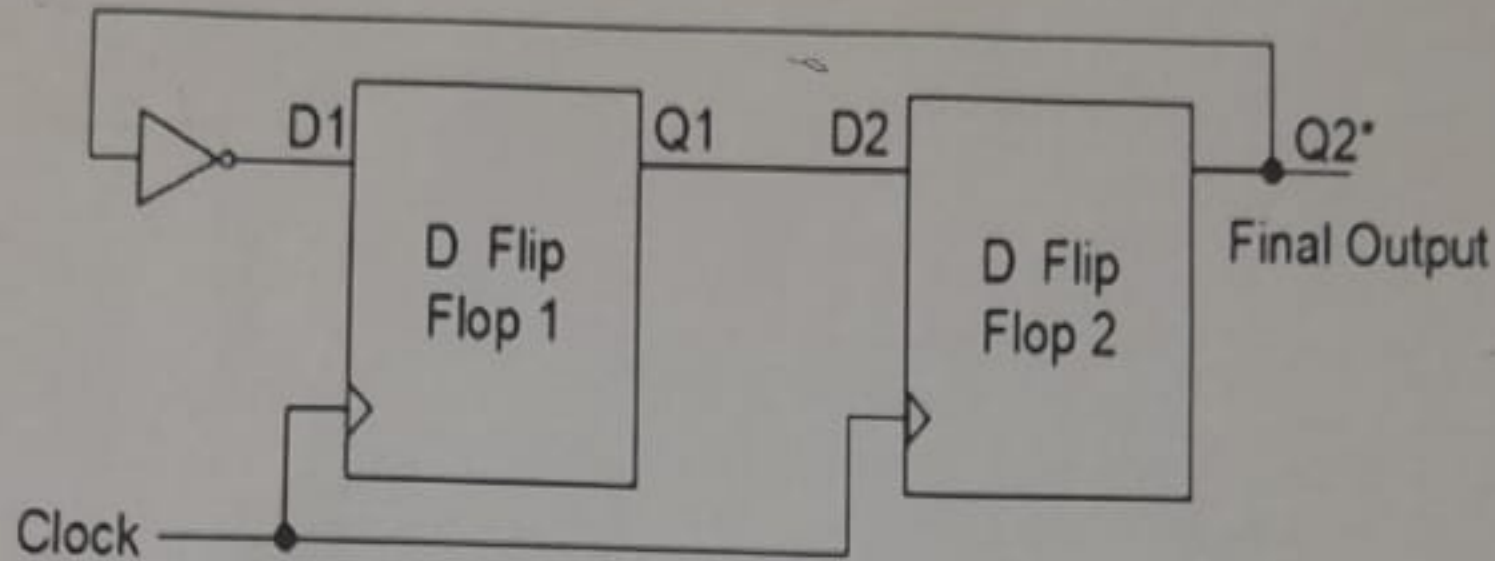
4.

a). Consider the following sequential circuit and the initial value of Q_2 is zero, which means the value of D_1 is one. Draw the waveform for eight clock cycles.



5

 b). Figure below shows the counter and draw the waveform for first 6 pulses of clock pulse input and also the name the counter.



5

5.

Design a sequence detector to detect sequence 1011.

10

