
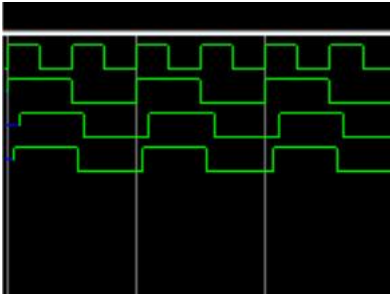


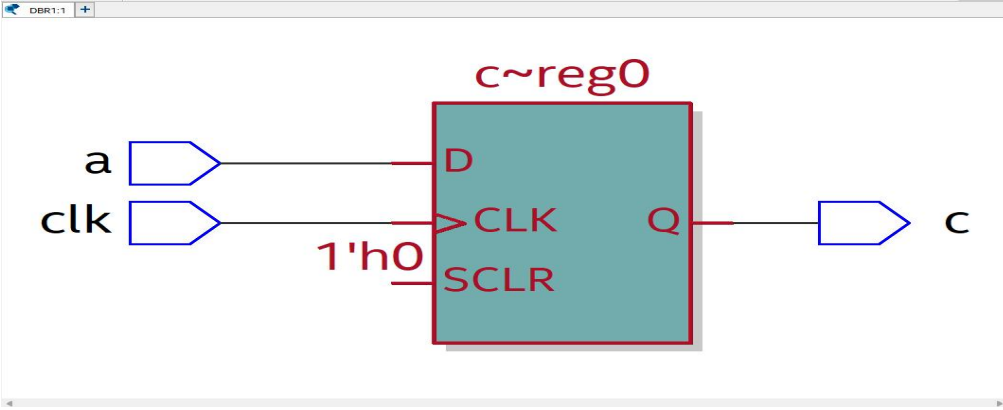



SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - II
FALL SEMESTER 2024-2025

Programme Name & Branch : BTECH ECE
Course Code and Course Name : BECE102L Digital Systems Design
Faculty Name(s) : Nithish Kumar V, Dhanabal R, Prayline Rajabai C, Tanmaya Kumar Das and Shilpi Ruchi Kerketta
Class Number(s) : 3678, 3677, 3670, 3680, 4052
Date of Examination : 16.10.24
Exam Duration : 90 minutes **Maximum Marks: 50**

General instruction(s):

Q. No	Question	M
1.	<p>Differentiate the circuit's functionality with Truth table, schematic Circuit diagram and output wave form for the following codes in detail.</p> <p>a. <code>module DBR1 (clk, a, c); input clk ; input a; output c; wire clk ; wire a; reg c; reg b; always @ (posedge clk) begin #10 b = a; #10 c = b; end Endmodule</code></p>   <p>b. <code>module DBR2 (clk ,a, c); input clk; input a; output c; wire clk; wire a; reg c; reg b; always @ (posedge clk) begin b <= a; c <= b; end</code></p>	10

SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - II
FALL SEMESTER 2024-2025

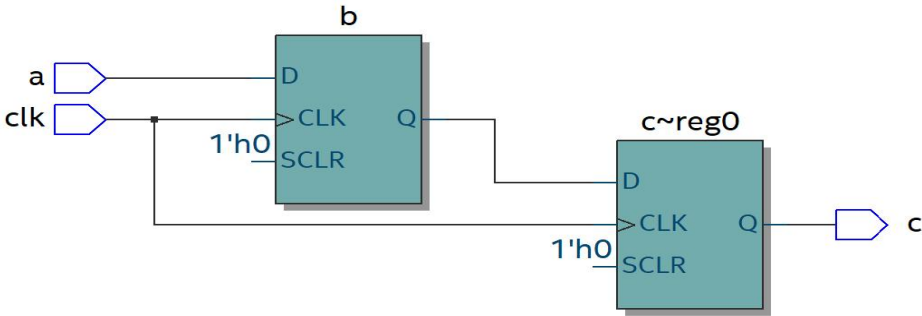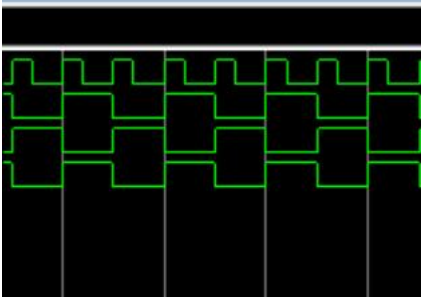	<p>endmodule</p>  <p>Answer key: Circuit : 4 marks Truth table: 4 marks Output wave form : 2 marks</p> 	
<p>2.</p>	<p>Design BCD adder using 4 bit ripple adders with internal circuits. Ans: Circuit for BCD Adder : 2 marks Internal circuit of 4 bit adder using full adder with or without half adder:2 marks Internal circuit of full adder and half adder : 1 marks</p> <p>Truth table : BCD Adder TT : 1 marks; 4 bit adder: 1 marks Full adder and Half adder:1 marks Flowchart /Algorithm : 1 marks Manual calculation and explanation or illustration of working principle with test cases: 1 marks</p>	<p>10</p>


Computer Arithmetic 19 BCD Arithmetic

BCD ADDER

If we can convert *Binary Sums* to *BCD Sum*, we can use a binary adder to add two BCD numbers

$SUM \leq 9$
BCD Sum = Binary Sum
BCD Carry = Binary Carry

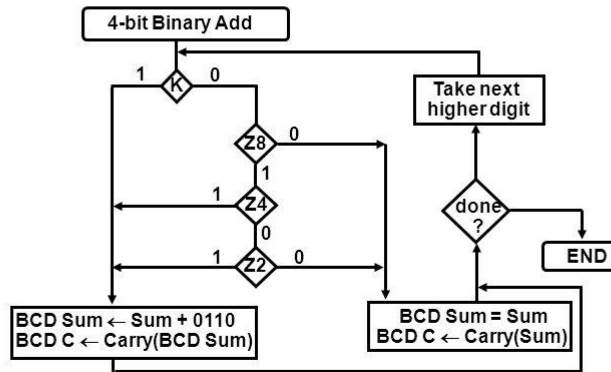
$19 \geq SUM > 9$
BCD Sum = Binary Sum + 0110
BCD Carry = Carry(Binary Sum + 0110)



Computer Organization

Prof. H. Yoon

Truth table

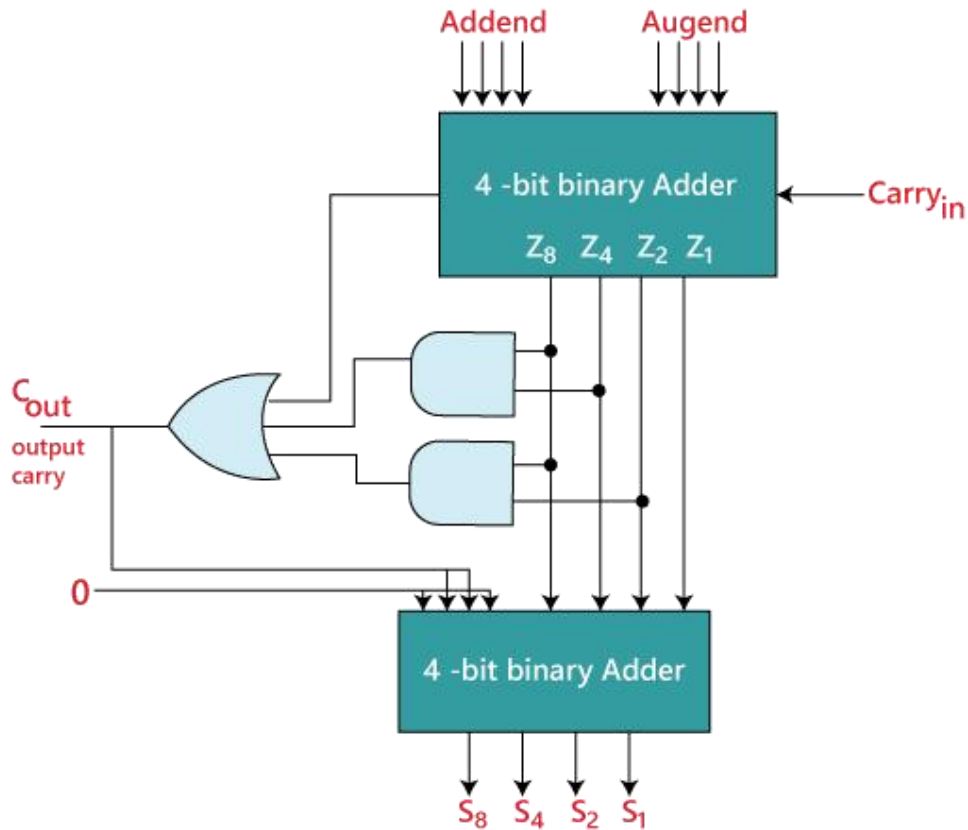

Block diagram of a BCD adder

SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - II
FALL SEMESTER 2024-2025

 


FIGURE 4.9
Four-bit adder

Truth table

Binary Sum					S A M E C O D E	BCD Sum					Decimal
K	Z ₈	Z ₄	Z ₂	Z ₁		C	S ₈	S ₄	S ₂	S ₁	
0	0	0	0	0		0	0	0	0	0	0
0	0	0	0	1		0	0	0	0	1	1
0	0	0	1	0		0	0	0	1	0	2
.
.
.
0	1	0	0	0		0	1	0	0	0	8
0	1	0	0	1		0	1	0	0	1	9
10 to 19 Binary and BCD codes are not the same											
0	1	0	1	0		1	0	0	0	0	10
0	1	0	1	1		1	0	0	0	1	11
0	1	1	0	0		1	0	0	1	0	12
0	1	1	0	1		1	0	0	1	1	13
0	1	1	1	0		1	0	1	0	0	14
0	1	1	1	1		1	0	1	0	1	15
1	0	0	0	0		1	0	1	1	0	16
1	0	0	0	1		1	0	1	1	1	17
1	0	0	1	0		1	1	0	0	0	18
1	0	0	1	1		1	1	0	0	1	19

SUM EQUALS 9 OR LESS WITH CARRY 0

Let us consider additions of 3 and 6 in BCD.

$$\begin{array}{r}
 6 \quad .0 \ 1 \ 1 \ 0 \quad \leftarrow \text{BCD for 6} \\
 + 3 \quad 0 \ 0 \ 1 \ 1 \quad \leftarrow \text{BCD for 3} \\
 \hline
 9 \quad 1 \ 0 \ 0 \ 1 \quad \leftarrow \text{BCD for 9}
 \end{array}$$

The addition is carried out as in normal binary addition and the sum is 1 0 0 1, which is BCD code for 9.

SUM GREATER THAN 9 WITH CARRY 0

Let us consider addition of 6 and 8 in BCD



SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - II
FALL SEMESTER 2024-2025

6	0 1 1 0	← BCD for 6
+ 8	1 0 0 0	← BCD for 8
14	1 1 1 0	← Invalid BCD number

The sum 1 1 1 0 is an invalid BCD number. This has occurred because the sum of the two digits exceeds 9. Whenever this occurs the sum has to be corrected by the addition of six (0110) in the invalid BCD number, as shown below

6	0 1 1 0	← BCD for 6
+ 8	1 0 0 0	← BCD for 8
14	1 1 1 0	← Invalid BCD number
	+ 0 1 1 0	← Add 6 for correction
0 0 0 1	0 1 0 0	
		← BCD for 14

After addition of 6 carry is produced into the second decimal position.

SUM EQUALS 9 OR LESS WITH CARRY 1

Let us consider addition of 8 and 9 in BCD

8	1 0 0 0	← BCD for 8
+ 9	1 0 0 1	← BCD for 9
17	0 0 0 1	0 0 0 1 ← Incorrect BCD result

In this, case, result (0001 0001) is valid BCD number, but it is incorrect. To get the correct BCD result correction factor of 6 has to be added to the least significant digit sum, as shown below

8	1 0 0 0	← BCD for 8
+ 9	1 0 0 1	← BCD for 9
17	0 0 0 1	0 0 0 1 ← Incorrect BCD result
	+ 0 0 0 0	0 1 1 0 ← Add 6 for correction
0 0 0 1	0 1 1 1	← BCD for 17



SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - II
FALL SEMESTER 2024-2025

Going through these three cases of BCD addition we can summarise the BCD addition procedure as follows :

- 1. ADD TWO BCD NUMBERS USING ORDINARY BINARY ADDITION.**
- 2. IF FOUR-BIT SUM IS EQUAL TO OR LESS THAN 9, NO CORRECTION IS NEEDED. THE SUM IS IN PROPER BCD FORM.**
- 3. IF THE FOUR-BIT SUM IS GREATER THAN 9 OR IF A CARRY IS GENERATED FROM THE FOUR-BIT SUM, THE SUM IS INVALID.**
- 4. TO CORRECT THE INVALID SUM, ADD 0110_2 TO THE FOUR-BIT SUM. IF A CARRY RESULTS FROM THIS ADDITION, ADD IT TO THE NEXT HIGHER-ORDER BCD DIGIT.**

Thus to implement BCD Adder Circuit we require :

- **4-BIT BINARY ADDER FOR INITIAL ADDITION**
- **LOGIC CIRCUIT TO DETECT SUM GREATER THAN 9 AND**
- **ONE MORE 4-BIT ADDER TO ADD 0110_2 IN THE SUM IF SUM IS GREATER THAN 9 OR CARRY IS 1.**

The logic circuit to detect sum greater than 9 can be determined by simplifying the boolean expression of given BCD Adder Truth Table.



SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - II
FALL SEMESTER 2024-2025

Inputs				Output
S ₃	S ₂	S ₁	S ₀	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Table 3.10

 


Fig. 3.31

$$Y = S_3S_2 + S_3S_1$$

With this design information we can draw the BCD Adder Block Diagram, as shown in the Fig. 3.32.


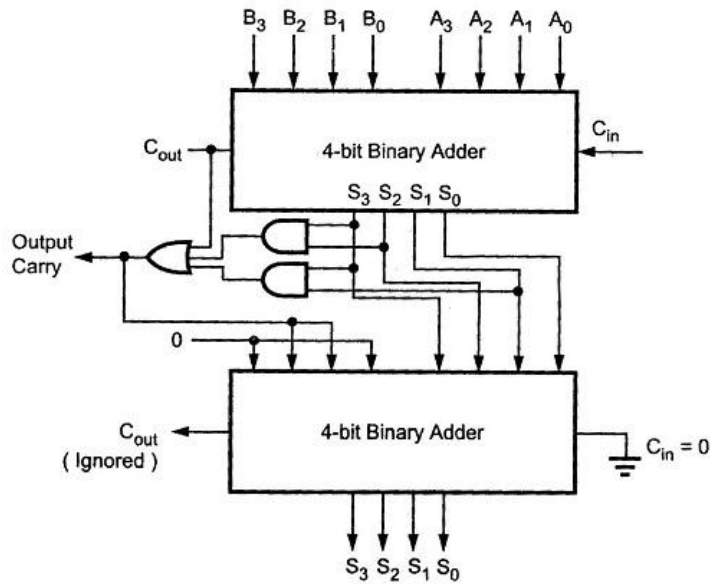
 
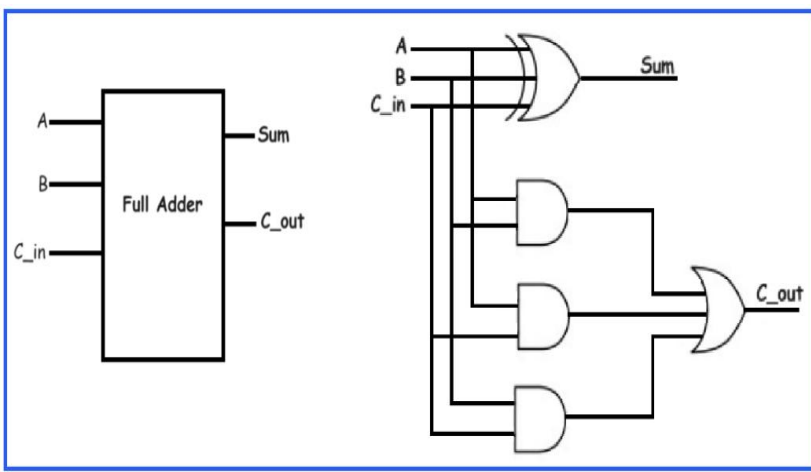
 


Fig. 3.32 Block diagram of BCD adder

As shown in the Fig. 3.32 , the two BCD numbers, together with input carry, are first added in the top 4-bit binary adder to produce a binary sum. When the output carry is equal to zero (i.e. when $\text{sum} \leq 9$ and $C_{\text{OUT}} = 0$) nothing (zero) is added to the binary sum. When it is equal to one (i.e. when $\text{sum} > 9$ or $C_{\text{OUT}} = 1$), **BINARY** 0110 is added to the binary sum through the bottom 4-bit binary adder. The output carry generated from the bottom binary adder can be ignored, since it supplies information already available at the output-carry terminal.

4 Bit adder internal circuit diagram

 SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - II
FALL SEMESTER 2024-2025



A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 


Fig 3.5 Logic gate half adder

3. Design a 4-Bit ALU and write a verilog code for the given function table.

S2	S1	S0	Function
0	0	0	A * B
0	0	1	A / B
0	1	0	A + B
0	1	1	A - B
1	0	0	A ** B
1	0	1	A + 1
1	1	0	A - 1
1	1	1	A >> 1

Verilog Code in BL/DFL/SL : 5 marks

Explanation /illustration of working : 2.5 marks

Design /circuit diagram/Block diagram: 2.5 marks

Sample Verilog code:

```

module ALU_4bit (
  input [3:0] A, B, // 4-bit inputs
  input [2:0] S, // 3-bit control signal
  output reg [3:0] Y // 4-bit output
);

always @(*) begin
  case (S)
    3'b000: Y = A * B; // A * B
    3'b001: Y = A / B; // A / B
    3'b010: Y = A + B; // A + B
    3'b011: Y = A - B; // A - B
    3'b100: Y = A ** B; // A ** B (Exponentiation)
    3'b101: Y = A + 1; // A + 1
    3'b110: Y = A - 1; // A - 1
  endcase
end

```

10



SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - II
FALL SEMESTER 2024-2025

```
3'b111: Y = A >> 1; // A >> 1 (Logical right shift)
default: Y = 4'b0000; // Default case
endcase
end

endmodule

Explanation
Inputs and Outputs:
A and B are the 4-bit input operands.
S is the 3-bit control signal that selects the operation.
Y is the 4-bit output result.
Operations:
3'b000: Multiplication (A * B)
3'b001: Division (A / B)
3'b010: Addition (A + B)
3'b011: Subtraction (A - B)
3'b100: Exponentiation (A ** B)
3'b101: Increment (A + 1)
3'b110: Decrement (A - 1)
3'b111: Logical right shift (A >> 1)
This code defines a simple 4-bit ALU that performs the specified
operations based on the control signals.

Or
module ALU (
    input [3:0] A, // 4-bit input A
    input [3:0] B, // 4-bit input B
    input [2:0] S, // 3-bit select input for function
    output reg [3:0] Y, // 4-bit output
    output reg Overflow // Overflow flag
);

always @(*) begin
    case (S)
        3'b000: begin // A * B
            {Overflow, Y} = A * B;
        end

        3'b001: begin // A / B
            if (B != 0) begin
                Y = A / B;
                Overflow = 0; // No overflow for division
            end else begin
                Y = 4'b0000; // Division by zero case
                Overflow = 1; // Set overflow flag
            end
        end
    endcase
end
```



SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - II
FALL SEMESTER 2024-2025

	<pre> 3'b010: begin // A + B {Overflow, Y} = A + B; end 3'b011: begin // A - B {Overflow, Y} = A - B; end 3'b100: begin // A ** B (A raised to the power of B) Y = (B == 4'b0000) ? 4'b0001 : 4'b0000; // Handle A^0 = 1, A^1 = A, others will be zero Overflow = 0; // No overflow end 3'b101: begin // A + 1 {Overflow, Y} = A + 1; end 3'b110: begin // A - 1 {Overflow, Y} = A - 1; end 3'b111: begin // A >> 1 (right shift) Y = A >> 1; Overflow = 0; // No overflow for shift end default: begin Y = 4'b0000; // Default case Overflow = 0; end endcase end endmodule </pre>																
4.	<p>a) Convert D Flip flop to AB Flip flop.</p> <table border="1" data-bbox="245 1621 632 1800"> <thead> <tr> <th>A</th> <th>B</th> <th>Q(t+1)</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>Set</td> </tr> <tr> <td>0</td> <td>1</td> <td>Q'</td> </tr> <tr> <td>1</td> <td>0</td> <td>Reset</td> </tr> <tr> <td>1</td> <td>1</td> <td>Q</td> </tr> </tbody> </table> <p>Ans key: <i>Explanation and Conversion procedure: 2 marks</i> <i>Circuit diagram: 2 marks</i> <i>Truth table/ k map simplification: 1 marks</i></p> <p>b) Write Structural level Verilog code for above design with Test Bench. <i>Verilog code with comments : 3 marks</i> <i>Test bench : 2 marks</i></p>	A	B	Q(t+1)	0	0	Set	0	1	Q'	1	0	Reset	1	1	Q	5
A	B	Q(t+1)															
0	0	Set															
0	1	Q'															
1	0	Reset															
1	1	Q															



SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - II
FALL SEMESTER 2024-2025

	<p>Expression for D</p> <p>The combined logic can be represented as:</p> $D = (A'B') + (A'B)Q' + (AB')Q + (AB)QD = (A'B') + (A'B)Q' + (AB')Q + (AB)QD$ <p>This simplifies to:</p> $D = A'B' + A'BQ' + ABQD = A'B' + A'BQ' + ABQD = A'B' + A'BQ' + ABQ$ <p>Implementation</p> <ol style="list-style-type: none"> 1. Use a 2-input AND gate to determine when $A'B'A'B'A'B'$ is true. 2. Use a 2-input AND gate to determine when $A'BA'BA'B$ is true and connect it to a NOT gate to find $Q'Q'Q'$. 3. Use another 2-input AND gate to determine when $ABABAB$ is true, allowing QQQ to pass through. 4. Combine the outputs of the three AND gates using an OR gate to generate DDD. <pre> module AB_FlipFlop (input wire A, input wire B, input wire clk, output reg Q); wire D; // D input for the D Flip-Flop wire Q_not; // Q' (complement of Q) not(Q_not, Q); // Invert Q to get Q' assign D = (A == 0 && B == 0) ? 1'b1 : // Set (A == 0 && B == 1) ? Q_not : // Complement (A == 1 && B == 0) ? 1'b0 : // Reset Q; // Hold // Combinational logic to determine D always @(posedge clk) begin Q <= D; end // D Flip-Flop endmodule </pre>	
5.	<p>Design a counter for the below sequence and write the behavioral verilog code with test Bench.</p> <p>If $PQ_n = NQ_n$ (0-0 or 1-1) then TQ_n is 0</p> <p>If $PQ_n \neq NQ_n$ (0-1 or 1-0) then TQ_n is 1</p>	10



SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - II
FALL SEMESTER 2024-2025

	Present state (PQn)				Next state (NQn)				TQn			
State	Q3	Q2	Q1	Q0	Q3	Q2	Q1	Q0	T3	T2	T1	T0
0	0	0	0	0	0	0	0	1	0	0	0	1
1	0	0	0	1	0	0	1	1	0	0	1	0
2	0	0	1	1	0	0	1	0	0	0	0	1
3	0	0	1	0	0	1	1	0	0	1	0	0
4	0	1	1	0	0	1	1	1	0	0	0	1
5	0	1	1	1	0	1	0	1	0	0	1	0
6	0	1	0	1	0	1	0	0	0	0	0	1
7	0	1	0	0	1	1	0	0	1	0	0	0
8	1	1	0	0	1	1	0	1	0	0	0	1
9	1	1	0	1	1	1	1	1	0	0	1	0
10	1	1	1	1	1	1	1	0	0	0	0	1
11	1	1	1	0	1	0	1	0	0	1	0	0
12	1	0	1	0	1	0	1	1	0	0	0	1
13	1	0	1	1	1	0	0	1	0	0	1	0
14	1	0	0	1	1	0	0	0	0	0	0	1
15	1	0	0	0	0	0	0	0	1	0	0	0

Design using T/JK/D flip-flop (using K map) and circuit diagram: 5 marks

Code with comments : 3 Marks Test bench :2 marks

Code:

```
module counter ( input clk, input reset, output reg [3:0] Q );
```

```
always @(posedge clk or posedge reset) begin
```

```
if (reset) Q <= 4'b0000;
```



VIT[®]

Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)

REG.NO.:

SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - II
FALL SEMESTER 2024-2025

SLOT: D1

```
else begin      case (Q)

    4'b0000: Q <= 4'b0001;
    4'b0001: Q <= 4'b0011;
    4'b0011: Q <= 4'b0010;
    4'b0010: Q <= 4'b0110;
    4'b0110: Q <= 4'b0111;
    4'b0111: Q <= 4'b0101;
    4'b0101: Q <= 4'b0100;
    4'b0100: Q <= 4'b1100;
    4'b1100: Q <= 4'b1101;
    4'b1101: Q <= 4'b1111;
    4'b1111: Q <= 4'b1110;
    4'b1110: Q <= 4'b1010;
    4'b1010: Q <= 4'b1011;
    4'b1011: Q <= 4'b1001;
    4'b1001: Q <= 4'b1000;
    4'b1000: Q <= 4'b0000;
    default: Q <= 4'b0000;

endcase

end

end

endmodule

Test Bench

module tb_counter;

    reg clk;  reg reset;  wire [3:0] Q;  // Instantiate the counter
```



VIT®

Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)

REG.NO.:

SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - II
FALL SEMESTER 2024-2025

SLOT: D1

```
counter uut ( .clk(clk), .reset(reset), .Q(Q) );  
  
initial begin // Clock generation  
    clk = 0;    forever #5 clk = ~clk; // 10ns period  
end // Test sequence  
  
initial begin // Initialize reset  
    reset = 1;    #10;    reset = 0;    // Let the counter run for a while  
    #160;    // Apply reset again  
    reset = 1;    #10;    reset = 0;    // Let the counter run for a while  
    #160;    $finish; // Finish simulation  
end  
  
initial begin    $monitor("Time = %0t, Q = %b", $time, Q); end  
  
endmodule // Monitor the output  
  
ref: https://www.youtube.com/watch?v=plhzOM8gcSA
```
