



VIT[®]

Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)

REG.NO.:

SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - II
FALL SEMESTER 2024-2025

SLOT:A1+TA1

Programme Name & Branch : B.Tech – in VLSI Design
Course Code and Course Name : BEVD204L, Electronic Circuits
Faculty Name(s) : Dr Abdul Majeed K K
Class Number(s) : VL2024250104065
Date of Examination :13/10/24
Exam Duration : 90 minutes


Maximum Marks: 50

General instruction(s):

- Answer All Questions
- M - Max mark; CO – Course Outcome; BL – Blooms Taxonomy Level (1 – Remember, 2 – Understand, 3 – Apply, 4 – Analyse, 5 – Evaluate, 6 – Create)
- Course Outcomes

CO4: Design and Analyse various Feedback Amplifiers

CO5: Build op-amp based circuits to generate various waveforms

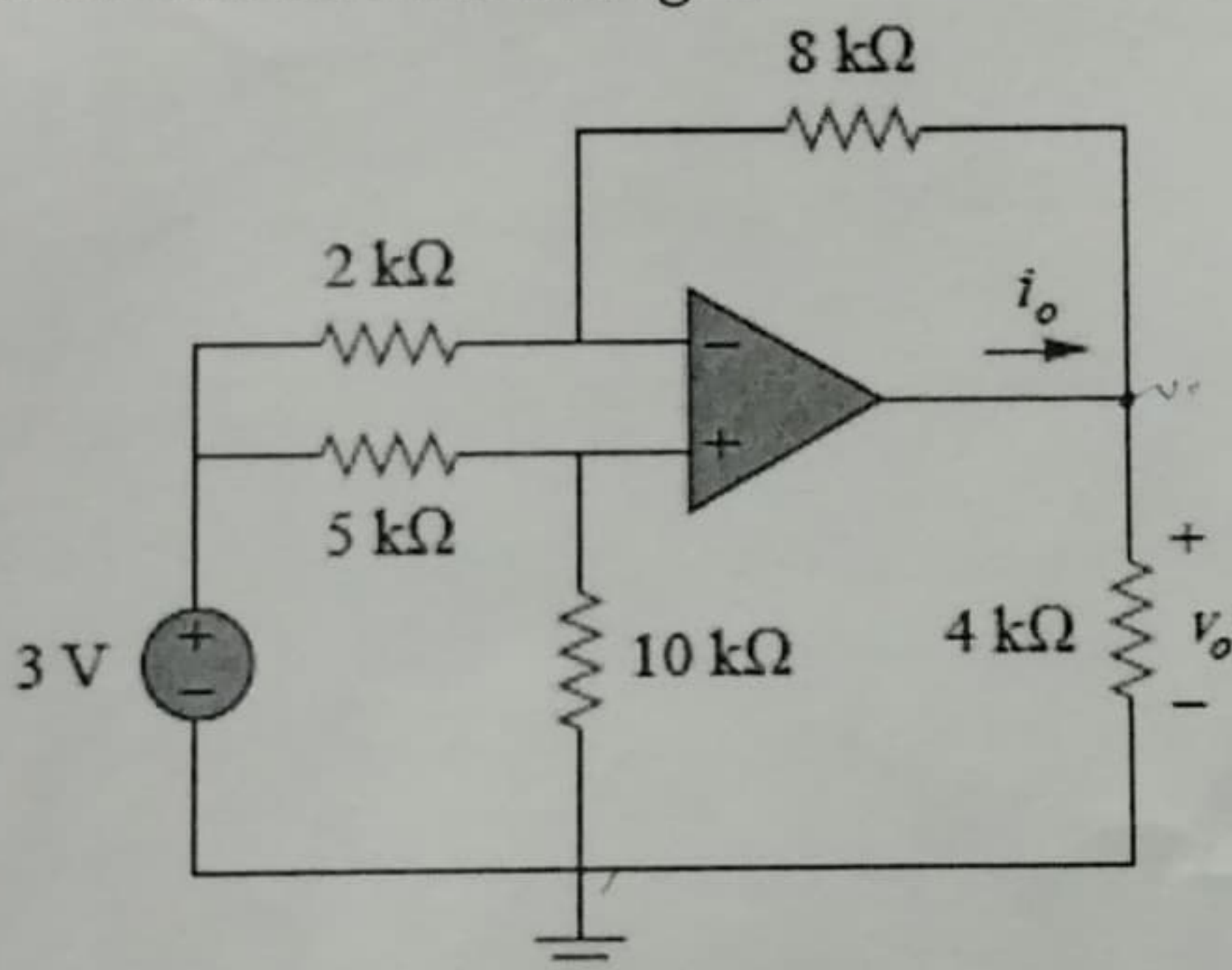Q. No	Question	M	CO	BL
1.	Design a circuit for $V_o = -4V_1 + 6V_2 - 10V_3$ using maximum two operational amplifiers.	10	4	3
2.	Find V_o and i_o in the circuit shown in Fig. 1  Fig. 1	10	4	4
3.	a) A noninverting amplifier incorporates an op-amp having an open-loop gain of 100 and bandwidth of 1 MHz. If the circuit is designed for a closed-loop gain of 16, determine the resulting bandwidth and time constant. (5 M)	5	4	4
	b) The internal circuitry of an op amp can be simplified to a 1-mA current source charging a 5-pF capacitor during large-signal operation. If an amplifier using this op amp produces a sinusoid with a peak amplitude of 0.5 V, determine the maximum frequency of operation that avoids slewing. (5 M)	5		
4.	Calculate the A_{vf} , R_{if} and R_{of} for the circuit shown in Fig. 2. Given values are $h_{ie} = 1K$ and $h_{fe} = 100$	10	5	5



SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - II
FALL SEMESTER 2024-2025

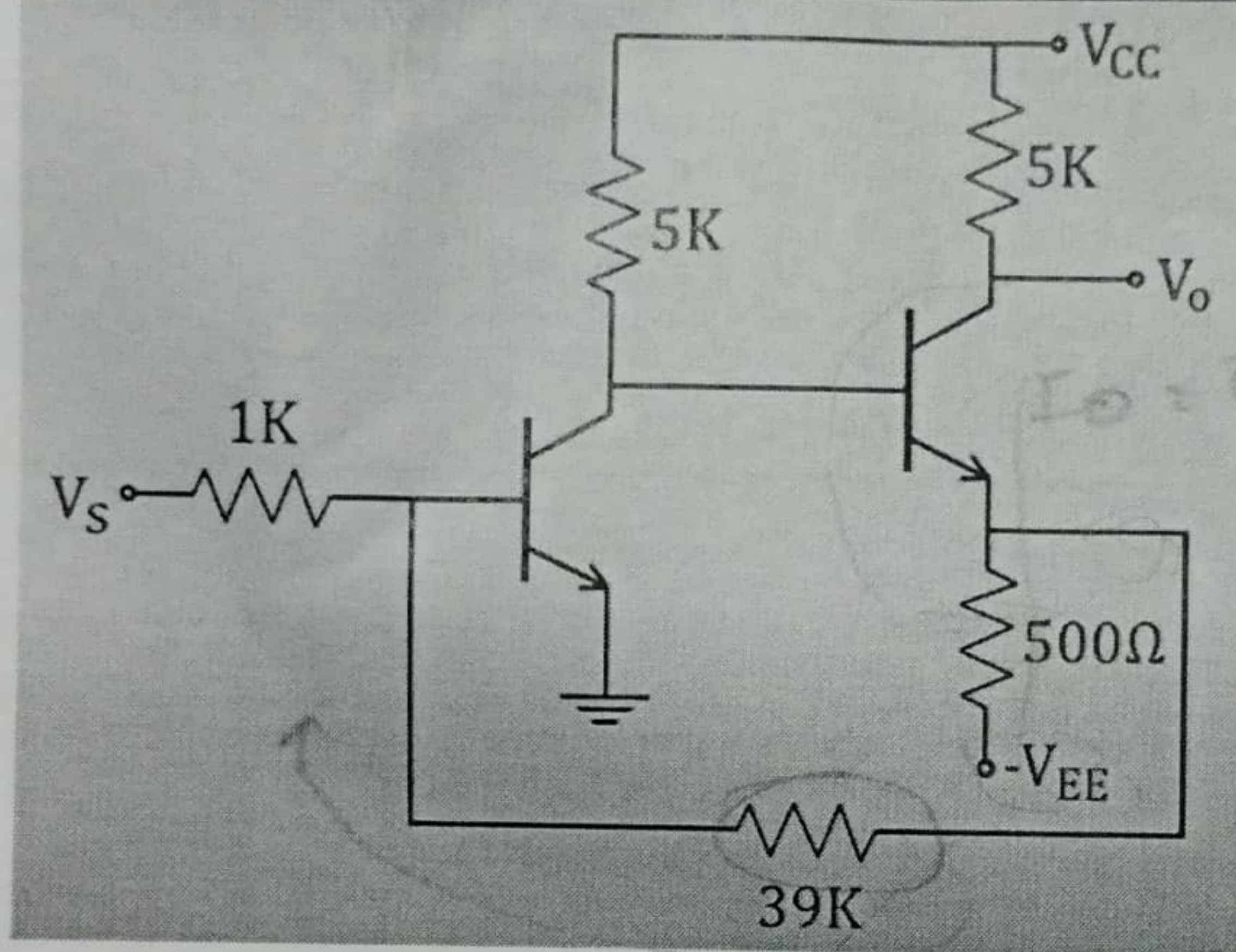


Fig. 2

5.	Design a voltage shunt feedback inverting amplifier, $R_1 = 470 \Omega$ and $R_f = 4.7 \text{ k}\Omega$. Assume that op-amp is a 741 having the following specifications. $A = 200000$, $R_i = 2 \text{ M}\Omega$, $R_o = 75 \Omega$, $f_o = 5 \text{ Hz}$, $V_{cc} = \pm 15 \text{ V}$. Calculate and compare the values of with and without feedback gain, bandwidth, input impedance.	10	5	5
----	--	----	---	---
