



VIT

Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)

REG.NO.:

SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - I
FALL SEMESTER 2025-2026

SLOT:D2+TD2

Programme Name & Branch :B.Tech, ECE

Course Code and Course Name : Analog Circuits-BECE 206L

Faculty Name(s) : Dr. M. Jasmin Pemeena Priyadarisini, Dr. Deepika Rani Sona,
Dr. P. Sathyanarayanan, Dr. Gautam Narayan, Dr. Veerapu
Goutham, Dr. Sandhana Mahalingam M

Class Number(s) : VL2025260100478, VL2025260103560, VL2025260100474,
VL2025260102659, VL2025260102656, VL202526010266


Date of Examination :20.08.2025

Exam Duration : 90 minutes

Maximum Marks: 50

General instruction(s):

- Answer All Questions
- M - Max mark; CO - Course Outcome; BL - Blooms Taxonomy Level (1 - Remember, 2 - Understand, 3 - Apply, 4 - Analyse, 5 - Evaluate, 6 - Create)
- Course Outcomes
 - Design the BJT and MOSFET amplifier circuits using suitable biasing techniques and analyze their frequency response characteristics.
 - Distinguish among different classes of MOSFET power amplifiers and employ them for various applications.

 Q. No	Question	M	CO	BL
1.	Determine I_c and V_{CE} for the network shown in the Fig.1. Assume $\beta = 100$, $V_{BE} = 0.7$ V, $V_{CC} = 12$ V, $R_1 = 20$ kΩ, $R_2 = 4.7$ kΩ, $R_C = 2$ kΩ and $R_E = 470$ Ω. Plot the load line and locate the Q point parameters for the circuit.  Fig.1	10	1	3
2.	(i). Calculate the midband gain A_M of a CS amplifier with a signal source having an internal resistance $R_{sig} = 105$ kΩ. The amplifier has $R_G = 2$ MΩ, $R_D = R_L = 10$ KΩ, $g_m = 2$ mA/V, $r_o = 100$ kΩ, $C_{gs} = 2$ pF and $C_{gd} = 1$ pF. (ii). For the same CS amplifier specified, find the values of A_M that result when the signal source resistance is reduced to 50kΩ.	10	1	3
3.	Consider the single-stage common-emitter amplifier shown in the Fig. 2, where $V_{CC} = 15$ V, $R_{sig} = 10$ kΩ, $r_x = 50$ Ω, $R_1 = 68$ kΩ, $R_2 = 27$ kΩ, $R_E = 2.2$ kΩ, $R_C = 4.7$ kΩ, $R_L = 10$ kΩ and $\beta = 200$. The collector current is 0.8 mA, $f_T = 800$ MHz, early	10	1	3



VIT

Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)

REG.NO.:

SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - I
FALL SEMESTER 2025-2026

SLOT:D2+TD2

voltage $V_A = 100V$ and $C_\mu = 0.8 \text{ pF}$. Construct small-signal high-frequency hybrid- π equivalent model of the CE amplifier and also compute the upper 3-dB cutoff frequency.

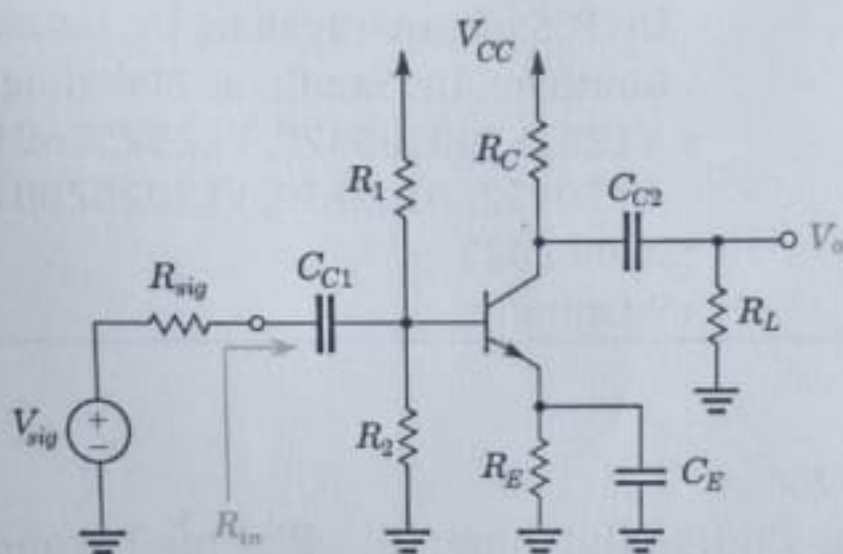


Fig.2

Explain how the Miller effect impacts the high frequency response of a single stage NMOS CS amplifier. For a given $C_{gd} = 1.2 \text{ pF}$, $C_{gs} = 3.5 \text{ pF}$, $R_G = 0.5 \text{ M}\Omega$, $R_D = 12 \text{ k}\Omega$, and $AM = -20$, Calculate f_H .

10

1

a) Consider the Class A output stage using common source circuit shown in Fig.3. Derive power conversion efficiency of the given class-A amplifier.

b) Consider the common source circuit shown below. The Q point is located at $V_{DSQ} = 6 \text{ V}$. (i) Find the quiescent current (I_{DQ}), (ii) Determine the maximum peak to peak amplitude of the sinusoidal output voltage if the $V_{DS \text{ max}} = 10 \text{ V}$, and (iii) Calculate the power conversion efficiency.

 


Fig.3

$$\begin{aligned} V_{DD} &= 12 \text{ V} \\ R_D &= 10 \text{ k}\Omega \\ V_{DSQ} &= -10 \text{ V} \end{aligned}$$

10

2