



**SCHOOL OF ELECTRONICS ENGINEERING**  
**CONTINUOUS ASSESSMENT TEST - II**  
**FALL SEMESTER 2025-2026**

SLOT:D1+TD1

Programme Name & Branch :B.Tech, ECE

Course Code and Course Name : Analog Circuits-BECE 206L

Faculty Name(s) : Dr. Deepika Rani Sona, Dr. P. Sathyanarayanan, Dr. Gautam Narayan, Dr. Veerapu Goutham, Dr. Pareshkumar Ramanbhai Sagar, Dr. Sandhana Mahalingam M

Class Number(s) : VL2025260100476, VL2025260100480, VL2025260102657  
VL2025260100482, VL2025260102667, VL2025260102660

Date of Examination : 8.10.2025

Exam Duration : 90 minutes

Maximum Marks: 50

**General instruction(s):**

- Answer All Questions
  - M - Max mark; CO - Course Outcome; BL - Blooms Taxonomy Level (1 - Remember, 2 - Understand, 3 - Apply, 4 - Analyse, 5 - Evaluate, 6 - Create)
  - Course Outcomes
3. To introduce MOSFET active biasing and design a MOSFET differential amplifier circuit and analyze its frequency response.
  4. To study the characteristics of Operational Amplifier and its applications
  5. To acquaint and demonstrate the concepts of waveform generators, filter configurations, Timer, data converters, and Voltage regulators.

 
 
| Q. No | Question                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                    | M           | CO | BL |
|-------|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-------------|----|----|
| 1.    | For the MOS differential pair with a common-mode voltage $V_{cm}$ is applied. Let $V_{DD} = V_{SS} = 12V$ , $V_t = 0.8V$ , $V_{OV} = 0.6V$ , $\mu_n C_{ox} = 4 mA/V^2$ , $W/L = 2$ , $R_D = 7K\Omega$ , and neglect channel-length modulation.<br>(a) Find $I$ and $V_{GS}$<br>(b) For $V_{cm} = -2V$ , find $V_S$ , $I_{D1}$ , $I_{D2}$ , $V_{D1}$ , and $V_{D2}$<br>(c) What is the highest permitted value of $V_{cm}$ for which the transistors remain in saturation?<br>(d) For $V_{cs} = 0.7V$ , what is the lowest value of $V_{cm}$ for which the transistors remain in saturation? | 10          | 3  | 3  |
| 2.    | (a) For the op-amp circuit shown in Fig.1, use the following values: $V_{S1} = 3V$ , $V_{S2} = 1V$ , $R_1 = 10k\Omega$ , $R_2 = 40k\Omega$ , $R_3 = 10k\Omega$ , $R_4 = 10k\Omega$ . Calculate the output voltage $V_O$ .<br>                                                                                                                                                                                                                                                                           | 4<br>+<br>6 | 4  | 3  |

Fig.1



**SCHOOL OF ELECTRONICS ENGINEERING**  
**CONTINUOUS ASSESSMENT TEST - II**  
**FALL SEMESTER 2025-2026**

SLOT:D1+TD1

|    |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                      |        |   |        |
|----|----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|--------|---|--------|
|    | (b) Design an ideal op-amp inverting differentiator with a differentiation time constant of $10^{-2}$ s and an input capacitance of $0.01 \mu\text{F}$ . What is the gain magnitude and phase of this circuit at $10 \text{ rad/s}$ , and at $10^3 \text{ rad/s}$ ?                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                  |        |   |        |
| 3. | <p>(a) For the non-inverting amplifier, <math>R_1 = 2 \text{ k}\Omega</math>, and <math>R_f = 15 \text{ k}\Omega</math>. Calculate the maximum output offset voltage due to <math>V_{ios}</math> and <math>I_B</math>. The op-amp is LM307 with <math>V_{ios} = 15 \text{ mV}</math> and <math>I_B = 380 \text{ nA}</math>, <math>I_{os} = 45 \text{ nA}</math>.</p> <p>(b) Determine the maximum possible change in output offset voltage in an inverting amplifier <math>R_1 = 1 \text{ k}\Omega</math>, <math>R_f = 100 \text{ k}\Omega</math> after 28 days if the op-amp is the <math>\mu\text{A}741</math> with the following specification <math>\frac{\Delta V_{io}}{\Delta t} = 35 \mu\text{V/week}</math> and <math>\frac{\Delta I_{io}}{\Delta t} = 0.5 \text{ nA/week}</math>. Assume that the circuit is initially nulled at that room temperature and the voltage across terminals <math>+V_{CC}</math> and <math>-V_{EE}</math> remains constant.</p> | 5<br>+ | 5 | 4<br>3 |
| 4. | <p>Refer to the circuit shown in Fig. 2. Using the given parameters, determine the waveform that would appear on Oscilloscope Channel A. Calculate the output signal time period and the hysteresis voltage.</p>  <p style="text-align: center;">Fig.2</p>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                       | 10     | 5 | 3      |
| 5. | Design an op-amp squarewave generator powered from a $\pm 12 \text{ V}$ supply to generate a rectangular wave with the following specifications: output frequency = $1.00 \text{ kHz}$ and duty cycle = $75\%$ .                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                     | 10     | 5 | 3      |