

SCHOOL OF ELECTRICAL ENGINEERING
CONTINUOUS ASSESSMENT TEST - II
WINTER SEMESTER 2025-2026

Programme Name & Branch : B.Tech (EEE & EIE)
Course Code and Course Name : BEEE208L - Analog Electronics
Faculty Name(s) : Dr.M.N. Venkataraman, Dr.R. Gnanavignesh
Class Number(s) : VL20252601012345, 2253
Date of Examination : 15/03/2026
Exam Duration : 90 minutes

General instruction(s): Maximum Marks: 50

- Answer All Questions.
 - Rough work should not be done on the question paper. It will be treated as malpractice.
 - M - Max mark; CO - Course Outcome; BL - Bloom's Taxonomy Level (1 - Remember, 2 - Understand, 3 - Apply, 4 - Analyse, 5 - Evaluate, 6 - Create)
- Course Outcomes Statements:
- CO. 3. Design the frequency of oscillation for different oscillators.
- CO. 5. Design ADCs, DACs and timer circuits for engineering applications.

Q.No	Question	M	CO	BL
1.	Draw the complete circuit of Hartley oscillator and obtain the frequency of oscillation.	10	3	3
2.	Design a 4-bit R-2R resistor type DAC whose feedback resistor value is <u>2.5kΩ</u> . Draw the complete circuit diagram with the exact components.	10	5	4
3.	Design a 4-bit flash ADC inclusive of the priority encoder with a clear diagram.	10	5	4
4.	Design a monostable multivibrator with $T_{ON}=1ms$ and using 555-Timer. Use $1\mu F$ capacitor. Draw the circuit and explain your design including the 555-Timer internal diagram.	10	5	3
5.	Design a adjustable regulator for voltage supply of 8V from voltage regulator using IC7805.	10	5	2