



Vellore – 632014, Tamil Nadu, India

SCHOOL OF ELECTRICAL ENGINEERING
FALL SEMESTER 2025-2026

CAT-I


SLOT: A2+TA2+TAA2

Programme Name & Branch:	B.Tech (EEE, BECS & EIE)	Course Code:	BEEE203L
Course Name:	Circuit Theory	Class Number(s):	
Faculty Members:	Dr. Vijayakumar D, Dr. Janaki M, Dr. Belwin Edward	Duration:	90 Mins
Date of the Examination:		Max. Marks:	50

General Instructions: Answer all the questions

Q. No	Questions	Marks	CO	BL
1.	<p>a). Figure below shows a graph of the network. Show all the trees of this graph.</p> <p> </p> <p>b). Draw the oriented graph from the complete incidence matrix given below.</p>	5+5		
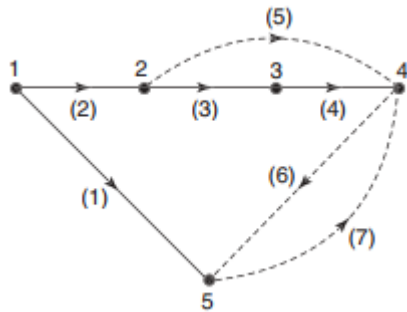
$$A = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & -1 & 1 & -1 \end{bmatrix}$$



2. For the network shown in figure below, draw the oriented graph and write the (a) incident matrix (b) tie-set matrix and (c) f-cutset matrix.

$$\text{Incidence matrix} = \begin{bmatrix} 1 & -1 & 0 & -1 & 0 & 0 \\ 0 & 0 & 0 & 1 & -1 & -1 \\ -1 & 0 & 1 & 0 & 0 & 1 \end{bmatrix}$$


$$B = \begin{bmatrix} 1 & 0 & 0 & 1 & 1 & 0 \\ 0 & 1 & 0 & -1 & 0 & -1 \\ 0 & 0 & 1 & 0 & -1 & 1 \\ -1 & 1 & 0 & 1 & 0 & 0 \end{bmatrix}$$

$$U = \begin{bmatrix} -1 & 0 & 1 & 0 & 1 & 0 \\ 0 & 1 & -1 & 0 & 0 & 1 \end{bmatrix}$$


10

3. Obtain the current I_o in the figure below using Norton's theorem.

Norton's Equivalent Network (Fig. 3.142)

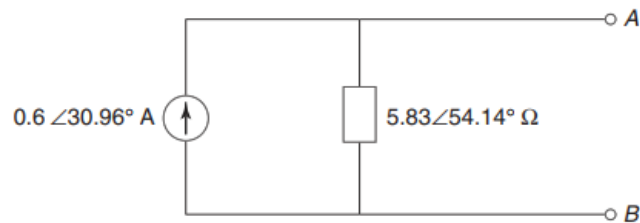

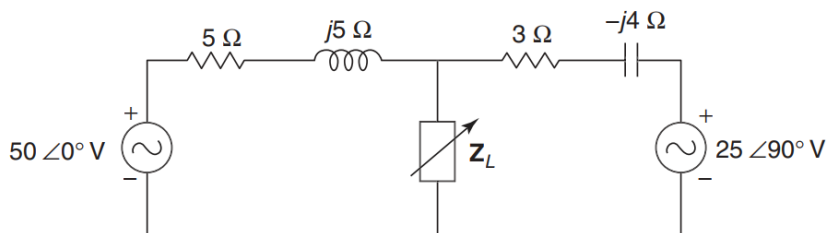4. In the network shown in figure below, what load Z_L will receive the maximum power using Millman's theorem. Also find maximum power.



Solution

Step I Calculation of V_m

$$V_m = \frac{V_1 Y_1 + V_2 Y_2}{Y_1 + Y_2} = \frac{(50 \angle 0^\circ) \left(\frac{1}{5 + j5} \right) + (25 \angle 90^\circ) \left(\frac{1}{3 - j4} \right)}{\frac{1}{5 + j5} + \frac{1}{3 - j4}} = 9.81 \angle -78.69^\circ \text{ V}$$

Step II Calculation of Z_m

$$Z_m = \frac{1}{Y_m} = \frac{1}{Y_1 + Y_2} = \frac{1}{\frac{1}{5 + j5} + \frac{1}{3 - j4}} = 4.39 \angle -15.26^\circ \Omega = (4.23 - j1.15) \Omega$$

Step III Calculation of Z_L

For maximum power transfer $Z_L = Z_{Th}^* = (4.23 + j1.15) \Omega$

Step IV Calculation of P_{max} (Fig. 3.196)


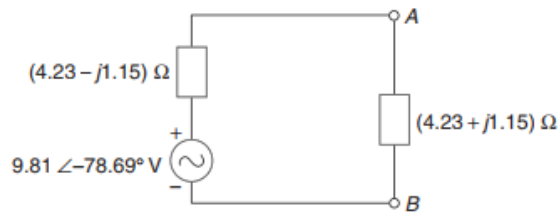


Fig. 3.196

$$P_{max} = \frac{|V_m|^2}{4R_L} = \frac{(9.81)^2}{4 \times 4.23} = 5.69 \text{ W}$$

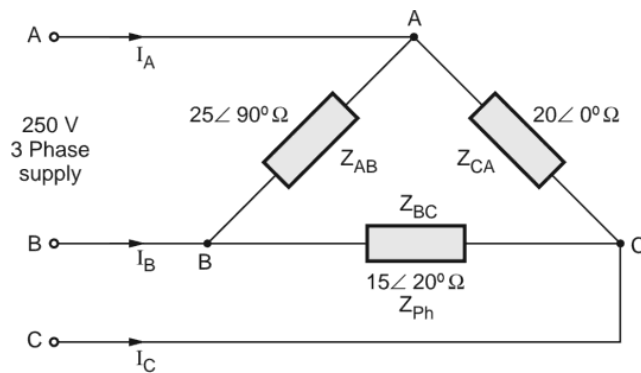5. A 3-phase supply with the line voltage of 250 V has an unbalanced delta connected load shown in figure below. Determine the line current, total active and reactive power if phase sequence is ABC.



$$\bar{V}_{BC} = 250\angle -120^\circ \text{ V,}$$

$$\bar{V}_{CA} = 250\angle 120^\circ \text{ V}$$

Fig. 1.8.13

$$Z_{AB} = 25\angle 90^\circ \Omega = 0 + j25 \Omega$$

$$Z_{BC} = 15\angle 20^\circ \Omega = 14.09 + j5.13 \Omega,$$

$$Z_{CA} = 20\angle 0^\circ \Omega = 20 + j0 \Omega$$

The phase current are given by,

$$\bar{I}_{AB} = \frac{\bar{V}_{AB}}{Z_{AB}} = \frac{250\angle 0^\circ}{25\angle 90^\circ} = 10\angle -90^\circ \text{ A} = (0 - j10) \text{ A}$$

$$\bar{I}_{BC} = \frac{\bar{V}_{BC}}{Z_{BC}} = \frac{250\angle -120^\circ}{15\angle 20^\circ} = 16.67\angle -140^\circ \text{ A} = (-12.76 - j10.71) \text{ A}$$

$$\bar{I}_{CA} = \frac{\bar{V}_{CA}}{Z_{CA}} = \frac{250\angle 120^\circ}{20\angle 0^\circ} = 12.5\angle 120^\circ \text{ A} = (-6.25 + j10.82) \text{ A}$$

The line currents are given by,

$$\begin{aligned} \bar{I}_A &= \bar{I}_{AB} + \bar{I}_{CA} = (0 - j10) + (-6.25 + j10.82) \\ &= -6.25 + j0.82 = 6.30\angle 172.52^\circ \text{ A} \end{aligned}$$

$$\begin{aligned} \bar{I}_B &= \bar{I}_{BC} + \bar{I}_{AB} = (-12.76 - j10.71) + (0 - j10) \\ &= -12.76 - j20.71 = 24.32\angle -121.63^\circ \text{ A} \end{aligned}$$

$$\begin{aligned} \bar{I}_C &= \bar{I}_{CA} + \bar{I}_{BC} = (-6.25 + j10.82) + (-12.76 - j10.71) = -19.01 + j0.11 \\ &= 19.01\angle 179.66^\circ \text{ A} \end{aligned}$$

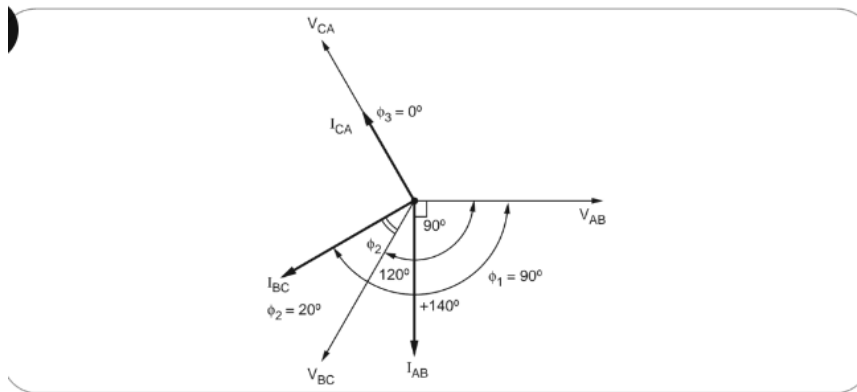


Fig. 1.8.13 (a)

$$\begin{aligned} \text{Total active power} &= V_{AB} \cdot I_{AB} \cos(V_{AB} \hat{I}_{AB}) + V_{BC} \cdot I_{BC} \cos(V_{BC} \hat{I}_{BC}) + V_{CA} \cdot I_{CA} \cos(V_{CA} \hat{I}_{CA}) \\ &= (250)(10) \cos(+90^\circ) + (250)(16.67) \cos(+20^\circ) + (250)(12.5) \cos(0^\circ) \\ &= 0 + 3916.16 + 3125 = 7041.16 \text{ W} = 7.04 \text{ kW} \end{aligned}$$

$$\begin{aligned} \text{Total reactive power} &= V_{AB} \cdot I_{AB} \sin(V_{AB} \hat{I}_{AB}) + V_{BC} \cdot I_{BC} \sin(V_{BC} \hat{I}_{BC}) + V_{CA} \cdot I_{CA} \sin(V_{CA} \hat{I}_{CA}) \\ &= (250)(10) \sin(+90^\circ) + (250)(16.67) \sin(20^\circ) + (250)(12.5) \sin(0^\circ) \\ &= 2500 + 1425.36 = 3925.36 \text{ VAR} = 3.925 \text{ kVAR} \end{aligned}$$