





Vellore – 632014, Tamil Nadu, India
SCHOOL OF ELECTRICAL ENGINEERING
FALL SEMESTER 2025-2026
CAT-II


SLOT: A2+TA2+TAA2

Programme Name & Branch:	B.Tech (EEE, BECS & EIE)	Course Code:	BEEE203L
Course Name:	Circuit Theory	Class Number(s):	VL2025260101020, 1021, 1019
Faculty Members:	Dr. Vijayakumar D, Dr. Janaki M, Dr. Belwin Edward	Duration:	90 Mins
Date of the Examination:	5th October 2025	Max. Marks:	50

General Instructions: Answer all the questions

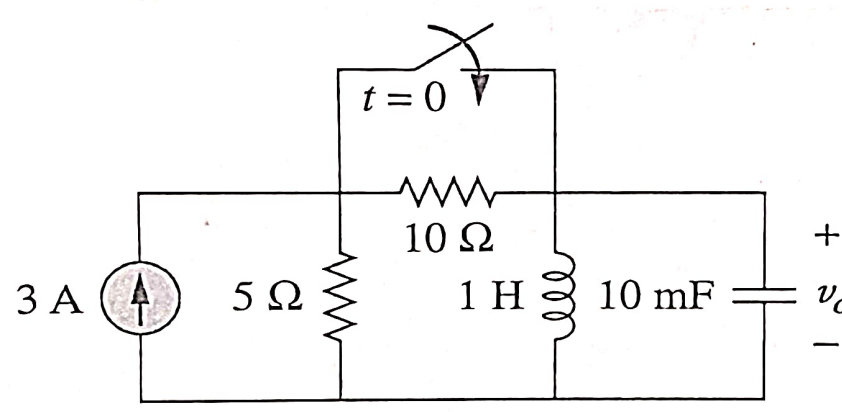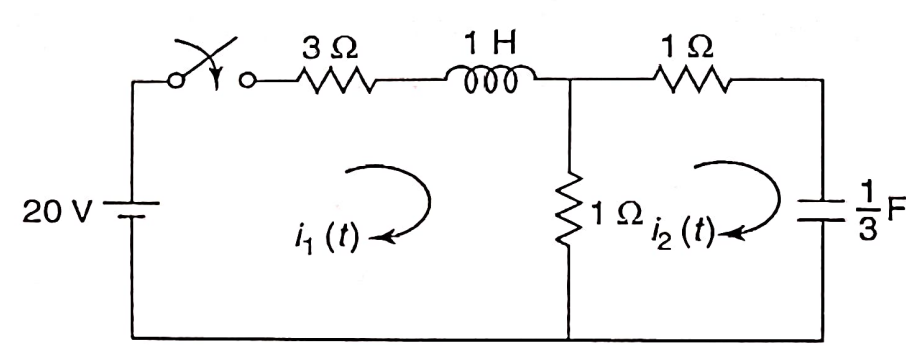Q. No	Questions	Marks	CO	BL
1.	<p>Find the output voltage $V_o(t)$ for $t > 0$ in the circuit shown below.</p> 	10	3	3
2.	<p>In the network shown in below, the switch is closed at $t = 0$. Find current $i_1(t)$ for $t > 0$. What is its value in steady state for $t > 0$?</p> 	10	3	3

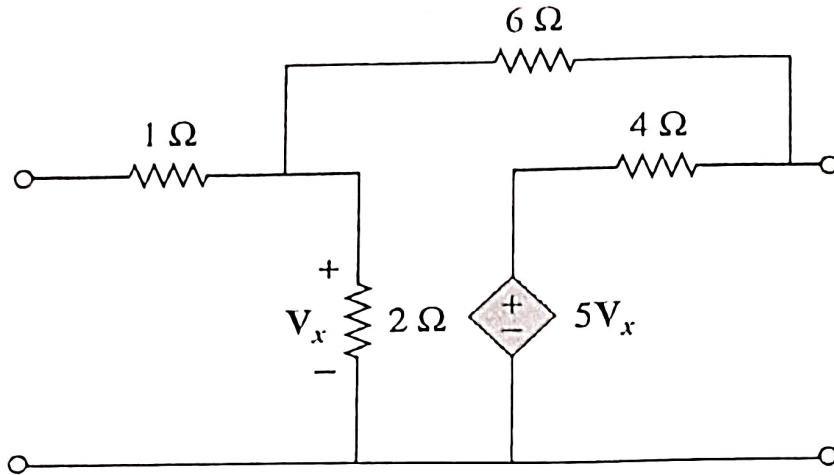3. Find the parameter equations that relate input voltage and output current to input current and output voltage for the given two port network.




10

5

3

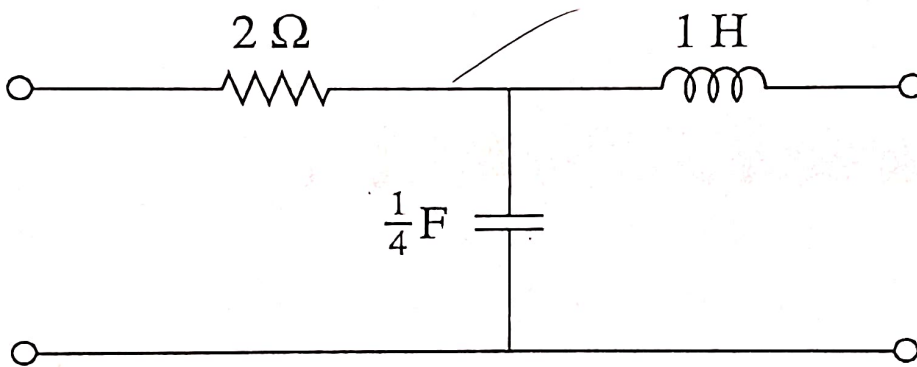4. For the network shown below, Calculate the parameters relate the currents at the ports of a two-port network to the voltages at the ports.




10

5

3

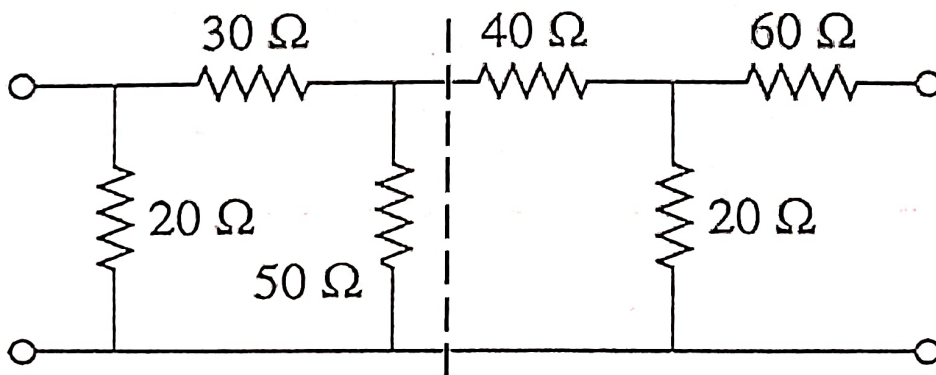5. Obtain the impedance parameters representation of the two port network with sub-networks and also considering the interconnections network as shown dotted lines below.



10

5

3