





SCHOOL OF COMPUTER SCIENCE AND ENGINEERING
CONTINUOUS ASSESSMENT TEST - II
WINTER SEMESTER 2025-2026

Room - 320
(10)

Programme Name & Branch : M.Tech (Integrated) & Computer Science and Engineering
Course Code and Course Name : IACSI202 - Digital Logic and Computer Design
Faculty Name(s) : Ashutosh Mahajan, Mangaiyarkarasi R, Sathyanarayanan P
Class Number(s) : VL2025260501083, VL2025260501087, VL2025260501085
Date of Examination : 17/03/2026
Exam Duration : 90 minutes
Maximum Marks: 50

General instruction(s): Answer All Questions

  Q. No	Question	Marks
1. ✓	Implement the following Boolean function $F(A, B, C, D) = \sum m(0, 1, 4, 6, 7, 9, 11, 15)$ using only one 4×1 Mux and external gates. Consider AB as select lines.	10
2.	Design a 2-bit magnitude comparator for the binary number $X = X_1X_0$ and $Y = Y_1Y_0$. The outputs A, B and C, Where A is 1 if $X > Y$, B is 1 if $X = Y$ and C is 1 if $X < Y$. Implement the comparator using two 3-to-8-line decoder.	10
3.	An XY Flipflop is designed with two inputs, X (set) and Y (reset), and a clock pulse. The Flipflop operates as follows: "On the rising edge of the clock, the output Q becomes 1 if $X=1$ and $Y=0$. If $X=0$ and $Y=1$, Q becomes 0. If both the inputs are 0, the state is held and if both inputs are 1, the output toggles. Identify the XY Flipflop and convert it to B flipflop. Refer the timing diagram of the B Flipflop shown below (Fig 1).	10
	 Fig1: Timing of B Flipflop	
4.	The given state diagram below has one input and one output. Obtain the state table and design the sequential circuit using a JK Flipflop? Consider the states a-00, b-11, c-10, and d-01, respectively.	10
		
5.	Create a synchronous counter that cycles through 0-3-5-4-1-0 using D Flipflop	10