



## SCHOOL OF COMPUTER SCIENCE ENGINEERING AND INFORMATION SYSTEMS

### CONTINUOUS ASSESSMENT TEST - I

FALL SEMESTER 2025-2026

SLOT: B1+TB1

**Programme Name & Branch** : B.Tech [IT]  
**Course Code and Course Name** : BAITE101 and Digital Logic Design and Computer Organization  
**Faculty Name(s)** : Dr.K.Santhi, Dr. M.Pradeepa, Dr. P.Suganya  
**Class Number(s)** : VL2025260105834, 7927, 5838  
**Date of Examination** : 18-08-2025  
**Exam Duration** : 90 minutes **Maximum Marks: 50**

#### General instruction(s):

- Answer All Questions
  - M - Max mark; CO - Course Outcome; BL - Blooms Taxonomy Level (1 - Remember, 2 - Understand, 3 - Apply, 4 - Analyse, 5 - Evaluate, 6 - Create)
  - Course Outcomes (Type the CO statements covered in this question paper. Use the CO number as per the syllabus copy)
- CO1: Outline the conversion of number systems and illustrate the simplification of Boolean functions and design combinational circuits
- CO2: Construct the design and analysis of various Sequential logic circuits using flip

| Q. No | Question                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                           | M  | CO | BL |
|-------|----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----|----|----|
| 1.    | a) Convert 132478.235 <sub>10</sub> to Octal and Hexadecimal number system.                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                        | 4  | 1  | 1  |
|       | b) Simplify the following Boolean function<br>$F(A, B, C, D) = \sum m(0, 1, 4, 5, 6, 7, 9, 11, 14, 15)$ and implement it using NAND gates                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                          | 6  |    |    |
| 2.    | Define 4 variable (w, x, y and z) scenario as given below <ul style="list-style-type: none"> <li>• w = 1 if the applicant has been involved in a car accident</li> <li>• x = 1 if applicant is married</li> <li>• y = 1 if applicant is male</li> <li>• z = 1 if the applicant is under 25</li> </ul> Find the Boolean expression which assumes the value 1 when the policy should be issued: <ol style="list-style-type: none"> <li>A Married female 25 years old or over</li> <li>A female under 25</li> <li>A married male under 25 who has not been involved in a car accident</li> <li>A Married male who has been involved in a car accident</li> <li>A married male 25 years old or over who has not been involved in a car accident. Reduce the Boolean expression using K-Map.</li> </ol> | 10 | 1  | 2  |
| 3.    | Refer to Figure below, where an analog-to-digital converter is monitoring the dc voltage (VB) of a 12-V storage battery on an orbiting spaceship. The converter's output is a four-bit binary number, ABCD, corresponding to the battery voltage in steps of 1 V, with A as the MSB. The converter's binary outputs are fed to a logic circuit that is to produce a HIGH output as long as the binary value is greater than 0110; that is, the battery voltage is greater                                                                                                                                                                                                                                                                                                                          | 10 | 1  | 3  |



# VIT


Vellore Institute of Technology

REG.NO.:

**SCHOOL OF COMPUTER SCIENCE ENGINEERING AND INFORMATION SYSTEMS**  
**CONTINUOUS ASSESSMENT TEST - I**  
**FALL SEMESTER 2025-2026**

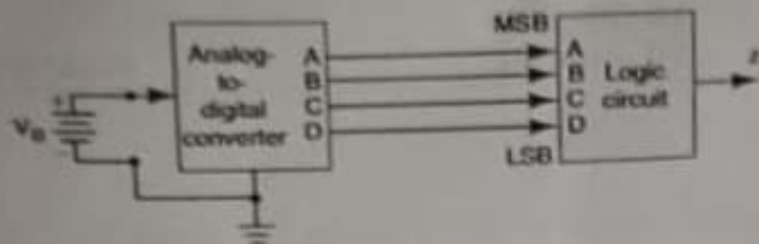**SLOT: B1+TB1**

than 6 V. Identify the Boolean function and design this logic circuit using 4\*1 multiplexer.



4.

A XY flip flop has four operations. When inputs X and Y are 00, 01, 10 and 11, the outputs are Toggle, 1, 0 and No change respectively. If you have a flip flop as specified above, then


- Tabulate the characteristic table.
- Derive the characteristic equation
- Draw the state diagram
- Derive the Excitation table.

10

2

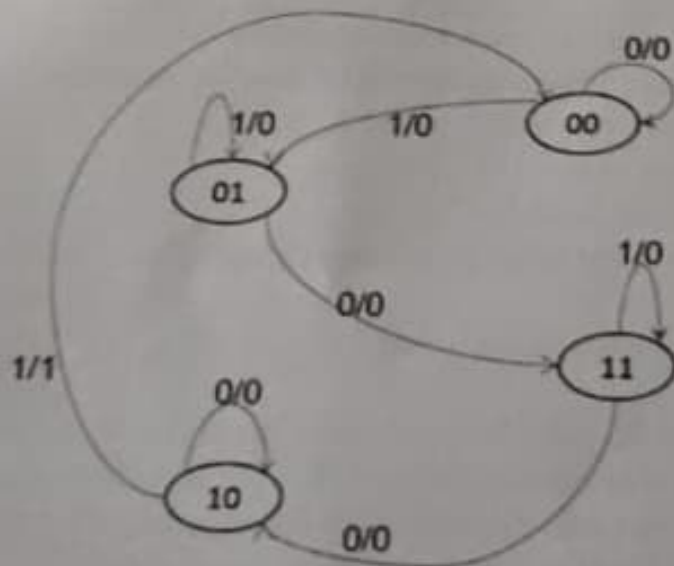5.

Find the state table and design a synchronous sequential circuit using T flip flop for the following state diagram shown below.



10

2