 


Programme Name & Branch : B.Tech &ECE/BML
Course Code and Course Name : BAECE102-Digital Logic Design
Faculty Name(s) : Dr Ravi S, Dr Rajeshkumar V, Dr. Hemanta Kumar Sahu,
Dr Deepikarani Sona, Dr. Abhishek Narayan Tripathi
Class Number(s) : VL2025260500805, 0807, 0810, 0812, 0814
Date of Examination : 23/03/2026
Exam Duration : 90 minutes
Maximum Marks: 50

General instruction(s):

- Answer All Questions
- Course Outcomes
- CO2 : Implement the various combinational and sequential circuits for customized specification
- CO3: Use the Verilog HDL constructs to model all the combinational and sequential logic circuits

Q. No	Question	M	CO	BL
1.	Design a 4-to-2 priority encoder with inputs I_0, I_1, I_2, I_3 where I_1 has the highest priority and I_3 has the lowest priority. ($I_1 > I_2 > I_0 > I_3$). (a) Construct the truth table considering priority conditions. (b) Derive the Boolean expressions for outputs Y_1 and Y_0 . (c) Implement the circuit using basic logic gates.	10	2	3
2.	Design and implement a circuit using a 4×1 Multiplexer with three inputs (A, B, C) and one output (Y). The output $Y = 1$ when the number of 1's in the input is <u>even</u> , otherwise $Y = 0$. Construct the truth table. Connect A and C inputs to the select line. Determine the required MUX input connections (I_0 - I_3). Draw the MUX implementation diagram.	10	2	3
3.	A new clocked X-Y flip-flop is defined with two inputs, X and Y. The flip-flop functions as follows: If X is not equal to Y, the flip-flop remains unchanged in its state (Q) at the next clock pulse, and if X is equal to Y, the flip-flop toggles its state (Q) at the next clock pulse. (a) Provide the truth table for the X-Y flip-flop. (b) Provide the characteristics table. (c) Provide the Excitation table for the X-Y flip-flop. (d) Implement the X-Y flip-flop using a J-K flip-flop.	10	2	3
4.	Design a synchronous counter for the count sequence 0-2-5-7-3-1-0 using a positive-edge-triggered D flip-flop.	10	2	3
5	Write the Behavioral Verilog code and test-bench describing the functionality of the circuit given in Figure 1.  Figure-1	10	3	3