


SCHOOL OF ELECTRICAL ENGINEERING
CONTINUOUS ASSESSMENT TEST - I
FALL SEMESTER 2025-2026

Programme Name & Branch : B.Tech & BEE, BEI
 Course Code and Course Name : BEEE205L & Electronic Devices and Circuits
 Faculty Name(s) : Sankardoss V, Chilukuri Venkata Mahendra, Uma Sathyakam P
 Class Number(s) : VL2025260101210, VL2025260101215, VL2025260101214
 Date of Examination : 20/08/2025
 Exam Duration : 90 minutes

Maximum Marks: 50

General instruction(s):

- Answer All Questions
- Rough work should not be done on question paper. It will be treated as malpractice.
- Use ordinary graph sheet.
- M - Max mark; CO - Course Outcome; BL - Blooms Taxonomy Level (1 - Remember, 2 - Understand, 3 - Apply, 4 - Analyse, 5 - Evaluate, 6 - Create)

Course Outcomes Statements:

CO. 1: Solve diode circuits for various applications.

CO. 2: Analyze and design BJT and MOSFET DC circuits and their amplifier configurations.

Q. No	Question	M	CO	BL
1a.	Sketch the input and output waveform of the clipper circuit shown in Fig. 1 on a graph sheet, when an input of 1 kHz sinewave is applied assuming ideal diodes. Describe the operation briefly. Fig. 1	5	1	3
1b.	Fig. 2 (a) shows the clamper circuit and the corresponding input waveform in Fig 2(b). Obtain the steady state output waveform and draw it on a graph sheet. (a) (b) Fig. 2	5	1	3



SCHOOL OF ELECTRICAL ENGINEERING
CONTINUOUS ASSESSMENT TEST - I
FALL SEMESTER 2025-2026

2. A crystal diode having internal resistance $r_f = 20 \Omega$ is used for half-wave rectification. If the applied voltage $v = 50 \sin \omega t$ and load resistance $R_L = 800 \Omega$, Find: (a) I_m , I_{dc} , I_{rms} , (b) a.c. power input and d. c. power output, (c) d. c. output voltage and (d) efficiency of rectification

10

1

2

3. With neat diagram, explain the input and output characteristics of a NPN transistor in CE configuration and draw it on a graph sheet.

10

2

1

4. Determine V_{CE} and I_C in the stiff voltage-divider biased transistor circuit of Fig. 3 if $\beta_{DC} = 100$.

 


Fig. 3

10

2

3

5. (a) For the transistor circuit shown in Fig. 4, what is V_{CE} when $V_{IN} = 0$ V?
 (b) What minimum value of I_B is required to saturate this transistor if β_{DC} is 200? Neglect $V_{CE(sat)}$.
 (c) Calculate the maximum value of R_B that will put the transistor in saturation assuming $\beta_{DC} = 200$ when $V_{IN} = 5$ V.

 


Fig. 4

10

2

3