



NAME OF THE SCHOOL
CONTINUOUS ASSESSMENT TEST - II
XXX SEMESTER 2025-2026

SLOT: A2+TA2

Programme Name & Branch : B.Tech - Electronics Engineering (VLSI Design and Technology)

Course Code and Course Name : BEVD304L - CMOS Analog IC Design

Faculty Name(s) : Dr Abdul Majeed K K

Class Number(s) : VL2025260500917



Date of Examination : 15/03/26

Exam Duration : 90 minutes

Maximum Marks: 50

General instruction(s):

- Answer All Questions
- M - Max mark; CO - Course Outcome; BL - Blooms Taxonomy Level (1 - Remember, 2 - Understand, 3 - Apply, 4 - Analyse, 5 - Evaluate, 6 - Create)
- Course Outcomes (Type the CO statements covered in this question paper. Use the CO number as per the syllabus copy)
 2. Design single-stage, differential amplifiers, and analyse the performance with respect to frequency and noise
 6. Understand the fundamentals of PLL

 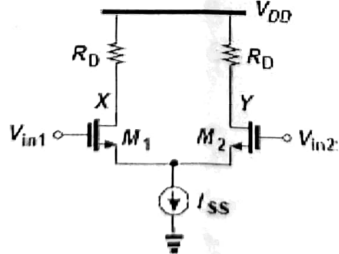Q. No	Question	M
1.	Consider the source follower shown in Fig. 1 where all the transistors have $(W/L)_{M1} = 100 \mu\text{m}/1 \mu\text{m}$; $\mu_n C_{ox} = 90 \mu\text{A}/\text{V}^2$; $\mu_p C_{ox} = 30 \mu\text{A}/\text{V}^2$; $I_{bias} = 100 \mu\text{A}$; $\gamma = 0.5 \text{ V}^{1/2}$; $2\phi_F = 0.8 \text{ V}$; $V_{SB} = 0.4 \text{ V}$; $R_S = 180 \text{ k}\Omega$; $C_L = 10 \text{ pF}$; $C_{GS1} = 0.2 \text{ pF}$; $C_{GD1} = 15 \text{ fF}$; $C_{SB1} = 40 \text{ fF}$. Determine the low frequency gain A_v and estimate the poles and zero frequency.  Fig. 1	10
2.	Consider a MOSFET differential amplifier in Fig. 2 operated at a bias current of 0.5 mA, using transistors with a (W/L) of $5 \mu\text{m}/1 \mu\text{m}$, $\mu_n C_{ox} = 0.3 \text{ mA}/\text{V}^2$, $R_D = 8 \text{ k}\Omega$ and $R_{SS} = 8 \text{ k}\Omega$, $C_L = 1 \text{ pF}$, $C_{GS} = 30 \text{ fF}$, $C_{GD} = 15 \text{ fF}$ and $C_{DB} = 15 \text{ fF}$, $\lambda_n = \lambda_p = 0.1 \text{ V}^{-1}$. Estimate the pole and Zero frequencies.  Fig. 2	10



VIT

Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)

REG.NO.:

NAME OF THE SCHOOL
CONTINUOUS ASSESSMENT TEST - II
XXX SEMESTER 2025-2026

SLOT: A2+TA2

3. Determine the input referred noise of CMOS inverter shown in Fig. 3 for $\lambda \neq 0$. Consider both thermal and flicker noises.

 


Fig. 3

4. Derive the input referred thermal noise of the opamp shown in Fig. 4.

 


Fig. 4

5. The PLL architecture is given in Fig.5. Calculate its open 1) loop transfer function, 2) closed loop transfer function, 3) natural frequency (ω_n), 4) Damping factor (ζ), 5) Output frequency (F_{out}) and 6) locking time for 1% tolerance.

The values of PLL components are as follows $F_{ref}=18$ MHz, $N=128$, $C=260$ ps, $b=10$, $R=1$ K Ω , $I_{cp}=150\mu A$, $K_{vco}=19$ GradV $^{-1}$.

 


Fig. 5
