



VIT

Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)

SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - I
WINTER SEMESTER 2025-2026

REG. NO.:

SLOT: A2+TA2+TAA2

Programme Name & Branch
Course Code & Course Name
Faculty Name(s)

: B. Tech., BEC & BML
: BAECE103 & Network Theory
: Dr. Elizabeth Rufus, Dr. Velmurugan V., Dr. Sathya P.,
Dr. Nithish Kumar V., Dr. Konguvel E.
: VL2025260500796, VL2025260500801,
VL2025260500798, VL2025260500800, VL2025260500803
: 27.01.2026 (02:00 - 03:30 PM)

Class Number(s)



Date of Examination

Exam Duration: 90 Minutes

General Instruction(s):

Maximum Marks: 50

- Answer All Questions
- M - Max mark; CO - Course Outcome; BL - Blooms Taxonomy Level
(1 - Remember, 2 - Understand, 3 - Apply, 4 - Analyze, 5 - Evaluate, 6 - Create)
- Course Outcomes:
CO1: Compute DC circuit parameters using circuit laws and theorems.
CO2: Determine the natural and step responses of RC, RL, and RLC circuits.

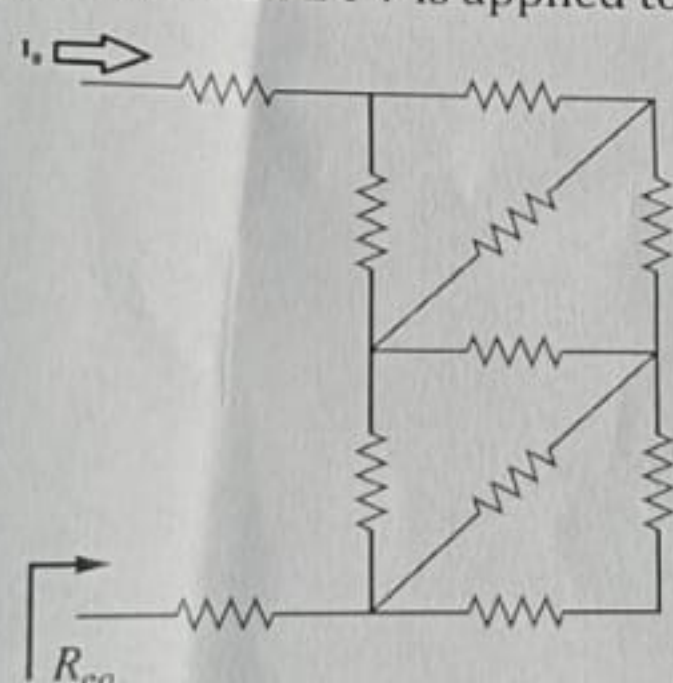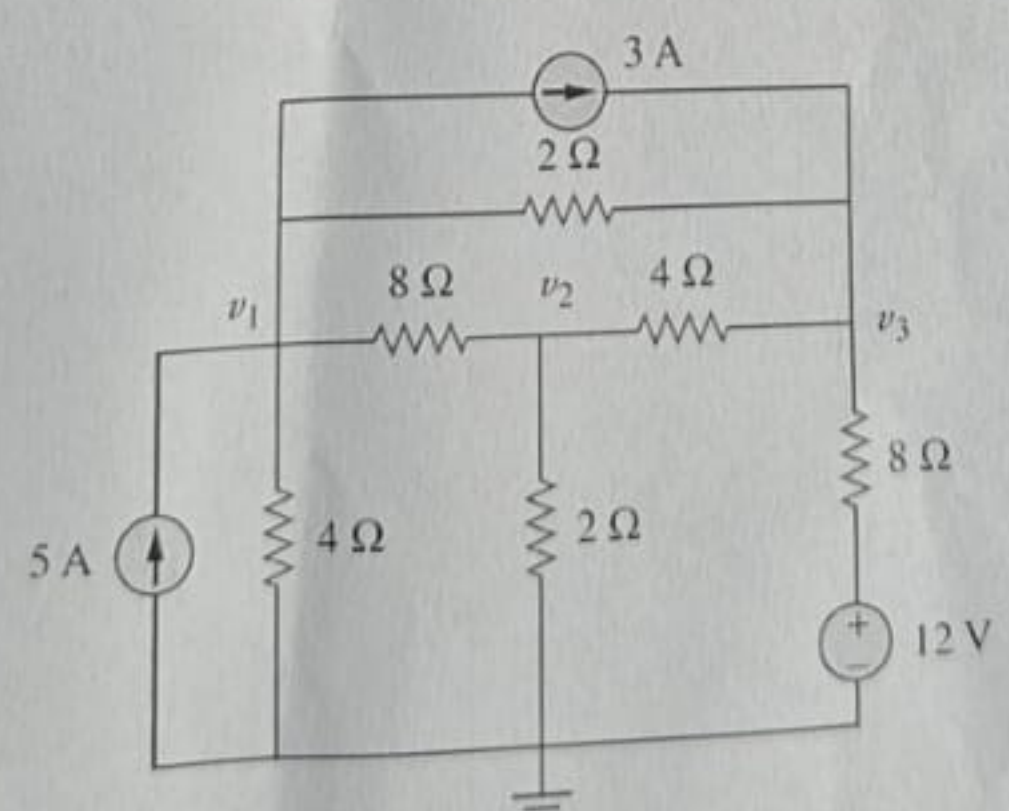No.	Question	M	CO	BL
1.	For the circuit shown in Figure 1, obtain the equivalent resistance (R_{eq}). All resistors are 3Ω. Calculate I_o when 24 V is applied to the resistive network.  Figure 1.	10	1	BL3
2.	Use mesh analysis to determine v_1, v_2, and v_3 in the circuit shown in Figure 2.  Figure 2.	10	1	BL3






VIT

Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)

SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - I
WINTER SEMESTER 2025-2026

REG. NO.:

SLOT: AZ+TAZ+TAAZ

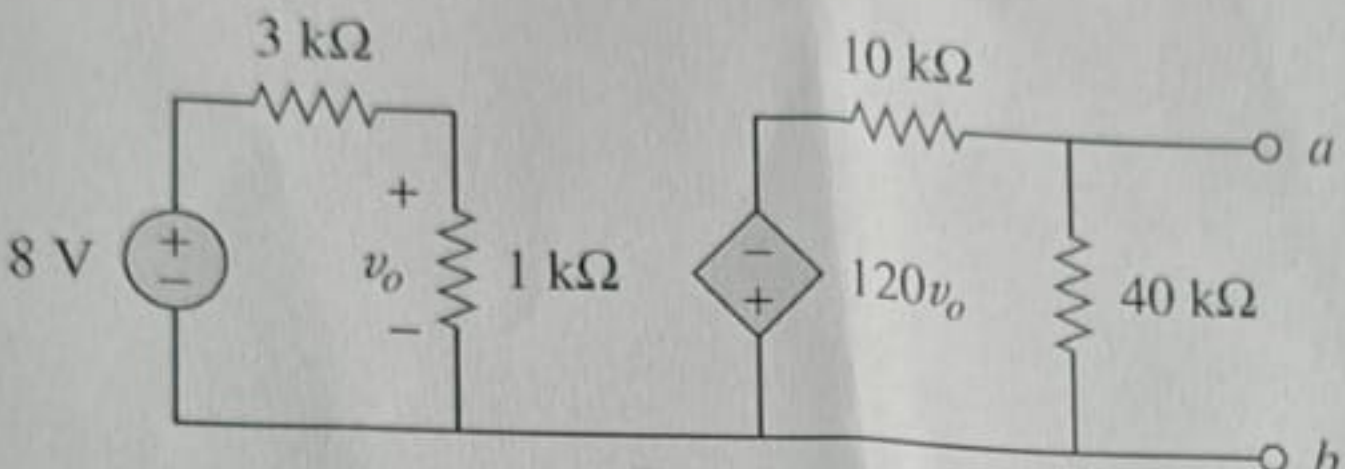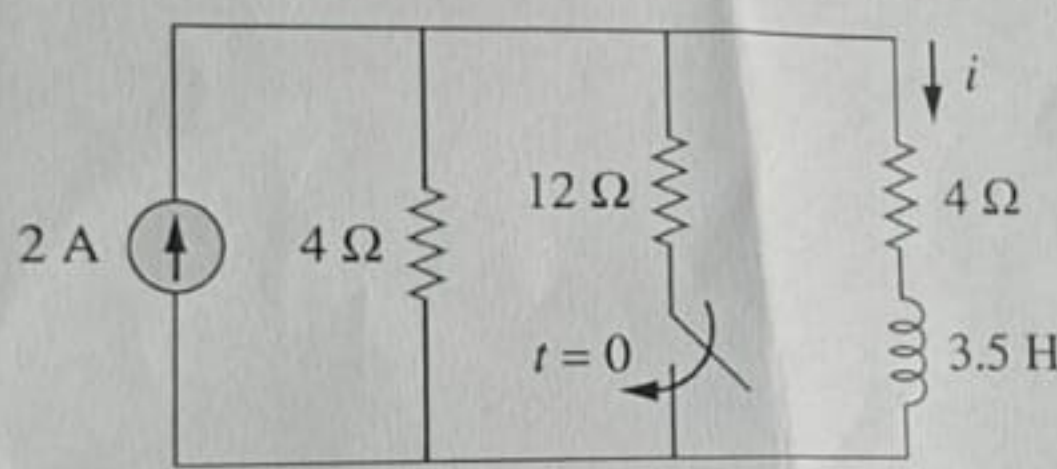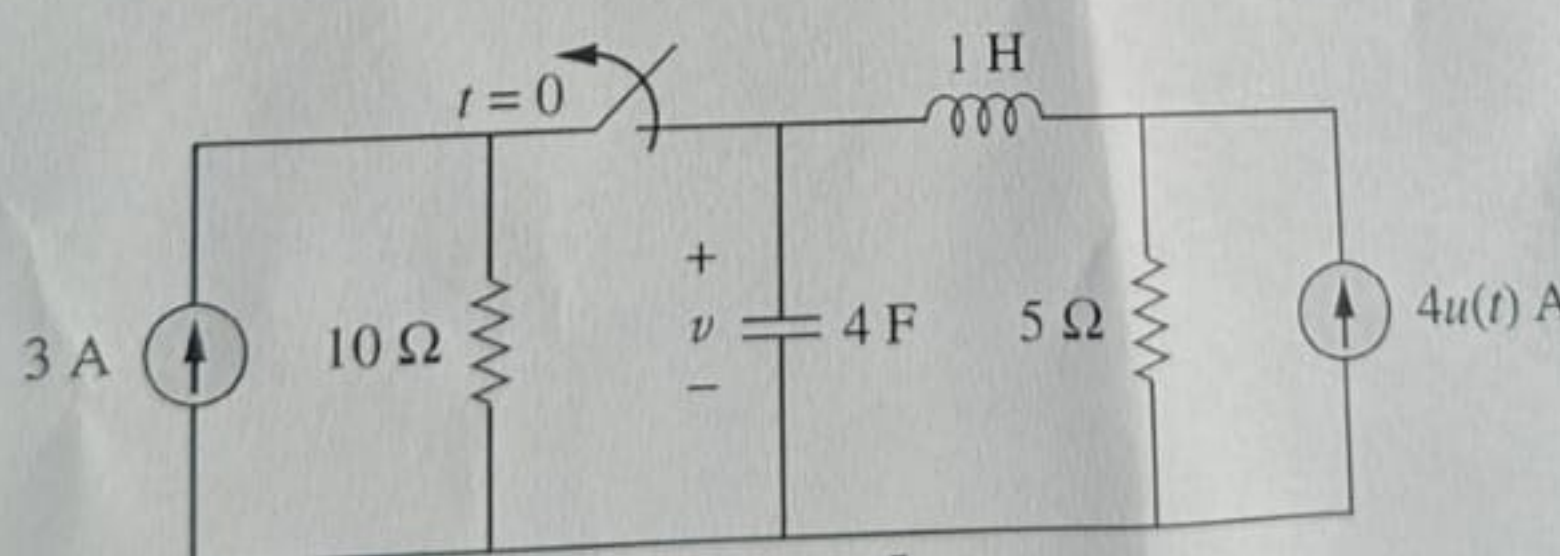3.	Obtain the Norton's equivalent for the circuit shown in Figure 3. What will be the resistance to be connected across the terminals a and b which will draw maximum current?  Figure 3.	10	1	BL3
4.	Obtain the inductor current for both $t < 0$ and $t > 0$ in the circuit given in Figure 4.  Figure 4.	10	2	BL3
	Determine $v(t)$ for $t > 0$ in the circuit shown in Figure 5.  Figure 5.	10	2	BL3
